
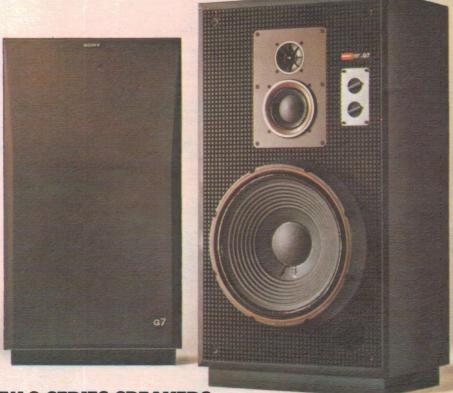

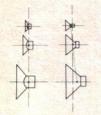
# WAY OUT FRONT BECAUSE THEY'RE WAY OUT FRONT



# SONY'S NEW G SERIES SPEAKERS. WE LINED UP THE SOUND SOURCES—NOT THE SPEAKER EDGES—TO GET THE EDGE ON THE FRONT-NAME SPEAKERS.



We admit it, for years our front name reputation in audio and video hasn't quite been matched by our speakers. So in 1972 we began a total new

So in 1972 we began a total new research programme specifically designed to put our speakers where all of our other stereo components have long been – out front.

After years of research and development our engineers

have found the answers:
First spring water. Like good whisky, good cone papers depend on the purity of the water used in making them. So we built an entirely new factory at Kofu at the base of Mt. Fuji where we can get all the spring water we need. Next there was the use of carbon fibre in our speaker cone paper. It's very strong and light. So our speakers are more efficient. And the carbon fibre prevents the cone from bending out of shape in the high frequency range. Moreover it doesn't resonate much. Which cuts out unwanted vibration.

Then so does our use of a cast basket rather than a cheap stamped one. Finally our big breakthrough came by breaking through the standard idea of simply attaching the front of each speaker to the hatfile board.

each speaker to the baffle board.

By moving our woofer and mid-range forward to a position where the sound waves originate in the same line, we aligned them acoustically. The result is transparently smooth and deep sound over the entire audio frequency range. It's a sound that specifications alone cannot describe.

But some of the toughest critics in the whole audio world can

But some of the toughest critics in the whole audio world can. They heard our new G Series speakers first at the last Japan Stereo Components Contest. Result? They awarded Sony the "Grand Prix".

Now hear this: The new Sony G Series speakers have arrived at your dealers. Listen to them and you'll hear just how beautiful five years' research can sound.

SONY


Research makes the difference.

# Australia's largest selling electronics & hisfi magazine


Australia's largest selling electronics & hi-fi magazine
On sale the first Monday of each month

VOL. 39 No. 9

DECEMBER, 1977

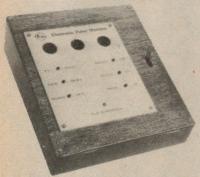

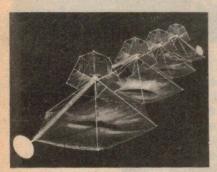This easy-to-build electronic poker machine will provide Christmas fun for the whole family. Turn to p56 for the details.



A bold new concept to solve man's energy problems has been proposed by Boeing Aerospace Company — power stations in space! The story is on p8.

## On the cover


Pictured is the recently released BWD 539D oscilloscope testing an AWA mobile transceiver at the laboratories of BWD Electronics Pty Ltd. You can find out more about the 539D on p108 of this issue, and how to win a unit for yourself on p49.

## **FEATURES**

	CHOOSING A CALCULATOR The things you need to know  BASF LUDWIGSHAFEN IS REALLY BIG A visit to the BASF plant in Germany DICK SMITH-ELECTRONICS AUSTRALIA MINI SCAMP	12 20
	CONTEST The winner	94
	HIFI NEWS & REVIEWS	
	HIFI NEWS New 2 x 350W class A+ system to be released by Technics  REVIEW EEI-Series-4000 magnetic cartridge  REVIEW Leak 3050 2-way loudspeaker system	29 51 53
	THE AUSTRALIAN CB SCENE	
	PHILIPS 40-CHANNEL UHF LOOKING GOOD A preview of what's to come	39 45
	MIDLAND 13-861 PORTABLE TRANSCEIVER This rig goes anywhere CB NEWS, OBSERVATIONS & PRODUCTS CB happenings in brief	45
	UHF CB CHANNELS List of frequencies	47
ı	DICK SMITH-EA CB CARTOON CONTEST The winner	48
	PROJECTS & CIRCUITS	
	ELECTRONIC POKER MACHINE Christmas fun project	56 64
	BATTERY CONDITION INDICATOR Simple unit gives good/bad indication	68
	BUILD YOUR OWN METAL DETECTOR Low-cost unit comes as a kit	70
	LOW-COST TESTER FOR MICROPROCESSORS Troubleshoot your system	86
	COLUMNS	
	[6] [6] [6] [6] [6] [6] [6] [6] [6] [6]	3
	FORUM Is it just trendy to listen to FM?	
	THE SERVICEMAN On aerials, feeders and exorcising ghosts	80
	RECORD REVIEWS Classical	99
	RECORD REVIEWS Devotional, popular, jazz THE AMATEUR BANDS Amateur radio is flourishing	117
	SHORTWAVE SCENE Radio Nederland using a satellite	123
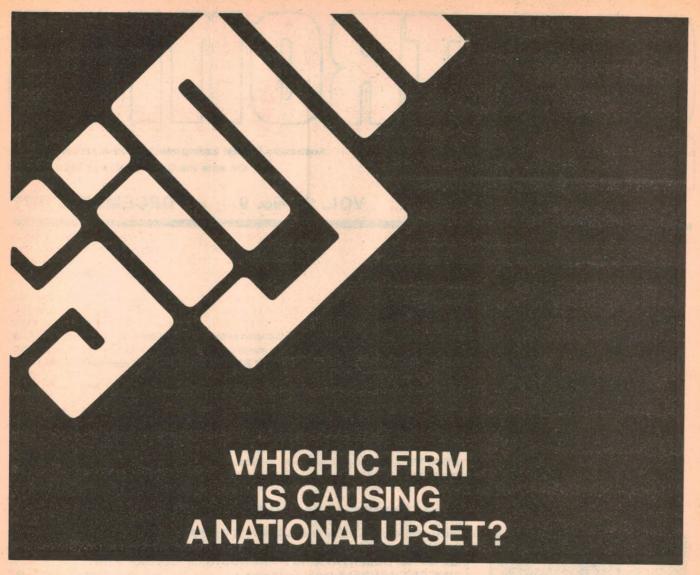
### **DEPARTMENTS**

NEWS HIGHLIGHTS—4/CIRCUIT & DESIGN IDEAS—76/LETTERS TO THE EDITOR—85/MICROCOMPUTER NEWS & PRODUCTS—96/NEW PRODUCTS—108/BOOKS & LITERATURE—112/INFORMATION CENTRE—125/MARKETPLACE—126/INDEX TO ADVERTISERS—128/NOTES & ERRATA—NIL



A new team is jostling the biggest names in ICs. When you see who it is you'll appreciate why. Signetics – known worldwide for reliability and high technology has become part of Philips with massive R & D, manufacturing, and servicing resources. That's important news for

you. Signetics offers a natural alternative for all your IC requirements. Signetics ICs are supported by a strong sales and technical team and are available nationwide through an expanded distribution network.

We'll supply all types of industrial and consumer

ICs. And we'll ensure the continuity of that supply short or long term.
Let us prove our IC capability. Ask us for a quote. Write today to Signetics IC Marketing Group at Philips
Electronic Components and Materials, P.O. Box 50, Lane Cove, N.S.W. 2066

# signetics

LOGIC - MEMORIES - INTERFACE - MICROPROCESSORS - LINEAR - MILITARY



Electronic Components and Materials

PHILIPS

HRME 153.0201



# **Editorial Viewpoint**

# 1978 — year of the microcomputer?

Well, here we are again nearing the end of another year, and it has been a fairly eventful one for the local electronics industry. The events have admittedly not been propitious for the manufacturing side of the industry, nor perhaps for the hifi marketing firms, but the importing and overall marketing situation seems to have improved significantly.

Without a doubt the main event has been the legalisation of CB radio, and the subsequent market growth. This has happened very rapidly, and things are still rather chaotic. There are dozens of brand names around, and almost every corner store is offering CB equipment. How many of them are likely to continue doing so is a matter of conjecture, as many of the imported transceivers have already been rejected for licensing by the PTT department. However local manufacturing firms are quietly preparing for production of UHF equipment, so that as marketing of 27MHz gear tapers off there should be a growth in the manufacturing sector to at least partly compensate.

Probably the other main event this year has been the accelerated growth in microprocessors and microcomputers. This area finally seems to be talking off now, here as well as overseas, and in both the industrial and hobby/consumer areas. New equipment manufacturers are appearing, hobby and consumer stores are springing up, new clubs have formed, and both academic bodies and industry

organisations are holding conferences and seminars.

It is evident that a new growth industry is emerging, even if its gestation time has

taken a little longer than many had predicted.

In the coming year the microcomputer area looks likely to be the main growth sector within the electronics industry. The biggest impetus is likely to come shortly with the appearance of complete low-cost systems suitable for really small businesses, schools and the home: the true "consumer" computer, as distinct from the hobby computer.

We have been doing our best, here at EA, to keep you abreast of these developments. And, judging from the reaction to many of our recent features, most readers seem to appreciate our efforts. It has been particularly encouraging to see the response to some of our construction projects - like the Mini Scamp microcomputer, for example, of which more than 700 have apparently been built to date:

It has been an eventful year, then, and one which seems to be drawing to a close on a reasonably optimistic note.

On behalf of all of us here, may I wish all of our readers, advertisers and friends a very happy Christmas season, and all the best for 1978.

Jamieson Rowe

EDITOR-IN-CHIEF Neville Williams M.I.R.E.E. (Aust.) (VK2XV),

**EDITOR** 

Jamieson Rowe B.A. (Sydney), B.Sc (Technology, NSW) M.I.R.E.E. (Aust.) (VK2ZLO/T)

> ASSISTANT EDITOR Philip Watson A.M.I.R.E.E. (Aust.) (VK2ZPW)

SCIENCE FEATURES Greg Swain, B.Sc. (Hons, Sydney)

> **PRODUCT REVIEWS** Leo Simpson

TECHNICAL PROJECTS David Edwards, B.E. (Hons, Tasmania) Ian Pogson (VK2AZN/T)

> GRAPHICS Robert Flynn

PRODUCTION Danny Hooper

**ADVERTISING MANAGER** Selwyn Sayers

CIRCULATION MANAGER Alan Parker

Registered for posting as a periodical — Category

Printed by Magazine Printers Pty Ltd, of Regent Street, Sydney and Masterprint Pty Ltd of Dubbo, NSW, for Sungravure Pty Ltd, of Regent St, Sydney.

\*Recommended and maximum price only.

**Editorial Office** 

57-59 Regent St, Sydney 2008 Phone 699 3622

Postal Address: PO Box 163, Beaconsfield 2014.

**Advertising Offices** 

Sydney - 57-59 Regent St, Sydney 2008 Phone 699 3622

Representative: Narcisco Pimental. Melbourne - 392 Little Collins St, Melbourne 3000. Phone 67 3131

Representative: Keith Watts.

Adelaide - Charles F. Brown & Associates Ltd, 168 Melbourne St, North Adelaide 5006 Representative: Tom Duffy, 267 4377. Perth - 454 Murray Street, Perth 6000

Representative: Jack Hansen, 21 8217.

Subscription Dept, John Fairfax & Sons Ltd, GPO Box 506, Sydney 2001. Enquiries: Harry Dale, Phone 663 3911, ext 342.


Circulation Office

21 Morley Ave, Rosebery, Sydney 2018 Phone 663 3911.

Distributed in NSW by Sungravure Pty Ltd, 57-59 Regent St, Sydney, in Victoria by Sungravure Pty Ltd, 392 Little Collins Street, Melbourne; in South Australia by Sungravure Pty Ltd, 101-105 Weymouth St, Adelaide; in Western Australia by Sungravure Pty Ltd, 454 Murray Street, Perth; in Queensland by Gordon and Gotch (A'asia) Ltd; in Tasmania by Ingle Distributors, 93 Macquarie St, Hobart; in New Zealand by Gordon and Gotch (NZ) Ltd, Adelaide Rd, Wellington.

Copyright. All rights reserved

Devices or arrangments shown or described herein may embody patents. Information is furnished without responsibility for its use and without prejudice for patent rights. All manuscripts, photographs and other material submitted to Electronics Australia for publication must be accompanied by a stamped, addressed envelope. Contributions are submitted at the sender's risk, and responsibility for loss cannot be accepted by Electronics Australia

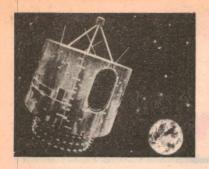

# News Highlights

# Chess Challenger — you play the computer!

It's you against the computer! The first microprocessor based chess game is now available in Australia.

Called the Chess Challenger, the new game is based on the Intel 8080 CPU. It also utilises an 8224 clock generator/driver, an 8228 system controller, 512 8-bit bytes of random access memory to store the position of the chess pieces, and a 16,384-bit read only memory.

The firmware (inside the ROM) contains such elements as the rules of chess, the relative importance of the various pieces, and allowable moves and strategies. The Chess Challenger plays by the book, working on the weighted value of the pieces, and completely scanning the board for the best available move each time. It plays aggressively, tries to control the centre of the board, and, if it's in trouble, will try for a stalemate.

The keyboard can be used to verify the position of each chess piece at any time during the game. The player can select from four levels of difficulty at the start of the game, can choose offence or defence, and can even commence in mid-game should he wish to set up a chess problem. All the moves of chess can be made, and the Chess Challenger is programmed to castle at the first opportunity.

Chess Challenger is easy to play and, according to the



manufacturer, can be beaten by an average player 25%-70% of the time, depending on the level of difficulty selected. It costs \$385.25 and is available from Futuretronics Pty Ltd, 527 Tooronga Rd, Hawthorn East, Victoria 3123.

## Communications for deep sea divers

In Britain, a cooperative formed by two specialist firms and the Admiralty Experimental Diving Unit has been working for some time on a fibre optics communications system for deep sea divers. One of the companies, J. and S. Marine, has developed a multiplex data transmission system. This encodes information for transmission along a single fibre line, and decodes and presents the data at the receiving end.

Conventional diving equipment involves an umbilical line that tends to be heavy and cumbersome. The big advantage of the fibre optic technique is that it reduces quite dramatically the diameter of the speech and data lines between the diver and the diving bell, or between the bell and the surface

The system developed by J. and S. Marine is designed to carry 16 of the diver's medical parameters, including pulse rate, body temperature, heartbeat, physiological and life support details, and diving suit temperature. This system now forms

part of a four-line communications system. Two of these lines provide two-way speech communication, whilst the fourth line is spare.

Apart from giving the diver freedom to work with the minimum of extraneous equipment and the lightest possible umbilical line, the system's most important contribution to safety is its immunity from outside electrical interference. In such a complex piece of equipment as the modern diving suit, designed for use at great depths, it is inevitable that a great deal of static electricity is generated. The effect in shallow water is likely to be negligible, but in deep conditions it can mean the loss of data essential to the survival of the man at the end of the line.

In fibre optic transmission no electric current passes along the line, and it therefore is immune from electrical interference. This is important because the diving suit and the support systems, to say nothing of the gear employed on the seabed, are all potential generators of interference.

# Device beats radar detectors

In their war on speeding motorists, traffic police have had a formidable weapon at their disposal for some years now — radar speed indicators. Just recently, though, motorists began to hit back, using radar detectors to (hopefully) detect the presence of a radar trap and provide adequate advance warning of its presence.

Now, according to the American magazine "Electronics", the police have another weapon. The device is a small traffic radar that uses a microprocessor to help in camouflaging itself from the barrage of radar detectors now on the roads.

The radar, from Kustom Signals Inc, is programmed with a hold feature that suppresses the microwave transmission until a target vehicle is within sight. That way, it is invisible to radar detectors until it is fired, and by the time it is seen, the radar has recorded the target's speed.

# **National** looking sharp!



A feature of the Haco Distributing Agencies stand at the recent Consumer Electronics exhibition in Sydney was an ultra-thin "National" pocket radio developed by the Matsushita Electric Industrial Company, Japan.

The new radio measures a compact 71mm wide by 127mm long, and is just 12.7mm thick. Weight is 130g with

batteries.

Recommended retail price for the new model, due for release last September, is around the \$40 mark.

## Record turnover for Dick Smith

Dick Smith Electronics Pty Ltd has announced a successful trading year for 1976-77

Mr Ike Bain, General Manager, said that turnover increased from \$3.5 million in 1975-76 to \$7 million in 1976-77, these figures representing tremendous growth. According to Mr Bain, CB radio contributed significantly to this increase, although the traditional hobby electronic lines were still responsible for the majority of tur-

# Omega agreement has been signed

The Minister for Transport, Mr Peter Nixon, recently signed an agreement between the Australian and US Governments for the establishment of an Omega long-range navigation facility in Australia.

The facility, which will be built in Gippsland, Victoria, will be designed, operated and maintained by Australians. Mr Nixon said that the Government had approved the purchase of the 308 hectare site at Darriman, about 25 kilometres from

The Omega establishment agreement between Australia and the US provided that:

• The Australian Government would

be solely responsible for operating, maintaining and staffing the facility;

- Australian made materials and resources would be used in establishing the facility; and
- The 400 metre aerial tower would be designed in Australia and built from Australian steel. Australian materials would be used throughout the project as far as practicable.

Mr Nixon said that the Australian Omega facility would complete a world-wide network of eight Omega stations. The others were in North Dakota, Hawaii, Argentina, Liberia, Norway, Japan and Reunion Island in the Indian Ocean.

# Touch tune Toshiba from EMI



Backed by a full 3-year parts and labour warranty, this Toshiba Model C-830 43cm colour TV receiver features electronic touch tuning and a "Blackstripe" picture tube with in-line guns. A hinged fascia panel conceals the major controls. Enquiries to Toshiba-EMI (Australia), 16 Mars Rd, Lane Cove 2066.

# GE to develop new electric vehicle

the development and construction of Research and Development Centre, two experimental four-passenger elec- Schenectady, NY, and by its team of tric cars has been awarded by the US consultants and subcontractors. GE also braking to permit braking energy to be Energy Research and Development Ad- will supply the electrical drive system. used in recharging the 18 batteries. Administration, now part of the Department of Energy (DOE), to the General Electric Research and Development Centre.

will deliver the two cars to DOE in the Chrysler will jointly test the integrated first half of 1979. Called "integrated test vehicle. vehicles", the new subcompact-sized electrics will be based on a design to be Corporation.

Chrysler Corporation, Detroit, Michigan, will design and fabricate the body and chassis. Globe-Union Inc., Milwaukee, Wisconsin, will provide Under the terms of the contract, GE high-energy lead-acid batteries. GE and

developed jointly by GE and Chrysler have not yet been detailed. However, trics be conducive to mass production, Electrical and mechanical in- excited direct current (DC) motor comparable to conventional cars.

A two-year \$5.98 million contract for novations will be developed by the GE powered by a 108-volt lead-acid battery system.

The GE cars will have regenerative vanced electronics will provide the vehicles with smooth and efficient per-

Built especially for stop-and-go urban driving, the new vehicles will have an urban driving range of 120km before the batteries need recharging and will be capable of cruising at Technical and mechanical speeds of 90km per hour. Another DOE specifications for the new electric cars objective is that design of the new elec-GE's program plan calls for a separately with purchase price and operating costs

# **NEWS HIGHLIGHTS**

# Canberra microcomputer conference



These two candid shots were taken at the recent microprocessor conference in Canberra, run by the Canberra branch of the Australian Computer Society and the Canberra College of Advanced Education. A lot of keen



enthusiasts attended, including both amateurs and professionals. The photos are by courtesy of Dr Bill Caelli, the conference convenor.

# Increase R&D spending, says ATDA

Australia, of all reasonably developed nations, is at the bottom the list for government funded industrial research and development according to the Australian Telecommunications Development Association.

The ATDA has made this claim in its submission to the Senate Standing Committee on Science and the Environment's inquiry into research and development in Australia.

The association says in its submission that technical and manufacturing capability and capacity are at present lower than they have been for many years.

The main causes for this are:

- the present economic recession,
- substantially reduced ordering of communications equipment by

Telecom Australia and by Government Departments,

 currency realignments, substantial tariff cuts, and an escalating wage struc-

"The reduction in available work has led to extensive retrenchments, resulting in a considerable loss of technical expertise and capacity. In the past three years the industry has reduced its R & D staff by about 30 per cent," according to the ATDA.

The association's submission points out to the Senate Inquiry that a healthy and active electronics industry is essential for Australia. The industry provides vital telecommunications equipment for Telecom Australia, for the defence network and in the private

## Changes at Arlunya

Arlunya Pty Ltd has advised that its manufacturing and importing activities are now being carried under a new name: The Arlunya Division of The Dindima Group Pty Ltd. Ownership and control of the Dindima Group Pty Ltd remains in Australia, and is essentially the same as for Arlunya Pty Ltd, prior to

The purpose of the change is to facilitate the growth of the company and to allow the gradual separation of the local manufacturing and importing activities into separate divisions. The company intends concentrating on increasing sales and improving support for high grade products from a limited number of top overseas firms.

# Australian developed electric car



An electric vehicle, currently under development at Flinders University, Adelaide, is reaching the stage where it could be put into full com-

mercial production.

The project, based on the Fiat 127 coupe, replaces the internal combustion engine with lead acid batteries and two printed circuit motors. The motors drive through the vehicle's original automatic transmission.

## "DXers Calling" scrapped

The Australian Radio DX Club (ARDXC) has been advised that its long running program "DXers Calling" will no longer be broadcast by Radio Australia. The program, especially for short wave listeners, had been on air every week since July 1946.

The ARDXC feels that letters of protest may succeed in reversing this decision, as "DXers Calling" had a wide audience in Australia and NZ. Readers should direct their letters to The Assistant Director of English Programs, Radio Australia, GPO Box 428 G, Melbourne 3001.

# Electronics is where it's all happening

# ...if you're into it you've got it made!

It's the world's fastest growing industry... with new discoveries...new products every day. And, every day, there are more jobs...bigger salaries...better opportunities...for people who are trained.

You can be part of this boom now by training with International Correspondence Schools. Learn to design, build, install, test, control and maintain modern electronic equipment...from your own colour TV or hi-fi set to a digital computer.

Your career opportunities are limitless...in broadcasting, industry, the military, aerospace programs, medical science and communications. With your enthusiasm and ICS tuition, a well paid job and a secure future in electronics is well within your grasp.

How do I get into it? ICS have put together a FREE Electronics Career Folder. It tells you all about the many courses open to you including Communications and Broadcasting, Industrial Electronics, Computer Servicing and Audio/Radio Servicing...courses endorsed by the Television and Electronics Technicians Institute of Australia. Post the coupon and the career folder will be on its way to you without obligation. Don't wait another minute...progress won't. The big developments in electronics are happening now and the demand for skilled people is growing all the time.

Special Colour TV repair course. Colour TV is booming all over Australia, beyond the To: International Correspondence Schools expectations of all the manufacturers, resulting in a shortage of qualified people to fill the service gap.

You could make a successful career in this growing field with the help of the ICS School of TV Servicing. You can benefit by this course – all you need is the enthusiasm to learn and enjoy rewarding work.

Your ICS course could be a start of an exciting new career or you can use your new-found knowledge to earn extra money in your spare time.

This special course is endorsed by the Television and Electronics Technicians Institute of Australia.

Send the coupon today. It could be the first step in an exciting new future for you.



Find out how you can be where it's all happening - in Electronics. Fill in the coupon and post today!

> **ICS Home Study** ...your passport to success in life!

Your	invitation	to join	the	thousands	of
successfu	I ICS grad	uates.			

400 Pacific Highway, Crows Nest. NSW. 2065 18-20 Collins Street, Melbourne VIC. 3000 182 Wakefield Street, Wellington. N.Z.

Please send me, entirely without obligation, a copy of the: ☐ ICS Electronics Career Guidance Kit ☐ ICS Colour TV Servicing Career Guidance Kit.

MR/MRS/MISS

**ADDRESS** 

POST CODE

PRESENT OCCUPATION

Take the first step -Fill in and mail this coupon today!

Space satellites the size of small cities — the concept sounds fantastic. But this is just what the US Boeing Aerospace Company is seriously proposing as a solution to the world's energy problems.

# Power stations in space!

That man must develop new sources of energy other than fossil fuel is a fact beyond question. It is the essence of the energy crisis. Most believe the solution will be found in the development of a non-depletable source of energy which can be transformed into usable electricity.

Man's primal energy source, the Sun, offers an attractive answer. By harnessing its rays in space, where they exist without night, and transforming this power into electricity usable on Earth, we would tap a power more durable than mankind.

This feat may be accomplished

through the use of solar power satellites, according to the Boeing Aerospace Company, Seattle, USA. Boeing's concept calls for the orbiting of a number of satellites, each capable of producing twice the usable power generated by Grand Coulee, the largest hydroelectric power station in the USA.


The Boeing satellites, each of the size of a small city, would be deployed some 36,000 kilometres above the equator in geosynchronous orbit, and would appear stationary when viewed from Earth. They would be bathed in sunlight 99% of the time, passing through the Earth's shadow only for

very short periods in spring and autumn when it is late at night on Earth.


The theory behind collecting solar energy in space is that the Sun's rays there are almost uninterrupted, and there is a virtual infinity of space for the collecting equipment. Boeing estimates that the solar energy available per unit area in space is six times as great as in the American deserts and 15 times as great as in typical north-eastern industrial areas.

The energy collected in space would be concentrated and transmitted back to collecting stations on Earth. These collecting stations would be elliptical in shape, measuring about 8km across and 12km in length. This represents a huge saving on space compared to the ground needed for direct collection of solar energy on Earth, and would greatly increase the chances of locating collector stations near industrial centres instead of in remote desert regions.

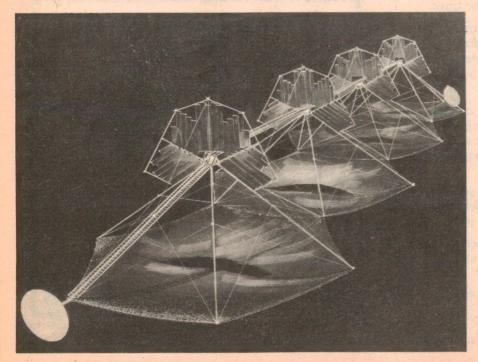According to Boeing, 45 to 50 of the satellites it proposes would be able to match the present electrical power generating capacity of the United States, freeing oil, coal and their derivatives for other crucial needs. A few more than as many again would



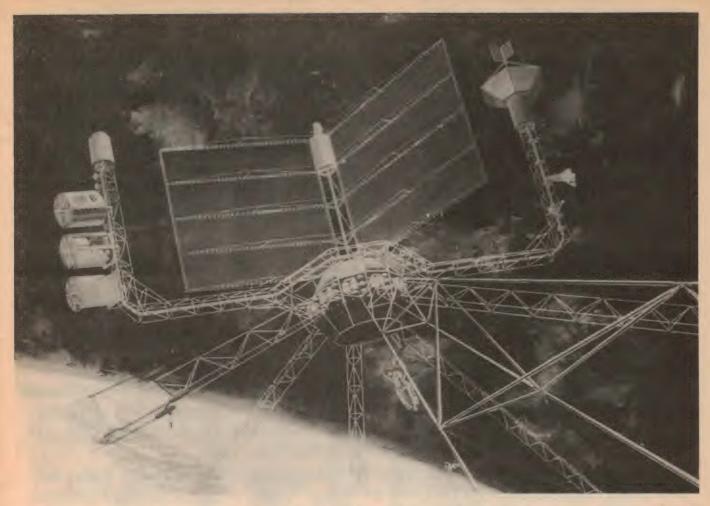Boeing concept for four-segment power satellite array stretching 23.7km across space. Structures above each solar collection module are panels which radiate unwanted heat from the spherical thermal generators which they girdle. The round discs seen lower left and upper right are transmitters which beam microwave energy back to earth for conversion into usable electricity.



This photograph shows Boeing's concept of the thermal engine section of a power satellite being assembled in orbit. Also shown are the spidery legs which would eventually

join the thermal engine to a huge array of mirrors serving as a solar concentrator. Scale is indicated by Space Shuttle docked to the structure, upper right.

provide the present energy requirements of the Earth.

Boeing has been involved in studies related to solar power satellites since 1972, both with its own research funds and under contracts from the National Aeronautics and Space Administration and other government agencies. Studies have centred on two basic configurations for the satellite — photovoltaic and Brayton heat engine. Each would be capable of producing 10,000 megawatts of usable power — enough to fill the needs of a million homes.

The photovoltaic satellite would be rectangular in shape and cover an area of about, 24.8 kilometres by 5.2 kilometres — an area of almost 128 square kilometres, or the size of a small city. On this vast platform would be mounted about 14 billion solar cells. This spacecraft would have a mass of about 80,000-100,000 tonnes.

The satellite's solar cells would transform sunlight directly into electrical energy, the same way solar cells power small satellites.

The Brayton heat engine satellite

would use a series of four parabolic dishes, each about 5.6 kilometres across. Together, they would stretch some 23.7 kilometres across space. Each dish would be made up of thousands of steerable, extremely thin plastic reflectors. These reflectors would direct the Sun's rays into a domelike cavity absorber — a solar furnace — located over each dish.

The concentrated sunlight would superheat gases which would expand and drive a series of turbo-generators girdling the absorber. These generators would produce the satellite's electricity

Once through the generators, the heated gases would be piped into large fin-like radiator panels in which the gases would cool before being recirculated back into the cavity absorber to begin a new cycle. The Brayton heat engine satellite would weigh about the same as the photovoltaic satellite — 80,000-100,000 tonnes.

The photovoltaic system is the less complex system, Boeing says, but solar cells at their present state of the art are less efficient than thermal cycle engines. They are also quite expensive and require exotic manufacturing techniques.

Brayton heat engine satellites, on the other hand, are complex systems using complex devices. They have a higher conversion efficiency, process large quantities of power and already have been proved through the large-scale production of energy on Earth.

Boeing says that while each system has definite attractions and drawbacks, both appear feasible.

The solar power satellites — whether heat cycle or solar cell — would produce direct current electricity. This would be converted to microwave energy which would be channeled through two transmitters on each satellite. The antennas would be about 1km across and, except for size, would be an extension of current radar technology.

The antennas would direct the microwave beam to ground receiving antennas which would rectify the microwave energy to produce direct current electricity.

These rectifying antennas — or "rectennas" — would resemble chain link fencing mounted in strips high

# OUR SECOND BEST IS BETTER THAN MOST OTHERS' FIRST BEST.

TDK's AD (Acoustic Dynamic) is one of the world's finest cassette tapes but not the best cassette tape made by TDK.

Our SA (Super Avilyn) has the edge but that's only if you're using the special bias/equalisation setting on your tapedeck.


However, if you're using the normal or standard setting, you'll have to settle for AD — second best.

Chances are you won't find anything better or with more consistent sound quality for decks with normal tape selector settings (or no selector switch at all). In other words, even if you don't own extravagant equipment, with AD you can still hear extravagant sound reproduction.

You see, because of AD's superior dynamic range at the critical high end, you'll hear any music that features exciting "highs", with amazing brilliance and clarity you won't get from any other tape.

But there is something else you should hear before you try TDK's AD. The price.

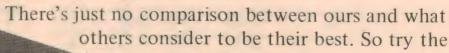Unlike other so-called "super premium" cassettes, AD's price is down-to-earth (that should make AD sound even better).



second best cassette

we've ever made - AD.

Available in: C45

C60

C90

C120





SOLE AUSTRALIAN AGENTS: CONVOY INTERNATIONAL PTY LTD 4 DOWLING ST WOOLLOOMOOLOO 2011 TEL 357 2444 TELEX AA23111

C1,P,2

# Power stations in space solution to the energy crisis?

enough off the ground for the area beneath it to be used for animal grazing or farming.

Microwave levels outside the antenna area and even beneath the antenna would be below the already stringent standards now in use in the United States. The beam itself would be of a low enough intensity to allow birds and other forms of life to pass through it without harm. The peak intensity at the beam centre would be far below lethal levels even at long exposure. It would have no effect on aircraft or their passengers.

"The construction of things in space the size of small cities is entirely outside human experience. But it is not beyond a reasonable extrapolation of the state of the art," says Boeing's official background sheet.

The satellites would be so large that 'they would have to be put together in space - either in low Earth orbit and then launched into the higher geosynchronous orbit, or else constructed directly at the higher orbit. The decision as to which is still under intense study.

The proposal is that large unmanned freighters, known as heavy lift launch vehicles, would carry outsize cargo pallets into low Earth orbit where these pallets would be deposited and directed to docking stations at a space construction base. These freighters would have to be entirely reusable and available for relaunch within a week to justify the economics.

Today's Space Shuttle Orbiter with minor modifications would be the backbone of the manned transportation system, carrying the several hundred men needed on the orbiting construction base.

Orbital transfer vehicles to carry men and equipment from near-Earth orbit to geosynchronous orbit would also be needed, as would propulsion units to carry satellites or their major segments to this stationary position.

In all, man may be shipping from Earth almost one million tonnes of hardware each year — an astounding amount. Engineers foresee the day, possibly within the next 20 years or so, when huge space freighters will be departing the likes of Kennedy Space Centre at a rate of four, or five - or even 10 - a day.

Far fetched? Yes, at first blush, but studies by Boeing and others show that no technological breakthroughs are needed for all this to come about, only a natural growth of today's technologies.

In fact, the greatest apparent stumbling block may be psychological, not technological. Ralph Nansen, Boeing Space-based Solar Power Program manager, calls it: "Concept shock."

Satellites the size of cities and the weight of battleships seem illogical. Launch schedules resembling airline timetables seem highly improbable. The manufacturing of complex structures from basic materials by hundreds of persons in space seems impossible.

But hardnosed engineering studies show that, while challenging, all this is technologically achievable within a

relatively short time.

In an engineering sense, Kubrick's "2001" is upon us. After all, 2001 is less than 25 years away, and for today's ideas to become reality in that time span, they must be visible on our drawing boards now.

The cost? We really don't know. Boeing and other manufacturers are currently attempting to determine this through government-funded and

company-funded studies.

We do know that, to be feasible, solar power satellites must be constructed and operated to allow amortization of their costs by the revenue collected from the users of the electricity they furnish.

Simple arithmetic shows that the revenue from one solar power satellite producing 10,000 megawatts of electricity sold at a rate of three cents per kilowatt hour would produce \$78.8 billion in 30 years. Forty-five satellites would produce more than \$3.5 trillion (three cents/kWh currently is the cost of electricity generated by new oilburning plants).

Of course, this is simple arithmetic, and such economics seldom are simple. Any power generator has times when it is not totally in service or is producing energy at a rate above that which is being purchased at the moment.

However, we do know that the cost of electricity produced from today's energy sources is headed only one way: up. As the cost of depleting fossil and nuclear fuels rises, so will the costs of power they generate.


Solar power satellites, on the other hand, may be expensive to bring on line but are not dependent on fuel costs. The Sun's rays are free.

A step-by-step studied approach to space-based solar power generation is needed. Boeing already has recommended in Congressional testimony that the US Government embark on a carefully phased plan which would progress from concept definition to technology verification to subscale demonstration. This would establish confidence that satellite power systems are technically and economically viable. Only then would the nation embark on the more expensive full-scale development.

As Jacques Cousteau, the French explorer, has observed, our present-day energy solutions either cheat on the past or cheat on the future. It is time we became honest with ourselves.

Photo below shows how 30 power satellites in geosynchronous obit would look, as viewed from eastern Washington.



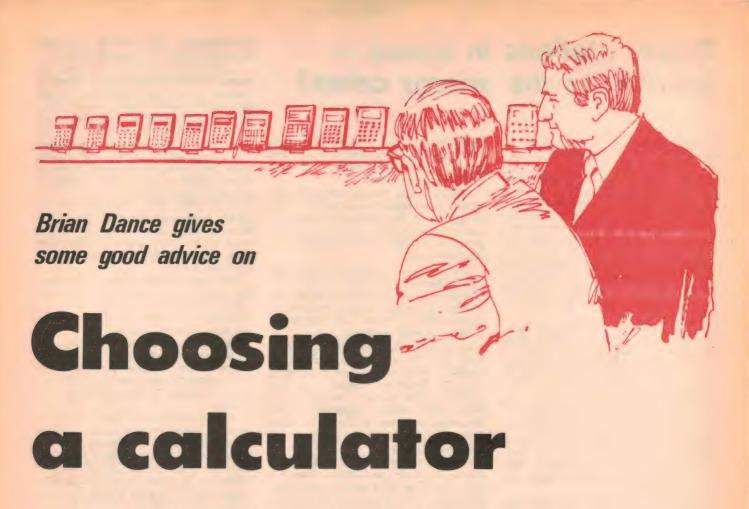

# ... a look at what's available and the things you need to know

The modern electronic calculator is a highly complex piece of equipment which can perform complex calculations very quickly and with great accuracy. However, there are now so many different types of calculator on the market that the selection of the type most appropriate to one's own particular requirements can pose quite a problem. This article has been prepared to help readers formulate the criteria they should consider when selecting a calculator.

An electronic calculator contains one or more lsi (large scale integrated) circuits of extreme complexity to perform the logic operations. In addition, the calculator must incorporate a suitable keyboard and a display (or possibly a printer). Even the display is more complex than one may think; when the instrument is just displaying a number, each digit is illuminated in turn at such a fast rate that the eye sees a continuous display.

This type of sequential display is necessary in order that an integrated circuit with a reasonable number of connecting pins (often 24) can be used to cause each digit to indicate one of 10

possible numbers and still leave enough connecting pins available for inputs from the keyboard, etc.

It is not so many years ago since the first electronic calculators replaced the large, noisy mechanical types of desk calculator. However, the early electronic types employed numerous digital integrated circuits and were therefore suitable only for use as large desk machines. The very rapid expansion of the pocket calculator market during the past few years has been made possible by work on lsi technology specifically for calculator use.

During the past five years, calculator prices have fallen by nearly a factor of 10. This is obviously due to the large market created by the falling prices, although prices are still tending to fall slightly even if one makes no allowance for inflation.

The early pocket calculators were simple four function machines, these functions being addition, multiplication, subtraction and division. Simple four function machines are now available at very low prices. At the

other end of the market, one can obtain complex programmable machines which can tackle problems for which a computer would previously have been required.

Indeed, the pocket or desk calculator has an advantage over a computer in that one does not have to learn a special programming language to use the instrument and one can feed the data in oneself; the disadvantages of a calculator are that the data and program memory stores are much more limited in volume that those of a computer and one does not normally have a fast line printer available.

IMPORTANT FACTORS: Perhaps the most important factors to be considered when choosing an economical calculator are (1) the type of power supply used; (2) the type of readout; and (3) physical size, layout of keyboard, personal preferences, etc. In the case of more complex calculators, there are many factors to be considered, such as the functions provided on the keyboard, the ease of programming, the size of the program memory, etc.

POWER SUPPLIES: The most economical types of pocket calculators are powered by small disposable "dry" batteries so as to keep the cost to a minimum. If such a calculator is used frequently, the cost of battery replacement will be fairly high because the current taken from the battery is typically about 100mA when all of the digits are glowing. However, the current is much smaller when only one digit is being displayed. These remarks are not applicable to the liquid crystal type of display which will be discussed shortly; indeed, the power supply requirements are very closely related to the type of display employed.

The typical operating time of a small calculator from disposable cells is around 12 hours. Apart from the cost, the necessity for replacing such cells can be a nuisance — especially if one does not have a spare cell at the time.

An alternative to the use of batteries is the use of a mains adaptor which usually consists of a small box with one lead going to the mains and the other to the calculator. The box contains a small mains transformer which, together with associated circuitry, supplies a low voltage to the calculator through a small jack plug. Such an adaptor can be used with many types of pocket calculators.

If the adaptor is an optional extra, it is normally well worth the extra cost unless one will be mainly using the calculator where no mains supply is readily available. In the case of desk type calculators designed mainly for use in an office, a mains power supply is almost universal. Mains power supplies are also often used with printing calculators, since they can easily supply the larger amount of power required by such instruments.

The most satisfactory type of power supply for a pocket calculator involves the use of nickel-cadmium rechargeable cells inside the instrument. It is unfortunate that such cells are quite expensive, but almost all high quality portable calculators incorporate such cells together with a mains adaptor for charging. A rechargeable battery pack and mains adaptor are available as optional extras with some calculators.

Nickel-cadmium cells should have a life of at least 500 charge-discharge cycles; so the extra cost is generally well worthwhile if one expects to use the calculator fairly regularly. The cells are automatically charged when a mains unit is plugged into the calculator; the time required for a full charge varies from one calculator to another, but is generally in the region of four to 12 hours. The calculator can also be used whilst being charged, although this does increase the time required for a full charge.

Excessive overcharging should be avoided, since this can result in the escape of gas from the cells with subse-

quent reduction in their storage capacity. The calculator should never be operated from the charger without the nickel-cadmium cells in position, as the supply voltage may be too large and the instrument may be damaged.

One should also appreciate that the time for which a nickel-cadmium cell can retain its charge is limited. A typical fully charged nickel-cadmium cell will lose about half its charge in two months, whilst very little charge will remain after a year. Thus regular charging is fairly important. The storage capacity of the batteries will, in any case, fall over a period of years.

Some calculators incorporate automatic switch off facilities in order to conserve the batteries. The display is automatically switched off about 30 seconds after the last entry is made on the keyboard, but the display can be restored for a further 30 seconds by operating a suitable key.

TYPES OF READOUT: Three types of visual display are used in currently available calculators. One of the first types to be used employed red light emitting diodes. The other type found in many cheap calculators employs a "Digitron" vacuum tube in which electrons cause fluorescence of a phosphor so that green light is emitted. Liquid crystal displays are generally somewhat more expensive than the other two types, but have the particular advantage that their power consumption is far smaller than that of either of the other types.

The digits used in the red light emitting diode displays are usually fairly small and it may not be easy to read them in bright light. However, such displays are very robust and reliable; indeed, as far as is known, the life of a light emitting diode display is indefinitely long. The digit height may be only about 3mm, but a magnifying lens is sometimes placed in front of each digit; this has the disadvantage that the field of view is restricted. Most of the more expensive programmable pocket calculators employ light emitting diodes in the display.

Green fluorescent displays employ digits which are generally larger than those used with light emitting diode displays. In addition, the green displays appear quite bright in a new machine, so they look impressive in a store.

Unfortunately the vacuum tubes used with such displays are likely to be broken if the machine is dropped. The Digitron tubes are also relatively expensive and fitting them can be quite difficult — a calculator with a broken tube is often just discarded. In addition, green fluorescent displays tend to fade over a period of a few years.

So if you expect a calculator to last for a long time, it may be wise to choose another type of display!

Green fluorescent displays require more current than most light emitting diode displays, but one should remember that a calculator with a



The HP-21 scientific calculator from Hewlett-Packard features Reverse Polish Notation.



This low-cost scientific calculator from Unitrex retails for around \$15.00.

bright display will normally consume a larger current from the battery than an instrument with small, less bright digits. After all, the light energy can come only from the battery. Many desk machines employ large green fluorescent digits, but as they are operated from the mains supply, the relatively large current consumption is unimportant.

Liquid crystal displays require a current in the microamp region, so a cheap disposable battery can last for a very long time. Indeed, the life of the battery may be virtually equal to its shelf life and one may forget to remove it after it has started to leak. Some calculators using liquid crystal displays therefore employ miniature silver oxide cells. In some cases the cells

provide a life of some 3000 hours of normal use.

As the power cells used with liquid crystal displays can be quite small, this type of display is usually employed in very thin calculators (perhaps only 5mm in thickness) which can be fitted into a small carrying wallet and not make one's pocket bulge. The life of liquid crystal displays has been somewhat suspect, since any electrolysis can damage the cells, but current types appear to have a much longer life than the early types used in watches. This type of display also has the disadvantage that a fraction of a second elapses before the display is clear.

Liquid crystal displays do not emit any light and therefore cannot be seen in darkness; they merely reflect different fractions of the incident light from various parts of the display. Unlike



Novus Mathematician PR, a specialist calculator from National Semiconductor



The now famous HP-65 programmable pocket calculator. Magnetic cards enable it to use pre-recorded programs.

the other two types of display, though, liquid crystal displays are easily read in bright sunlight. Note that liquid crystal properties suddenly disappear above a certain temperature (about 40°C), but reappear on cooling.

PRINTING CALCULATORS: Most printers are relatively large and have in the past been confined to desk-top machines. Recently, however, a pocket calculator with a printer has come onto the market. Although the "hard copy" provided by a printing calculator is very useful, printers are relatively slow, require considerable operating power and are relatively expensive. Most types operate with a roll of paper 75mm in width.

NUMBER OF DIGITS: Almost all calculators have a display which shows eight significant figures. A few of the earlier types had a six-digit display, whilst some of the more expensive types show 10 significant figures in addition to any of the exponential digits to be discussed shortly.

Four types of display may be used, namely "fixed point", "floating point", "exponential" (also known as "scientific") and "engineering".

In the fixed point display, the decimal point is fixed in position. This is convenient for financial calculations where one may require two digits after the decimal point to show the number of cents. Any further figures may be used in the calculation, but are automatically rounded off to the nearest cent. Some of the higher quality calculators have a facility whereby the number of decimal places in the fixed point mode may be set to any required value.

The type of display most commonly used in pocket calculators is known as a floating point display, since the decimal point automatically moves to any part of the display so that as many significant figures as possible are shown. If a small number is to be displayed, the decimal point is at the left hand side, whilst if a large number is to be shown the decimal point moves towards the right hand side so there is space for quite a number of digits in front of the decimal point.

In the "exponential" or "scientific" display, an extra two digits on the right hand side of the display show the power of 10 by which the number must be multiplied. A number such as 3.24 x 10<sup>74</sup> is displayed as 3.24 74. The greatest number which can be handled is just a little less than 10<sup>100</sup>. This type of display can also handle very small numbers, 6.8 x 10-86 (for example) appearing in the display as 6.8-86. A calculator equipped with this form of display will

automatically switch over to it when the quantity to be displayed is either too large or too small to be accommodated on the floating point system. Ideally the calculator should automatically return to the floating point display when the number to be displayed can be accommodated in this form.

In the "engineering" type of display, the exponential digits are always a multiple of three. For example, if one has just calculated a capacitance of 2.34 x 10-10F, this will automatically be displayed 234-12 so that one immediately knows that the result is 234pF. The writer feels that this form of display is no great advantage over a normal exponential display, since it is so easy to convert to the normal engineering form.

Most scientific calculators display eight digits as the mantissa plus two exponential digits. However, another type of display can accommodate eight digits which completely fill the display space; if the number to be displayed requires an exponential form, the number of digits in the mantissa is reduced to a maximum of five or six so that the two exponential digits can be accommodated on the right hand side.

The earlier Texas Instruments pocket calculators displayed 10 digits plus two exponential digits. Changes have been made to later models, however.

The TI-57 displays only eight digits in the floating point mode and eight digits plus two exponential digits in the exponential mode. The more sophisticated TI-58 and TI-59 calculators have a 10-digit floating point display available when no exponential digits are required, but for very large and very small numbers this 10-digit display is converted into an eight-digit mantissa plus two exponential digits!

The extra two digits can then be found by multiplying the displayed number by a suitable power of 10 to obtain a 10-digit display.

ACCURACY: In very simple calculations, such as addition, the calculator will usually give the answer as accurately as possible with the available display. However, all calculators show some errors when one uses trigonometric functions (especially in the degrees mode) and there may be some errors when using exponential and logarithmic functions.

High quality calculators work to a greater number of figures than those shown in the display; for example, an instrument which displays eight digits may calculate to 11 digits and round off the calculated result to the nearest eighth digit. The use of the extra digits (known as guard digits) greatly increases the accuracy of a calculator.

If one is considering the purchase of a medium priced calculator, it is well worthwhile testing for the rounding off facility. If, for example, one enters five and divides by three, the result 1.666666 is displayed. If one now multiplies the result by three, a cheap calculator without any guard digits will produce the result 4.999998 instead of five. However, any good quality instrument will produce the result five owing to the presence of one or more guard digits.

A more complex test is required to check the accuracy of a high quality calculator. One may, for example, put the machine in the "degrees" mode and enter a certain number of degrees. One then successively operates keys such as sin, cos, tan, tan 1, cos 1 and sin 1 so that each operation is cancelled by an inverse operation. Ideally this should result in one obtaining an answer equal to the number of degrees with which one commenced the calculation.

In the highest quality calculators, one may expect an error of the order of three parts per million, but some fairly good machines will produce errors of the order of 100 parts per million. The errors increase rapidly as one approaches 90° as the figure with which one commences the calculation.

Whilst carrying out this test, it is well worthwhile noting whether each of the answers appears without any delay, since some machines calculate much more quickly than others. If one attempts to enter a number whilst the calculation is still in progress, the new entry will be ignored and this could cause confusion. A slow calculator can cause problems and this would obviously be greatly accentuated in a programmable instrument where a whole sequence of operations must be performed.

CALCULATOR LOGIC: Almost all cheap calculators use an "algebraic" logic system in which one enters a problem more or less as it is written. For example, if one wishes to divide seven by three, one presses the four keys 7 ÷ 3 = in that order. The answer then appears virtually immediately. However, problems can occur with simple algebraic logic even when the problem is simple.

For example, if one enters  $1 \times 2 + 3 \times 2$ , one may hope that the calculator will perform the two multiplications before the addition so as to produce the answer 8. However, most cheap calculators will first multiply one by two and then add three to produce five before multiplying the last figure by two to produce a final answer of 10.

This trouble can be avoided by using a calculator employing an "algebraic logic system with hierarchy" in which multiplication and division are given priority over addition or subtraction.

The "Algebraic Operating System" or "AOS" used in Texas Instruments machines employs a particularly comprehensive hierarchical system. Trigonometric, hyperbolic and logarithmic functions which involve only a single variable number are evaluated first, followed by power



SR-51 and SR-50A scientific calculators from Texas Instruments. Both feature scientific notation with a 10-digit mantissa and an exponent up to plus and minus 99.

calculations and root extractions (y<sup>x</sup> and x<sub>y</sub>y). These are, in turn, followed by multiplications and divisions, with additions and subtractions performed last of all. This system enables the problem to be entered into the calculator almost as it is written down.

Brackets can be employed to change the normal order of operations. On a calculator with brackets, the problem discussed above could be entered as 1 x  $2 + (3 \times 2) =$ to ensure that the final multiplication would be completed before the addition. It is not necessary to place the first two items in brackets. since this multiplication will in any case be carried out as the first operation. Brackets are also known as parentheses, each item within brackets being regarded as a separate calculation in itself which must be evaluated so that the result can be used in the main calculation.

The use of brackets involves the storage of numbers. If, for example, we consider the problem  $2+4\times(3-2\div(5-2))$ , the initial 2 is stored with the + sign so that the addition can be carried out later. Similarly the  $4\times$  must be stored until the contents of the next bracket have been evaluated. In addition, the 3- must be stored and the first item to be evaluated is the innermost bracket, namely 5-2.

The fact that brackets involve memory operations implies that the number of brackets one can place inside other brackets is limited; the number of levels of nested parentheses (or brackets within brackets) may be 10 or 15 in some programmable machines, but in some relatively economical calculators, brackets are not permitted within other brackets.

REVERSE POLISH NOTATION: Another logic system which was widely used in some of the earlier scientific calculators, and which is favoured by Hewlett-Packard in their high quality instruments, is known as Reverse Polish Notation or RPN. The main difference between this type of logic and the algebraical systems discussed previously is that in RPN the operator key is pressed after both numbers have been entered.

Thus to multiply 2 by 3, one can press the four keys: 2 enter 3 x and the answer appears immediately after the operator key is pressed (x in this case). The "enter" key signifies that one has completely entered the first number and that the next digit will be part of the second number. Sometimes the enter key is marked with an arrow pointing upwards.

There is no = key on an RPN machine, so this can be used to distinguish the type of logic used. Brackets are not used in RPN. Both RPN and the algebraic system have their own advantages for certain types of problem and any user will quickly learn to use either system.

Basically, RPN machines solve the problems in the same order as they would be worked out by a person, starting with the innermost bracket; this is not the order in which the problems are written down. One of the advantages of RPN is that intermediate results can easily be inspected and corrected if necessary before the remainder of the



# **ESSOR STORES**

Build your own computer with components from Silicon Valley.

Silicon Valley are professional microprocessor stores carrying microprocessor kits from Motorola, Texas Instruments, AMI. Intel. National Semi-Conductor and Synertek; displays and monitors from Motorola, Burroughs and Elcoma; magazines which include Byte, Interface, Kilobaud and Dobbs, etc. Components such as ROMs, PROMs, EROMs, RAMs, UARTs, Registers, Multi-placers, OP Amps, LEDS, CMOS, S/TTLs and LS/TTLs. All this complemented by supporting software and in-store

Quality products backed by Cema experience. Cema, one of Australia's

programming.

leading suppliers of industrial microprocessor components, have backed Silicon Valley stores with experience and quality products normally available only to industrial buyers. Silicon Valley stores are stocked with necessary literature, books and a complete line of accessories.

Professional assistance and guidance.

Silicon Valley stores have a team of technical experts ready to assist you with any microprocessor problem. Beginners are welcome and kits are available to get you started on building your own micro-computer. Expert guidance is available on advanced projects, peripherals and software. Silicon Valley is the one shop for all your microprocessor needs.

Magazines

Current issues: Byte, Kilobaud and Interface all \$4.00 ea. Plus extensive range of handbooks, manuals, and microprocessor data.

Microprocessor Kits

6800D2 Motorola Intel SDK85 SC/MP National 2650 Signetics

Supported by at least 2,500 line items of semiconductors. from Motorola, Texas Instruments, Solid State Scientific, Harris, Unitrode, Signetics, Philips, American Microsystems, Precision Monolithic, Synertek and Litronix.

YOUR ONE STOP MICROPROCESSOR STORE

SYDNEY:

23 Chandos Street, St. Leonards, Tel: 439 2965

MELBOURNE:

380 Bridge Road, Richmond, Tel: 429 4780

AUCKLAND N.Z.

7-9 Kirk Street, Grey Lynn. Tel: 76 0019

calculation is completed. Intermediate results are stored in a register stack.

**PROGRAMMABLES:** A programmable calculator will store a set of instructions containing the information about the calculations it will be required to perform. If, for example, one wishes to calculate  $x^2 + 1/(e^y+1)$  for many different values of x and y, one could instruct the calculator to store the first number (x) fed into it and, after the second number (y) has been fed into it, the calculator can be instructed to compute the required function.

When the calculator has memorised the instructions, one merely enters the value of x, presses the program "run" key, enters the value of y and then presses the "run" key again. The value of  $x^2 + 1/(e^y + 1)$  will appear in the

display.

It can thus be seen that one of the main advantages of a programmable calculator is that any number of similar calculations can be performed when the instructions have been entered only once. A programmable calculator can also be used as a normal calculator whilst retaining the program instructions which have been fed into it.

It is clear that programmable calculators are very useful when one wishes to perform many similar calculations of the same type; apart from the fact that one only has to enter the operations once, one eliminates the possiblity of errors which could occur if one had to operate the individual keys each time one fed in a new set of numbers. However, the ability to perform repetitive calculations is only one of the advantages of a programmable calculator.

Almost all programmable calculators have conditional branching facilities which enable them to work in closed loops. The program works along a certain list of instructions until it comes to a conditional instruction such as "GO

TO 64 if x>y."

In this case if x is greater than y, the program execution will move to position 64 in the program memory and continue from there onwards until it comes to the same conditional test again. It will continue working around this loop until x no longer exceeds y, whereupon it will ignore the GO TO instruction and come out of the loop.

The simple example we have chosen includes a direct conditional address where the program is instructed to move to a definite place, namely step 64. However, it is also possible to have indirect addressing in which the program is instructed to move to a program location stored in a particular memory register. This stored number can alter during the execution of a

program and so the program can be instructed to move to different places at different stages of the program.

Other methods of transferring the program execution point are also available in some calculators. For example, one labels a point in a program by a symbolic label name, such as "A". One can incorporate an instruction "If a flag is set at a certain point, then transfer

the program to point A."

Another facility which adds greatly to the power of a programmable calculator is the "isz" (increment and skip on zero) or "dsz" (decrement and skip on zero) key. The program passes around a loop and each time it passes this key a memory register is increased or decreased by unity until the contents of this register become zero. The branching instruction that follows the key is then skipped and the program comes out of the loop.

Thus, by entering the appropriate number into the register before the calculation commences, the program can be made to pass around the loop any desired number of times.

Programmable calculators provide a means of quickly evaluating polynomial expressions and for carrying out many iterative procedures. Indeed, when used intelligently, they have an enor-

mous potential.

PROGRAM SIZE: The complexity of a calculation is limited by the amount of memory or storage space in a programmable calculator. The size of the memory is normally expressed as the number of program steps which can be stored, although this is not a very satisfactory way of quoting the maximum program size. Many high quality calculators have facilities whereby certain sequences of key steps occupy only one space in the program memory so that the memory in such machines is effectively much larger than one might expect from the number of key steps.

A typical programmable calculator is about three times the price of a good quality "scientific" non-programmable instrument, but provides far greater calculating power. The smallest programmable calculator currently available has a 36-step program memory; although the programming facilities of this Sinclair instrument are rather limited, one must remember the price is about one half to one third that of other programmable machines.

Pocket calculators having 72, 100 and 224 memory storage steps are common, whilst desk machines often have 500 to 1000 steps with the option of additional memory space. One should remember that it can be tedious to check a program having hundreds of steps if one does not have a printer available,



The CZ8100, a low-cost easy to use scientific calculator from Sanyo.



Another low-cost scientific calculator from Unitrex, the 901SN.

and the printer is likely to cost twice as much as the calculator itself.

If one has a long program, it requires some effort to enter it into the program memory using the keyboard. Unfortunately the program is lost in most machines as soon as the power is switched off. However, a few calculators have a "non-volatile" or "continuous" memory which retains a program even after the calculator is switched off.

Examples of instruments with a non-volatile memory are the Hewlett-Packard HP-25C, their new HP-29C, and the HP-19C pocket model incorporating a printer. The new National Semiconductor 7100 model will also have a non-volatile memory.

The CMOS memory used in such models consumes a negligible amount of power so that the rechargeable battery pack can ensure that the program is stored for an indefinite time. The ordinary data memories of





BWD539D Dual Trace DC—25MHz-3db 5mV sensitivity Colour TV, C.B. Radio, µ-Processors, Video & audio recording.

# BVD ELECTRONICS PTY. LTD.

Miles Street, Mulgrave, Victoria, 3170 Telephone 561 2888. Telex 35115 BWD540 Dual Trace DC-100MHz -3db 5mV sensitivity 5nSec. sweep speed

Computers, µ-Processors, Research and development, Field service



BWD504 DC-6MHz 10mV sensitivity Education, Hobbyists, X-Y monitor

N.S.W. Amalgamated Wireless (A'asia) Ltd., Sydney. Phone 888 8111

QLD. Warburton Franki (Brisbane) Pty. Ltd., Phone 52 7255

S.A. Protronics Pty. Ltd., Adelaide. Phone 51 4713
Rogers Electronics, Adelaide. Phone 42 6666

W.A. Cairns Instrument Services, Perth. Phone 25 3144

TAS. Associated Agencies Pty. Ltd., Hobart. Phone 23 1843

these machines can retain data even after the calculator has been switched off.

If one wishes to keep a program for later use without having to go to the trouble of entering all of the key steps again, one should consider obtaining one of the magnetic card programmable calculators. In most of these instruments a small magnetic card (rather like a credit card in shape and size) is drawn into the calculator by an electric motor and the stored program is magnetically recorded onto the card. When one wishes to use the program at some later date, the card is again passed into the machine. The program is then read into the calculator memory whilst still remaining recorded on the card for further use.

Magnetic card programmable calculators are very convenient to use and one can keep a small library of programs available on cards. Cards can be purchased with programs already recorded on them. One of the main disadvantages though is that magnetic card programmable calculators are about three to four times the price of a similar calculator which is only key programmable. The program storage process also takes a considerable amount of power.

The Casio PRO fx-1 machine is a card programmable calculator in which the card is passed across the reader by hand rather than by means of an electric motor; it is thus more economical than most other magnetic card programmable instruments.

An interesting development from Texas Instruments is used in their new TI-58 and TI-59 calculators. Small modules about the size of one's thumb nail can be plugged into these calculators and provide as much program material as can be accommodated on many magnetic cards. Unfortunately only programs recorded during the manufacture of the modules can be made available at present in this way. A single module contains 5000 x is bits of read-only-memory which is equivalent to some 5000 program steps, all of these steps being available through the keyboard as sub-routines, etc.

PARTITIONABLE MEMORY: The TI-58 and TI-59 calculators have another unique facility, namely a partitionable memory. This type of memory can be divided between program steps and data storage according to the requirements of any particular problem. When first switched on, the TI-58 provides 240 program steps and 30 memories, but memories and program steps can be interchanged on the basis

of 80 program steps being equivalent to 10 memories. Thus one may have 60 memories and no program steps, 50 memories and 80 program steps, 40 memories and 160 program steps, etc.; or even 480 program steps and no memories.

The still more powerful TI-59 has 60 memories and 480 program steps when switched on, but one can have 960 steps and no memories, 160 steps and 100 memories, or some other combination.

The facility to partition the memory between program and data storage greatly increases the versatility of a calculator. One can handle many data points with a simple program, or a few data points with a program which can be very complex.

POSSIBLE DEVELOPMENTS: Pocket calculators have developed extremely rapidly during the past few years and it



The state of the art: combined scientific calculator and digital wrist watch from National Semiconductor.

seems likely that many more advances are yet to come.

One of the limitations of present machines concerns the limited amount of data which a calculator can display at any time. One wonders whether there will not be some facilities on calculators of the future to enable them to be coupled to a television screen display.

Data could be modulated onto a radio fequency carrier which could be fed into the aerial of a television receiver. The amount of data on a single display could be quite large and graph plotting, etc., may be possible.

At the present time, magnetic cards offer the best form of long term program storage, but there is certainly a need for a less expensive technique for use with pocket calculators. It remains

to see what new techniques are eventually developed.

It seems certain that more calculators in the future will have non-volatile memories, but this enables only one set of program steps to be stored at any one time. It may well be that more plug-in modules will become available, for use with certain calculators, which contain a large selection of programs for use as subroutines. Both the new National Semiconductor calculators have plug-in facilities for program modules.

SOLAR CELLS: One unusual type of calculator requires no mains supply and contains no batteries, since its liquid crystal display is operated by light falling onto an array of solar cells at the top of the front face. This "Solar 1981" model made by Imperial Business Equipment Ltd of Leicester, England, has 36 solar cells, but is a simple model without any trigonometric or special mathematical functions. Although its price is considerably greater than that of other general purpose calculators, the savings on battery costs over a long period should be considerable and one never has to remember to recharge or replace a battery. Perhaps some sophisticated solar cell calculators will emerge in the fairly near future.

Calculators are also emerging in new forms and one of these types can be strapped to one's wrist like a watch. One very cheap wrist calculator with eight digits and a memory is available in Europe, whilst Hewlett-Packard have introduced a calculator/wrist watch in the USA at about US\$650; it will be available throughout the world later this year. This Hewlett-Packard HP-01 instrument has six finger-operated keys and another 22 "keys" operated by means of a stylus.

The HP-01 incorporates an alarm, timer-stop watch, a digital watch and the various functions can be combined in interesting ways to do such things as continuously display the increasing cost of a telephone call with time, store a telephone number, show the number of days between any two dates, etc.

A very small calculator has been made available in the USA in the form of a ball-point pen, and it seems likely that various other forms of miniature calculators will come onto the market. A crystal controlled calculator, stop watch and alarm clock is available from Casio as their CQ-1, the timing accuracy being ±3 minutes per year.

Some calculators have been developed which can calculate in fractions and display fractions in their readout, but it seems doubtful if there will be a great demand in the future for this particular facility.

The writer is indebted to Mr Peter New of Taylor-Wilson Systems Ltd of Solihull, Warwickshire, England, B93 8HQ for assistance in the preparation of this material.

# **BASF Ludwigshafen** is really big!

BASF is one of the industrial giants of Europe and its factory complex at Ludwigshafen is the largest in Europe - or near to the largest - depending on which statistics one chooses to quote. From Ludwigshafen comes a huge range of products including raw materials for the one for which BASF is best known amongst E.A. readers — BASF magnetic recording tape.

by NEVILLE WILLIAMS

Although BASF has been marketing its products in Australia for many years through distributors, it has only just recently set up its own Australian subsidiary, with operations currently centred in Melbourne and Sydney.

In setting up the new local subsidiary, one problem which faced Australian Managing Director Ross Whoell was that of getting across to Australians the true size and resources of

the company behind the name BASF

As Ross explained to the writer, BASF was well known in Australia as a manufacturer of high quality magnetic tape but, for many customers, the image stopped there. They did not know that the company was active in Europe in audio/video/computer hardware, as well — let alone the fact that the entire "electronic" activity was but one facet of a company with huge manufacturing, research and develop-

Learning the writer would be in Europe on holiday, Ross Whoell suggested as a "must" a visit to BASF. It was largely as a result of this, that I found myself in the Excelsior Hotel at Ludwigshafen on the Rhine, with a view over a mushrooming post-war pattern of rail lines, expressways and bridges and, in the somewhat murky distance, the huge BASF complex of factories and chimney stacks.

Murky distance?

A couple of weeks earlier, on a boat trip along the Rhine, the air had been clean and the sun had shone brightly but, in the dead calm of an autumn day during this second visit, the atmosphere was heavy with smog, at least as heavy as anything I've seen in Japan, Los Angeles - or Sydney!

My host for the visit, sales engineer Hinrich Spuhler hastened to assure me that very little of the smog could be attributed to the BASF complex despite its concentration and size, in a huge triangle embracing an area of 21/2 square miles and stretching for 31/2 miles along one bank of the

Rigid controls had virtually obviated harmful discharges into the atmosphere, while the Company's huge water purification plant, and an artificial river harbour to accommodate barges handling chemicals were not just preventing pollution; they were making a positive contribution to the purity of the water in Europe's busiest river, leaving it cleaner than they found it.

But, leaving aside such peripheral matters, a visit to BASF's Ludwigshafen complex is not just a matter of donning a regulation safety helmet and setting out on foot with a guide; it is much too large for that, unless you have a lot of

time and energy to spare.

The first stop is at a large landscape model in the fover of the administrative building, where the Ludwigshafen complex is revealed as a self-contained city of factory buildings, with a maze of internal streets and rail lines, its own amenities, medical and emergency services, and its own fully equipped fire brigade with a half-dozen or so tenders standing at the ready.

Strangely (for Europe) discarding metric terms, the handout literature points out that 56 miles of paved roads thread their way between 1500 permanent factory buildings, along with 120 miles of standard gauge rail track, 1160 miles of overhead pipelines, 220 miles of buried pipes, and 1438 miles of underground electrical cables. The plant absorbs about 1.3 million tons of fuel per year and uses 5250 million kWh of electricity, to produce 5000 product lines, aggregating eight million tons per year by weight. Almost half of the total inward/outward tonnage is carried by Rhine

But, immense as they are, the Ludwigshafen works are still growing, spreading into the rural land at the large end of the triangle, and also nibbling at the residential fringe to provide access, amenities and parking space for the 50,000 employees in this one complex.

Reverting to the model, the guide pushes buttons, in turn, which light up buildings throughout the site concerned in the manufacture of a few major product lines — these by way of example.

The patterns of light are seemingly random for each product line but the guide explains that this is due to the fact that individual chemicals can be the starting point of or involved in - a variety of different activities and that processes have been added over a period of many years. The dispersion and the varied array of buildings and structures along the factory streets is therefore partly the result of planning, partly of natural growth.

However, every effort is made to minimise the separate handling of chemicals from building to building and anything that can be piped from point to point is moved in that fashion. Not surprisingly, therefore, there are pipes overhead running in all directions, each painted in a distinctive colour to give firemen or other emergency teams some clue as to what is being carried inside.

To see the actual buildings and structures displayed in the model landscape, one has to board a company coach and be driven slowly along the streets - just as one might do a "city tour" anywhere in the world.



An aerial photograph of the BASF works at Ludwigshafen. The plant occupies most of the area covered by the photograph, and includes the artificial harbour at lower right. It employs 50,000 people, produces more than 5000 different sales products, boasts 56 miles of paved roads and 120 miles of standard gauge railway track, and consumes 5,250 million kWh of electricity each year.

The guide goes into his accustomed patter — facts, figures and well rehearsed quips, providing the continuity between reference to the installations on either side: "the building on the left is the heart of the . . . making plant. Of course, I could say we make dynamite in there, and you'd be none the wiser . . ."

Unless one happens to be a chemical engineer — and I do not — that last phrase is more a truism than a quip. One could recognise some installations; for example, the distinctive stain on the drums is sufficient to indicate the production of indigo dye, one of BASF's earliest activities, dating back to last century. But the hundreds of other buildings could as easily be devoted to the production of dynamite or hashish!

Nor is one necessarily much wiser after a visit to one of the many process control centres: row upon row of knobs, buttons, meters and pen recorders tracing out green graphs—electronic gadgetry that is at the one time familiar, yet no less inscrutable than the mountain of pipework outside that it monitors and controls.

But, overall, the prevailing impression that comes through to the visitor is the sheer scale of the BASF operation at Ludwigshafen — enormous by any standards — and larger than most people will ever be likely to see.

To get back to more familiar ground — BASF magnetic recording tape — the production and quality control of

such a product would appear to be no great problem for such a complex. In fact, however, the actual manufacture of coated tape, compact cassettes, video cartridges and reel tapes for audio and computer application is concentrated at an entirely separate factory at Willstadt — some 60km from Ludwigshafen. In the Black Forest area, the atmosphere is substantially free of the pollution that plagues the Rhine Valley and it is much easier to ensure that the only particles which are deposited on to the tape are the ones that are meant to be!

But the Ludwigshafen works are significant in another way to BASF activities in the tape and EDP field. Heinz Ritter, export manager for BASF EDP Productions, pointed out to me that the works provided a full-scale living laboratory in which his department could test EDP methods and systems. With a huge staff and wages bill — over 50,000 employees at Ludwigshafen alone — highly complex stock movements, and a proportionately large financial turnover, methodology was more likely to be scaled down to typical user needs, rather than up.

In developing new systems, BASF's EDP Department was able to operate in parallel with the Company's main computers to assess how the performance compared with that of an existing system.

(The manufacture of magnetic recording tape in the Willstadt factory will be described in a later issue.)

WIN A TRIP TO THE SOUTH POLE. FULL DETAILS IN OUR OLD FASHIONED CHRIST

# ANY MISCONCEPTIONS




# BOUT CASSETTE

To get a quality cassette tape you have to pay high prices, right? WRONG! Have a look at the cassettes below. They're Dick's own brand - he had them tested and believes they are equal, if not superior, to any of the 'quality' tapes around the place selling for much more - including TDK, BASF, Hitachi, Opus, etc etc . . .

THE GRAPH IS SHOWN BECAUSE WE ARE PROUD OF THE FACT THAT OUR CASSETTE TAPES COMPARE FAVOURABLY WITH BOTH HITACHI UD AND TDK SD. ALL WE ASK IS THAT YOU TRY ONE OR EVEN A DOZEN AND LET YOUR EARS DETERMINE WHAT WE ALREADY KNOW!!!

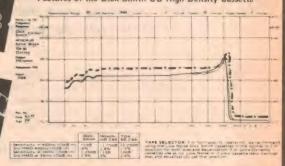Features of the Dick Smith UD High Density Cassette



(Dot and dash upper line represents Dick Smith UD tape)

YOU BE THE JUDGE: Try a few of these superb cassettes yourself. We know you'll agree that they are the equal of those cassettes you've been paying dollars more for. BUT! If you do not agree that they are all we claim, return them within 7 days with cash dockets to the point of purchase and

WHEN YOU'VE TRIED THEM AND WANT TO COME BACK FOR MORE, NOTE OUR SPECIAL PRICES FOR BULK ORDERS.....

C60 Low Noise.

C90 Ultra Dynamic.

Cat. C-3350. C90 Low Noise. Cat. C-3352.

Cat. C-3354.

Ten or more: \$1.50. Ten or more: \$1.99.

Ten or more: \$2.50.

TO ALL OUR CUSTOMERS & FRIENDS -

From all at Dick Smith **Electronics** 

# POWER MIC VITH ALC



What's better than a power mic? A power mic with Auto Level Control (ALC), A real boon in cutting down over modulation, one of the big causes of TVI! Comes with cord, slider control. Cat C-1108

# VISCAMP

MICROCOMPUTER

LOOK!

 $\mathbf{z}$ 

J

П

S

IJ

P

П

 $\mathbf{z}$ 

AND WHEN YOU'RE THROUGH PLAYING GAMES:

yourself the new Miniscamp, the brilliant microcomputer is within everyone's reach. Just 1/3 the price of the and potentially more powerful! You can really learn computers with this one - and in today's world, that's a skill that will take you a long, long way

0

with superb veneer base and acrylic cover, plus quality mag. cartridge all for \$135.00! Should be \$181, but our introductory special is just \$135.00! Cat A-3070



tenna adaptor

So you went and bought one of those small Australian antenna bases and find now that all those standard base antenn as won't fit! No worries! We now have a to 3/8" adaptor which will let you use any standard antenna - clever! Now there's no need to be tied to one brand of antenna - or one type. Go to the accepted standard 3/8, 24 TPI base - it's more versatile. Cat D-4504

We still have a few of the original FIBREGLASS printed circuit boards left for the 3.5MHz exciter project. If you want to build your own transmitter, grab one now before they go!

Cat H-8894 .. F'glass \$6.00

otographic Reflector

bought too many reflectors for our strobe kits. So you benefit! Use them for almost

See eti top projects book for original strobe project

Great for experiments! Use these fantastic little transducers for all sorts of control & communic ation circuits. (See EA Feb '74). Not many left - be quick!

Trans: Cat L-7050 \$6.95 Rcvr: Cat L-7052 \$6.95

## BEFORE COPIED!!!!

This fantastic helical antenna is SLUG TUNED that means you don't have to snip bits off it to SWR it Also, it's fully moveable from car to car (because of the slug tuning). The adjusting nut is simply turned for best SWR! So simple! Standard 3/8" 24TPI base, so you can throw away your old antenna and replace it with one of these! Don't buy one of the OLD SUPERCEDED HELICALS Insist on the slug-tuned!



Lge. Cat H-3740

REALLY BEAUTIFUL KNOBS they really make any unit look so-o-o good! These knobs are fully imported by Dick - and they are exclusive! If you want to give that amplifier a million dollar look

Also available: Extra large size Same as others, Cat H-3744 \$1.20

put some of these knobs on it!

**EMCO UNIMAT** 

203 Wright St

MAIL ORDER DEPARTMENT: PO Box 747, Crows Nest, NSW.

709-6600 Parramatta. Ph 683-1133 Gore Hill. Ph 439-5311
Thursday Now Open Aronica.



# Is it just trendy to listen to FM?

AM broadcasting need not be the poor relation of FM, according to a reader from the Australian National University in Canberra. If the hifi industry was to apply itself to the task, AM radio could be developed and promoted to a much more important role in the scheme of things.

The item which prompted this retort appeared in "Forum" for September under the title: "Is AM to remain the poor relation?" Perhaps the key paragraph read thus: "AM, on the other hand, has had its day of glory and is now filling mainly a utility role: news, current affairs, sport, talkback, pop music and background music, with a relatively small number of culturally based programs."

To this our correspondent replied:

I read with interest the letter from LJ and your reply about medium wave AM.

While it is true that AM has had its "day of glory" and that FM has upstaged AM, this is not entirely due to the superior audio and interference immunity qualities of FM. It is also more trendy to listen to FM and to extol its virtues!

That there is little pressure from consumers for better AM is no argument for lack of action from manufacturers. The assertion that the consumer is sovereign perpetuates the myth that there is a free market. Today, the situation is a complex interaction between advertising and consumer choice, amongst other variables. Therefore it seems to me, that if the electronic industry wanted to, it could promote AM and create a new market for itself. The promotion would probably have to be on a large scale, including press releases, so that promotion gets into editorial space.

Personally I still listen mainly on AM. I use a wide-band tuner designed by EA back in the fifties. It uses valves, a band-press aerial filter and band-pass first IF transformer and a switched in/out ordinary narrow band second IF transformer for variable selectivity. I shaped the pass-band of the first IF transformer by inserting IpF top coupl-

ing into an ordinary IF transformer. This achieved a more fixed pass-band shape across the tuning band than the arrangement you originally had. In the future I intend to connect the selectivity switch to switch top coupling in and, out the second IF transformer to try to lessen the gain change between the two selectivity positions.

As it is, I get good audio quality from wide-band AM. It's virtually indistinguishable from FM. My 10kHz whistle filter is always in, so no whistle is bothersome. These days there are ceramic IF filters and ICs. In fact EA has a wide-band tuner of much more recent design than mine using ceramic IFs.

All in all I can't understand why manufacturers haven't jumped in on a hard sell of "wide-band AM" as a means to sell more radio sets. If AM stereo is developed they would have even more scope.

As for interference, Telecom have long standing tricks to beat the manmade variety. These EA also published back in the fifties and they are still valid.

VB (ANU CANBERRA)

Perhaps there is some justification in our correspondent's observation that it is "trendy" to listen to FM, and trendy

## QUIET DAY IN NSW

It happened after our November issue was printed but before you had time to read it.

October 21 was nominated by the NSW State Government as "Quiet Day". The first such day in Australia, its purpose was to draw public attention to the problem of noise pollution.

And, guess what was demonstrated: A gadget which would silence a PA system automatically if an acceptable sound level was consistently exceeded.

to own an FM tuner that costs the earth and has "state-of-the art" specs. I have certainly not noticed any special modesty on the part of FM devotees and, if one was at all sensitive in this area, one could be excused for feeling that there is a certain amount of "keeping up with the Jones's".

However, one of the less fortunate overtones of the word "trendy" is the implication that it is the strongest reason for something being so. It may thus be trendy to wear long hair or short hair — without the need for any other or logical reason for so doing.

But it would be selling FM short to conclude that the world-wide swing to FM was merely, or even substantially, a matter of fad and fashion. Maybe such an element is present, and ably exploited by industrial stylists and advertising copy writers, but it is also a fact that FM has some very practical things going for it: lower noise, reduced interference and distortion, wide frequency response, balanced stereo and even matrix quad.

Similarly, if it is trendy NOT to listen to AM, the reaction would be reinforced by its very real technological limitations.

Nevertheless, without being quite as enthusiastic as our correspondent, I must agree with him that AM reception could be — and should be — a lot better than it is for a lot of listeners, and it is encouraging to read his appreciation of our own efforts.

It might also be conceded that the plight of AM radio around the world is, in part, due to (for AM) an unfortunate sequence of events. In the very early days of broadcasting, AM gained the ascendency and dominated the scene until the arrival of television in the post-war decade. In consequence, it was AM radio that took the brunt of competition from television, having to seek out a new "utility" image as a means of survival. It became thoroughly identified with that image.

When, later, the fascination of television began to subside, a new kind of radio with some highly saleable features was waiting in the wings having, in fact, been nourished by television itself — in the form of the FM sound channel. Tucked away inside millions of TV sets, one-time problems like limiters and discriminator transformers had been cut down to size.

But that is now history and, in practical terms, it is appropriate to view the two systems as they now exist, rather than dwell on the reasons why.

From this point on I tend to digress from the views expressed by VB. He writes off as a "myth" the idea that the consumer is sovereign, although he does concede that "the situation is a complex interaction between advertising and consumer choice, amongst other variables".

Presumably, this can be interpreted to mean that, if not "sovereign", the

consumer is at least an important factor in the formula.

You can say that again!

Back in the 1950s I was involved personally in some of our early efforts with wide-band tuners and they earned reasonable support from readers, partly because radio listening had only limited competition from disc records, none from tape and none from television. A number of suppliers found it worthwhile to market kits of components to meet the demand, and eveyone was happy!

More recently, and despite the availability of improved components and technology, our efforts in this area have been more sparse, being dictated as much by the feeling that "we ought to describe a tuner" rather than by any strong conviction that it would be reproduced by a significant number of

readers.

Missing also has been a conviction that suppliers would play their part by stocking the necessary hardware and other components. Without a ready, over-the-counter supply of "bits", any project is likely to wither and die. Would-be constructors simply become

discouraged.

But let's say that we did come up with a design that we felt was really exciting; that we took it around to every parts supplier we could find in the country, trying to get them to stock kits, advertise kits, arrange window promotions and so on; that we tried to arrange coverage in the hifi columns of daily papers and started a round of broad-

for a project that would ultimately increase their audience.

It would not take long to discover that mere enthusiasm for a technical design would not alone be enough to

casting stations, seeking their support

get it off the ground.

Before suppliers will invest in stocks, or editors or others will respond in a positive fashion, they have to be convinced that out there in the marketplace are people who are good prospects to buy, build and use such equipment.

But convincing them requires facts and figures rather than mere convictions, no matter how sincere

they may be.

I judge that that's the way it is right now with the manufacturers of consumer type receivers and tuners. The buying public will pay any amount of money for the presentation they like and the facilities they think they want. But they will baulk at paying extra money for something they have already convinced themselves — however wrongly — that they don't need.

This being so, the marketing manager of a big hifi manufacturer will hesitate to be a pioneer (no pun intended) and to commit his company to a development, manufacturing and marketing project which is not supported by marketing research, by positive feedback from his dealer chain, or by a



# -that's where the money is!

Stott's course is totally comprehensive — and includes both sophisticated electronic equipment and project materials you need to gain a thorough understanding of servicing techniques.

Divided into three self-contained sections, the course covers:

Part 1 — Introduction to Electronics (theory and practice)

Part 2 — Monochrome Television Receivers

Part 3 — Colour Television, including processing circuitry, service techniques, fault tracing and trouble shooting techniques. Like all Stott's courses, you work with your own instructor who is an expert in

this exciting and rewarding field, at your own pace, in your own home.

If you are a beginner, Stott's will teach you everything you need to know concerning television principles and receiver circuitry.

If you are already working in the field, or have completed some studies in electronics, you may be eligible to enter the course at an advanced stage. Whether your aim is to enter the TV service industry or whether you wish to gain a thorough understanding of television theory and servicing as an aid to sales experience, this is the course which will help you make it!

Other electronics courses offered by Stott's include:
Digital Electronics — AM Radio Receivers —
Radio for Amateurs — Amateur Operator's Certificate

TECHNICAL COR The name to trust in	RESPONDENCE COLLEGE In correspondence education Ition, full details of the following courses:					
(please PRINT)						
Stott's undertake that no sales counsellor will visit						
Mr., Mrs., Miss	Age					
Address						
	Postcode					
159 Flinders Lane, Melbourne, 3000. Tel: 635583 383 George Street, Sydney, 2000. Tel: 292445 290 Adelaide Street, Brisbane, 4000. Tel: 311627	66 King William St., Kent Town, S.A., 5067. Tel: 42 5798 89 St. George's Terrace, Perth, 6000. Tel: 22 5481 P.O. Box 3396, Singapore 1					

## FORUM: trendy to listen to FM?

success story from his competition.

He would have to be very convinced, very dedicated, very stubborn and very secure in his position to take the reverse view and try to force an unsought product onto an unwilling public.

Thinking back a while, I remember the well publicised attitude of Dr. Nakamichi that tone controls were both superfluous and undesirable on hifi equipment, provided all steps had been taken to ensure that the response of the equipment was intrinsically flat. Yet it is only a few months back that Dr. Nakamichi unveiled his latest superbly engineered FM tuner-preamplifier—with tone controls. When questioned about it, he admitted that the controls had been included because his dealers had reported that customers were demanding them!

Curiously, the very same hifi tuner that included the tone controls in response to dealer/customer demand, ignored the AM broadcast band altogether.

VB is convinced that wide-band AM reception could be popularised, if only the entire industry would co-operate with that end in view. Maybe it could be, but I wouldn't put my money on the chances of it happening.

With this much I will agree: if AM stereo is developed successfully and adopted by enough AM broadcast stations, it will supply a tangible reason for designers, manufacturers and the public to take a fresh look at AM. So motivated, they would logically look at judices.

the whole fidelity problem, whether for stereo or mono.

But well before that happens, I think that VB will have had to re-tune his adjacent channel filter to 9kHz and learn to live with a further increment in night-time "monkey chatter", as the broadcast stations are pushed that much closer together.

Last but not least, we have included in a panel a letter to Dr. R. Small of Sydney University from Professor Peter Felgett, of Reading University in the U.K. regarding recent developments in quadraphonic sound reproduction. We reproduce it as being of interest in its own right.

As a side issue, however, it might be argued that quadraphonic sound provides an example of how the combined resources of many powerful hifi manufacturers failed to create the kind of market which they had hoped for. For sure, they did a lamentable job of launching quadraphonics but, looking back on the enormous effort and expenditure involved, the many companies with egg on their corporate face may be less ready than our correspondent to dismiss the sovereign consumer as a myth.

Be that as it may, it would appear that the initiatives of Peter G. Felgett, of the BBC and IBA in Britain, together with Nippon Columbia and others, are gradually edging towards an acceptable universal formula. It will be interesting to see whether the industry will then be able to re-launch surround sound against some pretty strong "anti" prejudices.

# Recent developments in surround sound

Dear Dr. Small,

Because of the kind interest you have shown in the work, I thought it might be useful to outline briefly some recent developments.

As you may recall, the BBC encountered criticism of their "Matrix H" surround broadcasts. However, their engineering press statement 1500, dated 8th June 1977, revealed that they had approached us and were now collaborating with us in the choice of the best two-channel encoding specifications.

Meanwhile two broadcasts of Mahler's Eighth Symphony took place from Radio City, Liverpool, under the auspices of the Independent Broadcasting Authority, with more to follow, using our recommended encoding 45JB. We continue to co-operate closely with our Japanese colleagues in Nippon Columbia, who have constructed prototype domestic equipment compatible both with their UD-4

records and the Ambisonic recommendations.

All this means we are moving well along the road to practical commercial availability of surround material using the Ambisonic technology, and in particular international agreement on encoding specifications.

I have the feeling that there is in Australia considerable interest in surround reproduction which would go beyond the limitations of so-called "quadrophony" and I therefore thought that the availability of the Integrex unit might be of interest to you or your friends. Exact details of price etc, are not yet available.

Integrex will probably also wish to keep the design a little fluid until the BBC make up their minds.

Yours sincerely, Peter Fellgett.

# AVAILABLE FROM:

I.C.S. 16 GERTRUDE STREET ARNCLIFFE 597 1444

## DISTRIBUTORS:

### NORTH

J.A. SEVERN 50 BAMBARA CRESCENT BEECROFT 869 1058

## SOUTH

BRYAN CATT INDUSTRIES 105 MIRANDA ROAD MIRANDA 524 4425

## EAST

RADIO DESPATCH 869 GEORGE STREET SYDNEY 211 0191

### WEST

ELECTRONIC ENTHUSIASTS EMPORIUM 7-10 JOYCE STREET PENDLE HILL 636 6222

## NEWCASTLE

DIGITRONICS 186 PARRY STREET NEWCASTLE WEST (049) 61 4991

# DISTRIBUTORS FOR THE ELECTRONIC INDUSTRY

# Are you aware??

We offer Top Brand Products at market prices with one of the largest product ranges available from a single source of supply.

## PRODUCTS AVAILABLE AS LISTED:

Semi-conductors

DELCO

ELCOMA

GENERAL ELECTRIC

INTERMETAL

ITT

NATIONAL (NS)

NEC (RECTIFIERS)

R.C.A.

SANYO

SIGNETICS

T.I.

INTERSIL

A.M.D.

MONOLITHIC MEMORIES

**Passives** 

BEYSCHLAG

BOURNS

ERIE

ITT

SOANAR SPRAGUE

Electro-Mechanic

ALCO

AUGAT

ITT

J.A.E.

JEAN RENAUD

NATIONAL (RELAY)

POMONA

ROTRON

SWITCHCRAFT

T.I. (IC SOCKETS)

THERMALLOY

WELLER SOLDERING TOOLS

# Instant Component Service

16 GERTRUDE STREET, ARNCLIFFE

# Meet the New Leader....



# S.500D Specification Features

- \* Power output 340W R.M.S. into 4 ohms 500W R.M.S. into 2.5 ohms
- \* Bridged Mono output 900W R.M.S. into 5 ohms 640W R.M.S. into 8 ohms
- \* Intermodulation Distortion Less than 0.02% from 20Hz to 20KHz F1 60Hz.
- \* Integral "Force Cooled Dissipators" for reliable operation into adverse loads.
- \* Power Bandwidth +0, -1dB from D.C. to 20KHz.
- Very low Transient Intermodulation Distortion.
   Restricted rise time, fast slew rate.
- \* Input sensitivity 0.75V for 300W into 4 ohms.
- Noise 105dB Below 180W into 8 ohms 10Hz to 20KHz. Unweighted.
- Elaborate system protection against short and open circuit operation
- \* Small size 3 1/2" x 19" Rack mounting.
- 1KVA Toroidal power supply providing 55 joules of energy.



# The S500-D A higher standard of power amplification design

- PROFESSIONAL POWER AMPLIFIERS INSTRUMENT AMPLIFIERS P.A. SYSTEMS
- ECHO AND EFFECTS UNITS
   MIXERS



SOUNDS A LOT BETTER

Literature available from the Australian Distributors: W. C. WEDDERSPOON PTY. LTD., 3 FORD ST., GREENACRE, N.S.W. 2190 PHONE: 642-3993; 642-2595



# NEW 2x350W CLASS-A+ SYSTEM TO BE RELEASED BY TECHNICS

Whether or not all the current talk about crossover and transient intermodulation distortion is justified in terms of the subjective result, it has certainly intensified interest in unusual circuit design approaches. Latest on the list is the new SE-A1 power amplifier from Technics offering a power output of 350W RMS per channel from a system which they refer to as class A+.

## by NEVILLE WILLIAMS

Back in the days of valve-type hifi amplifiers, great store was set on operating the output valves (triodes, of course) under pure class A conditions. The appropriate supply voltage was applied to the plates and the bias was adjusted so that the no-signal current was about half-way between zero and the peak current which it was anticipated that the valve(s) might draw under full signal drive.

In consequence, a class A output stage drew considerable current, with or without signal, and this has always had to be considered, both in terms of the dissipation in the output valves (or transistors) and the load on the power

supply.


In a well designed class A valve output stage, the relationship between the input (grid) signal and the output (plate) current or voltage was almost completely linear and the intrinsic distortion of the stage was quite low. If used at all, negative feedback served as a final "touch up" rather than as a corrective for major distortion.

When designers began to swing over to solid state circuitry, they found that it was not very practical to operate power output transistors under class A conditions. If biased to about half their anticipated peak output current, they would become very hot, tending to become thermally unstable, with the danger of "running away" and self-destructing.

With class A virtually denied to them,

output tt, with always erms of eyes (or power a second and exercises of the exercise of the ex

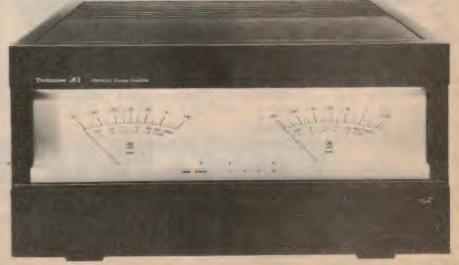Above: The Technics SU-A2 direct-coupled stereo control amplifier. Apart from impressive electrical specifications a most extensive range of controls, including touch type selector switches which have a fade-in fade-out characteristic, obviating plops.



At right, the direct-coupled power amplifier type SE-A1, which offers a response down to "DC". It weighs 51kg and measures 450 x 249 x 550mm. The control amplifier is about the same size but weighs 38.5kg.

designers resorted almost universally to the use of push-pull class B output stages, with the transistors biased so that they drew very little current in the absence of signal. Class B operation minimised heat rise in the output transistors and power supply alike, and allowed power output figures to be obtained generally well in excess of competitive valve amplifiers.

But practical class B output stages are comparatively poor in terms of input/output linearity and quite high orders of negative feedback have commonly been used to reduce the harmonic and intermodulation distortion,

as measured.

However, while the resulting specifications looked impressive on paper, and by valve amplifier standards, there was a persistent and significant level of complaint in hifi circles about "transistor tone". Initially, this tended to be discounted as a subjective bias against transistors but more careful observation established that, while many transistor amplifiers produced low distortion figures at high output levels, the distortion at low levels was bad. It followed from the fact that, at



# Rely on Lenco, if you can't be at the concert hall.

Swiss engineered to reproduce the music the way you want to hear it. The way it was played. Lenco. Precision equipment for the discerning enthusiast. And the next best thing to being where the music was.

## The Lenco R50

One of an excellent range of amplifiers, tuners and receivers ... including the T30 AM/FM stereo tuner, the A50 stereo amplifier and the R25 receiver. The Lenco R50 is designed and engineered to provide AM/FM reception and beautiful quality stereo amplification in one unit. Power: 40w x 40w RMS at 8 ohm.

Frequency: 10-40,000 Hz. FM sensitivity: 1.8 mV. Stereo separation: 40 dB.

Weight: 13 Kg.

Size: 490 x 132 x 320 mm





## The Lenco C2003

A cassette deck to satisfy even a music pro. Swiss engineered 3 head 2 capstan direct drive. Modern design and a host of advanced technical features to make a concert hall of your HiFi room.

## The Lenco L-833DD

The first direct-drive turntable with contactless high-frequency auto-stop. A top ranking, HiFi turntable. Gimbal-suspended tone-arm with excellent geometry. High-frequency electronic auto-stop switches off the turntable and lifts tone-arm. Simply superb. The L-830 has all the same excellent features except the high-frequency auto-stop.

Distributed by

# PHOTIMPORT

MELBOURNE ADELAIDE BRISBANE PERTH SYDNEY

For descriptive literature, send a 30c stamp to Qualitron Industries Division of Photimport (Australia) Pty. Ltd. Head Office; 69 Nicholson Street, East Brunswick, Victoria, 3057, Australia. Phone: 380 6922

# JOHANNUS RECITAL ORGANS USE FREQUENCY DIVIDERS

Electronic organs have become fairly well established in large churches and concert halls, those traditional strongholds of the pipe organ. However, most electronic organs installed in such places have been of two main types: the multiple-oscillator organ, in which each note is generated by a separate oscillator, or the more recently developed "digital computer" organ, in which note waveforms are stored and reproduced by digital means.

The frequency divider type of organ has gained only limited acceptance, despite the fact that such organs are widely used in homes and smaller churches and in popular entertainment situations. The usual explanation for the distinction is that, because the notes from a divider organ are derived from a single source, they are "locked" together with fixed phase relationships. This is alleged to make such organs sound acoustically less satisfying than instruments using multiple sources.

The problem with this explanation is that the "locked" phase relationships are broken up as soon as the signals are acted upon by reverberation — either natural or synthetic. It may well be that divider-type organs have been "looked down upon" in serious music circles through prejudice, coupled with a scarcity of instruments designed specifically

for demanding situations.

There is good evidence to suggest that if a divider-type organ is carefully designed and set up to suit a large church or concert hall, it can be just as satisfying musically as any other electronic instrument.

For the last six years, a Dutch organ builder named Johannus Versteegt has been putting this conviction to the test. A man with over 20 years' experience in the design of electronic organs, Versteegt has had some 60 of his designs manufactured commercially by versions firms.

manufactured commercially by various firms.

Around 1971 he decided to forego the "commercial" mass production approach, and try making instruments in the time-honoured "workshop" fashion used by the old pipe-organ builders. The idea was to produce organs based on modern electronic technology, but individually built to order and provided with the extensive voicing and tonal adjustment facilities necessary to allow true matching to the acoustic environment.

The degree of success he has achieved may be gauged by the number of "Johannus" organs now installed in churches and concert halls in many countries. Several hundred are now in use, including large concert instruments in cathedrals in Portugal, France, Italy and Canada.

There are nine basic models in the current Johannus range. The smallest, known as the Opus 15, is a small two-manual instrument with 31 stops and internal speakers designed for home practice. At the other end of the range is



the Opus 110, a three-manual concert organ with 76 stops and an external speaker system comprising 18 channels of 100 watts rating each.

The instrument pictured is the Opus 80, in the middle of the range. This offers two manuals, 48 stops and a baroquestyle console with five 60W speaker channels.

All of the organs are based on modern solid state circuitry, with its very high reliability and tuning stability. Two master oscillators and frequency divider chains are used, so that at least one complete manual is playable even if a major fault develops. To the basic tone generation facilities are added extensive voicing and tonal adjustments, to allow optimum results to be achieved.

Johannus organs are now available in Australia, thanks to the initiative of a young organ enthusiast named Charles Lamb. On a recent trip to Europe with his wife, Mr Lamb came across some Johannus organs and was so taken by their unique looks and performance that he made a special trip to Johannus Versteegt's workshop in Veenendaal, Holland. The result was a special agreement to allow Mr Lamb to become the Johannus organs representative in Australia.

As yet, there aren't many Johannus instruments installed in Australia. However the word is getting around, particularly as the instruments compare very favourably in price with other electronic organs suitable for church and concert use.

For those interested in hearing what a Johannus organ sounds like, Charles Lamb has demonstration discs and Dolby cassettes available. They feature the Dutch organist Feike Asma playing a selection of pieces by Bach, Franck and other composers, on one of the big Opus 110 organs.

For these and for further information on Johannus organs, readers can contact Charles Lamb at 5 Douglas Haig Street, Oatley, NSW 2223 or telephone (02) 570 2171.

## **HIFI NEWS** — continued

low signal levels, operation was predominantly centred around the "crossover" portion of the input/output transfer curve, where the linearity was poorest and the negative feedback least effective.

Therefore in the critical low-volume region where a class A valve amplifier showed negligible distortion (and gave its "sweetest" sound, &c), a class B transistor amplifier was at its worst.

More recently, the subject of tran-

sient intermodulation distortion has come in for a lot of discussion — a problem quite distinct from class B "crossover" distortion, but relating particularly to amplifiers using high orders of negative feedback.

As is commonly appreciated, negative feedback reduces the gain of an amplifier by feeding portion of the output signal back into an earlier point in the circuit in such a phase and amplitude as partially to cancel the input signal. But it takes a finite time for the signal to pass around the loop and it

is possible for a very abrupt transient to enter the amplifier and cause some portion of it to overload before the feedback signal has time to counteract it. And here's the rub: while the transient itself may be of such short duration as not to be audible, the overload condition may persist long enough to have a perceptible effect on other components of the signal; hence the term TID — transient intermodulation distortion.

Growing awareness of these potential problems has produced a variety of

## HIFI NEWS

reactions among the designers of hifi


amplifiers.

The most natural is closer attention to the design details of conventional class B amplifiers to ensure the greatest possible intrinsic linearity, unaffected by voltage or temperature changes; this along with precautions against TID effects. If manufacturers' literature is to be believed, the performance of such amplifiers leaves nothing to be desired in terms of subjective listening and there is no need to explore other approaches.

Another quite different reaction is to accept that class B has its problems and, for reasons which are variously purist or commercial, concentrate on the use of output transistors under pure class A conditions. Assuming that such an amplifier must offer sufficient power output to be competitive in the marketplace, it will inevitably involve large power transistors on large heatsinks, probably fan-cooled, plus a large and expensive power supply. Understandably such amplifiers have not had very wide appeal.

A more elegant approach, adopted notably by Yamaha and Sony for some of their models, involves the use of power FETs rather than conventional bipolar power transistors (Electronics Australia, May 1975). Power FETs have dynamic characteristics uncannily like those of a triode valve and make possible the design of a power amplifier which is a solid-state near equivalent to a class A or class AB1 valve unit.

Perhaps deterred by patent or supply problems, other manufacturers have come up with their own different and interesting answers as, for example, the QUAD "current dumping" amplifier described in our January 1976 issue. At low levels, output is delivered to the load from a small and economical class A stage. As the signal level increases to what would normally overload this stage, supplementary class B output transistors powered from a second supply take over automatically, the

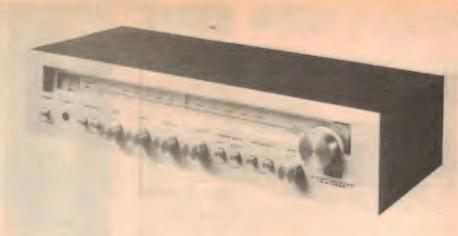

Styled to meet the needs of someone wishing to combine compactness with versatility and high performance, this AA-1125 AM-FM stereo receiver has just been announced by the Akai Electric Co Ltd. Power output is 25W per channel at 0.3% THD, with provision for two loudspeaker systems. Up to three tape decks can be connected with tape-tape dubbing possible or simultaneous recordings from a single source or two separate sources. Other specifications and facilities are in line with modern practice. For those with more modest needs, Akai are offering their new AA-1115 receiver, almost identical in frontal appearance but with somewhat reduced tape facilities and a power rating of 17+17W RMS.

whole system, including the feedback, being designed to ensure that the transition is smooth and distortion-free. At least, that is the claim.

Perhaps predictably, a significant number of hifi devotees have begun to question why we ever abandoned valves. Responding to this, various designers catering for the purist market have come up with amplifiers using valves in the power stages, or the ultimate (?): valves in all stages. Such amplifiers are often described as being basically "musical" and are credited with a quality of tone far superior to any solid-state amplifier, specifications notwithstanding. There is too much concurrence to dismiss such claims out of hand but, equally, considerable allowance has to be made for earnest self-delusion!

It is into this context that Technics have introduced their SE-A1 power amplifier, designated as all solid-state direct-coupled class A+. The immediate problem is that they do not clarify what is meant by the last term in

their introductory literature. They only hint obliquely at what it is not!

It is NOT pure class A; if it were, Technics would obviously have said so. It offers 350W RMS per channel into 4 ohms from a unit that, they claim, is not fan-cooled and not larger than what a normal 100+100W class A amplifier would be. Fairly obviously, the designers are using some dynamic modification to the output stage mode to allow it to idle like a 100W unit but to rise to the demands of 300W peaks.

But having made it clear that the SE-A1 is not a switching amplifier (not class-D), they question also the validity of existing circuits which operate class A for low-level signals and class B for high level; and circuits which operate from lower voltage for small signals and higher voltage from large signals. Such schemes, says the literature, involve switching or transitional phenomena within the signal path and merely exchange one problem for another.


But having made that point, the literature still leaves one with the impression that the SE-A1 exploits at least the last mentioned technique, although presumably in a way which avoids or minimises the disadvantages. By the time you read this, I may have been able to put the questions directly to the engineers involved but, in the meantime, the .SE-A1 can be classified only on the implications of the term class A+: augmented class A?

Terminology apart, the rest of the information about the SE-A1 could scarcely be more impressive. Eight distinct power supply branches separate the stereo channels and stages within the channels, involving four capacitors of 100,000uF each and another four of 22,000uF each. Entirely separate thermal servo amplifiers stabilise the unit against temperature effects, while
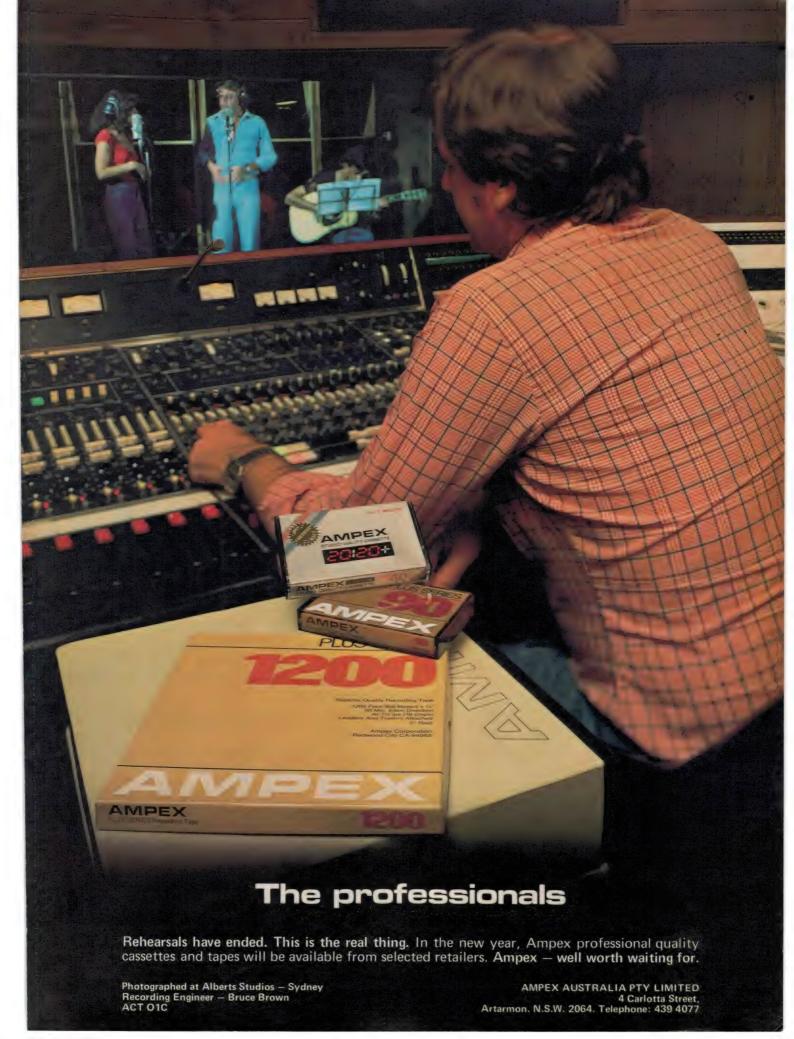
# AUDIOSOUND MONITOR AMPLIFIER



The Audiosound LD 40 PM is a professional monitoring amplifier, which offers high gain, low noise and low transient intermodulation distortion. It can be used in stereo mode with an output of 40W RMS per channel into 9 ohms, or bridge connected to deliver 120W into a single 8-ohm system. The LD 40 PM is being used widely by the Australian Broadcasting Commission. For details: Audiosound Electronic Services, 148 Pitt Rd, North Curl Curl, NSW 2099. Their telephone number is (02) 938 2068.



# WHY YOUR NEXT CASSETTE SHOULD BE A MAXELL UD



THE SHELL — Even the best tape can get mangled in a poorly constructed shell. That's why Maxell protects its tape with a precisely constructed shell, made of lasting heavy-duty plastic.

No fixed guide posts are used. Instead Maxell uses nylon rollers on stainless steel pins thus eliminating the major cause of skipping, jumping and unwinding.

A tough teflon (not waxed paper) slip sheet keeps the tape pack tight and flat. No more bent or nicked tape to ruin your recording.

Maxell doesn't use a welded seal, but puts the cassette together with precision screws. Result — Maxell doesn't jam.



THE RESEARCH — More than twenty years ago, Maxell produced their first reel of magnetic tape. At that time, Maxell made a commitment to produce and sell only the finest magnetic products their technology could create.

That commitment still stands today.

THE TAPE — This continuous research has lead to the development of the Maxell UD (ultra dynamic) cassette. A tape that has a coating of super-fine PX gamma ferric oxide particles with an extra smooth mirror-finish surface.

All of this adds up to high output, low noise, distortion free performance and a dynamic range equaling that of open reel tapes.


that has a four function purpose.

a) Non-abrasive head cleaning leader (cleans recording head for 5 secs.).

b) 5 second cueing line (recording function starts 5 seconds after the line appears).

c) Arrows indicating direction of tape

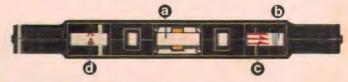 d) A/B side mark (indicates which side is ready for play).



Now you know why your next cassette should be a Maxell UD (ultra dynamic).



The sound expert's cassette. UD available in C60, C90 and C120. Distributed by **Hagemeyer (Australasia) B.V.** Branches in all States.




AKG P 8ES stereo cartridge incorporates a unique and brillantly designed single pivot pound suspension system which ensures that every instrument and performer will be produced not only with the highest possible fidelity and sound definition, but also with an almost uncanny aural sense of 'depth' and directional detail. Features: Unique AKG designed TS (transversal suspension) stylus system. Universal Sym-

metry in respect to transversal movements. Superb transient response. Ultra high tracking ability. Very low effective moving mass. Every P 8ES individually numbered and supplied with a calibrated frequency response/ crosstalk curve. Made with the same meticulous care as the world famous AKG studio microphones.

The P 8ES is the premier cartridge in a completely new range of five models.

SYSTEM



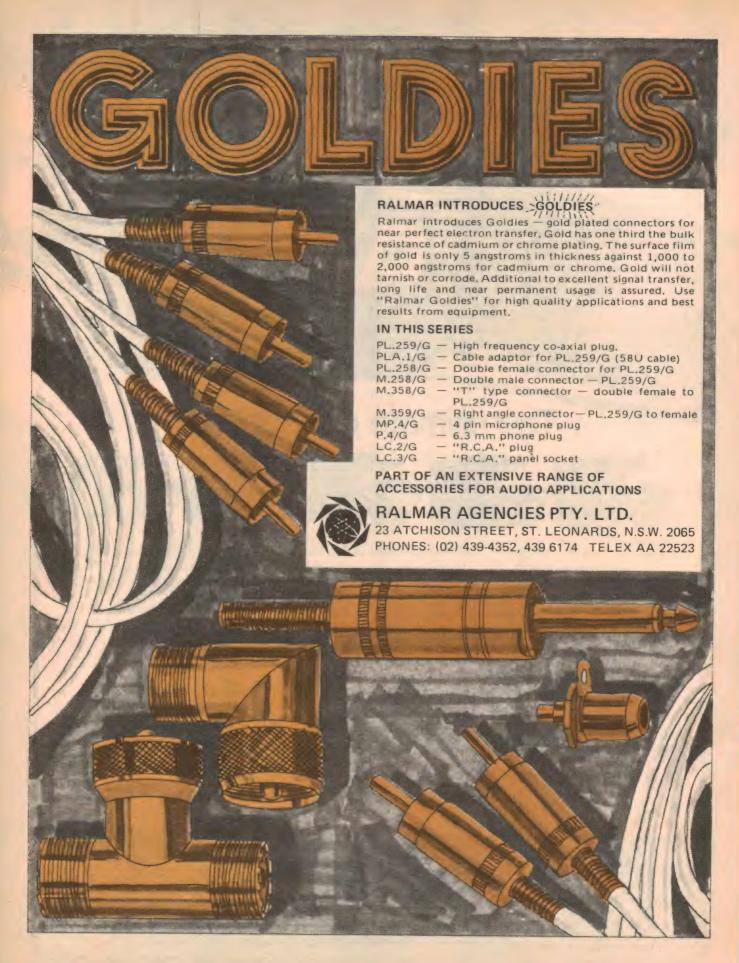

### A Course in **Synthesised** Music

Electronic music in Australia is growing rapidly both for professional performance and home use. Synthesizers seem to be appearing everywhere, and are finding acceptance as a musical instrument that can be understood, played, and enjoyed by all. To this end, a new opportunity is available to the public and the music industry — the System 100 Synthesizer Club.

The Club caters for synthesists using the Roland System 100 or System 700 as their basic instrument. Its aim is to increase awareness of electronic music, and the enjoyment of playing synthesizers, and to help synthesists reach their highest potential.

This will be achieved through an exchange of information and ideas,



Farrell Keyboards summer synthesizer school using the Roland System 100.

newsletters, and a cassette lending library. A board of advisers will be available as a resource, as well as product demonstrations and concerts, and a national yearly seminar.

The club is based on the Roland System 100 because of its sound flexibility, quality of construction and value for dollars spent. It is usually chosen as the smallest and least expensive synthesizer that qualifies as a quality musical instrument, having the controls and layout to lead on to a true understanding of synthesis.

The club is being sponsored jointly by Farrell Keyboards in Brookvale, Sydney, and the Roland Corporation of Australia.

Farrell Keyboards is so convinced of the status of the Roland System 100 that last January they held their first annual summer synthesizer school (25 hours of intense instruction based mostly on the two Roland systems). They are now holding a regular night course that is free and open to the public.

For further information about the System 100 Synthesizer Club, send a self-addressed, stamped envelope to the System 100 Synthesizer Club, PO

Box 393, Brookvale 2100.

#### HIFI NEWS: Class A+ amplifier

elaborate sensing protects the amplifier itself against traumatic malfunctions, and also protects the loudspeakers against unnatural voltage across the amplifier output terminals.

The SE-A1 delivers its full rated power between 20Hz and 20kHz at not more than .003% harmonic distortion. At half-power at 1kHz, the distortion is unmeasurable with any normal test equipment. Frequency response is extremely wide (DC to 200kHz at -1dB), and the power bandwidth is 5Hz to 100kHz at -3dB and .01% THD.

The peak reading power meters are credited with the ability to respond to a single transient at 20kHz, while their behaviour and accuracy are such that it is not necessary to switch ranges to read the amplifier output.

Connection is possible to four sets of speakers with level controls adjustable down to -20dB. This unusual feature makes it possible to adjust the volume level according to the needs of the different speaker locations or, alternatively, to match volume levels for effective A-B comparison testing.

Companion unit for the SE-A1 power amplifier is the stereo control amplifier SU-A21 also pictured. This is so far removed in concept, facilities and performance specifications from the usual control amplifier that it warrants a special article in itself.

Sufficient to say here that the internal circuitry is completely direct-coupled, offering harmonic distortion figures at full rated output of .003% or .005%,

depending on the function. Excellent as these figures are, they are overshadowed by the signal/noise ratio quoted for magnetic phono cartridge: 95dB relative to 2.5mV, which means in practice that the new Technics preamplifier is at least as quiet on phono input as the average amplifier is on the "Aux"

But more about the SU-A2 later.





## Hear your records the way hey were meant to be hear

The acoustic subtleties of great opera houses can be captured on record. Bringing them to life in your home is another thing.

Most record companies use Stanton Calibration Standard pickup cartridges to determine whether their recordings are as close to the actual performance as possible. They know that Stanton Calibration Standard Cartridges reproduce the acoustic and musical subtleties that they and the recording artists have worked so hard to achieve.

> If there were better cartridges made



And remember, you can't get the best out of your Stanton Cartridge unless you use a genuine Stanton Stylus.

Sole Australian Distributors

major record companies who guard their reputations with millions of dollars worth of recording equipment, would use them. Their reputations depend largely on what they hear through a Stanton pickup. The fact that the vast majority of recording companies, as well as nearly all radio and TV stations throughout the world, use Stanton is dramatic proof of Stanton superiority.

When you play your records you can hear them the way recording artists mean you to hear them. Use a Stanton Calibration Standard Cartridge the same as they do.

#### EROYA INDUSTRIES ET

Head Office, W.A.: 156 Railway Pde., Leederville 6007. Phone 381 2930. N.S.W. Office: 100 Walker St., North Sydney. 2060. Phone 922 4037. VICTORIA Office: 103 Pelham St., Carlton. 3053. Phone 347 7620.

LERI98

Tape, tape & more tape!


BELOW: By having selected tape packaged in selected cassettes under their own company name, Dick Smith Electronics claim that they have been able to market a very high quality product through their stores at modest prices: \$2.00 for a C-60 low noise ferric tape, \$2.50 for the C-90 equivalent. The C-90 ultra dynamic high density tape is a little dearer at \$3.00. These are 1-off prices; for bulk orders — 11 or more — considerable discounts apply.









 

M. R. Acoustics of PO Box 110, Albion, Qld 4010 advise that they have added two handy new hifi accessories which they are marketing in Australia on behalf of QED of Britain.

The first is the disc switch unit 10/1, which is suitable for wall mounting and which allows the user to select which of two turntables is to feed the hifi system. Its most obvious role is for domestic record players where a second, less exotic deck is provided for casual or party situations. The price is \$22.00.

For the other end of the amplifier chain, two types of loudspeaker faders or volume controls are available, type 4/8 for 8-ohm drivers, type 4/4 for 4-ohm speakers. M.R. Acoustics point out that the usual devices sold for this purpose are adapted from wire-wound potentiometers, with a power rating of about 3 watts. The QED controls use 5-position switches and PC boards to support the associated resistive network, with ventilation holes for heat dissipation. Suitable for wall mounting, their price is quoted as \$39.00.



ABOVE: Marketed by Pacific Film Laboratories Pty Ltd, Pacific C-60 and C-90 cassettes are intended primarily for the user who wants a good, reliable ferric oxide cassette, at an economical price from readily accessable sources. Pacific C-60 blank cassettes carry a maximum recommended retail price of \$1.65 (C-90 cassettes are \$1.85) and are available from local pharmacies and camera stores — the same outlets as handle Pacific colour film. For further details, contact Pacific Film Laboratories at 298 Railway Parade, Carlton, NSW 2218.

#### **But TDK says:**

that their AD (Acoustic Dynamic) blank cassette is the finest standard bias, pure ferric tape pack that you can buy. It's not quite as good, they admit, as their Super Avilyn (SA) tape but then not everyone has a deck with the appropriate bias and compensation to take advantage of the SA formulation. But, not to worry: AD tape ensures very low noise, low drop-out, wide dynamic range and an improved top-end performance, which is especially compatible with the requirements of Dolby noise reduction circuitry. Mechanically, AD tape has been housed in the same "super-precision" cassette as used for SA, adding up to a very impressive product.



2ND FLOOR TELFORD TRUST BUILDING, 79-85 OXFORD STREET, BUNDT JUNCTION, NSW 2022 PH. 387 2555 3RD FLOOR, EQUITABLE LIFE BUILDING, 301 CORONATION DRIVE, BRISBANE 4064, PH. 36 1257

#### FOCUS INTENSIFIER



Announcing our video focus intensifier to improve the playback quality of all VCR system video recorders. This consists of a small circuit board which fits inside the VCR (Philips etc.)

This circuit detects a change in picture contrast and inserts a transient — in effect an extra — signal at this point, which crispens the image. The effect if the size of this transient is adequate is to recover lost sharpness, and the principle is indeed very effective Full fitting instructions included. \$39.00 + P.P.

#### VIDEO EQUIPMENT-Sony,

Akai, Portopacks. Also agents for J.V.C. and National. All formats and brands Colour and BW recorders, editors, generators and blank video tape available. New and used equipment. Trade and terms. Specials. We have several BW Porotpacks traded on colour sets.



Record one channel while watching another No modification required to existing television sets

Will record while TV set is off ● Usable with any video recorder BW or Colour with an RF output which means this tuner allows video recording of TV programs and playback through aerial input of TV set. \$295.00 + P.P.

#### SPECIAL CLOCK TIMERS

Can be set to switch equipment up to 4 days



FRANCHISEES REQUIRED FOR S.A., W.A., VICTORIA AND TASMANIA

# Improve your connections with



Soanar introduce a comprehensive range of high quality connectors and accessories for CB Radio and Audio Equipment.

Particularly robust, with high transfer capabilities, the range includes plugs, sockets, elbows, T junctions, adaptors, cable joiners, lightning arrestors and dummy loads.

In addition there are microphone plugs and sockets, microphone holders, high performance antennae and a range of special, CB Radio interference suppressors.

See them at your local CB Radio or Electrical Store.

Soanar Electronics Pty Ltd
A member of the A & R Soanar Electronics Group
30 Lexton Road, Box Hill, Vic., 3128. Australia



SALES OFFICES PHONES VICTORIA: 89 0661 N.S.W.: 78 0281 S. AUST.: 51 6981 QUEENSLAND: 52 5421 W. AUST.: 81 5500 SOANAR (JAPAN) LTD. TOKYO

# The Australian CB SCENE

#### PHILIPS-TMC 40-CHANNEL UHF IS LOOKING GOOD

Having spent the best part of a day at Clayton, Victoria, looking through the Philips-TMC factory, and talking to production executives, I came away convinced: not only is the company committed absolutely to local CB production, but to a kind of CB communication that is a world away from the current schermozzle on 27MHz. If you're disillusioned with the present situation, read on.

#### by NEVILLE WILLIAMS

The philosophy of Philips-TMC in relation to CB radio was reported in very broad terms in our last issue but what was said there was based mainly on press releases, and in print before we had a chance to look at their ideas and preparations at first hand.

The interest by Philips in CB-style communication is not new, of course. Earlier in the year they had strongly backed what was then one of the options open to the Minister for Posts and Telecommunications: the licensing of Citizens Band transceivers only on the UHF band, typically in the region of 470MHz.

Consumer reaction to the company's stated policy was immediate and spirited, and highly reminiscent of what had been said of local support for relegating FM broadcasting to the UHF portion of the spectrum:

It would delay practical development, perhaps for years;

 It would prevent consumers from buying and using readily available imported equipment;

 Local manufacturers were motivated not by the best interests of consumers but by a desire to create a "closed shop" for Australian produced equipment.

In due course, the Minister for Posts and Telecommunications settled for what, in retrospect, was the inevitable compromise: to legalise CB operation on both 27MHz and UHF, the former to be phased out by mid 1982.

The numerous and highly vocal champions of US-style CB interpreted the announcement as a decisive victory on the basis that, having been granted legal access to the 27MHz band, the sheer weight of numbers would make it

most unlikely that the allocation could ever be effectively withdrawn.

In the face of competition from 27MHz, locally inspired UHF CB could never be more than an exercise in futility! So said the knockers.

But things have changed, in the past few months, to modify sharply this easy dismissal of UHF CB:

 Legalisation and cut-price marketing have released a flood of 27MHz transceivers to the public, adding to the 100,000-odd units that were already operating illegally. Many individuals with identifiable communication needs have become thoroughly disillusioned by the mass of jargon-ridden chatter on the channels. To this whole group, UHF CB has emerged as a highly desirable alternative.



General Manager of Philips-TMC, Ian McKenzie (left), and CB Radio Product Manager, Ian Miller, with a prototype of their Australian made UHF CB unit.

 Philips-TMC has promised to supply the vital missing link — a highperformance 40-channel UHF
 transceiver, to be on sale in early 1979, for about \$300, including antenna.



The Philips FM320 will be marketed in a distinctive carton, complete with a detailed operating manual and a booklet detailing the warranty and back-up services.

### At last: Dick's Australian SSB CB

SCORPION SSB BASI

What have the Hy-gains, the Cobras, the Presidents, the Kracos, the Trams, the Universes, etc etc etc got in common? They're all American rigs, in some cases 'dumped' in this country. What have the Scorpion, Hornet, Wasp & Bumblbee got in common? They're DESIGNED FOR AUSTRALIA, by Australia's No. 1 CBer, Dick Smith!

Here it is — Dick's brilliant new 'Scorpion' SSB/AM base station. 18 channel, designed for Australia — with built-in power supplies for both 12V & 240V. Has LED readout, SWR meter (both meters are huge, easy-to-read types) and the finish is the latest 'black is beautiful' with contrasting chrome trim. An

absolutely brilliant apppearance — our drawing just can't do it justice! If you want outstanding value for money in an outstanding set, you can't go past the Scorpion!

OUR SPECIAL INTRODUCTORY OFFER: SAVE \$50!!

Retail price will be \$349.50 (as per our press release) but buy now and the price is just \$299.50

Cat D-1740

NEW

\*\*\*\* DICK SMITH CB

\*ALL DICK SMITH CB

\*ALL DICK SMITH CB

CHANNEL

SERVICE BACK-UP!

SERVICE BACK-UP!

SERVICE BACK-UP!

\$259.50

OUR OTHER TRUMP CARD: The 18 channel 'HORNET' SSB/AM set. The mobile SSB which will soon have everyone talking — to each other as well as talking about this superb set. LED digital readout: of course! Again, 'black is beautiful'. And look at the knobs. They're those large, specially shaped knobs which everyone wants — but very few have! Ideal for Australians! Up-to-the-minute electronics, full service back up (with spares!),not forgetting the 90 day warranty — a set you'll be proud to own, and one which will keep you happy for years! Cat D-1720



### TEAGE YOURSELF ELECTRONICS

with 150 in 1 experimenter's kit

A magnificent educational kit for both the inexperienced and advanced experimeter. Beautifully detailed manual describes in step by step instructions, how to make up to 150 different electronic projects. No soldering is required and the complete kit operates off harmless low voltage battery power. An enlarged transparent I.C. (integrated circuit) clearly shows the electronic layout of these most complex space age devices. As no soldering is required (connections are spring terminals) all components can be re-used time and time again. The kit includes the following electronic devices: Cadmium sulphide cell, solar cell, micro-ammeter, radio tuner, poteniometer, relay, I.C., speaker, signal light, microphone, earpiece, morse key, slide switch, transformer, etc. The separate projects are too numerous to list however, it has been said that the only thing that cannot be made is a television! Supplied in a sturdy wooden case. Dimensions 406 x 216 x 89mm. Batteries required:1 x 9 Volt, 2 x 1.5 Volt. Cat. K-2030 .. .. ..



### The Perfect Xmas Gift \$39.95

DICK SMITH ELECTRONICS GROUP

SYDNEY: 125 York St City. Ph 29-1126 Open 'til 8PM Thursday

SYDNEY: 361 Hume Hwy Bankstown. Ph 709-6600 Open 'til 8PM Thursday

SYDNEY: 30 Grose St Parramatta. Ph 683-1133

SYDNEY: 162 Pacific Hwy 33 Gore Hill. Ph 439 5311 Ample parking at store MELBOURNE 656 Bridge Rd Richmond, Ph 42-1614 Handy location

MELBOURNE 399 Lonsdale St City. Ph 67-9834

BRISBANE: 166 Bridge Rd Buranda, Ph 391-6233 Open 8.30AM ADELAIDE: 203 Wright St City

### The Australian CB SCENE

Their "exercise in futility", so called, may well turn out to be a real winner and a trend-setter on an international basis!

Looking at the emerging position back in July last (for publication in the August issue) we foresaw the possibility that Australia could be "in a position to set a lead with switched channel receivers operating around 470MHz". However, we were less than optimistic that Australian electronics manufacturers could "learn to manufacture transceivers down to a price, while still meeting the requisite standards".

"... it would be quite unrealistic to think in terms of beautifully made Australian transceivers at \$700 apiece, when the up-market CB limit is less

than half that figure."

Right now it looks as if Philips-TMC is going to show up our pessimism for what it possibly was and this is one time we won't mind in the least being proved wrong!

But how are they managing to pull the UHF rabbit so neatly out of the hat?

Seeking to answer that question, Philips-TMC General Manager Ian McKenzie said that the Philips organisation had a long-standing connection with radio communication and had played a prominent part in the development and installation of such things as mobile radiotelephones, "wireless" telephone systems, personal paging systems, and so on. His company was communications orientated, with a particular interest in "personalised" communications.

They saw the present high interest in CB radio not as an isolated phenomenon, but as a natural flow-on from every person's urge to communicate. When motoring, for example, he/she would like to know about road conditions; be able to summon assistance, and to inquire ahead about accommodation, etc — the things on which the case for CB was largely built.

But, according to Ian McKenzie, the allocation overseas of 27MHz was an unfortunate "technical accident", being just about the worst frequency possible for such a service:

It suffers badly from electrical interference;

 It penetrates readily into audio and other electronic equipment;

 Antennas are too large to permit efficient operation on vehicles;


 While not optimum for short-range communication for the above reasons, 27MHz signals are still subject to ionospheric "skip", making them randomly audible hundreds, or even thousands, of miles away from the transmitter.

In terms of planned communication, the 27MHz CB band therefore tends to be something of an aberration — an uncomfortable mix of point-to-point communicators, and would-be amateurs and DXers, and a "cult thing" for teens and twenties, as well.

By comparison, operation on 470MHz would largely eliminate interference problems from both reception and transmission, simplify antenna requirements, provide much more predictable local communication, obviate ionospheric skip and generally shift the whole bias back towards the

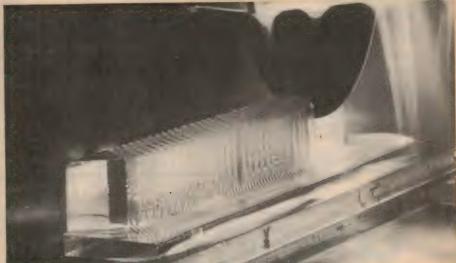On Philips UHF transceiver assembly line each assembly operator is responsible for their own quality checks, including a multifunction test of the subassembly. Each completed transceiver is ultimately tested under simulated customer operating conditions.





Philips-TMC is the only electronics manufacturer in Australia set up to cut and grind crystals for use in their own communications equipment. The photo shows crystals being cut from a rod of synthetic quartz after the precise cutting angle has been determined to ensure optimum oscillator characteristics. The FM320 UHF CB rig uses one such crystal for the basic frequency source and two other crystals in its filtering and frequency division circuitry.



In the crystal filter assembly and tuning section of the Philips-TMC manufacturing centre at Clayton, Vic, operators individually tune each crystal to its correct frequency by depositing gold particles on to the crystal face with a vacuum process.



#### **ELECTROCRAFT PTY LTD**

FULL 1/4 WAVE

SPIRAL TUNED

GROUNDPLANE

Full omnidirectional radiation,

excellent

characteristics. SWR of better than 1.2:1 possible with one sim-

ple adjustment. \$37.75°

106A HAMPDEN RD, ARTARMON (2064). Phone: 411-2989, 411-3772.

Distributors of Belling Lee, Channel Master, Ecraft, Hills, HI.Q, Lab Gear, Kingray, Matchmaster. Largest Television range of aerial equipment in Sydney.

TELEVISION AERIAL AND DISTRIBUTION EQUIPMENT . CB RADIO AERIALS & ACCESSORIES

#### TV DISTRIBUTION AMPLIFIERS

NEW FROM ECRAFT. A range of Medium & High gain R.F. DISTRIBUTION Amplifiers, suitable for all TV & FM radio transmissions within the VHF & UHF Bands I to V APPLICATION. Suitable for small home unit, showroom or household type installations. D16 & D25 amplifiers have good signal to noise ratio. As such this makes them suitable as a booster in semi-fringe or fringe areas
1.75 D16 16 dB \$45.90 1.75 D25 25 dB gain \$53.55

All types of TV & FM aerials in stock. HILLS, CHANNEL MASTER, MATCHMASTER, HI.Q.

#### CABLE & AERIAL HARDWARE

All types of twin & coaxial cable in stock from 30c/metre 75 & 50 ohms.

Also wall brackets, chimney mounts, "J" brackets, guy wire, masts from 8ft to 50ft etc

#### FILTERS & ATTENUATORS

A complete range of TV1 filters and attenuators for all applications available

3000

CLEARANCE SALE of all our CB radio stock to make way for new shipments.

"COBRA" 132/SSB transceivers "COBRA" 21X transceivers
"COBRA" 19M transceivers

PRESIDENT GRANT" AM/SSB

CB Mobile aerials - Royce, Belling Lee. Gilco (heavy duty), Topix, Channel Master

PHONE FOR SPECIAL PRICES

FROM ELECTROCRAFT

#### CB BASE STATION AERIALS

1/2 OR 5/8 WAVE WITH "RING TAPPED" FEED AND "HALO" TOP HAT



This aerial is ideal for those locations where space does not permit the use of a full groundplane. By the use of the halo" top hat it out-performs other aerials of similar design. ½

FULL 5/8 WAVE GROUNDPLANE



This aerial has the maximum omnidirectional gain of any antenna and is ideal for those locations where space is not a problem \$54.95\*



All of the above aerials are supplied with:

"U" bolts and saddles, for quick and easy fixing to up to 1¾" aerial masts.

• PL 259 input sockets.

input

 Detailed instruction sheet. No expensive extras to buy


ABOVE PRICES ARE APPLICABLE TO NSW ONLY DISTRIBUTORS REQUIRED - All states

### CITIZENS BAND ANTENNAS

QUALITY SCALAR ANTENNAS ARE DESIGNED AND MANUFACTURED IN AUSTRALIA
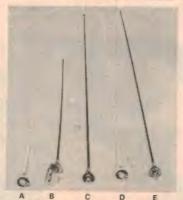
#### MOBILE MARINE. BASE STATION

Scalar Citizen Band Whip Antennas are designed to provide efficient performance with reduced length. Either helical, centre or top loading on fibreglass rods. They are available for vehicle or marine installations on standard. or marine base, or for gutter or for trunk lid mounting.



TYPES ILLUSTRATED

A) CB 1220 42" Centre Loaded.

B) CB 1120 30" Centre Loaded.

c) CB 1420 60" Helical.

D) CB 1520 60" Helical / Sector / Top Loaded.

E) CB 1320 60" Centre Loaded.

A WIDE RANGE OF SCALAR CB ANTENNAS (FROM 30" TO 108" LONG) AND ACCESSSORIES ARE AVAILABLE FROM LEADING RETAILERS AND DISTRIBUTORS THROUGHOUT AUSTRALIA

TRADE ENQUIRIES WELCOME



#### SCALAR INDUSTRIES PTY. LTD.

COMMUNICATION ANTENNA ENGINEERS 18 SHELLEY AVENUE, KILSYTH, VICTORIA, 3137. TELEPHONE: 725-9677. Cables: Welkin. Telex: AA 34341

N.S.W. 20 THE STRAND, PENSHURST, 2222. Telephone: 570-1392 QLD. (STD 07) 371-5677. WA. (STD 092) 57-1555. SA. (STD 08) 42-6666

## The Australian CB SCENE

utility service that CB radio should

provide.

For the time being the Philips Consumer Division will almost certainly handle an 18-channel 27MHz transceiver, but only to maintain a complete presence in the marketplace. As far as Philips-TMC is concerned, their whole emphasis will be on the production, distribution and servicing of Australian-made UHF CB. And, for this role, the company is particularly well placed.

Of the 11-odd companies supplying the Australian mobile radio market (excluding CB) Philips-TMC claim to have the "lion's share" with about 45% of

the total market.

A great deal of effort has been directed towards minimising production costs and their success is shown by the fact that, in round terms, the price level of mobile radio units has remained substantially unchanged since 1955. They still average around \$500.

At the present time, according to Ian McKenzie, Philips-TMC transceivers are fully competitive in Australia against units manufactured overseas. More than that, they are competing very successfully in the Pacific and Asian regions, even to the point where they dominate the market in Hong

Kong.

Because a significant proportion of the systems operate at UHF, a great deal of Philips-TMC research at Clayton has been concentrated in this direction. In fact, the design team at Clayton provides project leadership in UHF mobile technology for the entire Philips group, worldwide. About 7% of Philips-TMC turnover is diverted to research and development, and to what they define as "quality assurance".

When the possibility emerged of a CB allocation in the UHF band, it was natural that the Clayton team should take it up, partly to meet the immediate challenge in Australia, and partly with a view to the possibility of other coun-

tries following suit.

And the stakes could be quite high. Based on figures from the USA, and allowing for a higher rate of acquisition (as happened with colour TV), it seems likely that one Australian in every 10 will own a two-way radio five years from now.

That adds up to a million or more sales!

So, in April of this year, TMC's lan Miller was named as CB Product Manager, heading up a team covering every facet of the new venture — planning, design, procurement, production, marketing and so on. Within six months, the team had generated provisional specifications in collabora-

The HMV Electronics Division of EMI have recently announced release of their "Roadhound"

range of CB transceivers. Designed to meet Australian specifications, the TX44 is an AM unit intended to retail at \$119. The TX55, illustrated, has similar electrical speci-fications to the TX44 but has additional controls and a LED channel readout. The price quoted is \$139. Top of the range is the TX77, featuring AM and SSB operation and retailing at \$239.



tion with the P&T Department, produced mockups to test customer reactions, run propagation tests with adapted existing transceivers, and produced their first working prototypes.

On the occasion of my visit to Clayton — and despite the crippling Victorian power strike — work was in progress to relocate offices and stores in order to clear a space for an assembly line that, next year, should be turning out many thousands of UHF transceivers.

Present expectation is that addition of the CB line will treble the number of units flowing from the Clayton factory. This has made it possible to order a whole new array of tooling, automatic production equipment and test jigs, which will not only speed the production of the new CB units, but also expedite production of existing

radiotelephones.

To my question about price, Philips say they are still sticking with their figure of "about \$300", announced earlier, for a 5W mobile transceiver, complete with microphone, cradle and antenna. This is possible, they say, mainly because the CB transceivers will be completely standardised and produced in a long, unbroken run. Transceivers for commercial users have to be produced to smaller orders, set up for different frequencies, etc, and this adds to the cost.

Specifications for the CB units may also not be quite so tight, but the differences will not be all that great. Because of the number of CB transmitters which are likely to be in use, there will be little room to relax specifications on spurious radiation, in particular.

The production prototype of the

FM320 CB transceiver, which I handled at Clayton, is smaller than the average AM/SSB transceiver and also much lighter. It has a particularly versatile cradle arrangement, which should allow it to fit neatly beneath the dash of most cars. It has a built-in loudspeaker, a socket for an external speaker and an audio power output of 2W. No provision is made for public address — an omission with which the writer heartily concurs!

Unlike the usual 27MHz CB transceiver, the FM320 employs narrow band FM rather than AM or SSB. This confers a high degree of immunity against noise interference, heterodyne whistles and crosstalk — the latter due in part to the "capture effect" of an FM

system.

Also, unlike the usual 27MHz CB transceiver, the FM320 has no channel selector knob, although it does have a LED readout to indicate which of the channels is in use. To change channels, the operator pushes a spring-loaded toggle switch on the panel, which causes the transceiver to cycle through the 40 channels in the direction required.

A second toggle switch has three indexed positions. In the centre, it allows the selector to operate as described. The outer positions override the sequencing and tune the transceiver respectively to the emergency channel, or to a particular channel which the user can have preset by a simple internal adjustment.

Responding to would-be user reaction at the NCRA CB conference in Canberra, in September, Philips engineers decided to bring forward one or two modifications which they had envisaged for a Mark II version.

## Putting in a Plug for TV.

At last we have the opportunity of putting in a plug for ourselves. On television yet! It's our brand new 75 ohm Coaxial TV antenna outlet socket (P/N C27-24). Completely re-styled and attractively finished, the all-new ACME TV Plug is the simplest of all to install. Provision is made for either back entry or side

P/N C27-24

entry of the cable and you don't have to solder either! You'll be pleasantly surprised at the ingenuity of ACME's new TV Plug and likewise with price.

Standard socket to accept Push-on type co-axial plug.

Attractive, strong, high-impact resistant poly carbonate cover.

- Surface mounting.

ACME

Easy crimp connection, no need to solder.

Suitable for terminating foil and braided shield cables.

Knock-out provided for external cable entry.

Ask for the ACME 75 ohm Coaxial TV antenna outlet socket at all leading suppliers or contact the ACME office or agent in your State for further information.



ACME ENGINEERING CO. PTY. LTD. 2-18 Canterbury Rd., Kilsyth, VIC. 3137.

Ph. 729 6211

N.S.W. Ph. 648 4638 A.C.T. Ph. 95 9138

QLD. Ph. 58 2011 (Brisbane)

Ph. 71 4131 (Townsville) Ph. 51 4422 (Cairns)

S.A. Ph. 74 1162 W.A. Ph. 28 1022

TAS. Ph. 34 2811 (Hobart) Ph. 31 5545 (Launceston)

ACME 1293

## CB SCENE

Chief of these was the provision of a second channel-select toggle on the body of the microphone. It has occasioned a small delay into the start of production but it means that the up-date will be included right from Mark I, No. 1.

No less interesting than the transceiver itself were the prototype antennas which I saw in the Clayton conference

room.

At 470MHz, the length of a conventional quarter-wave antenna is only about 15cm; mounted on the roof of a car—which provides an effective groundplane at this frequency—the radiation pattern should be a relatively symmetrical "doughnut". Compared with 27MHz antennas, the 470MHz spike looks very tiny indeed, yet it radiates at full efficiency.

However, at about 38cm overall, a five-eighth wave basefed antenna is also entirely practical for rooftop or gutter mounting and offers about 3dB of gain relative to the

quarter-wave spike.

Yet another antenna I was shown comprised a base-fed five-eighth bottom section, surmounted by a lumped inductor self-resonant on 470MHz with a half-wave on top of that again — broadly equivalent to a two half-waves in-phase configuration and giving a dB or so of gain above that of the five-eighth radiator alone. But the length is still only about 70cm, making it practical for mobile and very attractive for a base station installation.

But the really smart antenna was a skirted quarter-wave (or dipole) in which the coaxial cable passes up through a metal skirt, one quarter-wave long, to feed a quarter-wave spike on top. This still-tiny assembly is mounted on top of a suitably modified broadcast antenna, with the 470MHz feed cable passing down through the latter to the CB set. A single-hole mount suffices for both antennas and, because the CB antenna is mounted high up and well clear of the car body, it gives a good all-round pattern with an effective gain, Philips claim, of about 5dB over a quarter-wave spike at rooftop level.

And what does all this add up in terms of that final and

vital consideration — range?

In a typical situation, neither notably good nor notably bad, car-to-car range is typically around 10km. From base-to-car, with the base antenna just above roof height, about 15km. But the range can double, triple, or quadruple quite predictably if either end of the circuit is operating from a topographical prominence.

On the assumption that most users, for most of the time, will be working from average locations, there is room in a typical large city for three or four station groups to be using the same UHF channel without mutual interference. Since there will be 40 channels available, these multiply to 120 or

more.

As I said at the outset, I came away convinced!

#### SHORTER IS SAFER

Mr Len Francis, Chief Electrical Inspector for Victoria, has emphasised the need for care when installing the tall antennas which are commonly used for 27MHz CB base stations. He said that, during 1976, one insurance company in the USA had 26 reports of do-it-yourself installers fouling overhead power lines when erecting CB radio or television antennas.

"Fifteen of these accidents were fatal and, in the other cases, most survivors received severe burns."

Mr Francis said that accidents with CB antennas had most commonly involved lightweight vertical omni-directional antennas mounted on top of long metal masts. While publicity had already been given to the dangers of long, mobile whips, it was necessary to be no less careful with base station antennas.

## CB SCENE

#### 'Go anywhere' CB transceiver

With about four weeks to go before the P&T Department ceases to license 23-channel CB transceivers, Dick Smith Electronics are offering their customers a last chance to acquire one of their 13-861 Midland portables at a very attractive price — \$135.00.

As will be evident from the photographs, the 13-861 is styled rather like a military packset, allowing it to be carried and operated while bush walking, etc, using its own self-contained batteries. Alternatively, it can be operated in a car, slung from an underdash cradle, or as a base station, powered from a mains unit and coupled to a standard 50-ohm antenna.

The basic transceiver is conventionally styled — although very small — with a black and chrome front panel, chrome surround, and two vinyl covered metal lids to provide the main housing. It measures 11mm wide, 50mm high and 171mm deep, not including the knobs at the front or the connection facilities at the rear.

For portable use, the unit slips into a black leather-like carrying case, being retained by two knob-screws and with access holes for the speaker/microphone, antenna and battery charger. A separate pocket on the side of the case accommodates the battery pack which can take either eight penlight cells or 10 equivalent rechargeable nickel cadmium cells. It is for the latter that access is provided for a separate charger.

The antenna for portable use comes with the 13-861, along with a shoulder strap, as pictured. The antenna is actually in two parts — a swivel base which screws into the socket at the rear, and a centre-loaded telescopic rod which can be adjusted to a near-vertical position, irrespective of whether the transceiver is being carried, or resting on a flat surface.

An unusual feature, but a logical one in a portable set, is that the microphone serves a double role — as a mic. for transmission and as a speaker for reception. There is ample acoustic output for portable work but, for fixed situations, an external loudspeaker can be plugged into the rear of the transceiver, to make best use of the rated 2.8W of audio power.

To conserve battery power in portable service, a hi-low switch is provided on the panel, allowing the transmitter output power to be reduced for short-range working.

For use in a car or boat, alternative



cradle brackets are provided, a shallow one to accommodate the bare transceiver in what would be a very compact installation, and a deeper one to accommodate the complete portable case. A normal red/black twin lead is provided for connection to a 12V electrical system and, as mentioned



Modest in size and weight, the Midland 13-861 lends itself readily to portable applications, as above. With batteries delivering normal voltage and using its own telescopic rod antenna, the transmission range is about 3 miles in average terrain. In the Lo-power position, it is likely to be about 1 mile.

The Midland 13-861 in its "Texon" carry case and with the speaker/microphone plugged in ready for use.

earlier, there is provision for use with a separately mounted loudspeaker. A standard antenna socket at the rear allows for direct connection of any ordinary 50-phm CB style antenna.

The same general remarks would apply to where the 13-861 is used in a base station role, except that the power

#### Teleview









18-Channel AM/SSB Mobile CB Transceiver.

Teleview recommend this one as the better one on the market.



#### EVERSONIC 23-CHANNEL AM

with \$13 base-loaded antenna. Ultra-cheap way to CB.



Shakespeare GBS 5000 \$180 Hy Gain 5 \$199 Power Supplies 3 amp \$45. PA Horn \$10.95.

Phone, write, or drop in and see us at ...

#### Teleview

218 Chapel Street, Prahran, Vic. 3181. Melbourne: Phone (03) 51 6743

We also do confined area installations eg. farms, race clubs etc.

Million VI RINGO \$49.95 PMG LICENCE REQUIRED

Prices subject to change. Correct at press time.





THE CB550 AM/SINGLE SIDE BAND MOBILE A POWERFUL TRANSCEIVER CAPABLE OF LONG DISTANCE CLEAR COMMUNICATION.

EASY TO OPERATE CONTROLS ON AN ATTRACTIVE BRUSHED ALUMINIUM FRONT PANEL, AN L.E.D. ELECTRONIC CHANNEL SELECTOR MAKES CHANNEL CHANGING QUICK AND ACCURATE, AN INBUILT S.W.R. METER FOR AERIAL EFFICIENCY CHECKS

THE MODEL CB550 FEATURES CONTROLS FOR S.W.R. CALIBRATION, S.W.R. REFLECTED POWER, NOISE BLANKER, R.F. GAIN, CLARIFIER, VOLUME, SQUELCH, DIMMER, AND A 3 WAY METER MEASURES RECEIVE AND TRANSMIT LEVELS AND S.W.R. MATCHING.

THE LATEST DESIGN IN C.B. CIRCUITRY FROM THE WORLD'S LARGEST C.B. MANUFACTURER, A DOUBLE SHIELDED OUTPUT STAGE TO MINIMISE RADIATION

- PROTECTED TRANSMITTER CIRCUITRY
- S.W.R. METER INBUILT
- FLOATING GROUND SYSTEM FOR POSITIVE OR NEGATIVE

#### Other Electrophone Models

(Full Details on Request)

18 CHANNEL C.B

CB510 COMPACT AM \$99.50 CB530 DELUXE AM WITH LE.D. CHANNEL

SELECTOR, IN-BUILT S.W.R. METER \$148.52

CB590 SSB BASE STATION 12 VOLT/240 VOLT WITH IN-BUILT S.W.R. METER \$299.00

DISTRIBUTED THROUGHOUT AUSTRALIA BY

6 CHANNEL MARINE • GME 275 WITH RF GAIN

562 SPENCER STREET, WEST MELBOURNE — (03) 329 7888 1103 DANDENONG ROAD, EAST MALVERN — (03) 211 8122

To make way for the new 18 channel stock we are offering special discounted prices to clear all our existing 23 channel units

Remember a P.M.G. licence can be obtained for the units listed here. If a licence is bought before December 31st, these 23 channel units can be operated until 1982.

#### AM UNITS

American Electronics "Spirit" with delta tune and S/RF meter	<b>\$</b> 73.37
inbuilt SWR meter	\$122.92 \$125.86

SSB/AM UNITS	
Shakespeare GBS 5000 with RF gain	\$211.50
Johnson Viking 352D with RF gain	\$225.80
Stingray by Lafayette, inbuilt noise limiters	\$228.50
Bengal base station 240/12 volt with microphone and RF gain	\$249.50

### The Australian

supply would normally be from a mains unit delivering around 13.5V.

Controls on the front panel include the channel selector, the hi-low transmit power switch mentioned earlier, squelch control, volume control with off/on switch and a checklite switch. This latter provides temporary illumination for the channel selector and meter when the unit is operating from its own batteries. When powered from an external source, the illumination remains on.

The small edgewise meter serves three functions. With no input signal, it registers the supply voltage on a red/blue scale and therefore indicates the condition of internal batteries.

With normal input signal, it serves as a reverse reading S-meter and, on transmit, indicates relative power output. In practice, the battery condition reading is probably the most important of the three.

Electrically, the receiver is specified as a double-change superhet with intermediate frequencies of 11.275MHz and 455kHz. It features AGC and inbuilt anti-noise limiting. Sensitivity is given as 0.5uV for a 10dB S/N ratio, selectivity 8kHz at 6dB down and spurious rejection better than 40dB. Frequency control, by crystal synthesiser, is within  $\pm 0.005\%$ .

The transmitter is similarly crystal controlled and is rated to deliver an output of 1W (lo) or 3W (hi) in portable service or 4W in mobile or base station configuration.

\$155.00

A typical 13-861 was made available for our examination and we had no fault whatever to find with the presentation of the unit, complete with all accessories and a comprehensive manual in carton and rigid foam pack.

In the time available we did not have the opportunity to take the unit on a bush walking expedition, but we did set it up in base station configuration, with mains power supply and a 5/8-wave antenna.

Its behaviour on receive was completely normal for an AM transceiver, the only obvious difference being that the sound issued from the microphone rather than from the body of the transceiver. Gain, selectivity and S/N ratio were all well inside the requirements for normal CB working and a further check with a signal generator indicated that very little had been sacrificed in compressing the unit into its existing size.

On transmit, power output was generally in line with specifications and the modulation clean.

The Midland 13-861 is available, while stocks last, from the Dick Smith Electronics Group. (W.N.W.)

## The Australian CB SCENE

#### **NEWS, OBSERVATIONS & PRODUCTS**

PIRATE STATIONS: A press release from Vicom International, over the signatures of Russell Kelly and Peter Williams, draws attention to the fact that about 50 per cent of all CB stations in the USA are currently unlicensed, despite the fact that licences are available free, on application. What hope, they ask, is there for CB licensing in Australia at a figure of \$25 per set?

If the CB airwaves are not going to be dominated by "pirates", the money will have to be ploughed straight back into the system by way of an adequate team of inspectors equipped with adequate detection equipment.

UNITREX OF AUSTRALIA PTY LTD, part of the group which also includes Chiba Communications Aust Pty Ltd, advise that they share a new and common address at 12 Terracotta Drive, Blackburn, Vic 3130. Telephone number is 03 877 2922.

EXTERNAL SPEAKERS: Audio Telex Communications Pty Ltd point out, quite correctly, that the voice quality from the average self-contained CB transceiver is compromised by the necessarily small in-built speaker — as often as not directing sound towards the driver's feet, or to the floor or table-top in the case of a base station.

For all those situations where space is available, Audio Telex are recommending their AFS-KRIKET brand external speakers, housed in an acoustically

Above, a typical external speaker unit and below, a Kiket "Kamel" combination speaker and transceiver mount, with a Telex CB73 power microphone attached.



treated Naugahyde case, and swivel mounted so that they can be directed conveniently and appropriately towards the operator.

Also available are special all-weather speakers and larger, higher quality units for specialised base station operation

Their address is 54 Alfred St, Milson's Point, NSW 2061, or 828 Glenferrie Rd, Hawthorn, Vic. 3122.

MIDLAND CLAIM: No. 1. Figures released in the USA, indicate that Midland is the top selling CB there. Midland enjoy No. 1 position with 21.4 per cent of the US market in 1977. The next most popular set is Cobra with 12.9 per cent, the Realistic 11.9 per cent, followed by Johnson, Royal, Pace and Hy-Gain.

The figures were published in July 1977 Electronic Retailing and are based on figures supplied by Clarion Corporation of America and are accurate to plus or minus five per cent.

#### UHF CB CHANNELS

The frequencies nominated by the Authorities for the UHF CB band are set out in the table below:

Ch.	Freq.	Ch.	Freq.
1	476.425	21	476.925
2	476.450	22	476.950
3	476.475	23	476.975
4	476.500	24	477.000
5	476.525	25	477.025
6	476.550	26	477.050
7	476.575	27	477.075
8	476.600	28	477.100
9	476.625	29	477.125
10	476.650	30	477.150
11	476.675	31	477.175
12	476.700	32	477.200
13	476.725	33	477.225
14	476.750	34	477.250
15	476.775	35	477.275
16	476.800	36	477.300
17	476.825	37	477.325
18	476.850	38	477.350
19	476.875	39	477.375
20	476.900	40	477.400

Of the above, channels 1-10 and 36-40 may be used immediately and without restriction. Channels 11-35 will become available to the Citizens Radio Service (CB) at a date to be announced.

UHF licensing is on the basis of frequency modulated telephony with a maximum bandwidth emission of 16kHz and a maximum transmitter output power of 5 watts (mean power).



Div. of Electron Tube Distributors P/L

94 ST. KILDA RD., ST. KILDA Victoria 3182. Tel. 94 6036

## The Australian CB SCENE

WINNING ENTRY —
The Dick Smith CB Cartoon Contest

The Australian supplier of Midland CB radios is Dick Smith Electronics. Dick Smith said recently, that "Midland has a significant share of the Australian market, possibly higher than the 21.4 per cent quoted as the US market share. Midland is a popular brand because of its quality control standards at the point of manufacture."

ANTENNAS: A new range of CB antennas has been released by Antenna Engineering Pty Ltd of Garden St, Kilsyth, Vic. The range includes both base and mobile antennas.

AEA model HT27 is a special high performance, low SWR, top loaded 5ft helical. Other mobile antennas include heavy duty 7ft bumper mounting helicals, base loaded roof mount models and 12-inch compact helicals. Accessories and mounting kits are available to suit.

For base operation, there is the model HV-27 helical dipole, as well as vertical ¼ and ½-wave base loaded types.

AEA manufactures a wide range of antennas and associated equipment for TV and radio stations, military and government services, local government bodies, etc.

G.F.S. ELECTRONIC IMPORTS is a new company which has been formed to import and distribute CB accessories, along with novice and other amateur radio equipment. Its principals are Greg Whiter and Fred Stewart, both of whom have had considerable experience in the electronic communications field. The address of the company is given as 15 McKeon Rd, Mitcham, Vic. 3132.

OBC INTERNATIONAL MARKETING PTY LTD have been named as the sole agents in Australia for the HY-GAIN Electronics Corp, USA, according to a statement by Mr Roger Wilson, Manager of the General Products Division of OBC. The new arrangement will replace what were previously more diverse marketing methods.

OBC have arranged for one of their top technicians to visit HY-GAIN's plant in Lincoln, Nebraska, for training.

HY-GAIN technical staff will also visit OBC's plant in Melbourne to assist in setting up full local service facilities.

Pride of the HY-GAIN line at the moment is their model 16, described as "the world's first microprocessor-controlled, practically burglar-proof Citizen Band Radio system". It employs two modules — the main unit fitting in the boot and a dash-mounting control unit, which can be readily removed for safe keeping.



Literally hundreds of entries were received for the CB cartoon contest announced in our September 1977 issue, ranging from primitive to professional. This one scored highest in a staff poll conducted by Editor Jim Rowe. The prize, a Hy-Gain 23-channel SSB/AM CB transceiver, goes to Mr William Chambers, 11 Valder Avenue, Hobartville, NSW 2753. We plan to publish other selected cartoons in coming issues, for which a publication fee will be paid.



### Win this BWD 539 25MHz oscilloscope

#### The Project Competition:

Announced recently by BWD Electronics, the BWD 539D oscilloscope is a dual trace instrument with a bandwidth from DC to 25MHz and beyond. It is highly suited to such fields as colour TV servicing, education, microprocessor testing, and testing and adjustment of

communications equipment.

BWD Electronics, in conjunction with "Electronics Australia", is offering EA readers an opportunity to win the unit pictured at right. It will go to the reader who can write the best article on how a modern CRO, with the specifications of the 539D, can be used for servicing and adjusting 27MHz CB or other transceivers, and/or amateur equipment operating up to 30MHz. (Note: specifications for the 539D are published in a separate review in the "New Products" pages.)

#### **Rules and Conditions:**

(1) The article must be submitted in a form suitable for judging and for possible publication in "Electronics Australia". It should typically be able to fill three pages of the magazine, including diagrams and/or photographs. It will need to be neatly written or, better still, typed double space. Diagrams should be clearly legible.

(2) All entries will remain the property of "Electronics Australia". Those suitable will be published with credit to the author, and will be paid for at ruling rates. Copyright of the article in the form published will then be vested in

"Electronics Australia".

(3) Senior staff members of "Electronics Australia" will judge the contest. The decision will be final, and no correspondence will be entered into. The winner will be announced in "Electronics Australia" as soon as possible after the contest closes.

\*See review elsewhere in this issue



Donated by BWD Electronics: Total value, \$465.00.

CONDITIONS OF ENTRY: Entries should represent the entrant's original work. Employees of Sungravure Pty Ltd, BWD Electronics Pty Ltd or any associated companies are not eligible to enter. Entries postmarked or delivered by hand later than February 28, 1978, will not be eligible.

#### **ENTRY FORM**

Complete this form and attach it to your entry, posting them not later than 28th February, 1978, to Oscilloscope Contest, c/o Electronics Australia, Box 163, Beaconsfield, NSW 2014. A letter may be used instead of the form in States where this requirement is illegal.

NAME:	/·····
ADDRESS:	. =

## CET PARADOIC The original marketers of parabolic in Australia

can you afford not to use an EEI parabolic

#### WHAT IS AN EEI PARABOLIC?

EEI is the brand name that you can rely on when you need a replacement stylus or complete cartridge for your hi-fi. If you look at our drawing "A", you will see the greater contact area of the natural diamond parabolic stylus in the record groove, compared with a standard elliptical, drawing "B" The parabolic with its increased contact area greatly reduces the stylus pressure on the record groove, thus virtually eliminating any gouging effect on your records. This feature also allows the EEI stylus to trace the complicated recorded signal with greater accuracy. Some of the many benefits are listed on our chart "E' An EEI parabolic assembly is a brand new "slip-in

#### WHY YOU NEED AN EEI

One of the hardest working items in your hi-fi is the record stylus, sometimes called "the needle".

Your stylus travels about 1/3 of a mile for each side of an L.P. record, and any appreciable wear means that the stylus will lose its original shape and therefore lose its ability to trace the recorded signal precisely, any sharp edges produced by wear will begin to shear the record groove walls.

The EEI parabolic greatly extends stylus life and the life of your valuable records—see wear comparison illustrations "F".

GREAT PERFORMERS
Ask anyone that uses an EEI
REFUSE SUBSTITUTES
INSIST ON AN EEI

#### HOW LITTLE DOES AN EEI COST?

EEI Series 500 parabolio	
cartridge	\$49.75
EEI parabolic replaceme	ent styli
to suit the following:	
SHURE V15III	\$49.75
SHURE N95ED	\$44.75
SHURE N91ED	\$41.75
SHURE M55E & M44	\$24.75
<b>ORTOFON M15E super</b>	\$41.75
STANTON 681EE &	
EEE	\$41.75
EEI Series 500	\$37.75
PIONEER PN135	\$34.75
SHURE N75ED	\$29.75
PIONEER PN11	\$24.75
PIONEER PN12	\$24.75
Plus many other types.	QL 7.70
NEW DELEACE, EEL AND	

NEW RELEASE: EEI-400 ultra low tip weight elliptical cartridge \$29.75.

Enquire about the new EEI Moving Coil Cartridge with Pre-amp. or EEI Moving Coil High Output Cartridge — does not require a Pre-amp.

prices quoted are Recommended Retail Only.

#### HOW TO OBTAIN AN EEI

If you live in New South Wales you can phone Max Townshend of Townshend Electronics (02) 827 2937 for the name of your nearest suburban dealer, or if you live out of town, just add \$1.50 to the price indicated and mail your order direct to Townshend Electronics, P.O. Box 185, Rozelle, N.S.W., 2039,

If you live in Victoria or any other state, phone Peter Wright of Elite Electronic Industries Pty. Ltd. (03) 93 1201 for the name of your nearest suburban dealer, or if you live out of town, add \$1.50 to the price indicated and mail your order direct to Elite Electronic Industries Pty. Ltd., 36 Luxmoore Street, Cheltenham, Victoria, 3192.

Depending on availability, we guarantee same day despatch.

#### This is what AUSTRALIAN HI-FI has to say about EEI parabolic

replacement for your cartridge

On all counts the EEI Parabolic is an excellent cartridge It gives performance comparable with units at a much higher price

- Much better all round sound
- Diamond parabolic needle lasts up to 5 times longer
- Record life increased up to 10 times

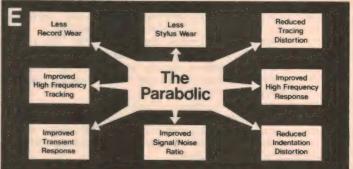
Tests conducted in suppliers laboratory using SME arm, EEI 500 Parabolic and EEI 500 fitted with .0008 x .0003 elliptical natural diamond











EEI is used as standard equipment for FM broadcasting.



Elliptical Stylus caused excessive wear after 100 playings – magnified 12000 times



Same magnification – note almost complete lack of wear after 100 playings with an EEI Parabolic Stylus



#### **ELITE ELECTRONIC INDUSTRIES PTY. LTD.**

Manufacturers, Importers and Distributors of EEI products.

36 LUXMOORE STREET, CHELTENHAM, VICTORIA, AUSTRALIA, 3192 Interstate Agent — TOWNSHEND ELECTRONICS, P.O. BOX 185, ROZELLE, N.S.W., 2039.

## EEI-Series-400 magnetic cartridge has elliptical stylus

Already known for their Series 500 magnetic cartridge with parabolic stylus, Elite Electronic Industries Pty Ltd now introduce this lower-priced unit with an elliptical stylus.

The EEI Series 400 cartridge works on the "induced magnet" principle and so, like most other cartridges, it has a removable stylus assembly. The Series 400 model also has the standard 12.7mm mounting centres and standard colour coded output terminals.

Mass of the cartridge is quoted at 6  $\pm$  0.5 grams. Thus it is easily balanced by

all current tone arms.

One point we should comment on is the lack of branding on the cartridge. Our sample had no identification on it at all. This could be a drawback in years to come, when the user wants a replacement and cannot find the original packing.

Mounting the EEI cartridge in most headshells is a straightforward process. The regular shape of the cartridge body makes correct alignment easy, and the body has drilled mounting holes rather than the abbreviated mounting feet on some other brands which make moun-

ting a tedious process.

We found it necessary to remove the stylus assembly while the cartridge was being mounted, to avoid the possibility of stylus damage. Our sample cartridge was a pre-production model, supplied without the standard packaging or printed specification sheet. When their regular production models become available, EEI would do well to include a stylus protector of some sort, whether it is a clip-on or flip-down type.

According to EEI the elliptical stylus is a "natural" diamond, but we are not sure whether this means that it is a "naked" diamond rather than a diamond tip on steel shank, or merely that it is not a synthetic type. Either way will have minimal effect on the quality of reproduction. Tip mass is calculated by EEI at less than 0.4 milligrams.

Impedance of the cartridge is quoted as 2.5k at 1kHz, but this is fairly useless information to a user who wants to calculate the effects of cartridge loading. It would be more useful to quote the inductance and resistance.

Recommended load for the cartridge

is 47k, with no figure specified for shunt capacitance. Recommended tracking force is 1.5 grams minimum, 1.75 grams optimum and 2 grams maximum. We found that the optimum figure was in fact 1.75 grams, with little to be gained by increasing the tracking force to 2 grams.

At the optimum tracking force the EEI 400 tracked the ±12dB drum test track of the W&G 25/2434 disc. On the Shure "Audio Obstacle Course" the

3dB from 4kHz to 12kHz. Channel balance is within 1dB and channel separation is 24dB in both directions at 1kHz and greater than 20dB from 200Hz to 16kHz. These are good results.

Waveform in the region of 10kHz to 16kHz is not good but this is fairly typical for most magnetic cartridges. Square wave response at 1kHz is good.

Output voltage of the cartridge was 3mV at 5cm/sec which is a little on the low side. EEI state that this will be higher in their regular production models. Fortunately the cartridge appears to be reasonably well shielded, and problems with hum induction were not experienced.

The EEI Series 400 cartridge works on the induced magnet principle and has a removable stylus assembly.



tracking performance of the EEI 400 equates with typical medium quality magnetic cartridges.

Frequency response tests were made using the CBS STR 100 disc and with the cartridge loaded with a 47k resistor and cable capacitance of about 120 picofarads. The output voltage was monitored by a Hewlett-Packard 331a (functioning as an AC millivoltmeter) and oscilloscope.

Under these conditions the frequency response was within +1 -3dB from 30Hz to 20kHz. The response is actually slightly above reference 0dB at the two extremes, but has a droop of about 2 to

Sound quality of the cartridge is very good, particularly on stringed instruments. This is to be expected from the well-maintained HF response. Bass response is also fully up to standard.

In short, the EEI Series 400 cartridge can be regarded as providing good performance at reasonable cost. Recommended retail price of the unit is \$29.75 plus \$1.50 post and packing. Enquiries should be directed to Elite Electronic Industries Pty Ltd, 36 Luxmoore Street, Cheltenham, Victoria 3192 or their interstate agent, Townshend Electronics, PO Box 185 Rozelle, NSW 2039. (L.D.S.)



#### Transform your room into a synthesizer studio.

System 100 7 Model 101 Synthesizer

An amazing range of musical effects. A rich variety of tones and sound qualities at your fingertips. The musical sounds produced by a single Roland synthesizer are almost limitless. The Roland System-100's "Basic Unit 101" is a fully independent synthesizer designed specifically for use with home tape recorders. Simply connect it to your unit and

enjoy the kaleidoscopic sound effects it has to offer Original compositions, improvisations or imaginative arrangements of your davorites— wherever your musical imagination takes you, the "101" goes there with you. Let the Roland "Basic Unit 101" open up new worlds of sound creation for you

#### ROLAND CORPORATION AUSTRALIA PTY. LTD.

13 CHARD ROAD, BROOKVALE, 2100. PHONE: 938-3811

## Leak 3050 loudspeaker has time-delay compensation

Like the other units in the Leak 3000 series, the 3050 is "time-delay compensated". This is achieved with a staggered baffle, although the outward appearance is quite conventional. The Leak 3050 is a two-way system but has two woofers and one tweeter. Power rating is 50 watts.

With the trend to odd-shaped loudspeaker cabinets, the Leak 3050 is a fence-sitter. It has an irregular baffle, but manages to conceal it with the grille cloth frame. The reason for the staggered baffle is to apply "time-delay compensation" to the tweeter. This approach is otherwise entitled "linear phase" (or similar) in other brands of loudspeaker.

The time delay results in any multispeaker system where the voice coils are in differing vertical planes, as they must be when all the loudspeakers are mounted on the same vertical baffle. The solution, as provided by a number of manufacturers, is to tilt, bend or stagger the baffle so that the wavefronts from each of the drivers in the cabinet all arrive at the listener's ears at the

Naturally, the time-delay compensation provided by these methods is a compromise and will only be ideal at a specified distance from the cabinet. In the case of the Leak 3050 the staggering of the baffle appears to be optimised for a listening position some three to four metres from the unit, with the cabinet sitting on the floor.

Instead of being made of timber the complex baffle of the Leak 3050 is a large plastic injection moulding. It is quite heavy and rigid and appears to be non-resonant. It is attached to the timber cabinet by four wood screws and a cleat at the bottom. This does not look very impressive, but the cabinet did seem to be airtight.

Two woofers, each with an effective diameter of 125mm, handle the bass and mid-frequencies up to 4kHz. Above that, a 20mm dome tweeter takes over and carries on to well above the limit of audibility. The crossover network has a stack of inductors and other components, and gives attenuation slopes of 18dB/octave.

We were pleased to note that the dome tweeter has a measure of protection from clumsy fingers and errant screwdrivers, in the form of a light mesh cover. We would still prefer that the grille cover be not so easily removable (as with most other loudspeakers) but the Leak grille is at least better in this respect that the foam grilles of some of its competitors.

Volume of the sealed enclosure is 40 litres and most of this is packed with an acrylic fibre material to control the system resonance. The enclosure panels are also treated to reduce unwanted resonances. Connections to the

amplifier leads are made via DIN socket or thumbscrew terminals.

Nominal impedance of the Leak 3050 is 8 ohms. Measurement showed that the actual impedance (modulus) was between eight and 12 ohms over the range from 20Hz to 20kHz, except at the system resonance of 60Hz and also at 1kHz where the figure was about 23 ohms.

Power rating of the system is quoted at 50 watts (DIN) and the manufacturers recommend amplifiers of 12 to 60 watts. Our experience indicates that amplifiers under about 30 watts would be run into overload.

Frequency response tests revealed a strong and well-maintained bass response down to below 50Hz. At the high end, the treble had a rising characteristic above about 8kHz and this tends to give an impression of higher than actual efficiency. In the midrange, two deep troughs at around 700Hz and 2kHz could cause a few problems, depending on the tastes of the listener.





The staggered baffle of the Leak 3050 is concealed by the grille cloth.

## Christmas Gift Ideas for Hi Fi Enthusiasts

If you are looking for a gift for a "hi-fi buff" you'll find the perfect answer at Arrow Electronics. Say "Merry Christmas" with something that will give a discerning music lover many years of added listening pleasure.



Shure Pick-up Cartridges
The sure way to up-grade a
stereo system-a phono cartridge
he would choose himself...
from \$18.




Famous Koss Stereo Headphones The choice of discerning music lovers the world over...from \$30 pair.



Discwasher System A superior record cleaner system comprising specially designed brush and a bottle of D3 fluid, \$19.95.



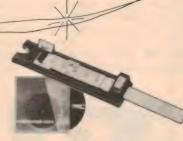Shure Microphones
Shure Unidirectional Dynamic
Mikes are used by Paul Anka and
other wellknown artists in show
business. From \$24.50.



Shure Stylus Pressure Gauge For accurate adjustment of Tracking force for maximum trackability. Priced at \$12.75. Shure Test Record

Shure Test Record Cartridge Test Record for testing sound quality and performance of cartridges, \$10.00.



Zerostat Anti-static Guns Eliminates dust-attracting static charge on records, dust-covers, film, etc. Price \$27.50.

Dust Bugs for \$2.99 Decca Brushes \$12.95

Whether you require a single component or a complete Hi-Fi system the Specialists at Arrow Electronics can help you. Come in and let us tell you about our special deals on some of the world's finest equipment. Open daily till 6 pm. Thursday 9 pm.

ARROW ELECTRONICS ET

342 Kent Street, Sydney (between King & Market Sts.) Phone 29-6731

AE 126/FP

Listening tests confirmed the bass response of the 3050. In fact, with program material other than rock, the bass tends to predominate. We found that for best overall results the cabinet should be raised about 30cm above the floor and kept well out of the corners of the room. This not only prevents undue augmenting of the bass response by floor and corner reflections, but it

At low listening levels the 3050 sounds very pleasant, probably as a result of its general response giving a degree of "loudness" compensation. At higher levels, the irregularities in the midrange can make the music sound distant. In some ways this is a good deal better than the exaggerated forward sound resulting from the excessive midrange response of some Japanese



With the acrylic fibre filling removed the interior of the Leak 3050 is still fairly busy. The baffle is a large injection moulding which has a rubber gasket to achieve an airtight seal.

also cleans up the lower midrange and American loudspeakers. response.

Unfortunately, raising the cabinet off the floor negates any beneficial effect of the time-delay compensation. So be it. Time-delay compensation is an arguable advantage anyway.

The rising treble response above 8kHz will be preferred by those listeners who like a clean and well defined treble end. But it needs to be modified a little with the treble control, otherwise tape hiss and disc imperfections are over-emphasised.

To sum up, the Leak 3050 is a system which can give good results on rock and most instrumental music but some listeners may find its reproduction of vocal material somewhat lacking.

Recommended retail price of the Leak 3050 is \$682 for a pair. Further information can be obtained from hifi retailers or from the Australian distributors for Leak products, Rank Industries Australia Pty Ltd, 12 Barcoo St, East Roseville, NSW 2069. (L.D.S.)

#### N TR(O)D)U(c **OUR GREAT**



Model 125 has the same woofer as does the Model 18 and therefore the same enclosure, and therefore the same incredible bass response. It has the same tweeter, too. And therefore the same lucid shimmer on higher frequencies.

Most of all, it allows you to make another choice within the class of great for the price of good.



**Bolivar Speaker Works** REAT FOR THE PRICE OF GOOD.

HARMAN AUSTRALIA PTY. LTD. P.O. BOX 6, BROOKVALE, N.S.W. 2100 PH. (02) 939-2922. TLX. 24873.

## Electronic Poker Machine

For those interested in games of chance, we present here a simple Electronic Poker Machine. The completed unit is fully solid state, and is easy to build at low cost. Unlike normal "one-arm bandits" you don't have to pay to play!

by DAVID EDWARDS

A poker machine is essentially a random number generator, coupled to a payout mechanism. Electronically, it is fairly simple to implement an effectively random number generator, and to light up payout indicators on specified numbers. Implementing the mechanics of accepting and paying out tokens or coins, however, is much more difficult, and is beyond the scope of an electronics magazine. So this article will be confined to describing only the required electronics.

Part of the attraction of a poker machine is in the visual display it provides, involving wheels rotating and stopping at random. A typical machine will have three wheels, which will stop one after the other, with any prizes showing only when all wheels or reels are stopped.

We have elected to represent these reels using three seven segment displays. Each display is driven by a BCD to 7 segment decoder, which in turn is driven by a decade counter. The clock pulses for each counter are supplied by a voltage controlled oscillator, which is arranged to run rapidly at first, and

PAYS 1 PAYS 2 PAYS 12 77
Mystery PAYS 1 PAYS 8 -77

PLAY IN PROGRESS

then to slow down progressively before finally stopping.

The outputs of the decade counters are sampled by logic circuits when all the oscillators have stopped, and appropriate lights turned on to indicate any prizes which may have been won.

In order to keep the project simple, and hence to minimise the cost of components, we have provided only basic scoring circuitry. This provides visible indicators of wins, with the main jackpot producing an audible indication as well.

All components are mounted on a single printed circuit board, which is intended to mount directly behind an appropriately lettered front panel. In order to further minimise costs, we have not specified a case. Instead, we have left it up to individual constructors to suit their own preferences. Our prototype was mounted in a wooden case assembled from scrap materials, and the main cost involved was that of the author's time.

Details of the construction of the prototype case, and the way in which the play switch was implemented, can be gleaned from the accompanying photographs. The play switch consists simply of a momentary action toggle switch, whose toggle was extended using a piece of plastic rod obtained from an old alignment tool.

A full size reproduction of the front panel accompanies this article, and it may be traced or used direct as required. Alternatively, we have made copies of our artwork available to those companies which normally supply front panels for our projects, and these should be available through the normal channels in due course.

Before discussing the circuit in more detail, we will consider first the theory

This photograph of a winning combination shows both the displays and the prize indicating LED. behind the payout logic. The major prizes have all been chosen to involve various combinations of 7s, as this number is relatively easy to detect electronically. Thus the major jackpot is 777, and the probability of obtaining this in any one "pull" is one in 1000, or .001.


Similarly, the two minor jackpots are 77- and -77. These both have an equal probability of occurring, which would normally be one in 100 or .01. But since 777 is reserved here for the main jackpot, the probability of achieving each of these combinations reduces to nine chances in 1000. To make the machine a little more interesting, we have given the two combinations different "payout" scores.

The remaining prize based upon 7 is 7--. This has a probability of occurring in any one pull of 90 in 1000 or .09, after allowing for those combinations which produce the previously mentioned prizes. The remaining two prizes are rather unusual, and will be considered in more detail.

The prize labelled "Evens" occurs whenever all of the three reels show even numbers. Thus typical winning numbers are 246, 082, 444 and so on. There are a total of 125 numbers such as these, giving the chance of winning this prize as 125 in 1000 or 0.125.

The remaining prize, labelled "Mystery", is just that. To a casual glance, it appears to pay on numbers which are unrelated, such as 319, 001, 191 and 987. However, an astute observer may be able to see a pattern in these and the remaining 176 paying combinations.

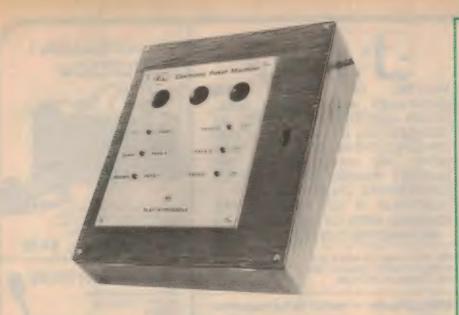In fact, there is a pattern in these numbers. Firstly, they are all odd. Secondly, the middle digit, when expressed in binary, does not contain a 2. In other words, only the following digits can form part of the prize: 0, 1, 4, 5, 8 and 9. And the most significant digit of the number must not contain a 4



when expressed in binary, allowing only the following digits: 0, 1, 2, 3, 8 and 9.

The significance of these strange combinations of numbers is that they are all easily detected using digital logic. In fact, the "Mystery" prize requires only one three input gate and one inverter. The probability of pulling this prize is 180 in 1000, or 0.18.

The values of the payouts for the various prizes were determined so that overall, the machine would have a payout rate of 95%. In other words, if you play for long enough, you will get back 95% of your input, assuming that one token is required for each pull. If you want the machine to be completely fair, increase the jackpot "prize" value from 70 to 120.

The Payout Calculation Table shows in condensed form the way in which the individual prizes are combined to give the total value of the payout. As you can see, there are 414 different winning combinations, so that on average a prize should be awarded at least once every three pulls.

For example, a test run on the prototype showed that after 100 pulls, 41 prizes had been awarded. The total value of the prizes was only 67, made up as it happened from the three smaller prizes.

Turning now to the circuit diagram, we can examine the operation of the circuit in more detail. At the heart of the unit are three 555 oscillators. A voltage controlled current source has been added to each oscillator, in place of the usual charging resistor, so that they function as voltage controlled oscillators.

The control voltages for the oscillators are developed across the three 22uF capacitors. When these are discharged, the oscillators are stopped, while their frequencies increase as the control voltage increases. When the play switch, which is debounced by two cross-coupled gates, is operated, gate

1a turns on the BC548 transistor, which charges the three capacitors to approximately 1/3 of the supply potential.

The diodes in series with the charging path are intended to isolate the capacitors from one another after the play switch is released. The capacitors then discharge via the base bleed resistors, which have been chosen so that the oscillators stop in sequence from left to right.

The rate at which the oscillators slow down, and their maximum frequencies, have been chosen to provide an acceptable display, while at the same time ensuring that the number of oscillations is suitably random.

The 555 outputs are used to clock 74C90 CMOS decade counters. The counter outputs are converted into seven segment format using 74C48 decoders, and used to drive 0.3" high common-cathode displays.

After the displays stop cycling, the number displayed is essentially random because the total number of oscillations depends on the total length of time the play switch is depressed, and this will vary from player to player and from play to play by the same person. Extensive tests with the prototype failed to show any bias whatever.

The payout detection circuitry consists mainly of combinations of gates. The gate inputs are connected to the BCD outputs of the decade counters, and the logic is arranged so that only one of the six outputs can go high at once. If no prize combination occurs, all outputs stay low.

Each output turns on a LED indicator, using a BC548 transistor. The positive supply line for the LEDs is controlled by another BC558 transistor. This transistor is controlled by gate 1c, which also drives the green "play in progress" LED. The input of gate 1c is connected to the debounced output of the play switch, via a time delay network.

This ensures that the payout LEDs are disabled while the 555s are still

#### PARTS LIST

#### **SEMICONDUCTORS**

3 555 timers

3 74C90 decade counters

3 74C48 BCD to 7-segment decoders 3 DL704 or similar common-cathode

1 4011B quad 2-input buffered NAND gate

1 4023 triple 3-input NAND gate 2 4025 triple 3-input NOR gates

1 7805, LM340T-5.0 or similar three terminal regulator

4 1N914 or similar silicon diodes 2 EM401 or similar silicon diodes

4 BC558 or similar PNP transistors

8 BC548 or similar NPN transistors

6 red LEDs

1 green LED

#### CAPACITORS

1 2500uF 16VW electrolytic

3 22uF 16VW tantalum

1 10uF 35VW tantalum 3 1.5uF 35VW tantalum

6 0.1uF polyester

3 0.01uF polyester

#### RESISTORS (all 1/4W)

1 680k, 1 220k, 1 150k, 1 100k, 11 10k, 1 3.9k, 1 3.3k, 1 2.7k, 3 1k, 1 220ohm, 28 150ohm, 1 100ohm.

#### MISCELLANEOUS

1 printed circuit board, coded 77pm12, measuring 152 x 177mm

1 transformer, 240V to 15V CT. DSE 2155, A&R 2155 or PL1.5-18/20VA or similar

1 mains plug, 3 core flex, cord clamp and terminal block

1 momentary contact SPDT toggle

1 front panel and case (see text)

1 miniature buzzer, 6VDC operating voltage

Circularly polarised red film, 130mm x 30mm.

Scrap aluminium, solder, hookup wire, tinned copper wire, PCB pins, tapped spacers, machine screws and nuts.

NOTE: Resistor wattage ratings and capacitor voltage ratings are those used for our prototype. Components with high ratings may generally be used provided they are physically compatible.

oscillating, so that false payout indications are not given. The diode ensures that there is no delay when the play switch is first operated, so that the "play in progress" LED is illuminated immediately. After the play switch is released, the 10uF capacitor is charged via the 680k resistor, and holds the gate output high for about 6 seconds.

Note that a buffered gate must be used in this position, as otherwise the

#### Zener Diodes

.5 Watt	volts	1 Watt	volts
BZX83C-3VO	3	IS3006A	6.1
BZX83C-3V3	3.3	IS3007A	6.8
BZX83C-3V9	3.9	IS3008A	8.2
BZX83C-4V7	4.7	IS3009A	9.1
BZX83C-5V1	5.1	IS3010A	10
BZX83C-5V6	5.6	IS3012A	12
BZX83C-6V2	6.2	IS3015A	15
BZX83C-6V8	6.8	IS3016A	16
BZX83C-7V5	7.5	IS3020A	20
BZX83C-8V2	8.2	IS3024A	24
BZX83C-9V1	9.1	IS3027A	27
BZX83C-10	10	IS3030A	30
BZX83C-12	12	IS3033A	33
BZX83C-13	13	IS3036A	36
BZX83C-15	15	IS3039A	39
BZX83C-16	16	IS3047A	47
BZX83C-18	18	IS3051A	51
BZX83C-20	20	IS3056A	56
BZX83C-22	22	IS3062A	62
BZX83C-24	24	IS3068A	68
BZX83C-27	27	IS3075A	75
BZX83C-30	30	IS3100A	100
BZX83C-33	33	IS3150A	150
BZX83C-47	47	IS3180A	180
- A		IS3200A	200

All .5W only 30c ea. All 1W only 65c ea.

#### SPECIAL SAVINGS

6V Batt. Box

вн4 30с Battery Clip for

above and 216

CL5 10c

Better buy while the price is right

#### PRINTED CIRCUIT **ELECTROLITIC CAPACITORS**

	1-9	10 up
4.7 mfd 16 volt	11c	90
10 mfd 16 volt	11c	9c
22 mfd 16 volt	12c	10c
33 mfd 16 volt	15c	12c
47 mfd 16 volt	15c	12c
100 mfd 16 volt	15c	12c
220 mfd 16 volt	20c	18c
470 mfd 16 volt	40c	35c
1000 mfd 16 volt	55c	50c
2.2 mfd 25 volt	12c	10c
4.7 mfd 25 volt	12c	10c
10 mfd 25 volt	12c	10c
22 mfd 25 volt	12c	10c
33 mfd 25 volt	15c	12c
47 mfd 25 volt	15c	12c
100 mfd 25 volt	16c	14c
220 mfd 25 volt	35c	30c
470 mfd 25 volt	35c	30c
1000 mfd 25 volt	55c	47c
1 mfd 50 volt	18c	13c
3.3 mfd 50 volt	18c	13c
4.7 mfd 50 volt	20c	18c
10 mfd 50 volt	206	18c
22 mfd 50 volt	20c	18c
33°mfd 50 volt	20c	18c
47 mfd 50 volt	20c	18c

#### **VEROBOARD**

Copper strip 0.1" x 0.1" No. 122 17 9" x 3 15" 34 w 2 17.9" x 3.15" 34 way Only \$6.20

No. 123 17.9" x 4.7" 36 way Only \$8.30

**Veroboard Cutter Tool** 

2022 \$2.95

Vero-pin Inset Tool

2150 \$3.95

Veroboard Pins. Large or small. Only \$1.75 per 100



AND SHORTAGES WITH OTHER ORDER ELECTRONIC SUPPLIERS. AT 'DAVRED' WE GUARANTEE TO SHIP OR REPLY WITHIN 24 HOURS. ONCE MORE, WE HAVE ONE OF THE LARGEST RANGES OF ELECTRONIC COMPONENTS UNDER ONE ROOF IN AUSTRALIA. IF YOU HAVEN'T DONE BUSINESS WITH US BEFORE, YOU'VE BEEN MISSING OUT! ON SERVICE.

FH6 Fuse Holder for auto or project use. Bayonet action, nylon moulded body. Suitable for 3AG fuses



#### Microphones - never to be repeated! Value

We did a bulk buy and we're passing the savings onto you. Our best seller,

EX-220 Electret condenser uni-directional microphone is being offered until the 31st Dec. at the incredible price of \$14.95

Freq. response 50-12,000Hz, 600 ohm imped. Uses 1.5V penlight battery. Sensitivity .63 db (at 1 KHz.).

Now trace signals or trouble shoot fast. Inject signals or wire unused circuits into existing boards. Scope probes, Test leads lock into Dynagrip inset. Plastic construction - no springs or pivots. Thousands of operations. PC14 14 pin PROTO-CLIP PC16 16 pin PROTO-CLIP



#### Davred' Metal Boxes

If you've been searching for some handy little project boxes, look no further

These little beauties are finished in two-tone duco and easy to work on.

	Length	Width	Depth	Price
No. 1	82	70	56	\$1.95
No. 2	100	82	54	\$2.25
No. 3	127	89	54	\$2.50
No. 4	140	120	90	\$2.90
All din	nension a	are mm.	No. 4 E	юх
	commis			

Exclusive from \$1.95



#### Plastic Box PB2

Black with aluminium base. Is ideal for all projects etc. Size 100 mm x 60 mm x 27 m

Only \$1.50

#### Mail Order ADDITIONAL POSTAL CHARGES Instructions

Minimum P . P \$1 00 Orders over \$9.99 must include additional postal charges (see right)

Charge \$5 - \$9 99 \$10 - \$24 99 \$0.50 \$1.50 \$49.99 \$99.99 \$2 50

#### 'Davred' Electrokit 1

One Transistor Radio for boys (and girls) aged 8 to 88.



Ideal for the beginner. No soldering required and comes complete with full instructions. Capable of receiving local radio stations. Requires 216 battery

Special Price \$4.95

37/

#### MJ-020 Test Prods

Not only available in Red and Black but we have changed

to the new better grip, longer prod ONLY 65c each

Help! We ordered the wrong knobs but you're the one to save. Never to be repeated.

Out they go. No. 5070 1/4" Ø shaft. 13 mm diam.

Black plastic with aluminium end.

Only 45c

#### Miniature Wafer PT9 **Trim Pots**

Suitable for 0.1" grid boards. Rated ± 20 %, 0.1W at 40° C. 100, 200, 500 ohm. 1K, 2K, 5K, 10K, 20K, 50K, 100K, 250K, 500K. 1 meg.

Look 15c ea.

#### Dip Board

0.1" matrix.

Plug-in. \$13.50



ORDER AS DIP BOARD

#### CO-AX PLUGS P75A

Standard co-ax. plugs with plastic covered body.

Stock up at this price.



#### Meters

50uA, 500uA, 1mA, 10mA, 100mA, 500mA, 1A, 10A, 10V, 30V, 300V

MR38P 42 mm \$6.25 MR52P 60 mm \$7.00 MR65P 78 mm \$7.50



Special 10 mA MR38P \$4.50

#### DAVRED ELECTRONICS PTY. LTD.

104-106 King Street Newtown Sydney Australia P.O. Box 317 Newtown, N.S.W. 2042. THE NEW BREED IN ELECTRONICS SERVICE Telephone 516-3544


output of gate 1c changes too slowly. Suitable gates are coded CD4011BC (National), SCL4011AE (Solid State Scientific), HEF4011P (Philips) or CD4011BE (RCA).

The power supply consists simply of a three terminal regulator, a filter capacitor and two diodes, fed from one of the commonly available power transformers.

Construction of the unit should be quite easy, as all components except the power transformer mount on a single printed circuit board (PCB), coded 77pm12. Commence construction by fitting the links. There are 16 of these, none of which need to be insulated. Do not omit the links under the 74C90 devices.

Next fit PCB pins at points where external connections to the PCB are required. We recommend that PCB pins be used at the mounting holes for the 2500uF electrolytic capacitor, as this component must be mounted under the board, and this will reduce the possibility of strain on the copper tracks.

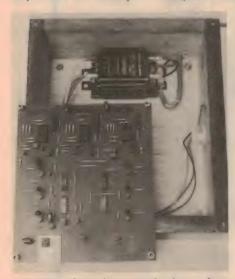
Then fit the passive components, keeping them as close to the board as possible, and observing any polarity requirements. The bipolar components



ABOVE: This photograph shows how the PCB and other components are arranged in the box. Note how the toggle on the play switch has been extended.


should be fitted next, but do not at this stage mount the LEDs. The three terminal regulator bolts directly to the board, with an L shaped piece of aluminium used as a heatsink. Mount the display ICs as far from the board as their lead lengths will allow, remembering to allow for the front panel clearance.

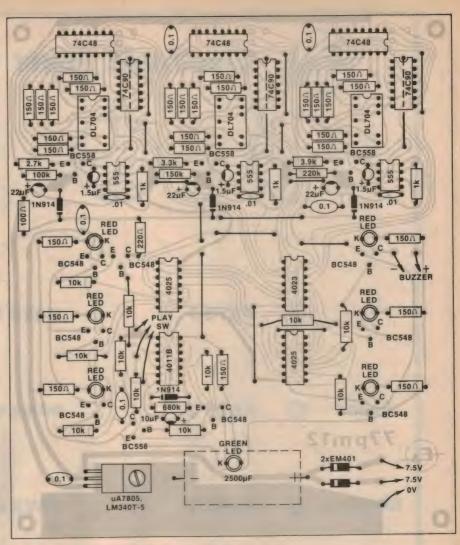The next step is to insert and solder the CMOS ICs. Earth the barrel of your soldering iron to the earth track of the board, and insert and solder the ICs one at a time. Solder the two supply pins first. These are 5 and 10 for the 74C90s, 8 and 16 for the 74C48s, and 7



guide you in the construction of the PCB assembly. Note the links under the the regulator heatsink. 74C90s.

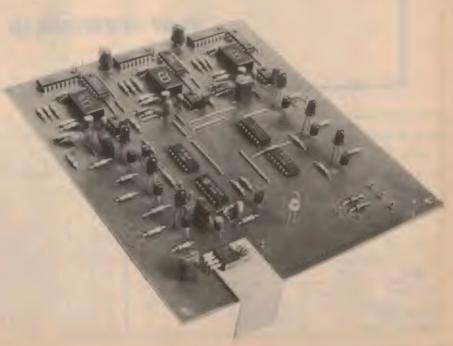ABOVE: Use the overlay diagram to BELOW: Photograph showing the finished PCB assembly, complete with





#### **Electronic Poker Machine**







PAYS 3

PAYS 70

Evens PAYS 2

PAYS 12

Mystery O PAYS 1

PAYS 8



#### **PLAY IN PROGRESS**

PAYOUT CALCULATION TABLE				
PRIZE	NUMBER OF WINNING COMBINATIONS	VALUE OF PAYOUT	NUMBER OF WINNING COMBINATIONS x VALUE OF PAYOUT	
777	1	70	70	
77-	9	12	108	
-77	9	8	72	
7	90	3	270	
EVENS	125	2	250	
MYSTERY	180	1	180	
TOTAL NUMBER OF WINNING 414 COMBINATIONS  TOTAL VALUE OF PAYOUT 950				


ABOVE: The full sized reproduction of the front panel can be copied or used directly as required.


LEFT: This table shows how the values of the various prizes are combined to arrive at the total payout value and the total number of winning combinations.

and 14 for the gates.

The only components remaining to be fitted should be the LEDs. Mount the front panel to the PCB using 13mm spacers, in the position that it will occupy when fitted to the case. Insert the LEDs in position, and solder them only when they are correctly mounted to the front panel, remembering to check their polarity.

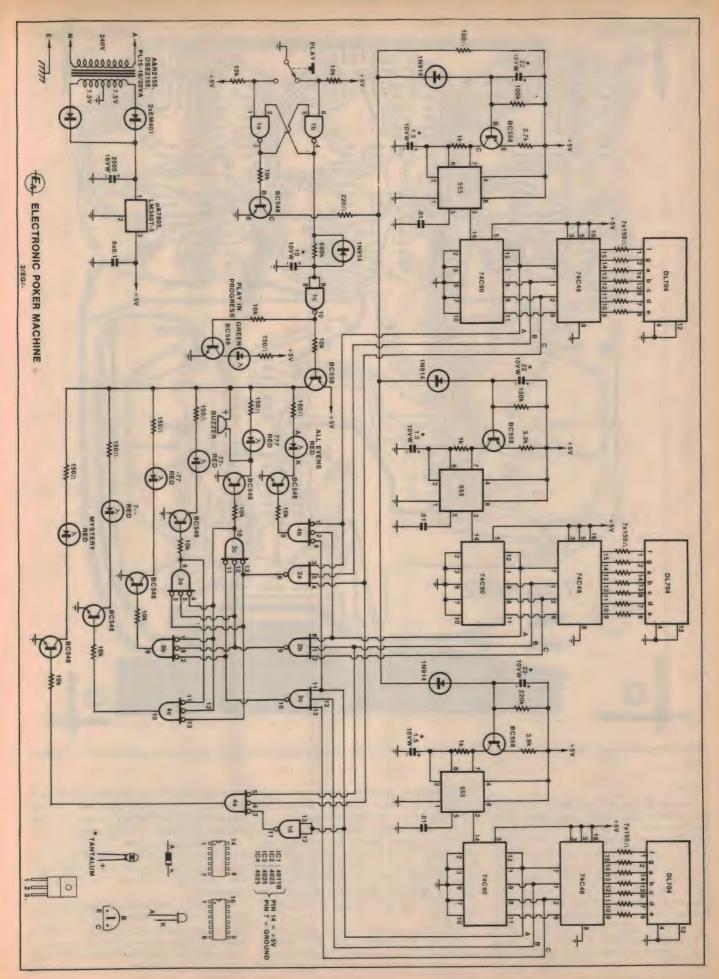Connect up the transformer and the play switch, and while monitoring the output voltage of the regulator, switch on. The voltage should rise to 5V, the green LED should emit, and the three displays should come on. If the displays cycle without stopping, switch off and recheck the connections to the play



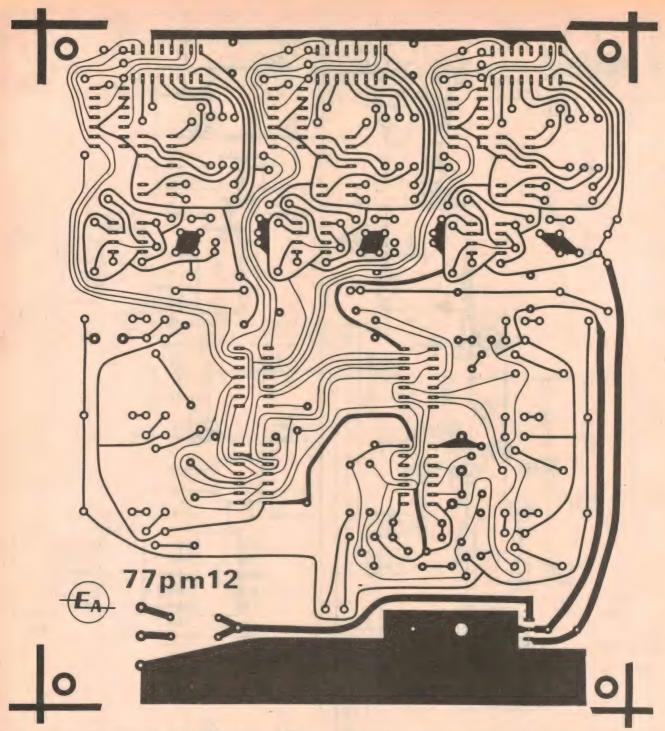

Shown above is a full sized copy of the PCB pattern which can be used to make your own board. It is shown from the copper side.

switch.

Assuming that all goes well, wait until the green LED goes out, and then depress the play switch. The displays should all commence to cycle, and when the switch is released, they should slow down, stopping in order from the left. A short time after the right hand display has stabilised, the green LED should go out, while a prize may or may not be displayed.

If a prize LED is illuminated, check that a valid number is displayed. Since the counters cannot be preset, it is impossible to check all possible prize combinations quickly. However, the jackpot and other high prizes can be checked in the following manner.

checked in the following manner.

Operate the play switch repeatedly, until a 7 appears on any of the displays. Then use a clip lead to short out the 1.5uF capacitor connected to the appropriate 555. This can be done by connecting between the lower end of the 1k resistor and the lowest transformer PCB pin.

This will "freeze" that oscillator. Continue to operate the play switch until a second 7 appears. Freeze this in the same manner, and repeat the

process until the display reads 777. When the green LED goes out, the top right hand LED should emit, and the buzzer (if fitted) should sound.

In a similar manner, 77-, -77 and 7-can be tested. The remaining prizes should occur often enough for them to be checked without freezing the oscillators.

Once you are satisfied that all is correct, the final assembly can be carried out. If any faults are evident, check for solder bridges and incorrectly mounted components. Only if all else fails should you suspect the ICs.



#### **AUTOMOTIVE** TUNE-UP INSTRUMENTS

#### Three-In-One Tune-Up Meter

Ideal for "Weekend Mechanics" or Pro's



- Pays for itself with just a couple of tuneups Helps you keep your car in top shape for
- best operating performance and
- Measures dwell, engine rpm and voltage on an easy-to-read colour coded 41/21
- Easy to use just connect two leads to your engine

Kit CM-1073, \$48.00

#### **Deluxe Timing Light**

flashes brighter than daylight



Helps you keep your car properly timed for better driving efficiency, cleaner running, smoother performance and increased gas economy. Features a handy inductive pickup that snaps directly around the #1 spark plug wire without removing wire, using adaptors, etc. (Recommended for GM-HEI and other systems, where high voltage may be present.) Has a super-bright xenon flash bulb that can be seen easily even outdoors. Can be hooked up while the engine is running, and won't interfere with other auto test equipment either. Comfortable pistol-grip handle, insulated blue-plastic housing. Polarity protected. Powered by your car's battery or a separate 15-volt supply. With all cables, pickup and clips.

Kit CI-1040, \$63.00

#### Low-cost professional-grade Engine Analyzer

Shows dwell, rpm, amps, volts, ohms, spark output, alternator and point condition

- Keep your car running like new
- Easy-to-read colour-coded meter
- Outstanding ± 3% accuracy on all ranges
- Complete with all leads and accessories



This professional-grade instrument performs the tests you need to tune up your car for improved performance and best fuel economy. Tests conventional, magneto, transistorized, and most capacitive discharge ignition systems - both positive and negative ground, any voltage, on any 3, 4, 6 or 8-cylinder engine. The CM-1050 Analyzer permits rapid testing and servicing of the storage battery, generator or alternator, voltage regulator, starter, distributor, ignition circuit (points, condenser and coil), accessories and all the electrical wiring. Easy to connect and use — makes home tune-ups a snap. The large 6" meter is colour-coded for easy reading. Unlike most other engine analyzers, there is no need to recalibrate the for easy reading. Unlike most other engine analyzers, there is no need to recalibrate the unit between functions — all you do is turn the rotary switch to the desired range and you're ready to test. Accuracy is  $\pm 3\%$  on all settings, over a wide range of operating temperatures. Operates on 3 standard "C" batteries (not supplied). Has convenient carrying handle. Comes complete with all leads and accessories, ready to build quickly and use.

Kit CM-1050, \$143.50



#### **Exhaust Gas Analyzer**

checks fuel efficiency-Shows air-fuel ratio and percent carbon monoxide

Monitors your car's exhaust for minimum air pollution and maximum effi-ciency by measuring thermal conductivity of the exhaust gases. Shows the air-fuel ratio, combustion efficiency and the percentage of carbon monoxide in the exhaust. The CI-1080 is essential when you're tuning up a car which must meet specific requirements for exhaust emissions, or when you simply want peak operating efficiency. Comes with all cables and tubing for easy connection.

☐ Kit CM-1073

☐ Kit CI-1040

\$106.50

	Carlo			(it CI-1080,
		-		-
ORDER BY C	OUPON NOW	OR COME T	O OUR SHO	WROOM
Please rush m	ne the kit of my	choice. My ch	neque for	

is enclosed plus \$2.50 for package and post. Name .....

Address ☐ Kit CM-1050

☐ Kit CI-1080 Send to: W. F. Heathkit Centre

220 Park St., South Melb. 3205. Phone: 699-4999

WF 516/7

# Making your own printed circuit boards

Producing printed circuit boards for your own circuit designs or for projects described in this and other magazines can be very satisfying. This article shows that doing so is not as daunting as you may have thought.

by ROBERT FLYNN

There are a number of methods available to the constructor who wishes to make his own printed circuit boards (PCBs), and in this article three of them will be described. Method one entails drawing the required wiring pattern directly on the copper laminate using a suitable resist "ink" as the drawing medium, followed by the chemical etching of the board.

Method two again requires the pattern to be prepared directly on the copper laminate, but this time rub-on transfers are used as the resist medium. Etching of the board is the same as

method 1.

Method three calls for the production of the board pattern (or artwork) on a transparent plastic film, coating of the board with a photo resist, exposure of the board to light through the transparency and subsequent development of the pattern on the board. The board is then ready for etching.

For fairly simple circuits method one is a cheap and quick way of producing a board. But for complex circuits or circuits that have to be produced on a board with high component density or many closely spaced conductors, it is very difficult to achieve sufficient accuracy to produce a satisfactory board. Because of this we will only deal briefly with the direct ink-resist method.

To produce a PCB using this method, the blank material should be cleaned on the copper side using a scouring pad, water, and some proprietary cleaning powder such as Bon Ami or Ajax. Once the copper is bright it should be dried with a paper towel and from then on handled on the copper side as little as possible.

Assuming that the layout of the circuit has been drawn on a piece of paper or is to be copied from a PCB layout reproduced in a magazine, the next step is to place the board copper side up on the workbench and cover this with a piece of carbon paper.

Next place the circuit layout diagram

over the carbon paper and once you are certain that it is in position over the board, trace the pattern outlines using a hard pencil or a ball point pen. The centres for holes can be transferred to the copper using a small hammer and centre punch to make a light pop mark through the paper into the copper.

The paper layout and carbon paper can now be removed from the laminate and the outline on the copper can be filled in with resist. The type of resist most often used is bituminous paint. This paint is very thick and it is a good idea to stand it in a dish of hot water while using it, in order to make it flow more freely. Use an artist's paint brush or a sign writing pen to apply the paint, taking care not to run adjacent lines into each other. After the paint has been applied satisfactorily and it has been allowed to dry the board is ready for etching.

by rubbing the carrier film with a smooth pointed instrument such as a ball point pen or knitting needle. Because the transfers are machine made, it should be possible to produce a more complex board using them than using the paint method.

Both methods described so far are very near "total loss" systems as far as board artwork is concerned, for, even though the paper pattern remains after the board is etched, the tedious business of re-tracing the pattern and painting-in the outline has to be repeated if any further copies of the board are required.

The photo-etch method of producing PCBs, using artwork prepared with stick-on pads and tapes on a transparent plastic film, enables anyone to produce boards of a high quality while retaining the artwork for repeated use. These pads and tapes are

The Dalo printed circuit board pen referred to in the article.



An alternative to using paint as a resist for this method is a "Dalo" pen. This is a felt tipped pen with a resist solution as its ink. It can be used alone or in conjunction with bituminous paint to produce the board pattern.

The author has not tried method two, but the procedure is similar to method one except that instead of painting-in the traced image on the PCB blank, dry rub-on transfers are used for the resist. These transfers can be bought in various shapes such as termination pads, lines, corners, groups of pads etc. They are applied to the copper by placing the carrier film with the transfers on over the copper.

When the transfer is in the required position it is transferred to the copper

manufactured by Bishop Graphics Inc. of the USA and are available from Circuit Components Pty Ltd, P.O. Box 70, Bexley, 2207. This same company also supplies the photo resist and developer used in the system to be described.

The resist used (CCPR12) is a positive one, which means that when it is exposed to ultra-violet light through the artwork and then developed, the areas of the artwork that are clear will wash away in the developer while the areas that are opaque will remain on the copper as the board pattern resistant to the etchant.

The following materials are required to make photo-etched printed wiring

poards:

Bishop stick on pads and tapes;

Model makers knife (X-Acto, etc)

Clear plastic film;

Printing frame (this may be improvised using a piece of glass and a piece of particle board clamped together with bulldog clips);

Twin twenty-watt fluorescent batten with 20W blue actinic tubes, such as Philips TLA20W, GE F20R12.BL, etc;

One or two plastic dishes;

CCPR12 Photo resist;

CCPD16 Developing powder;

Ferric chloride etchant;

Kitchen oven (gas or electric).

Starting with a circuit layout drawn on paper or taken from a magazine, the next step is to produce a transparency from this. Cover the diagram with a suitable size piece of plastic film and stick it to the drawing beneath with adhesive tape. Using a model-makers' knife, lift the pads from their backing paper and stick them down on the film at component termination points. After all the pads are positioned, make the necessary interconnections between them with suitable width tapes. Start by pressing the tape onto a pad and then pressing it along the required conductor path to the next pad. To cut the tape place the knife blade onto the tape, above the pad, and pull the surplus tape upwards against the blade. This will produce a neat cut without damaging the pad below.

When all of the pattern has been completed it should be checked to make sure all is correct and then turned over and rubbed firmly all over with a small roller, such as the squeegee type used by photographers. The transparency is now complete.

Before proceeding to preparation of the board material, now is a good time to mix the developer. The developer is sold in powder form and 30 grams is mixed with each litre of water. This mixture can be stored in a bottle until

required.

Cut a piece of blank PCB about 5mm larger all round than the pattern, and clean it as described earlier using a clean scouring pad, such as "Scotchbrite", and either "Ajax" or "Bon Ami" powder cleaner. The degree of cleanliness required is far higher than that for the painted-on pattern methods, and the board should be scrubbed until when rinsed clean and held under a running tap, the surface becomes completely wetted without the water contracting into streams across the copper.

When the board passes this test dry both sides with a paper towel, taking particular care that the copper surface is not touched with the fingers. Place it copper side up on the work bench and dust off with a CLEAN paint brush to


remove any lint, dust, etc.

Before coating the cleaned board with resist, the oven should be preheated to 80°-90°C (176°-194°F) and turned off when this temperature is reached.


Returning to the cleaned piece of



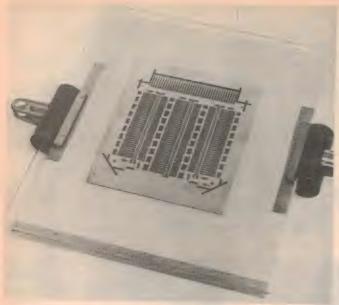The top picture shows a completed piece of artwork and some of the materials used to produce it. Centre, the photo-resist being spread over the copper laminate. Bottom, the materials required to improvise a printing frame.



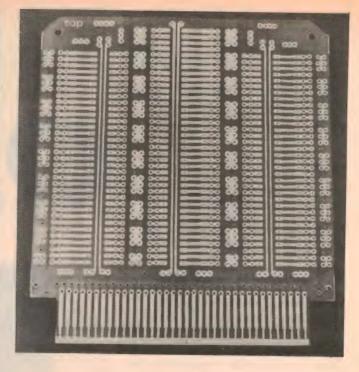Above, printing frame assembled with board and transparency, ready for exposure. Right, the etched board, stripped of resist and partially drilled.



board, pour a small pool of the resist onto the centre of the copper and spread it smoothly over the board with a CLEAN 12mm paint brush. If the resist looks streaky when wet, don't worry as this usually evens out during the drying process. The paint brush used should be later cleaned with methylated spirits and then soap and water, and kept for future use in board making only.

Place the board resist side up on an asbestos mat or biscuit tray and put it into the upperhalf of the preheated oven for about 15 or 20 minutes. The resist should now be dry and the board should be removed from the oven and allowed to cool — without being exposed to direct or reflected sunlight, fluorescent or red lighting. (Low level incandescent can be used, however. Darkroom conditions are not required for any part of the process.)

When the board is cool, place the previously prepared transparency face down on to the glass of the printing frame. Cover this with the board, copper side down and then close the frame. The board is now ready for exposure and the light batten should be placed on the bench with the tubes to the top. Exposure time will depend on the thickness of the resist coating, the transparency of the film and the distance of the board from the light source. If the printing frame is placed directly on the light tubes, glass side down, then an exposure of three to four minutes should be sufficient. If the exposure time exceeds four minutes no harm will be done, but a shorter time may result in underexposure and a board that will not develop.

The pre-mixed developer should now be poured into a plastic or glass developing tray and the board removed from the printing frame and put into the developer copper side up. The liquid should be agitated gently by tilting the tray from side to side and after about half a minute the board pattern should begin to appear. Within about two minutes all the exposed area of the resist should be dissolved and the board should be removed from the developer. Rinse it well under the tap and dry with a soft cloth. After this the board should be put aside in free air to stabilise for about half an hour.

The etchant can now be mixed and, though there are many to choose from, anhydrous ferric chloride is about the safest to use as well as being the most readily available in electronic parts

Mix 500 grams of the ferric chloride with 1.5 litres of COLD water in a plastic dish. The powder should be added slowly to the water and the mixture stirred continuously till all the powder is dissolved. While this operation is taking place a lot of heat is generated, so be careful in handling the dish. When mixing is complete pour the etchant into a plastic developing tray and slip the board into the solution, copper side up. Agitate the dish continuously, taking care not to spill etchant on any surface it may damage.

The time required to etch a board depends on many factors: the strength, temperature and age of the solution, the amount of copper to be removed, etc. New etchant may etch a board in five minutes, but etchant that has been used many times may take a lot longer than this.

When etching is complete, remove the board from the etchant and wash well in water. Apart from drilling the necessary holes the board is finished. Although the resist is not a flux, it can be left on the board as a protective finish through which it is possible to solder. As an alternative, the resist can be removed from the board with methylated spirits and a coat of flux made up from 15 grams of powdered resin dissolved in 115 millilitres of methylated spirits applied to the full surface of the copper side of the board.

The above etchant and etching procedure is also used for making boards by methods one and two. Both bituminous paint and the resist from "Dalo" pens can be removed with kerosene or mineral turpentine. The PCB transfers can be removed with household powder cleaner. After cleaning a coating of the flux previously described should be given to the boards.

Remember that the chemicals used in the board making methods described in this article are injurious if swallowed. Decant them into clearly marked bottles after use and store them out of the reach of children. Clean up any spillage of solutions immediately. Cleanliness not only aids safety, but also helps achieve good results in board making.

- Resist and miscellaneous materials. Positive photo resist, developer, ferric chloride, ammonium persulphate etchants, opaquing paint, flux, laminate in stock sizes 5" x 3", 6" x 4", 8" x 6", 12" x 10" both fibreglass and phenolic.
- For detailed price list, instructions and supplies contact

#### CIRCUIT COMPONENTS (A/ASIA) PTY LTD

383 Forest Rd, Bexley, NSW 2207 Telephone 59-6550 — 59-3720

#### SUPER CLOCK FROM TECHNIPARTS

#### **New from National**



#### MA1010A

- \* Same as Popular MA1002B except with .84" Digits
- ★ 50/60HZ Operation
- \* Price \$23.50 Post Free
- \* Transformer JT197 \$6.50 Post Free

#### **TECHNIPARTS LOW COST CRYSTAL TIMEBASE KIT**

- \* Using National MM5369 3.58 MHZ to 60HZ Divider
- \* Includes PCB, Crystal, Divider, Trimmer etc.
- \* PCB has allowance for \$ 6 and \$ 10 Counters also TTL buffered output = 3 IC'S.
- \* Great to use with Clock Modules, Timers etc.
- ★ Power Supply 3—15VDC

PRICE: \$6.75 Post Free

1HZ + 10HZ + TTL Out Option \$3.20 extra

Sydney 709 5293

Adelaide 42 6655

Perth 381 5500

Launceston 31 2511

Melbourne 848 3777

Brisbane 52 3166

Hobart 34 2233

We will be closed between Christmas and New Year

#### **NATIONAL MA1003** CAR CLOCK MODULE

- \* 12VDC operation
- \* Maintains Timekeeping Down to 5VDC
- ★ Display Blanking with Ignition off Draws 5MA.
- ★ Draws 100MA with Ignition on.
- ★ Just add 3 switches + DC 12V.
- \* On board 2MHZ crystal.

PRICE \$27.00 Post Free.

**ECHNI** Woolworths Arcade, 95 Latrobe Terrace, PADDINGTON, 4064 P.O. Box 118, PADDINGTON, 4064

Ph: Brisbane (07) 36 1474 Trading Hours (8.30am - 5.00pm Mon. - Fri., 8.00am - 11.15am Sat.)



Screwdriver temperature selection, close

temperature control.

to sensitive solid state components.

Temperature is controlled within a

narrow band. Selector dial on cabinet.

## **Low-cost Battery Condition Indicator**

by B. J. SIMPSON\*

Monitoring the condition of dry batteries in battery-operated equipment can be inconvenient if no meter is fitted, as in the case of compact or inexpensive devices. This article describes a simple, low-cost battery indicator which is small enough to fit to most appliances and which gives a clear "good/bad" indication.

A problem with battery-operated apparatus is that the performance tends to fall off as the supply drops below the nominal battery voltage, with an increase of the battery impedance. Thus, it is necessary to check the battery voltage regularly to ensure good performance, and this check should be done on load.

Therefore a need often arises for a cheap built-in battery checker, suitable for retrofitting to existing apparatus. These two requirements usually rule out a meter.

Furthermore, if the load imposed on the battery varies with operating conditions, it is desirable that the battery checker impose a predetermined, fixed load, selected as being representative.

A precise measurement of battery voltage is unnecessary if one can ensure that the voltage, under test, lies between the nominal voltage and a predetermined lower voltage at which performance starts to deteriorate. In other words, one can use a simple good/bad indicator.

The circuit of the battery checker is given in Fig. 1(a). It contains two transistors which form a bistable switch, which triggers into one of its two states in response to an input voltage applied between the slider of R2 and negative rail. When the input voltage is high enough to produce slightly greater than unity gain in the Q1, Q2, R5, R6 loop, the switch snaps on and current flows through the light-emitting diode D1 and the series resistor R4.

When the input voltage falls below the threshold voltage, the switch snaps back to the off condition.

In all trigger circuits of this kind, the circuit triggers off at a slightly lower voltage than that at which it triggers on. This will vary with the nominal battery voltage employed but, in this application, it is only the on-threshold that is of interest.

The important thing about this circuit is that the on-threshold voltage is remarkably constant over a wide range of battery voltages. It varies typically only

from 0.94 volt with a 3V battery supply to 0.955 volt at 18 volts.

The fact that the on-threshold voltage for this circuit is constant over a range of a few volts renders the circuit very suitable for use in a good/bad indicator. In practice R2 is so adjusted that the off-threshold condition is just realised at a predetermined battery voltage selected as the lowest at which the apparatus will operate satisfactorily.

The LED will then light when the circuit is connected, via the push button, to a supply having a higher voltage than the

tery load for many applications.


The value of R4 is selected for the specific application, depending on the nominal voltage of the battery to be tested. The value of R4 can be calculated from the expression R4=(E-3)52 ohms, where E is the nominal battery voltage. The result may be rounded off to the nearest preferred value.

It seems unlikely that a battery load lower than 20mA would be required, and below 10mA the illumination of the LED becomes rather poor. It is more likely that a higher load current may be required and it is possible to connect a further load resistor in parallel with the LED/R4 combination to draw extra current. The maximum recommended current for the transistors used is 100mA, and then only for a brief test.

The value of the extra load resistor is easily found by experiment, however, an approximate value is given by (E-0.75)/A, where E is again the nominal battery voltage, and A is the additional current (over the 20mA) in amperes.

The values of R1 and R2 in the circuit are suitable for batteries up to 18 volts or so, and therefore cover most applications. They draw a negligible current of 0.4mA at 18 volts and less at lower voltages.

Resistor R1 could be omitted if desired, and R2 made, say, 10K ohms, but this would reduce the sensitivity of set-

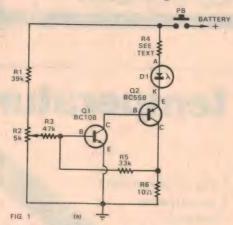

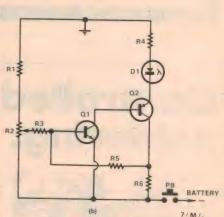


Fig. 1. The basic circuit (a) is quite simple and is intended for a positive active circuit. The negative active arrangement is shown at (b). It can also be used where both sides of the circuit are active, see text.

predetermined minimum. When the LED does not light the battery needs to be replaced. A green LED is therefore a good choice.

The minimum battery voltage at which this circuit will operate is set by the sum of the voltages across the LED, Q2 and R6, with the circuit in the on condition. This amounts to about 3 volts, which means that the circuit is limited to nominal battery voltages of 4.5 and above.

Resistor R4 determines the current through the LED, and also the load on the battery whilst being tested. In the original design, a load of 20mA was selected; a value which provides good LED illumination and a reasonable bat-

ting R2 for the minimum acceptable battery voltage. Conversely, juggling the values of R1, R2 and possibly adding a further fixed resistor between R2 and ground could provide greater sensitivity of adjustment for a specific application.

To install this circuit, only the LED and a miniature push button are required on the panel; items which can usually be accommodated in an existing unit without too much trouble. The rest of the checker circuit can be located as convenient.

To set-up it is necessary to decide the minimum acceptable battery voltage. For most dry cells, this is often taken as 1.25 volts per cell. This is a margin of a little over 15%, but specific cases may suggest

<sup>6</sup> Eden Avenue, Turramurra, NSW 2074

a closer or a wider margin.

Apply to the checker circuit a voltage at the minimum value which has been selected. This is conveniently done by using an external variable supply; positive to the junction of R1 and R4, negative to ground. Then adjust R2 so that the LED just comes on. Check the on voltage (not the off voltage) by varying the variable supply voltage, readjusting R2 until, with a rising voltage, the LED comes on at the selected minimum.

The physical assembly of such a simple circuit hardly needs comment. Nothing is critical. For those who may wish to use a printed board layout, Fig. 2 gives a pattern and component layout. An alternative circuit for negative active systems is shown in Fig. 1 (b).

Where two batteries are used to give positive and negative voltages about ground, Fig. 1 (a) can be used to check both batteries in series. Connect the push button to the positive active pole and the R2, R6 junction to the negative active pole.

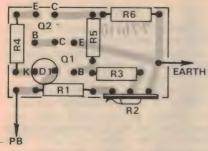



Fig. 2. While simple enough to construct without a printed board, a suitable pattern may be useful where the indicator is to be included in a new board design. The pattern is shown from the component side, full size.

Readers may envisage other applications for this circuit. For example, it will provide a simple monitor of an automotive system during operation. The monitoring can be permanent if the push button is omitted, the low current drain permitting this. In this application it would be necessary to remember the effect of the switching hysteresis, and it may be necessary to set up the circuit for the off-threshold instead of the onthreshold.

There is also the possibility of providing a universal battery checker, which could cater for batteries with voltages ranging from 4.5V to 30V or so. Provision could be made for two or more values of load current to be drawn from the battery under test.

The cost of components for this circuit at present retail prices works out at less than \$2.00; nearer \$1.50 if the transistors are bought at bargain prices. The transistors are not critical, and almost any equivalent or near-equivalent types will work well. The cost and convenience of this circuit compares favourably with any alternative that is available, and is certainly cheaper and easier to install than a meter.
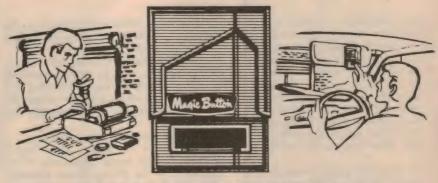
# magic button do-it yourself automatic door operator



The Magic Button Electrolift G5460A
is made to be easily installed
by the experienced handyman.
All parts, hardware and simple step by step
instructions are included.

Special Direct
Over The Counter Price for December


\$330

including tax and one transmitter.

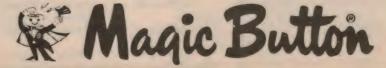**Magic Door Centre** 

147 York St., Sydney. Opposite Town Hall 241-245 Mitchell Rd, Alexandria. Opposite St Peters Station

please include \$8 for delivery in N.S.W. \$15 interstate.



771933

## Metal locators are fun-try one!

One electronic device to capture the imagination in recent years is the metal detector or, as it is sometimes called, treasure detector. While we have not heard of anyone finding any vast quantities of treasure with these devices, they do have their serious uses and learning how they work can be an interesting exercise.

#### by WALTER NEVILLE

Metal detectors in one form or another have been around for many years - since well before World War II in fact. Their main role initially was a military one - to detect mines in the path of advancing troops. We have all seen pictures of an army sapper wearing a pair of headphones and holding a search coil ahead of him on a long handle. Hopefully, his metal detector will find the mine before the mine finds

More peaceful uses for metal detectors are to locate buried water pipes, electric cables in walls, nails in timber which is to be sawn and, at a more imaginative level, to find coins, jewellery, watches etc buried in the sand on the beach.

Unfortunately, these devices are often portrayed in somewhat exaggerated style, implying that they can detect quite small pieces of metal at great depths. In fact, the sensitivity of most of them is quite limited, usually to a few inches unless a very large mass of metal is involved. And even if it's as large as a pirate's treasure chest (or a filing cabinet) it is unlikely that a typical metal detector will find it if it's more than a couple of feet under the surface.

In short, any pirate treasure that is buried more than a few feet below the surface is pretty safe as far as metal detectors are concerned. If your pirate treasure map tells you to walk 40 paces east, 30 paces west, then dig, we are afraid the only way to confirm the authenticity of the map is to do just that

But, pirate treasure jokes aside, what of the other suggested uses? Just how good are these devices at locating such objects? Not as good as we would like. might be a fair answer, but the performance of one of the units we are about to describe would seem to be fairly typical. It will detect an Australian 20c

coin at about 125mm (5in) in air, on the basis of a minimum discernible indica-

worth serious consideration. Anything above it would be most welcome, but may be difficult to achieve within the normal constraints of reasonable size and cost

How do these devices work?

There are at least two broad approaches to metal detection. What appears to be the original concept, developed as the army mine detector, is the beat frequency system. This is the system used in the units we are about to describe.

It uses two RF oscillators, both designed to operate at the same nominal frequency, usually somewhere between 100kHz and 300kHz. The output of the two oscillators is fed to a common detector, followed by an audio amplifier driving an earphone or speaker.

The system is designed to detect the difference in frequency between the two oscillators, which appears as an audio tone equal to the difference frequency. Thus, if both oscillators are

tion after a little practice. Any performance below this is hardly on exactly the same frequency there will be no audible tone generated. But if one oscillator is, say, 200Hz lower or higher than the other, then a 200Hz tone will appear at the output.

One oscillator, called the reference oscillator, is a conventional arrangement using an ordinary coil and capacitor as the frequency determining elements. The other oscillator, the search oscillator, uses a similar or identical circuit, but with a different form of

This is the search coil. It is relatively large - 10 to 15cm across - and consists of only a few turns. It is normally mounted on the end of a long handle to enable it to be moved over the surface of the ground.

In the presence of metal this coil will change its inductance (not its "conductance" as stated in one explanation) and this will change the oscillator frequency.


Suppose that the search oscillator was running 200Hz higher in frequency than the reference oscillator, producing a 200Hz tone in the earphone. If we now bring the search coil close to a mass of metal this will (normally) reduce the inductance and cause the search oscillator to increase in frequency to, say, 250Hz higher than the reference oscillator. Thus the audio tone will shift from 200Hz to 250Hz.

This is what the operator looks for when searching; a change of note, no matter how slight, as he moves the search coil back and forth. With practice, quite small changes are readily discernible, particularly if the coil is moved rapidly over a suspect area.

The other main system uses two coils in the search head, mounted at right angles to each other. The electronics consist of a high gain audio amplifier, feeding an earphone or speaker, and with the input connected to one coil

#### SENSITIVITY TABLE

	28-134	28-181
Copper water pipe		
(½in)	90mm	180mm
Side cutters	50mm	100mm
Razor blade	65mm	90mm
Aust. 5c coin	50mm	90mm
Aust. 2c coin	65mm	100mm
Aust. 20c coin	75mm	125mm
370ml drink can	,	
(aluminium)	125mm	225mm
Scissors	75mm	110mm
Filing cabinet	375mm	600mm
Man's watch with		
metal band	50mm	100mm

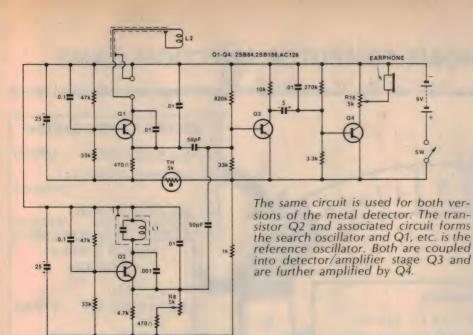

and the output to the other.

With the two coils at right angles there is minimum coupling between them, thus preventing the amplifier from going into oscillation. In operation the gain would be advanced until the amplifier was on the verge of oscillation.

If, in these circumstances, the search head is brought near a mass of metal, the critical minimum coupling between the coils is upset and the amplifier, already on the verge of oscillation, spills over and gives out an audible note.

(Editorial note: A metal detector employing this principle was described in E.A. for January 1970. File No. 3/MS/20.)

So much for some of the background to metal detectors. Is it practical for the home constructor, even a beginner, to construct one?

The answer is yes, particularly as there are now a couple of kits on the market which not only use proven circuitry, but eliminate the hassles normally associated with getting together all the bits and pieces. In particular, a kit of this kind can solve many of the hardware problems which might otherwise be beyond the mechanical resources of the home constructor.

But just because we have written this story around these kits, it does not mean that this is the only way they can be built. Virtually all the electronic components are routine devices which should be available from almost any parts supplier. We will have more to say about some of these later on. As far as the mechanical side is concerned, the individual reader can make up his own mind as to what he can construct himself and how elaborate he can make it. There is even scope for experiment in improving the original performance.

Both kits are Science Fair products, distributed through the Tandy stores. One is the Science Fair kit No. 28-134

The simpler version of the detector, built on a plastic chassis. Note how the search coil is wound on the clear plastic portion of the original box. Sticky tape holds the coil in place and the two halves of the box together.



is to be mounted.

single compact unit.

and the other is kit No. 28-181. Both use the same circuit, and similar components, but there is considerable difference in the finished product.

The 28-134 kit is the cheaper of the two (\$9.95) and should not really be considered as anything more than an instructional device to demonstrate, in a practical way, how this kind of metal detector works.

A study of the accompanying circuit will help explain how the theory discussed earlier is put into practice. The transistor Q2, along with the coil in its collector circuit and associated components, forms the reference oscillator. The output of this oscillator is fed via a 50pF capacitor to the base of Q3, which functions as a detector and amplifier.

Transistor Q1, with the search coil in its collector circuit and a similar circuit configuration, forms the search oscillator. Output from it is also fed to the base of Q3 via a 50pF capacitor, where it is mixed with the output from the reference oscillator. Output from Q3 is the audible difference frequency which is fed to Q4 for further amplification and then to the earphone via a volume control.

vantage.

The first thing to do with a kit of this kind is to check off the components against the list in the instruction folder. Quite apart from the obvious reason for doing this, it provides an opportunity for the beginner to acquaint himself with, and identify, components with which he may not be familiar. Resistors, in particular, need to be identified by their colour code (supplied) and the experience gained from this exercise will prove invaluable.

The 28-134 kit is packed in a small plastic box, the bottom of which, when inverted, becomes the chassis on which

the device is built. The box is perforated and each row of vertical holes is identified by letters, and each horizontal row by numbers. This enables the instruction sheet to identify any group of holes in which a particular component

In most of these kits only the bottom

of the box is used but, in this case, the top is also used. Note how these two fit together before the package is opened,

so that they can be fitted back together.

The top of the box (clear plastic) is used

as a former for the search coil, making a

comprehensive set of building instruc-

tions, there is little point in duplicating these in this article. We will content ourselves with commenting on one or two points which we feel can be emphasised or enlarged upon with ad-

Since the kit comes complete with a

Other components, capacitors, transistors, diodes etc are also portrayed pictorially as an aid to their recognition and lead identification. One of these which is not quite up to date is that for the electrolytic capacitor. The current trend is to identify the negative lead with a black band running the length of the capacitor body, sometimes accompanied by a negative sign (—) in a small circle.

Other capacitor markings can also be confusing. For example, the figures "104" on a plastic capacitor can easily throw the beginner who is looking for the 0.1uF quoted in the parts list. In fact, they mean the same thing. The

#### 2650 HOME COMPUTOR SELECTION GAME

DO YOU WANT TO BUILD A POWERFUL, LOW COST HOME COMPUTER START HERE

SELECT A BASIC SYSTEM

A. EA BABY 2650 \$75.00

B. KT 9500 COMPLETE \$199.00

C. EA 2650/KT9500 CONVERSION \$142.00

#### POWER SUPPLY DECISION

+5, -12V

8

9

Q

18

79

21

A. 1A LCPS KIT \$15.00

B. AT 512 ASSEMBLED UNIT -12

\$27.50

C. AT 1250 HI-CURRENT \$47.50

#### LOW COST TV TERMINAL

A MUST TO GET THE MOST OUT OF YOUR SYSTEM - INCLUDES AUTOMATIC SCROLLING, CURSOR, FULL EDIT FACILITIES

LIMITED

QUANTITY

ONLY

CASSETTE INTERFACE

For Low Cost Bulk Storage

CT750 (Assembled) \$37.50

Radio Electronics low cost kit with test tape and

instructions

\$22,50

#### SOFTWARE GAMES PACK

TAPE WITH LISTINGS \$12.50

ASTRO TREK, HANGMAN, NIM. POKER MACHINE, MASTERMIND ETC

#### MEMORY

4K STATIC RAM KIT ..... \$100,00 1K RAM STICKS .....\$ 25.50

#### YOU WIN!!

YOU NOW HAVE A MOST COST EFFECTIVE HOME COMPUTER SYSTEM

22 23 24

14

16

15

2650 USERS GROUP

INITIAL MEMBERSHIP INCLUDES PROFESSIONAL DOCUMENTATION PACKAGE CONTAINING A MOST COMPREHENSIVE SOFTWARE LISTINGS INCLUDING

> TEXT EDITOR ASSEMBLER **BLOCK MOVE** ASTRO TREK BAUDOT ROUTINES VARIOUS GAMES SORTING ROUTINES MATHEMATICS PACK-AGES ETC, ETC \$40.00

ALSO INCLUDES UP DATE SERVICE

**NEED MORE INFO send** \$1.00 and return address for full details

2650 HOME STUDY PROGRAMMING COURSE CASSETTES AND WORKSHOP NOTES

Available soon

## APPLIED

#### APPLIED TECHNOLOGY P/L

109-111 Hunter St., Hornsby 2077.

Phone: 476 4758, 476 3759

Hours: Mon - Fri. 9 - 5, Sat All Day.

#### **Metal Detector**

combination "10 4" stands for 10 followed by four zeros, or 100,000 (pF). And 100,000pF equals 0.1uF.

A small magnifying glass is a handy addition to your tool kit, since many modern components are so small that the information printed on them is almost impossible to read unaided. It will also help to identify some of the more subtle colours used to code small resistors.

There were some changes in our kit (transistor type numbers was one) but all were covered by appropriate notes. Check these before pressing the panic button in the event that there appears to be an error. If there really is a mistake, take the kit back to your nearest Tandy store and explain what is wrong.

Assembly is best performed by simply following the step-by-step instructions, ticking off each step as it is completed. This approach may prove frustrating to those who can read a circuit and we admit that, half way through the exercise, we had doubts that the thing would ever work. But it did — immediately it was switched on. We imagine you will be similarly successful.

In a simple project of this kind there is not much incentive to make a neat job of the underside wiring, particularly as one may wish to ultimately salvage the components for other experiments. For this reason we trimmed the leads by only minimal amounts, leaving most of the components sitting well above the chassis. In a few cases, however, the full length of the pigtail is needed to reach the appropriate junction point.

One part of the job which is a little tricky is soldering to the coil pins. These are barely long enough to come through the plastic, and some damage to the plastic around this area is almost inevitable. Also, the pins are quite close together and some care may be needed to prevent bridging them with solder.


Winding the coil calls for a little care, although ours turned out very neatly. The first thing to do is to unwind the hank of wire supplied, and wind it onto some kind of holder. (We used the cardboard box in which the kit was packed.) It is almost inevitable that it will tangle while being unwound, and the middle of a coil-winding operation is no time to untangle six or seven metres of fine wire! Wound onto a holder it will be much easier to use.

The coil is wound on the lid of the box and, for obvious reasons, should be as close to the top of this as possible. On the other hand, the box is slightly tapered, creating a tendency for the winding to slip off. Plenty of sticky tape is the answer, particularly for the first turn. Once that is held firmly in place it will support the remaining turns. (Secure the tape dispenser so that

lengths of tape may be withdrawn with one hand.)

To secure each end of the coil we pulled an old trick from the days of home wound radio coils. Where the winding is to start drill two small holes (1/16in or smaller) about 5mm apart, parallel with the top of the box. Drill two similar holes where the coil is to finish, allowing that the coil will be about 4mm wide. (Leave, say, 6mm.)

The beginning of the coil is anchored by passing the wire back and forth through the two holes several times, leaving enough free wire for ultimate

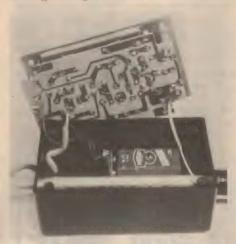

The 28-181 kit, showing how the board is mounted on the front panel. Note how the battery is wedged in the case.

connection to the chassis. Wind on 13 turns which, in our case, left insufficient for another turn, but plenty for connection to the chassis. Again, secure the wire by passing it back and forth through the two holes. Finally, tape the winding in several places to protect it.

The ends of the coil should be trimmed, cleaned, and soldered into the circuit. The two halves of the box are then mated and secured with sticky tape. The battery is a miniature 9V type, such as the 216, or similar. Current drain is modest, between about 4mA and 10mA, depending on the level of note being generated.

The circuit is set up by setting the pitch control (R8) to its mid position and the volume control (R16) fully clockwise. Adjust the slug in the coil of the reference oscillator until a whistle is heard in the earphone. It should be possible to adjust this for decreasing frequency down to zero (zero beat), then increasing frequency as the slug is turned further in the same direction. Leave it set for zero beat.

In use, R8 is adjusted to give the lowest audible frequency and on that side of zero beat where the presence of metal causes an increase in frequency. Under these conditions the ear is most sensitive to small changes in frequency.

As we said earlier, the 28-181 kit is designed around the same circuit, but is a much more serious approach as regards hardware and the final form of

the instrument. The price of this kit is \$26.95.

A good idea of its general appearance can be obtained from the accompanying photographs. The electronic circuitry, battery, controls etc are housed in a small plastic box mounted on a telescopic shaft, and fitted with a convenient handle. The search coil is mounted on the other end of the shaft, connected by a coiled cable. The angle of the search coil can be adjusted relative to the shaft.

The circuit is built on a printed board, which makes wiring a good deal easier, and this board is secured to a metal panel which mounts in the plastic box. An attractive decal is supplied which, attached to the front panel, identifies the controls and gives a professional appearance.

The search coil is ready-made and equipped with an electrostatic shield on the underside. This latter feature appears to be very effective.

As with the simpler kit, it is supplied with extensive constructional details, such that almost anyone should be able to construct the device and have it work first time. And, as before, we will confine our remarks to those points which may stand elaboration.

The printed board, as supplied, needed a little trimming in the corner cut-outs before it would fit easily between the panel support pillars. This needs only a few moments' work with a small file.



The search coil supplied with the 28-181 kit. It is fitted with an electrostatic shield on the underside.

The larger section of the telescopic shaft passes right through the box and extends out the other side by sufficient (about 90mm) to support the plastic handle. In our case the holes in the box needed to be enlarged slightly to admit the shaft but, as it is intended to be a push fit, do not be heavy handed.

The black plastic handle proved to be quite a tight fit on the shaft and we finished up hammering it on with a piece of wood. Make sure that the thread on the other end of the shaft is protected by the ferrule before doing this. Note that the end of the box with the larger hole (to take the coiled cable) goes towards the search coil. This cable hole also needed enlarging slightly in our case.

## NOW HEAR THIS!

Our new magnetic cartridge, the Ortofon M 20 Super, will almost certainly be found among the best in every review and test report you are likely to see.

But if you feel weighed down by curves and diagrams, maybe you should skip the reading for a change and concentrate on listening.

When you agree that no other cartridge sounds better than our new M 20 Super—go ahead and buy it.

You can always ask for the literature afterwards. Just to prove that your ears told you the truth and nothing but the truth.

Ortofon accuracy in sound



Latest from Ortofon is the M 20 Super—a unique magnetic stereo cartridge, based on our exclusive world-patented Variable Magnetic Shunt (VMS) principle.

Harman Australia Pty. Ltd. P.O. Box 6, Brookvale, NSW 2100 Telephone: (02) 939 2922. Tlx: 24873

#### **Metal Detector**

The decal is a self adhesive type, and a little care is needed to line up the holes in it with those in panel. However, it appears strong enough to stand pulling off and repositioning if necessary.

The other main points to watch are careful identification of component values, particularly the resistors, the polarity of electrolytic capacitors, and the identification of the transistor leads.

Our unit worked first time, except that the pitch control did not work. This turned out to be our fault, as we had mistaken a 4700 ohm resistor (yellow, purple, red) for the 470 ohm resistor (yellow, purple, brown) in series with the R8 moving arm. The mix-up did not effect the rest of the circuit, but shows how careful one needs to be.

Watch the height of the components above the board, particularly those located under the slide pots, but all

RINGING UP A GOOD 'SWEEP'

YOUNG honeymoon bride Mrs Sharrin Langlands was extremely upset when she lost her wedding and engagement rings in the surf near Mackay late last week.

After hours of searching with her husband, Dern, they had virtually given up hope of finding them until Dern thought of asking the Army for help.

Help arrived at the weekend in the form of two soldiers from Townsville's Lavarack barracks and two mine detectors.

Sgt Barry de Bomford and Pte Michael Jones spent six hours "sweeping" the beach with the mine detectors before success.

The rings were found under 15cm of sand about two metres apart.

This news item appeared in the Sydney "Sun" for October 24, 1977. It gives some idea of what can be done with the best equipment and training.

must clear the front panel. Regarding the slide pots we suggest that surplus lead be cut off, rather than bent over, where it comes through the board. Once bent and soldered it would be almost impossible to remove a pot without wrecking the board.

How do the performances of these two units compare? Rather interestingly, the more elaborate model is significantly more sensitive than the cheaper version, in spite of the fact that they both employ the same circuit. We can only conclude that the difference is due to design of the search coil in each case. Suffice it to say that the 28-181 model will detect some objects at up to twice the distance possible with the simpler version.

For those who feel competent to work from the circuit and who are prepared to do their own collecting of bits and pieces there should not be too



The 28-181 kit fully assembled. The decal on the front panel gives a professional finish.

many problems. Alternative transistor type numbers are given on the circuit and most of the other components are quite straightforward.

About the only ones requiring special mention are the reference oscillator coil and the search coil. The reference oscillator coil is a 455kHz IF transformer, with the secondary widing and any primary tap ignored, but with the internal capacitor retained.

To make a search coil we suggest starting with the design used in the 28-134 kit. This used 13 turns of enamelled wire, approximately 0.28mm, 29B&S, or 32SWG, around a plastic box measuring 120mm x 95mm. Both oscillators are designed to work at about 300kHz.


Finally, the accompanying table will give some idea of the performance to be expected from these two units. All the measurements were made in air, and may need to be modified for buried objects.

It will be noticed that the difference in sensitivity varies from about 1.5 to 1 to 2 to 1. This inconsistency appears to be due to the shape or area of the object (rather than its mass) relative to the size of the coil. It would seem that a large coil may be less sensitive to a small object than would a smaller coil.

It was also noted that both units are less sensitive to ferrous metals (iron and steel) than to non-ferrous metals. It would seem that losses in the search coil tend to be somewhat offset by the magnetic characteristics of ferrous metals, whereas non-ferrous metals cause losses only.

But, these finer points aside, one thing is obvious. If you take it out on the beach these days, there is a far better chance that you will find drink cans than 20c pieces! But it's still fun trying.

#### YOU HAVE SPOTTED A WINNER

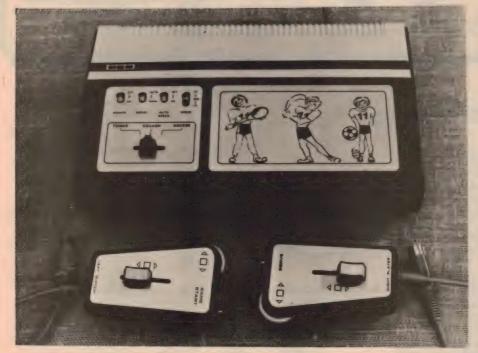

»DELTA 78«

THE MOST ADVANCED COLOUR TV GAME WITH VERTICAL & HORIZONTAL BAT CONTROL \$59.50

#### GAME DESCRIPTION

#### TENNIS:

TENNIS:
The game is designed to simulate playing methods and rules of table tennis as closely as possible. The display consists of a rectangular court with dotted centreline in white on a green background. The left player is RED and the right player BLUE.



Each player has vertical and horizontal movement within the confines of his own half of the court. The bat is blanked out on entering the opponents half of the court. The game is started by resetting the score which sets initial conditions and gives the first serve to the left hand player. The serve will then alternate every 5 points. Foints are won by deflecting the ball past an opponent and contacting either left or right baselines to score. To win the game 21 points must be reached with a clear margin of 2 points. If 20-20 is reached then the deuce circuitry operates and the winner is the first player to gain a 2 point advantage. The game also contains a double hit protection in that if a player does hit the ball is served from the relevant baseline) and the player whose serve it is hits the ball before his opponent. This feature is included to prevent a player from staying near the baseline for serves. It means he must move away and get back quickly for the serve return which at fast speed makes the game more interesting and skilful.

SOCCER:
This game is designed to simulate English football but could equally be called hockey. The display consists of a rectangular court as in tennis but the left and right baselines are broken to create "GOAL AREAS". The court outline and centreline are again white. To provide a more realistic simulation of the game, "STATIC DEFENDERS" are positioned in front of the goal areas, to act as goal keepers. Both players can move over the whole court area. The background is green and the static defender colours are RED and BLUE to match the normal players

colours



To score points the ball must pass through the goal area. The ball will then serve from the loosing players side but from the centre line (is. if left wins, the ball will serve from right to left and will appear from the centre line to simulate a kick off). Since no point target is set in football or hockey the game is won by the number of goals scored in a given time. When score reset is pressed at the start of the game the first kick off is given to the left player and an internal timer is reset, which times out after 3 minutes. This then operates the end of game signal, The player with the highest score being the winner. Double hit circuitry does not operate in football. This enables players to "DRIBBLE" and hit the ball as many times as required. This of course will operate the speed incrementer and a player can quickly loose control by too many hits.

SQUASH:
This game follows the rules and scoring methods of squash but could be equally called handball. The display again consists of a white court outline with the right hand side totally white to simulate a "WALL". The background is again green and players are RED and BLUE. The ball is white.



Both players can move over the whole court area. The ball is served from the "WALL" and left (RED) has the first serve after depressing the game start button. To win a point, a player must win on his own service by deflecting the ball past his opponent and contacting the left hand baseline. If a player wins a point on his opponents serve

then he only gains a service and not a point. This simulates the normal scoring procedure of squash. Double hit feature in squash as follows:
When the ball comes off the wall either from a serve or in normal play, then only one player is eligible to play the ball, (ie. if RED last hit the ball, then BLUE is due to play). If RED hits again then BLUE is automatically awarded a point and the next serve. Similary, when a player has played the ball and hits again before the ball has contacted the WALL, he looses a point and the serve. The first player reaching 9 points is the winner if a margin of 2 points exist. If 8.8 is reached, then the deuce circuit-ry operates and the winner is the first player to gain a 2 point advantage.
BALL SPEED:
The ball has three pre-settable speeds: slow, medium and fast. When the AUTO-SPEED switch placed in the "ON" position, the ball speed will increase to the next higher speed to that previously set by the user after four player hits have occured. At the end of each point the ball speed reverts to the original set speed and the "SPEED: INCRE-MENTER" will operate again. These speed-up features can be inhibited to enable any particular speed to remain constant by setting the Auto-Speed Switch in off position.

SCORING:
The score is displayed only during the time that the ball is out of play and leading zeros are always blanked. At the end of a point the new score is displayed and at the end of a game the score is displayed flashing on and off as an indication that the game is over. Operation of the game start button (located on the left player control box) will reset the score to zero and initialize the conditions to start a new game.

SERVE: When the serve switch is placed in "AUTO" position the game is started automatically after each score. When the switch is placed in "MANUAL" position, the game can only be started after depressing the serve button located on the right player control box.

SOUND:
Sound is provided to indicate various events as follows:
1) When the ball is served into play - short bursts of high
frequency. 2) When the ball hits a bat - medium burst
of medium frequency. 3) When a point is won - long burst
of low frequency. 4) When the game ends - medium and
low frequencies alternating.

-	Simple	connection	to	the	aerial	socket	of	vour	TV	se
-			-				-		6	A

#### LABORATORY DESIGN DELTA

COURT RED BANK ST. ALBANS VIC. 3021 **TELEX 33321** PHONE (03) 396 3742

15	a point on his opponents serve Simple connection to the aerial socket of your	IV set.
	To: Delta Design Laboratory: Please send me Delta 78 Colour TV Game(s) at \$59,50 plus for post, pack & insurance, I enclose cheque/money order for \$	£.A. \$3.00
-	Name:	
	State:Postcode:pay by bank card if you wish	
-	Name on Bank Card:	ď

## Circuit & Design Ideas

Conducted by Ian Pogson


Interesting circuit ideas and design notes selected from technical literature, reader contributions and staff jottings. As they have not necessarily been tested in our laboratory, responsibility cannot be accepted. Your contributions are welcome, and will be paid for if used.

#### Resettable fuse with SCR and relay

Most direct current power supplies rely on a circuit breaker, current sensing circuit, or fuse for current overload protection, but this simple resettable fuse circuit has advantages over all three. Built around a silicon controlled rectifier and line relay, it is faster than a circuit breaker, less complex than most current sensing circuits, and never in need of replacement.

How the circuit operates is evident from (a). Momentarily depressing \$1 closes the relay so that current flows from the supply to the load. In normal operation, the voltage across points PQ will be equal to the nominal supply voltage, and the normal operating voltage will appear across the relay winding. The relay and resistor R2 are selected according to the DC supply voltage used and the relay's rated coil voltage, respectively.

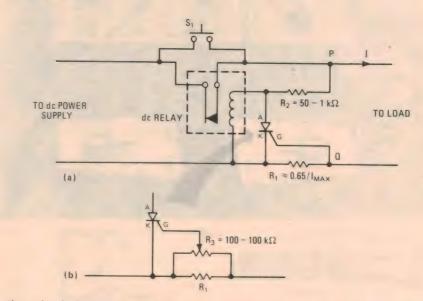Excessive current to the load causes a voltage drop across R1 greater than 0.65V and switches on the SCR. The anode-to-cathode voltage of the SCR in the conducting region is approximately 2V. This voltage, also across the relay



coil, is far below the relay's holding voltage. Consequently, the relay opens, disconnecting the load from the supply. The relay may be reset by depressing \$1 again.

If a variable threshold point for SCR

switching is desired, the SCR's gate can be connected to R1 through potentiometer R3. Resistor R1 is calculated as before.

(By Russell Quong, in "Electronics".)

#### Simple phase-locked loop

The conventional to-transistor multivibrator can be converted into a simple audio frequency phase-locked loop by the addition of a few components. Transistor Tr1 and the diode are connected as a logic gate and conduct during alternate half cycles of the input and VCO waveforms respectively.

The output of this phase-detector, when filtered, is most negative when the waveforms are in phase, and most positive when they are in antiphase. Because the diode conducts only when Tr2 is saturated, the action of the multivibrator remains unaffected. Once phase-lock has been established the VCO settles to an equilibrium phase, lagging the phase of the input by an angle which depends on the difference between the frequency of the input and the free-running frequency of the VCO.

With the component values shown, phase-lock is maintained from 100Hz to

around 3kHz. Within this range, the output changes linearly at about 14mV/Hz. The response to a sinusoidal

frequency modulation is 3dB down at about 50Hz.

(By J. B. Cole, in "Wireless World".)

## **Test instruments from Dick**

Measure-generate-inject-compare-inspect

Give yourself a Xmas present that you'll appreciate for years





## **8 HANDYMAN RANGES**

You don't need an expensive meter for most of the 'handyman' tests around your home, etc. This little beauty is ideal for checking power points, continuity, car wiring, etc etc etc. 15, 150 & 1000 volts AC & DC, plus a resistance scale (ohms) and a current scale (150mA). It's low sensitivity is very handy at times, especially in non-service work.

Cat Q-1010

## 20 RANGES PLUS dBs

Our most popular multimeter lately: and no wonder! This really is very good value for money. High sensitivity (20k ohms/volt) makes it ideal for most service work as well as general handyman testing. Incredible 20 ranges plus dB scales for every test: 0.1 – 1000V DC (6 scales) 2.5 – 1000 V AC (5 scales) 0.05 – 500 mA (4 scales) plus resistance 5k – 5M ohms!

Prices must increase soon!

Cat Q-1024



PROFESSIONAL QUALITY

We have sold thousands of these! Not just a multimeter — it checks out transistors too! That's right! This high impedance unit also doubles as an Ico & Hfe checker to give you a go/no go transistor test. It has 34 ranges inc. AC & DC current to 10 amps! There are too many ranges to list so suffice it to say thay well chosen!


Optional case available!
(Cat Q-1137 — \$15.00)



FET V-O-M WITH REVERSING SWITCH PLUS dB SCALES!

Ideal for service work, this 10 meg meter replaces that old VOM you've had for too long! Completely solid state (FET) so there's no need for mains power. Big banana sockets take your normal test leads, too! (plus ensure better contact for accuracy!) Incredible price for such a prized instrument!

Cat Q-1200

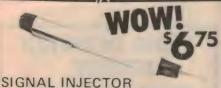

ully transistorised unit has a signal output from audio through to F. frequencies — a must for all servicemen — will pay for itself in

WAS \$8.75 Now only \$6.75

CHECK OUR PRICES AGAINST COMPARATIVE **INSTRUMENTS!** 

(but prices must rise shortly — so hurry!)

#### EQUIP YOUR LAB OR WORKSHOP WITH EXTRA VALUE 'TRIO' TEST GEAR . .

Trio VT108 FET meter Trio AG202A Audio Generator Trio CO1303D CRO Trio CS1560A 15MHz dual CRO Cat Q-1241 Trio CS1562 10MHz dual CRO Trio CS1570 30MHz dual CRO

Trio SG402 RF generator

Cat Q-1220 \$155.25 Cat Q-1230 \$228.85 \$557.75 \$481.85 Cat Q-1242 \$1007.40 Cat Q-1246 Cat Q-1250 \$110.40

ALL PRICES INCLUDE SALES TAX!

#### MODEL TE22D

#### RE SIGNAL GENERATOR

6 fund & 1 harm, bands, dual output RF terminals plus

Tube Complement:



120 kHz - 500 MHz 12BH7A 6AR5 Silicon Diode and Germanium Diode 105/125, 220/240 volts, AC, 50/60 Hz 140 x 215 x 170 Weight: 2.8kg

#### TE20D

#### AUDIO GENER-ATOR: QUALITY!

This unit has both sine & square wave output at less than 2% distortion. Frequency goes down to 20 Hz and up to 200kHz (sine) and 30kHz (sg). Output voltage is 7V p-p for square.

Frequency Range:

Output Impedance: Frequency Accuracy

Distortion: Tube Compleme Power Supply:

Sine Wave - 20 to 200 kHz in Square Wave - 20Hz - 30 kHz



#### AC MILLIVOLTMETER

This meter is ideal for all audio system voltage and sound level

FOR SERVICE, RESEARCH OR DESIGN

SPECIFICATIONS:

Measuring range

200μV to 30V in 8 ranges 20Hz to 100KHz ± 1dB 1KHz reference

-42 dB to -28 dB -32 dB to -28 dB -22 dB to -8 dB -12 dB to 2 dB -2 dB to 12 dB 8 dB to 22 dB 18 dB to 32 dB


Weight: 300 gr

City Ph 67 9834



York St. 361 Hume Hwy 30 Grose St. 162 Pacific Hwy. Ph 29:1126 Bankstown. Ph 709-6600 Parramatta. Ph 683:1133 Gore Hill. Ph 439-5311 itil BPM Thursday Open Itil BPM Thursday Now Open Ample parking at store MAIL ORDER DEPARTMENT PO Box 747, Crows Nest NSW, 2065. Post & Pack Extra, Bankcard w

#### Another colour TV thief trap

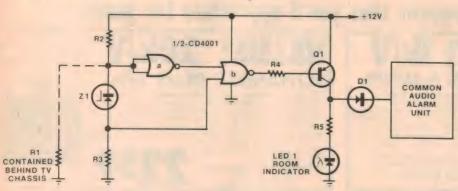


In Circuit & Design Ideas for October 1977, a colour TV thief trap was described. It was suggested that this device may be useful for such places as motels. My experience is that many motel installations have the coax cable connected to earth at the "delivery" and thus all the sets on the same run will be connected to the shield. This means that the simple system as described would be ineffective.

The circuit which I have developed and installed in some motels is at least one answer to the thief problem. It is based on the CMOS quad NOR gate 4001 and requires only half of a chip per

Resistor R1 must be contained within the TV receiver chassis. The resistor is soldered onto its wires after they have first been passed through a hole in the chassis. Operation is basic logic except the values of R1, R2 and the zener diode may need some brief explana-

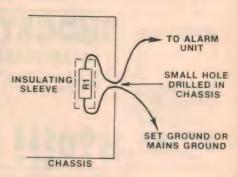As I have made use of the voltage threshold (45% Vcc) that the gate switches on, R1, R2 and the zener diode are chosen to keep gate (a) on and gate (b) off during normal conditions. Should the wire to R1 be opened the



zener diode conducts causing gate (b) o/p to go low and switching on Q1. Should the wires be shorted gate (a) switches off causing gate (b) o/p to go low, switching on Q1.

Typical circuit values — R1, 3.9k; R2, 2.2k; R3, 220k; R4, 47k; R5, 470 ohms; zener diode, 5.1V; Q1, BC557; D1,

(By Mr G. J. Brand, 15 Gwinganna Crescent, Holden Hill, SA 5088.)

#### Charger for nicad batteries

This battery charger has two charging rates, selected by \$1. The circuit is a simple one and based on the fact that a forward biased silicon diode has about 0.6V drop across it. CR1 and CR2 have a combined voltage drop of 1.2V and the emitter-base junction of Q1 has a 0.6V drop, causing the net voltage drop across R1 or R2 to be 0.6V.

The charging rate is equal to the emitter current of Q1 and since the base current is small, may be considered to be the same as the Q1 collector current. This current is determined by dividing 0.6 by the value of the selected resistor. R1 and R2 should be 5% tolerance resistors of wattage rating

chosen to dissipate the calculated amount. The values of R1 and R2 may be found by dividing the desired charging rate in amperes by 0.6.

One definite advantage of this charger is that any battery rated up to 12.5V may be charged. The author selected charging rates of 60mA and 3mA, yielding resistance values of 10 ohms and 200 ohms, respectively. The transistor should be capable of handling the current and power involved. A type MJ2955 mounted on a heat sink should be suitable for most applications.

(By Michael Alterman, WA3KXT, in

#### 11 12 6 V 117 V A C R2\* CRI 0 CR2 CR1, CR2 - General-purpose silicon diodes, 1N914 221 or equiv. Radio Shack RS2025 transistor. Should be mounted on heat sink. BATTERY \*-SEE TEXT

#### RADIO DESPATCH SERVICE

869 GEORGE STREET, SYDNEY 2000 PHONE 211 0816, 211 0191

- Wide range of gold plated UHF connectors. adaptors, etc. for CB use
- Extensive range of "TELEX" C.B. Power mics. and mic headsets
- "Copitar" binoculars with leather case, three models - 7x50 zcf, 10x50zcf, 12x50zcf
- Electronics project kits ideal for Xmas gift.
- Good range of Veroboard for projects in stock "Consound" AM & AM/FM Pocket & Portable
- size transistor I/RADIOS
- CA2 Electronic Whooper multi-purpose car
- "Seiko" battery operated digital alarm clock white only.
- "Gannon" D-Subminiature 9-50 pin connector range available with covers Selective range of N.S. Ladies' & Gent's L.C.D
- digital watches. Gold or s/steel finish Good stock of transformers, battery chargers &
- power supplies.
- Cables to suit audio, T.V., Mic, CB, Speakers and Power. Good range carried Selective range of L.V. Relays. Cradle & P.C.B. types available
- Patchcords for audio, radio, phono and tape
- recorder connections available
  E.A. & E.T.I. Project P.C. Boards carried
- aerials & accessories stocked to suit colour and black and white

Open Mon. to Fri 8.00a.m. to 5.30p.m. Saturday 8.00a.m. to 11.45a.m. TRUST R.D.S.

#### Guess Whose Dad's Got a SINGER?

\*DAVID WILLIAMSS DAD USES ONE TO

Service land, marine and airborne 2-way systems, CB, amateur and commercial transceiver equipment operating in the 50 KHz to 1.3 GHz range including AM, FM & SSB. The Singer FM-10CS is a combination instrument and includes the functions of a:

- SIGNAL GENERATOR
- FREQUENCY METER
- SPECTRUM ANALYSER
- SWEEP GENERATOR
- NETWORK RESPONSE INDICATOR
- AM MODULATION MONITOR
- FM DEVIATION MONITOR
- AUDIO OSCILLATOR
- MONITORING RECEIVER.

#### **Pertinent Operating** Specifications:

- 2 uV Sensitivity
- 1 Hz Frequency Resolution
- 1 ppm/year Accuracy
- Instant "On"
- 0 dBm Output
- 12V DC Operation

\*PETER WILLIAMS OF VICOM

### INSTRUMENTATION




W.A. PHONE 212651. S.A. PHONE 2672246



telephones 6997614



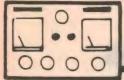

## The Serviceman

#### On aerials, feeders, and exorcising ghosts

"When in doubt, blame the aerial". This would seem to be the slogan of some TV technicians when faced with a degraded TV picture for which they have no immediately obvious solution. It is an unfortunate situation because enough people have been caught to spread the word, making it difficult to convince a customer when the aerial really is at fault.

It is also unfortunate that a lot of advertising has been aimed at convincing the public (without actually saying so) that a colour TV set requires nothing less than a special aerial—coloured for preference— and coaxial cable.

There are, of course, situations where a better aerial installation can be justified. Not because the customer happens to have bought a colour set, but for the simple reason that the existing aerial system has either deteriorated since it was first installed, perhaps 20 years ago, or because it really never was adequate.

The best advice I can offer a customer when they raise these points is quite simple: If the present aerial is giving good results on a monochrome set then it should give equally good results on a colour set. Mind you, much depends on the viewer's interpretation of "good". For some people it only has to move; for others every tiny blemish on the picture is a cause for concern.

Much the same reasoning applies to the feeder. If an existing ribbon feeder is giving good monochrome pictures it will give good colour pictures. On the other hand, coaxial cable can be useful where localised electrical interference is a problem. But the point is that it can be just as desirable for a monochrome installation as for a colour one.

As for coloured aerials — well their value is debatable. The colour is normally aluminium anodising and, on the credit side, there is little doubt that this provides good protection against corrosion in seaside or industrial areas. Otherwise it has little to offer; the fact that it is coloured makes no difference to its ability to receive colour signals! And on the debit side is the fact that such an aerial is a clear indication that there is a brand new colour set in the house; a point which the light fingered gentry are not likely to overlook.

All of which, as you probably guessed, has been prompted by some recent experiences with aerials. The main one was a situation which occurred outside normal business hours and which, because I was unprepared, called for a certain amount of ingenuity and improvisation.

Having closed the shop one Saturday lunchtime I returned home to find that Mrs Serviceman had arranged for us to visit some friends the following day; a family who had just moved into a new (for them) house on the other side of the city, and were anxious for us to see it. In fact, it turned out that they were well into the scrub on the other side of the city, close to a couple of hours' drive away, so it was to be an all-day visit.

And, oh yes, they were having some trouble with their colour TV set and they hoped I might be able to offer some advice. No one seemed to know exactly what the problem was, except that someone had told them they were in a poor reception area. All I knew about the situation was that they had had the set for some months and that it had apparently performed satisfactorily at the previous location.

With so little to go on there wasn't much I could do in the way of preparation. However, I gathered up a handful of tools, the soldering iron and a multimeter, and hoped that it was nothing serious.

When we finally arrived the following day, after what seemed like an eternity on lonely country roads, my first instinctive reaction was to look for the aerial. It turned out to be a 215 type, which should have been quite adequate. I didn't buy the "poor reception area" claim because the location looked to be quite reasonable and, in spite of the distance I had travelled, they were not all that far from the TV stations; well, not as the CRO flies! (Sorry about that.)

But then I noticed something else. There was a slight wind blowing and the low band dipole was see-sawing up and down with each gentle gust. I wasn't really surprised when I walked inside and found the picture flipping at regular intervals, together with bursts of snow and white horizontal streaks.

"It looks like we will need to do a major job on that aerial." I told my friend, "Do you think we can get it down?"

"Should be easy enough," he replied, "I've got plenty of ladders."

But before we tackled that I fetched the multimeter and tried the low ohms range across the socket on the skirting. Normally I should have been able to read a dead short across the folded dipole but in fact the needle didn't even flicker. It looked as though we had more than one problem.

At that point my friend filled me in on the history as he knew it. It seemed that the previous owner had originally owned a monochrome set, which operated from the aerial in question. More recently he had purchased a colour set and for this a brand new aerial had been installed, complete with coaxial feeder. When he left, he had taken the new aerial with him but had not bothered to take the coax.

It was this last fact that had confused my friend initially. Faced with a choice of two feeders, one of which was visible and obviously coax, he automatically chose the latter. (After all, everyone knows that a colour set should be fed with coax)

Unfortunately, the results weren't very encouraging. Only two of the four local stations could be received, and even these were obviously weak. On the other hand, it wasn't really surprising. The other end of the coax was lying on the tiled roof with, at most, a couple of inches of bare wire exposed.

And it was apparently this performance, when described to a local serviceman, which had prompted the comment that it was a poor reception area.

To give my friend his due he didn't buy the idea either, but he didn't feel confident enough to argue about it. But it did prompt him to trace out the feeder cables and change over to the ribbon which was, nominally at least, connected to the aerial. This had improved matters to the point where all four channels were available, though a

couple were still a bit noisy, and all suffered from the flips and flashes when the wind blew.

I was a little puzzled over the open circuit I had read on the multimeter, and suggested to my friend that we should trace the feeder through to the aerial, just to be on the safe side, It was quite a long feeder, running nearly the full length of the house above the ceiling, then through the wall cavity to the outlet on the skirting board.

Up in the roof we started at the set end and headed for the aerial. My first surprise was a kind of junction; a crude assembly of finger twisted joints from which a length of ribbon ran off either side at right angles and disappeared into other cavities. "Oh yes," said my friend, "there are outlets in the first and second bedrooms, as well as the lounge room."

"Well," I replied, "they'll have to come out, at least for the present. We can put them back if you want them, but it will have to be done properly." As it turned out, however, he had no real need for them, so that solved that problem.

Having found a break in the cable I took the opportunity to check continuity. Looking towards the aerial it was still open circuit, so we moved on. We found another joint, just before the cable disappeared through the tiles and the meter told the same story, meaning that it was almost certainly a break right at the aerial.

We climbed down from inside the roof and prepared to tackle the aerial itself. My friend fetched a ladder and we lowered the mast until the aerial was within reach of the roof, then unfastened it and brought it down to the ground level. The first thing I did was examine the cable where it was terminated. It was intact mechanically, though corroded, but the meter insisted that there was no connection between it and the elements.

Closer examination revealed that conventional terminal lugs had not been used, the bare copper wire having been simply twisted around the bolts and secured against the aluminium elements by the wing nuts. This could well have contributed to the corrosion, since copper and aluminium are electrolytically incompatible.

My friend produced an aerosol of penetrating fluid and gave the terminals a good squirt, which we left to soak in while we had a cuppa. Then I gingerly tackled the diecast wing nuts with a pair of pliers, only to have my worst fears realised. They were frozen solid; I had no option but to wreck them to get them off.

Then I took a closer look at the aerial. Whoever had assembled it in the first place had done a very rough job. Apart from the bare copper wire terminations they had obviously neglected to tighten various bolts properly. The most obvious one was that holding the low



#### **XENON FLASHLAMPS**

for

STROBE, HIGH SPEED PHOTO FLASH & NEWSPRINT TYPE SETTING.



FROM THE WORLD'S LARGEST MANUFACTURER

E. G. & G. INC.

Also Available is the World's Largest Range of Light Measuring Instrumentation, Photometers, Radiometers, Etc.

exclusively supplied by

#### LASER ELECTRONICS PTY. LTD.

P.O. BOX 359, SOUTHPORT, QLD. 4215. PHONE: (075) 32 1699 TELEX: 41225.

#### BRIGHT STAR CRYSTALS PTY LTD

35 EILEEN ROAD, CLAYTON, VICTORIA, 546 5076 (ALL MAIL TO:— P.O. BOX 42, SPRINGVALE, VIC. 3171)

## WE WISH OUR CUSTOMERS A MERRY CHRISTMAS AND A HAPPY NEW YEAR

Please note that we will be closed from 22nd Dec. 77 to 2nd Jan. 78



Watch crystals 32.768 KHz advertised in Oct. and Nov. '77 are imported. We regret any impression given that they were made in Australia.

HOSE & EQUIPMENT CO. PTY. LTD. SYDNEY. PHONE 666-8144

COMMUNICATION SYSTEMS PERTH. PHONE 76 2566

FRED HOE & SONS PTY. LTD. BRISBANE. PHONE 47 4311 ROGERS ELECTRONICS ADELAIDE. PHONE 42 6666

DILMOND INSTRUMENTS HOBART. PHONE 47 9077

## From Electronic Relays, Inc. ERI all solid-state and reed-coupled solid-state relays



#### **Features**

- Input 3-32 V DC (0-70°C), 2mA (0°C)
- Output 0.5 A, 2 A (PCB) 2 A, 10 A, 25 A, 40 A (Chassis Mount)
- Input to output isolation voltage up to 4000 V AC.
- Built-in RC snubber networks.

AVAILABLE FROM

R. & D. Electronics

23 Burwood Rd, Burwood 3125 Tel.: 288 8232, 288 8262 Please send me details on the range of E.R.I. Solid State Relays.

NAME\_

ADDRESS\_\_

COMPANY \_

PRODUCTS \_



Melbourne: 407 Highett Rd, Highett. Tel. 95 9203

band dipole. This had been loose for so long that the continual see-sawing of the dipole had elongated the mounting hole in the boom, laterally, further aggravating the situation.

Similarly, the nuts securing the connecting bars to the high band dipole had never been tightened properly, so that these rattled up and down the bolts as the low band dipole see-sawed. All in all, it was one horrible mess.

Fortunately, my friend has a pretty well stocked workshop and we managed to rustle up a goodly assortment of steel nuts, bolts, washers, lock washers etc, with which I was able to reassemble the faulty sections.

Then it was back up on the roof to replace the aerial on the mast, raise it, and tuck the length of feeder under one of the tiles. Back inside the roof I spliced the ribbon, soldered the joints, and wrapped it in tape. I did the same for the other break, and checked things

over generally.

A check on the lounge room outlet with the multimeter told a different story this time — a virtual short circuit. I connected the set and all four channels came up clear and strong. I discreetly nudged back the colour control, which was running a little on the high side — though not as bad as many that I have seen — and touched up the brightness and contrast controls. The set was then delivering a perfect picture.

My friends were delighted and, I then realised, much relieved. It had come as a nasty shock to them to discover that, apparently, they had moved into an area where, at best, they might have to spend a lot of money to get reasonable reception or, at worst, they might not get a viewable picture at all.

Naturally, it was a bit of a busman's holiday for me, and also a bit of a challenge, since I had not the slightest inkling of what was in store when I set out that morning. The last thing I expected to do was to have to rebuild an agrial

But my friends' gratitude was ample compensation, though we didn't knock back some fruit from their orchard, and I did snaffle the coax — with their permission. I'm sure I'll find a use for it.


One of the points to be learned from this exercise is that aerials can deteriorate, particularly where they have not been properly assembled in the first place. Maybe they don't need to be replaced as often as the aerial manufacturers would like, but it's not a bad idea to check them over every few years.

Another point is the readiness with which the local serviceman offered the glib explanation that it was "... a poor reception area". In fact, I proved that it was an excellent reception area; plenty of signal, no ghosts, and far enough away from industry to avoid electrical interference. It would be hard to find a better spot.

And finally there is the obvious fact

that the previous owner had been talked into a brand new aerial and feeder system when he bought a colour set, whereas a few repairs to the existing system were all that were needed to bring in first class colour pictures — ribbon feeder notwithstanding!

Talking about aerials — or, at any rate, the ghosts which they can introduce — reminds me of yet another report from overseas regarding ghost suppression circuitry. Readers may remember that I touched on this subject in my January notes, based on a report in the Japanese magazine JEE. The more recent report comes from the American magazine "Electronics", but still concerns work being done in Japan. ("Electronics", August 4, 1977, p55.)

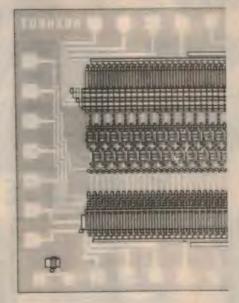

Portion of the large scale integrated circuit ghost canceller developed by Toshiba. Top row is the CCD delay lines, middle row weighting circuits, and bottom row analogue memory and demultiplexing circuits.

As before, the Japan Broadcasting Corporation (NHK) is well to the fore, this time in conjunction with the Tokyo Shibaura Electric Co (Toshiba). As nearly as I can gather, NHK have developed the basic idea, while Toshiba aim to package it all in a single chip.

One of the interesting comments in the report states, "Manually adjustable cancellation systems ..." (the type referred to in my January notes) "... are unattractive because they must be readjusted for each channel, and ... for the same channel over a period of time". (Nevertheless, I'd be prepared to bet that many people would gladly accept this limitation as a small price to pay for a good picture.)

But the current aim goes far beyond that. It is to produce a universal ghost suppressing circuit which will need no adjustment and will automatically suppress any ghosts (plural) by an order of

30dB — more than enough in almost any practical situation. The only restriction, at present, appears to be that the ghosts must be displaced not more than 27us from the main image, or half the active line period. (Half the width of the screen.)

As nearly as I can make out from the brief report the basis of the idea is to look for ghosts during the vertical blanking period and, more specifically, between the last pre-equalising pulse and the commencement of the vertical pulse block. (I had to fish out some of my old text books to work that one out, so don't be ashamed to do the same.)

Any reflected signal will cause a ghost of the pre-equalising pulse to appear somewhere in the period of 27us before the commencement of the vertical sync block. From this the position and amplitude of any ghost(s) can be readily determined, and this information is stored and used to create an anti-ghost signal which is applied during the following vertical scanning period.

(Presumably, if the reflecting surface were to move during this time, as would an aircraft, a new set of antighost data would be created at the end of the vertical scan, to suit the next

scan.)

The manner of creating the antighost signal is more difficult to follow. The heart of this system is a delay line using CCD (charge coupled devices) with access to each stage in the CCD. The video signal is fed in parallel to each stage, via field effect transistors (one for each stage), which controls the amount of video signal, if any, fed to any particular stage.

The point at which the video is admitted to the delay line, and its amplitude, is determined by the first part of the system — that which observed the ghost in the vertical blanking period. This biases on the appropriate FET which controls entry to the CCD. If there is more than one ghost, more than one entry point will be opened, each by an amount appropriate to the ghost amplitude.

The video signal which emerges from the delay line will be delayed by an amount determined by its entry point. Suitably phased, it is then fed back into the video line so as to cancel the ghost.

I know that takes a lot of digesting, and leaves a lot of the details unanswered. But apparently it works, even though most of the work so far has used only a small delay line, about 6us. At a practical level most of the problems involve producing a suitable chip, of reasonable size and at reasonable cost. The present aim is for a chip no larger than that currently used for calculators, but it is expected to take up to two years to develop.

So, some time in the future, it should be possible to buy a TV set guaranteed free from ghosts.

Here's hoping!



assemble your own superb quality Speaker system

75 OR 53 LIT **SYSTEMS** 



International musician Geoff Harvey builds

according to Geoff: 'Magnificent!'

his Playmaster speaker system. The end result



A: Glue and 'fold' the box sides around the front baffle. The box sides are pre-grooved to make the job child's play



B: Screw in the speakers and wire then as shown in the detailed instructions. A pre-assembled loom' is supplied - no soldering required

6 PAGE

FREE!

BOOKLET



C: Insert the acoustic filling material and place the rear panel in position. Lay the acoustic grille on the front baffle and press home

They're just so easy to build! And the finished job is more than the equal of systems at least twice the price! Our 6 page booklet gives step-by-step instructions you can't go wrong. All you need is a couple of hours, a tube of glue and a few small tools - see drawings above! You have the choice of two different systems: a 75 litre 3-way with twin faders and 12 inch woofer (system 1) - or a 53 litre budget enclosure with a 10 inch woofer - ideal for smaller rooms (system 2)

You really can't beat this incredible value from Dick Smith - ideal Christmas present for the hi-fi enthusiast who wants real quality. It's a present that keeps rewarding you with hi-fi for years to come!

#### SYSTEM 1:

Speaker kit (pair) Cat. C-2042 .. .. \$130.00 Enclosure kit (pair) Cat. C-2622 .. \$124.00 TOTAL SYSTEM PRICE (PAIR) ..\$254.00

#### SYSTEM 2:

Speaker kit (pair) Cat. C-2044 ....\$99.75 Enclosure kit (pair)Cat. C-2624 .. \$89.50



MAIL ORDER DEPARTMENT: PO Box 747, Crows Nest. NSW; 2065. Post & Pack Extra: Bankcard welcome



## Letters to the editor

#### Laser critic

A brickbat at your laser. Surely relinquished responsibility is worse than irresponsibility or ignorance.

While a good device can be made foolproof, it can never be made idiot-proof. Yet freely available information may be construed to form a lethal weapon in the hand of individuals hell bent.

The price is no retardant. The power source is readily available from any automotive battery. Lack of restricted access has now placed yet another weapon in the arsenal of deliberate trouble-makers. Another arrow in their quiver.

Visualise it, if you will, in the hands of a highly imaginative youth, playing imaginary space war. Or unsupervised students in a school intended upon mischief. (Many a time I have been victim of some such prank, with scars to prove it.) You cannot guarantee that only serious, intelligent, educated and responsible individuals will be the sole users of lasers.

John Vasar Padstow, NSW

COMMENT: You appear to have greatly over-estimated the output from our laser. With an output of only 1.2 milliwatts, it is scarcely a lethal weapon. In any case your criticism would appear to apply to a multitude of everyday items — including your brickbat.

#### Advertisement

I refer to the September issue, 1977, of Electronics Australia regarding an advertisement placed therein in respect of a Playmaster loudspeakers system as advertised by Dick Smith Electronics Group. There are aspects of the above advertisement which are incorrect and

therefore, in our opinion, misleading in advertising content. The advertisement compares the AD12K12 loudspeaker kit with the Playmaster, and we would hasten to point out that the AD12K12 ceased to be available as such on July 1 and has since been upgraded and replaced by a Mark II version, and there are, therefore, certain aspects of the table display which are incorrect.

We would like to take the opportunity of also thanking yourself and Dick Smith Electronics for reference to our loudspeaker systems and component loudspeakers in a previous article published in Electronics Australia, May 1977. It is quite obvious that both your magazine and Dick Smith hold our products in such high regard that they are a reference point by which the quality of other products should be judged.

I would also like to point out that whilst in the advertisement previously mentioned, the Dick Smith Group have gone to some pains to display a comparison between a speaker kit of their own creation, and our own superseded AD12K12, there is, of course, no indication of the specifications for certain of the components used, which could, therefore, be regarded as a comparison of quality. Quantity, you will appreciate, is no substitute for quality.

Kevin L. Gest, Philips Electronic Components and Materials.

## COMPUTER CHESS

It's you against the computer

The first microprocessor based chess game, using an 8080A C.P.U. It utilizes an 8224 clock generator/driver, 8228 system controller, 512 8-bit bytes of random access memory, that stores the position of the chess pieces, and a 16,384-bit read only memory. Software contains such elements as the rules of chess, the relative importance of the pieces, allowable moves and strategies. The micro computer plays by the book, working on the weighted value of the pieces, and completely scanning the board for the best available move each time. It plays aggressively, tries to control the centre of the board, and, if it's in trouble, will try for a stalemate.

The keyboard can be used to verify the position of each chess piece at any time during the game.

It's easy to play: Just plug in and bring a new dimension of suspense and excitement to this internationally famous game.

This is a beautifully finished, top-quality product at the special introductory price of \$385.25 delivered free anywhere in Australia.

NOW AVAILABLE: Reprogrammed version with user selectable 3 levels of difficulty, plus choice of black or white pieces together with increased flexibility in problem setting. \$485.00.



527 Tooronga Road, Hawthorn East, Victoria TELEPHONE (03) 82-3732



## Low-cost tester for microprocessors



by DAVID EDWARDS

This simple inexpensive test unit will enable you to troubleshoot your microprocessor system. At the same time it will enable you to gain an insight into how a microprocessor operates, and how it transfers information using its data and address busses.

Apart from the ubiquitous multimeter or electronic voltmeter used to measure DC voltages, traditional electronic servicing tends to rely fairly heavily on the cathode ray oscilloscope or "CRO" as a means of checking dynamic circuit operation. In most types of equipment the CRO has been very suitable for this purpose, as the signals are generally repetitive and with characteristic waveforms.

Unfortunately a CRO becomes rather limited when non-repetitive signals are involved, and where system operation depends upon the interaction of a relatively large number of signals. These are just the sort of situations that abound inside computers, including microprocessor-based hobby computer systems.

Things are further complicated, when it comes to troubleshooting in computer systems, by the interaction between hardware and software. When something goes wrong, it can often be the devil's own job to find out whether it is being caused by an electrical fault in the hardware, or an error in the software.

For example if your program fails to store some data in a particular memory location, it could be because you have made a mistake in the program; or alternatively it could be because there is a fault in the memory decoding or write strobe circuits, or even in the microprocessor itself. (Generally speaking, in 99 cases out of 100 you have made a mistake in your program, but in this article we are going to consider what to do in those rare cases where the trouble is due to a hardware fault.)

Attempting to analyse a fault in a com-

puter system can be very frustrating and time-consuming. One tends to spend all one's time trying to catch pulses only 2us wide, which occur almost at random. Logic probes and similar devices can be quite useful, but have the disadvantage that generally you can't monitor all 40 pins of the microprocessor at once, nor is it easy to control the operation of the system while you watch the probe.

In order to try and cope with problems like this, commercial logic analysers have been developed, which enable the operator to trace and locate typical faults such as that proposed earlier. They are usually based on microprocessors themselves, and unfortunately tend to be rather expensive, placing them well out of reach of the average home experimenter or enthusiast.

We were discussing this problem recently with Ed Schoell and Chris Mason, who are both microprocessor applications engineers with NS Electronics Pty. Ltd. Our ears pricked up when they replied that they had worked out a simple but very effective way of getting around the problem.

Their basic idea was to have an array of 40 LED indicators, one for each pin of a typical microprocessor chip, forming in effect a 40-channel logic probe. But the LEDs are not connected continuously to the processor pins; instead they are connected to a set of 40 latches, with circuitry provided so that the latches can "strobe" or briefly sample the logic levels at the pins only at specific times.

To avoid the problem of not having known conditions, their idea was to initially hold the system in the reset state.


and then let it start running at a predetermined time. At the same time, a delay monostable with adjustable pulse width would be triggered, and the end transition of the monostable used to trigger the LED display latches.

By varying the delay pulse width, the LEDs could thus be arranged to sample the logic levels on the microprocessor pins at any desired time after starting up from reset. By having the resetting occur repetitively, say every 20 milliseconds or so, and providing the delay monostable with a vernier control, we thus end up with the digital equivalent to a 40-channel CRO, whose viewing "window" can be moved along in time to analyse system operation following start-up.

When we started to consider the logic required to implement such a system, we were surprised to find just how little was required, and how little expense would be required to achieve such a test unit. So without further ado, we started to develop the idea into the tester described in this article.

Before describing just what the unit can do, we will first give a brief physical description of it, as this will aid your understanding of how it works. Essentially, the tester consists of a single printed circuit board (PCB), measuring 282 x 226mm, mounted in a wooden case. The PCB forms the lid or front panel of the case, and has an array of components fitted to it.

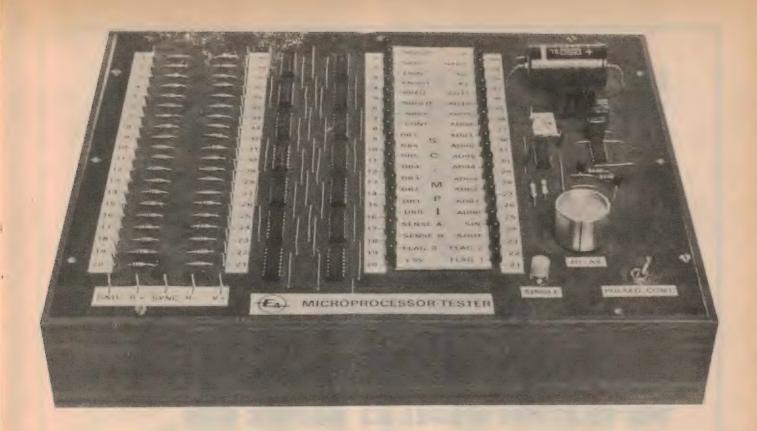As you can see in the photographs, the most conspicuous feature is the array of 40 LEDs, and a corresponding array of 40 PCB pins. The LEDs and pins are numbered from 1 to 40, while in the centre



of the LEDs is a replaceable card, which carries the pinout designations of the microprocessor chip being tested (in this case the SC/MP).

The LEDs and PCB pins are separated by two rows of seven integrated circuits (ICs), while to the right of the LEDs is a small control panel, containing a knob and two switches. A large "umbilical cord" emerges from the upper left hand corner of the case, and is terminated in a 40 pin DIL test clip.


The 40 leads in the umbilical cord are connected in order to the underside of the 40 PCB pins, so that pin 1 of the microprocessor clip is connected to the PCB pin numbered 1, and so on.

A small number of additional PCB pins are provided below the main array. These are used to allow interconnections between the system under test and the tester—power supply lines, reset signal, and so on. There is also an output pin providing a trigger signal for a CRO, if you want to use one in conjunction with the tester.

Turning now to the circuit diagram, we can examine the operation of the circuit. One section of a 74C14 hex Schmitt trigger device is connected as the reset driver. Switches S1 and S2 allow it to be used either as an oscillator with a period of about 20ms, or as a manual "one-shot" pulse generator.

The output pulse (positive going) from the Schmitt trigger is used to trigger a monostable element, which has a pulse width of about 22us.

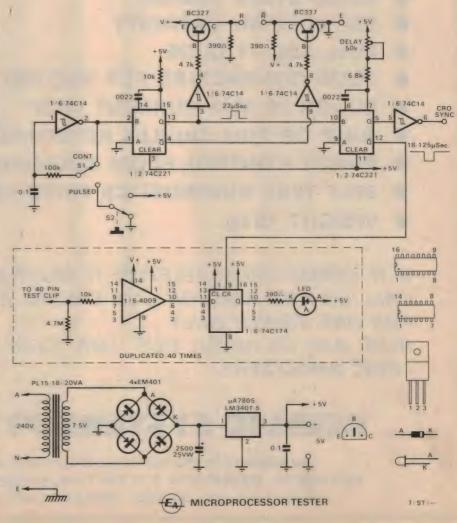The Q and Q-bar outputs from this monostable are passed via further 74C14 inverters to complementary transistor



## HOW DOES THIS GRAB YOU MICROCOMPUTER NUTS?



#### THE TELETYPE MODEL 43 MATRIX KSR

- SOLID STATE DESIGN
- 132 COLUMN CAPACITY
- FULL ASC 11 CODE
- 10/30 CHARACTERS PER SECOND
- EIA OR 20 M/A CURRENT LOOP
- HALF OR FULL DUPLEX KEYBOARD CONTROLLED
- PARITY CONTROL FROM KEYBOARD
- SELF TEST DIAGNOSTICS FROM KEYBOARD
- WEIGHT 15 kg.

IF IT COMES FROM TELETYPE IT MUST BE GOOD CALL US AND ASK FOR OUR SPECIAL CHRISTMAS PRICE FOR ONE MONTH ONLY.

ALSO ASK US ABOUT OUR (LOW COST — UNDER \$600)
LOGIC ANALYSERS.

#### KENELEC SYSTEMS PTY. LTD.

142 HIGHBURY ROAD, BURWOOD, VICTORIA 3125.
TELEPHONE: MELBOURNE (03) 288 7100. SYDNEY (02) 439 3954
ADELAIDE (08) 223 2420. BRISBANE (071) 44 1259

#### Microprocessor tester

huffers, capable of driving TTL inputs. These buffered outputs are made available at the small row of PCB pins on the PCB, and the appropriate output is then connected to the reset pin of the microprocessor by a flying lead. Thus the microprocessor is reset, either periodically or on a "one-shot" basis, as required, for about 22 microseconds duration.

As well as driving the reset circuitry, the Q output of the first monostable is also used to drive a second monostable. This is the actual delay monostable, with its pulse width adjustable from about 15 to 125 microseconds. The Q-bar output of this monostable is connected to the clock inputs of the 40 LED latches, so that they are strobed at the end of the delay pulse. The delay is adjusted by means of a 50k ten-turn potentiometer, giving a resolution of less than 1us.

Each of the 40 device pins is buffered

by a 4009 type inverting buffer. The V+ (VDD) supply pins of the seven ICs used are all connected together, and made available at one of the PCB pins in the small row. A flying lead is then used to connect this point to the positive logic supply pin of the microprocessor. This means that a logic level conversion can be made between the system under test and the tester.

The transistor buffers used for the reset function are also connected to this V + line, so that the reset pulses are automatically of the right amplitude.


10k resistors are fitted in series with the inputs to the buffers, so that if voltages above or below the supply rails of the buffers are present, the current through the static protection diodes is limited.

The 4.7M resistors shown on the circuit diagram are optional extras. They serve to pull the inputs down when the microprocessor pins go into a high

impedance or "tri-state" mode. Without these resistors, the inputs to the buffers tend to respond to adjacent inputs (due to capacitive and leakage effects on the PC board), and also to the magnetic field of the transformer. The values of the resistors are not critical, any value between 1M and 4.7M will be satisfactory.

The Q outputs of the latches are used to drive the LEDs, via current limiting resistors. The pattern of the PCB has been arranged so that when pin 1 of the test system goes high, the LED labelled 1 is lit, and so on.

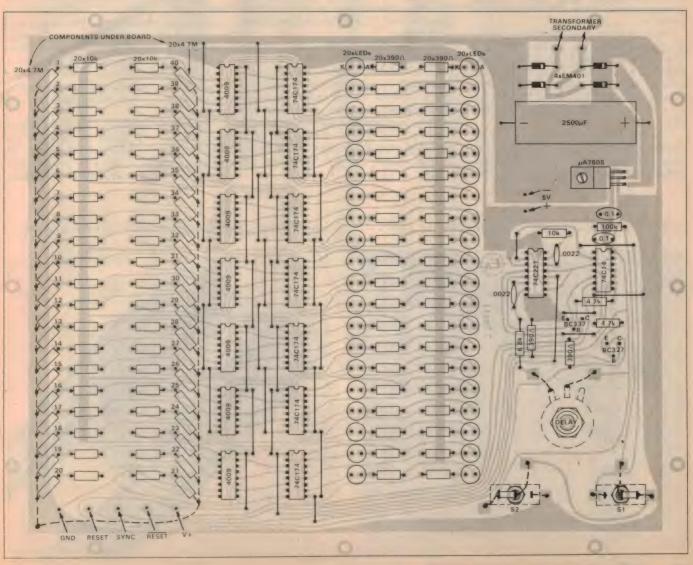Now that you have an insight into how the tester is arranged, we can discuss what it is used for, and how it shows the workings of your microprocessor system. It is assumed that when the system is reset, it commences to run with a particular program. This can be either a monitor program, or one that you have written.



#### Microprocessor tester

Initially, S1 is set to the continuous position, and the delay control is set to minimum. Then the microprocessor is reset and commences to run the test program once every 20mS. With the delay control set to minimum, the latches are clocked just before the end of the reset pulse.

Let us suppose that our system has a positive reset pulse, and that this is being applied to pin 1 of the microprocessor chip. Then LED 1 will be lit, and the remaining LEDs will show the state of the other pins during the reset period. Typically, output flags will be cleared, and the data, address and control lines will be in a high impedance state.

If the delay control is now operated slowly, a point will be reached when the latches will be clocked just after the reset pulse has ended, so that the reset LED will be out. The remaining LEDs will now show the state of the microprocessor at this time. Let us now suppose that the first instruction of the program is stored in location zero, and is XY in hexadecimal notation.

If we now increase the delay slowly, while monitoring the address and data pins we should be able to see the address and data appear. Of course, the address will not be very obvious, as all address LEDs will be unlit (for address 0000), but the data (XY) should appear on the data pins.

Continuing on with this process, we should be able to see the microprocessor obtain and act on the second and subsequent program bytes. It will also be

possible to see the system using its various control lines, such as read/write and operation request.

Thus we can use the tester to analyse the operation of a working microprocessor, and can also use it to trace through the operation of a faulty system, to see where it is going wrong. The delay control allows us to look at various parts of the machine cycles, and at all the various input and output pins.

The tester can also be used in the oneshot pulsed mode, to enable the effects of circuit or program changes to be evaluated. The total range of the delay control in terms of instruction cycles will depend on the clock rate of the system under test. Typically, however, it will be of the order of 50 or so.

Construction of the tester should be relatively simple. All components are mounted on a single PCB, coded 77up11. This is identical in size with the board used for the digital logic trainer described in the July 1977 issue. We have done this intentionally, so that it can be mounted in the same case as used for the logic trainer.

The case used for the prototype was supplied by Dick Smith Electronics Pty Ltd. Alternatively, a home-made wooden case could be used. The board measures 282 x 226mm, and requires approximately 50mm clearance underneath it. A steel or aluminium case could also be used, as a 10mm clearance has been provided around the edge of the board so that metal will not short out any tracks.

49 PCB pins are required, along with about 1.5m of tinned copper wire. This is used for the numerous links on the board, which are necessary because we did not use a double sided board. These should all be fitted before any other components.

The passive components should next be fitted. The only polarity sensitive one is the 2500uF electrolytic capacitor. Next fit the bipolar components, such as the diodes and transistors. The three terminal regulator can also be fitted, along with its heatsink. The latter can be either a commercial unit, such as we used, or a small piece of scrap aluminium.

The input pulldown resistors are wired on the copper side of the board, as shown in the photograph. First solder all the resistors to the PCB pins, and then bend their free ends so as to form a bus line, which need only be connected to the earth track of the board in one place.


The mains cord enters through a hole in the rear of the case, and is securely clamped to the bottom. The active and neutral leads are terminated in a BB strip, and then routed to the transformer primary. The earth lead is soldered to a solder lug, and securely clamped to the transformer chassis. No connection is made between the mains earth and the circuit earth.


Before the CMOS ICs are fitted, the 40 pin DIL test clip should be wired to the board. There are two possible ways of obtaining the test clip, a simple but relatively expensive way, and a less simple,

Commercial 40-pin DIL test-cost around \$20



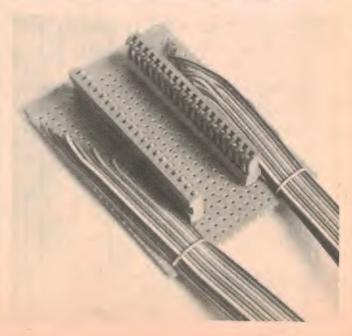Inexpensive test clip fabricated from a PCB edge connector.



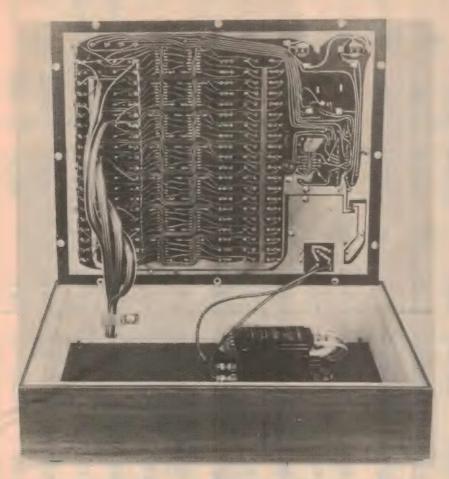

Internal view showing transformer mounting and cable anchoring details.

less expensive way. The first method is to buy a ready made commercial 40 pin DIP clip, and simply solder the required wires to it. It will cost you around \$20, but the result is a very neat and straightforward job.

The second method is to obtain a 40 pin, double sided PCB mounting 0.1" spacing PCB edge connector, and a small piece of Veroboard. The basic idea is to separate the edge connector lengthwise into halves, and solder them to the Veroboard at the appropriate distance apart.

Radio Despatch Service, of 869 George Street, Sydney, kindly supplied us with samples from the U.E.C.L. range of connectors, and we were able to modify them satisfactorily. The first step is to cut the connector to the correct lengththere should be 20 connectors on each side. Make the cut with a hacksaw, and then use a file to clean up the ends.

The next step is to cut the connector lengthways. This can also be done with a hacksaw, but care is required. First protect the edge connector contacts by taping two strips of paper in the slot where the board normally goes, and then clamp the socket in a vyce, with the jaws clamping each end of one side of the socket. Then gently insert the hacksaw into the board slot, between the paper strips. Keeping the blade parallel to the bottom of the slot, saw the connector in

Clean up the edges of the cut with a file, and then solder the rear pins of the two halves to the Veroboard. We found that if we spaced them 0.7" apart, the actual contacts were then 0.6" apart, the required spacing for a 40 pin DIL IC. Solder only the end pins at first, so that you can check the spacing. If it is not quite right, a little judicious bending will put it right. Finally, solder the remaining

We used rainbow cable to make the connections from the DIL socket to the PCB. Care is required not to short out any of the terminations, and to ensure that pin 1 of the test clip is connected to pin 1 of the PCB pin array. At this stage you should clearly mark the test clip so that it will not inadvertently be connected to a device the wrong way round(!).

Clamp the cable where it enters the box, so that the flexing due to normal use

#### LOGIC INTERNATIONAL



PO BOX 187. COBURG, VIC. 3058.



#### TRANSISTORS

AC128	.84c	BC559	.24c	2N2102	.92c
AD161	\$1.76	BD 135	.75c	2N2369	.38c
AD 162	\$1.76	BD 136	.80c	2N2646	\$1.44
BC107	.27c	BD 137	.87c	2N2904A	.80c
BC108	.27c	BD 138	.87c	2N2907A	.45c
BC109	.270	BD 139	.87c	2N3019	.87c
BC317	.22c	BD 140	.87c	2N3053	.73c
BC318	.22c	BD232	\$2.30	2N3054	\$1.61
BC319	.22c	BF115	.80c	2N3055	\$1.15
BC327	.22c	BF180	\$1.10	ZN3565	.23c
BC328	.22c	BF199	.45c	2N3566	.22c
BC338	.22c	BU126	\$3.44	2N3638A	.33c
BC547	.22c	FT2955	\$2.18	2N3644	.73c
BC548	.220	FT3055	\$1.19	2N3819	.73c
BC549	.22c	TIP31A	.83с	2N4032	\$1.26
BC557	.24c	TIP32A	.83c	2N4936	\$1.10
BC558	.24c	2N301	\$2.51		

#### TTL

7400	.29c	7432	.32c	7475	.66c
7402	.29c	7447	\$1.07	7476	.51c
7404	.29c	7472	.41c	7490	\$1.15
7413	.52c	7473	.41c	74121	.52c
7414	\$1.44	7474	.71c	74123	.76c

#### **VOLTAGE REGULATORS** 1amp. POS. (to 220)

uA7805	\$1.42	uA7812	\$1.42	uA7824	\$1.42
uA7806	\$1.42	uA7815	\$1.42	SPECIAL	
µA7808	\$1.42	uA7818	\$1.42	PRICE(T	03)
UN1000				1 M309K	\$2.74

#### LINEAR

LM301N	.73c	LM380N	\$1.67	LM741N	.55c
LM311N	.90c	LM555N	.640	LM3900N	\$1.07
LM324N	\$1.19	LM723N	.79c	LM3909N	\$1.15

#### DIODES-POWER RECTIFIERS

TOTTE ITECTION	
N4004 400V 1A .18c W02 200V 1.5A	.92c
N4007 1Kv 1A .33c W04 400V 1.5A	.97c
N5062 800V 1A .52c PK40 400V 10A \$4	.42
N5625 400V 3A .87c DIODES-SIGN	ΔΙ
N5626 600V 3A .94c IN914 .10 OA90	-

BRIDGE

#### OTHER ENQUIRIES WELCOME

Prices correct at press time. Subject to change.

PACKING AND POST FREE IN AUSTRALIA

MINIMUM MAIL ORDER

\$5.00

A11-	A14	A13-	A12-	A15-	A9—	A8—	A7-	A6 -	A5 —	A4 -	A3-	+120-	A2-	A1-	- OA	WAIT-	READY -	0 1	HLDA -
A10	GND	D4	D5	90	-D7	-D3	- D2 8	-D1 0	- D0 8	-50	RESET	-ногр	TNI -	- \$2	-INTE	DBIN	WR	SYNC	- +5V
RESET	TSC-	nc –	02-	DBE-	nc	R/W-	- DO	D1-	D2	D3-	D4-	D5-	- 9Q	D7	A15 -	A14-	A13-	A128	GND-
							9	$\infty$	0		0								
-GND	- HALT	-01	-IRQ	- VMA	NMI	-BA	-+50	- A0	-A1	-A2	- A3	- A4	- A5	-A6	- A7	- A8	- A9	-A10	-A11
- VT-	NADS -	X2 —	X1	AD11-	AD10-	- 60QY	AD08-	AD07-	AD06-	AD05-	AD04 -	AD03-	AD02-	AD01-	AD00-	NIS	SOUT	FLAG 2 -	FLAG 1-
- NWDS	NRDS	ENIN	ENOUT	BREQ	-NHOLD	- NRST	CONT	DB7	DB6 5	DB5 C	34 /	DB3	82 IVI	<b>P</b>	DB0	SENSE A	SENSE B	-FLAG 0	-+5V
	1	Ī	Ī	Ī	Ī				-0	ā	- DB4	-D	-DB2	-DB1	0	- SE	S	1	i
D05-	- 90G	D07-	- 80G	- 60d	D10-	D111-	D12-	D13 D	D14D	D15DI	-12V-	BPS - DE	EXTEND - DI	NINIT - D	CLK - D	NCLK - SE	VBBSE	F14 - F	F13
		D07-				D111-										- 1			
_ 500g	-90Q		A D08 -	-600 O	E D10-	D111-	D0 - NADS D12-	D1NHALT D13-	D14-	D15-	-12V-	D5JC13 BPS-	EXTEND-	LININ	CLK	NCLK -	VBB	F14 -	F13-

#### Microprocessor tester —

will not break the connections to the PCB. At this stage, only the CMOS devices should remain to be fitted. IC sockets should not be necessary. To commence, earth the barrel of your soldering iron to the earth pattern of the board.

Then remove the ICs, one at a time, from their protective wrapping, and insert them into the board. Solder the power supply pins first (7 & 14 or 8 & 16), and then the remaining pins. It is not necessary to solder those pins which are not connected to the circuit.

The final stage of construction is to label the various points on the board. We made up a suitable artwork, and used this to make labels from Scotchcal, which we then stuck to the board. Some of the PCB manufacturers may make silk screened boards available, making this unnecessary.

We also made up artwork for the removable cards used to identify the pin functions of the various microprocessors currently available. These have been printed full size with this article, and we suggest that you cut them out and paste them to cardboard. We have provided five cards, covering the Signetics 2650, the National PACE and SC/MP, the Motorola 6800 and the Intel 8080.

Before you cut the cards to their final size, check the width between the two rows of LEDs. The cards should fit between the LEDs, underneath the rim at the bottom.

The leads used to make the required interconnections on the unit are the same as those used in the new logic trainer. You will only require about 5 or 6, and these can most conveniently be made using the clips from a miniature valve socket. Extract the clips from the socket, and connect them together with short lengths of hookup wire.

To test the completed unit, connect a test lead between the V+ PCB pin and the +5V PCB pin, and then apply power. Monitor the output of the regulator while you do this, and switch off immediately if the output is other than 5V. Assuming that everything is OK, switch to the continuous mode, and set the delay to minimum.

Connect the reset pin to pin 1, and reset-bar to pin 2. LED 1 should emit, while LED 2 should not. Now increase

the delay. After a small rotation, LED 1 should go out, and LED 2 should come on. Now connect reset-bar to each of the remaining 38 pins in turn, and check that all LEDs are operative.

If, on first turning on, you find that you cannot reduce the delay sufficiently so that LED 1 comes on, reduce the value of the 6.8k resistor in series with the delay control. The minimum allowable resistance is 470 ohms. On the other hand if you find the delay control has to be rotated more than about half a revolution to get LED 2 to come on, increase the value of the resistor.

Finally, switch to the pulse mode, and check that the display changes only when the pushbutton is operated.

Use of the completed tester is quite simple. Firstly, determine which pin of the system you are to test is the reset pin, and the polarity of the signal required, and connect the appropriate reset pin of the tester to that pin. Then determine which is the positive logic supply pin, and connect the V + pin to it. Similarly determine the negative or ground pin, and connect the E pin to it.

Then fit the test clip to the microprocessor chip, observing the correct polarity, and switch on the microprocessor. After setting the delay control to minimum, switch on the tester.

Now set the mode switch to continuous, and slowly increase the delay. By comparing the patterns produced by the LEDs with the listing of the program running in the microprocessor, you should be able to see the system in operation. Do not operate the delay control rapidly, as otherwise you may skip right over some steps in the program.

If you have access to a cathode ray oscilloscope (CRO), this can be used to examine the waveforms at the various pins. A positive going sync signal is available at the PCB pin marked sync. This occurs at the same time as the latches are clocked, so that the CRO is automatically triggered at the same time the LED samples are taken, if you connect the signal to the external sync or trigger input.

When the delay is at a minimum (i.e., during the reset period), you may notice the LEDs corresponding to tri-state outputs flickering. This is normal, and is caused by the varying time taken by these pins to return from a high logic level to the low logic level as determined by the pull down resistors.

Finally, switch off the tester before you switch off the system under test, and do not remove the test clip till everything has been turned off.

The total current drain of the tester is about 400mA (when all the LEDs are on), so that about 600mA @ 5v is available for

#### PARTS LIST

- 1 74C14 hex Schmitt trigger
- 1 74C221 dual monostable
- 7 4009 hex inverting buffers
- 7 74C174 hex D flipflops
- 1 uA7805, LM340T-5.0 or similar three terminal regulator
- 40 red LEDs
- 1 BC327 PNP transistor
- 1 BC337 NPN transistor
- 4 EM401 silicon diodes

#### CAPACITORS

- 1 2500uF 25VW pigtail electrolytic
- 2 0.1uF polyester
- 2 0.0022uF polyester

#### RESISTORS (all 1/4W)

- 40 4.7M, 1 100k, 41 10k, 1 6.8k, 2 4.7k, 42 390 ohm
- 1 50k ten-turn potentiometer

#### MISCELLANEOUS

- 1 printed circuit board, coded 77up11, 282 x 226mm
- 1 transformer, 240V to 7.5V, PL1.5-18/20VA or similar
- 1 SPDT miniature toggle switch
- 1 SPDT miniature momentary action pushbutton
- 1 knob
- 49 PCB pins
- 5 connecting leads (see text)
- 1 mains cord, mains plug, cord clamp and terminal block
- 1 case, wooden or metallic as required (see text)
- 1 40 pin DIL test clip (see text)
- Hookup wire, rainbow cable, solder, tinned copper wire, machine screws and nuts, insulating tape, scrap aluminium

NOTE: Resistor wattage ratings and capacitor voltage ratings are those used for our prototype. Components with high ratings may generally be used provided they are physically compatible.

external use from the two pins near the heatsink. If you draw this much, however, a large heatsink will be required.

NOTE: When using the Microprocessor Tester with either of the current National Semiconductor microprocessors (SC/MP I or PACE), it will be necessary to connect the GND pin to the circuit ground directly.

This is because this connection cannot be made via the 40 pin connector and umbilical cord, as these devices do not have a ground connection at the chip itself. In all other respects, operation will be the same as for other systems.



RIGHT: Pin identification cards for Signetics 2650, National PACE and SC/MP, Motorola 6800, and Intel 8080 microprocessors.

#### ELECTRONICS courses at COLLINGWOOD

5 min. from the centre of Melbourne

- INDUSTRIAL ELECTRONICS
   Post Apprenticeship level
   Preliminary course available for people
   without prior experience
- DIGITAL (part time) for experienced technicians
- AMATEUR RADIO OPERATOR
   Certificate of Proficiency A.O.C.P.
   Limited Certificate A.L.O.C.P.
   Novice Certificate A.N.O.C.P.
- CERTIFICATE of TECHNOLOGY
   Electrical Operating Testing
   Distribution Communications
   Electronics
   Electrical Design Drafting

**Further Information** 

#### COLLINGWOOD TECHNICAL COLLEGE

35 Johnston St., Collingwood, Vic. 3066

#### DANDY ELECTRONIC DISCOUNTS

(CHEAPEST IN TOWN)

508 BRIDGE ROAD, RICHMOND, VIC. 3121 Tel. After Hours: 799-1869

Resistors from 1c, Switches from 30c, Capacitors from 3c, Coils from 20c, Electrolytics from 5c, Trimmers from 10c, Knobs from 3c.

SPEAKERS (Wide range, e.g.)

Twin/Cone 8" 8 OHMS \$5.50 Twin/Cone 5" 8 OHMS \$3.00 Twin/Cone 5" 15 OHMS \$3.00

Balarce Meters \$1.50, Transformers from 60c, Coaxial Cable 75 OHMS 13c per metre, Hookup Wire 4c per metre, AC Leads 3 Core 45c, AC Leads 2 Core 30c, Slider Pots single 20c, dual 40c, TV Aerials \$2.50, Transistors from 15c, Speaker Cloth \$1.50 per yard, Heat Sinks from 5c, Earth Strips from 10c, Suppressors — various TV Tuners, B/W, FHT Coils, Deflection Coils, Sockets, Din Sockets (Globe Sockets).

#### NEW WIDE RANGE OF EQUIPMENT COMPONENTS

Heavy Duty Transformers, etc., Bags Mixed Caps (100) \$4, Bags Mixed Electrolytics (50) \$5, Bags Mixed Colls (10) \$1.50, Bags Mixed Trim/Pots (15) \$1.

MAIL ORDERS AND TRADE ENQUIRIES WELCOME OUR MOTTO CHEAPEST IN TOWN

Mon.-Thurs. 9 am-5.30 pm Fri. 9 am-7 pm. Sat. 9 am-12 noon.

## Announcing the winner of the Dick Smith-Electronics Australia

## Mini Scamp Contest

The winner of the Dick Smith-Electronics Australia Mini Scamp microcomputer contest is Mr Kurt Deininger, of Melton, Victoria. Mr Deininger's entry, a microcomputer-controlled swimming pool alarm, was chosen by our judges Dr John Kennewell, Dick Smith and Jim Rowe from the many impressive entries received. It wins for Mr Deininger the microprocessor development system pictured below, valued at more than \$2000.



Mr Deininger (second from left) is congratulated by Allan Greening of Dick Smith Electronics during the prize presentation. At left is EA's Victorian representative Keith Watts, while at far right is Mr Deininger's son, Hans. Mr Deininger is a computer programmer for TAA.

Mr Deininger's winning entry fulfilled the aims of our contest particularly well. It represents a practical, down-to-earth application for a microprocessor, although one which at the same time reflects a great deal of design ingenuity.

A swimming pool alarm, it uses the flexibility and "intelligence" of the microcomputer to overcome the drawbacks of conventional designs. A simple scanning-type sensor is used to allow Mini Scamp to continuously monitor the pool water level, but the software performs a number of tests on both average level and wave characteristics, to allow reliable detection of a child or adult having fallen in.

Although Mr Deininger based the alarm on Mini Scamp, to qualify for our competition, it could easily be produced as a very compact dedicated SC/MP system with the program resident in a ROM or PROM. We hope to give a full

description of the winning entry in our next issue.

Although they were not rated by the judges quite as highly as the winner, two other entries were highly commended and deserve particular mention. One was an intermittent fault detector for electronic servicing, submitted by Mr John Barry, of Liverpool, NSW. The other was a microcomputer-controlled model train layout, submitted by Mr Stephen Dart of East St. Kilda, Victoria.

These and a number of the other entries were so good that we believe readers will find them of great interest and value. We therefore intend trying to publish as many of them as we can, in forthcoming issues. So stay with us!

And to all those who entered the contest, thanks for your interest and efforts.

## INCREDIBLE OFFER!

#### 2 new revolutionary, portable electronic games! No TV set needed!

FUTURETRONICS HAVE DONE IT AGAIN. THE PEOPLE WHO BROUGHT TO YOU THE WORLD'S FIRST MICROPROCESSOR BASED CHESS GAME NOW BRING YOU THE ULTIMATE IN PERSONAL ENJOYMENT AND RELAXATION. TWO NEW PORTABLE HAND HELD ELECTRONIC GAMES FULLY ASSEMBLED, WITH L.E.D. DISPLAY, PRECISION LENS, SOLID STATE CIRCUITRY AND REALISTIC SOUND EFFECTS. USES STANDARD 9 VOLT BATTERY (NOT INCLUDED). IT'S YOU AGAINST THE COMPUTER FOR A WHOLE NEW KIND OF EXCITEMENT, FUN AND CHALLENGE.

#### MISSILE ATTAC

ICBM alert! Computer-controlled missiles attacking! You command anti-missile missiles! Push the fire button. Intercept. Save "Your City"! (Lose and you'll hear part of

Game features automatic digital scoring, launch and quidance controls, and realistic sounds.



The race is on! Computer-controlled cars coming straight at you. Steer! Shift! Avoid a collision and beat the clock! (Hear the sound of victory!)

Game features automatic digital timer, steering and gear shift controls, plus realistic race sounds.



	To order or	for Information contact:
Fire	ro	
		·
527 100R0564 R045 H2	WINDS AND WITHOUT PARTY	pty. Itd.

PLEASE	SEND	AUTO RA	CE I ENCI	LOSE \$49.65	
PLEASE	SEND	MISSILE	ATTACK I	ENCLOSE \$49.6	5

NAME ..... D PLEASE SEND ADDRESS

**BOTH GAMES I ENCLOSE \$89.90** 

STATE .. . . P/CODE PHONE 82 3732

#### Microcomputer News & Products




#### RAM "sticks"

An innovative memory product designed for the home computer market has just been released by Applied Technology. It is a 1k x 8-bit RAM "stick" module, whose design allows ready stacking for memory system expansion.

Announcing the new product David Brown, Applied Technology's sales manager, said the RAM stick filled a real need for the microprocessor user who wanted to build up his system's memory in convenient, practical and easily affordable increments. "We chose low power 2102 chips for the design because these are one of the most cost effective RAMs on the market today — and being static they are by far the easiest to use."

The RAM sticks are supplied fully assembled, 100% tested and burned-in for 24 hours using a processor-controlled test routine. The test routine checks continually for fundamental memory errors as well as complex "pattern errors" which plague some


memory systems.

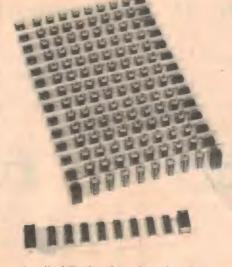

Applied Technology has also designed a 32k x 8-bit memory unit with power supply and standby rechargeable battery, which mounts in a standard instrument case or rack mounting. The memory can also be configured as 16k x 16 bits for use with 16-bit microprocessors.

Enquiries to Applied Technology Pty Ltd, 109 Hunter St, Hornsby, NSW 2077.

#### Low cost graphics

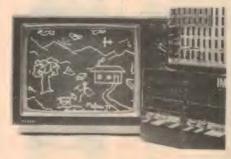

Modified CRT graphics controllers with external sync capability are now available from Matrox. The modified controllers are their MTX-256, ALT-256 and MDC-256. The external sync facility permits the use of multiple cards to build up a variety of high resolution graphic imaging systems, with either grey scale or colour capability.

The graphics system can also be synchronised to external sources such as the Matrox MTX2480 alphanumeric VRAM (video RAM), or a TV camera, where video mixing is desired. A light pen capability can now be implemented in hardware or software. Demanding graphics applications can thus be handled at a fraction of the cost of competing systems.

Enquiries to the Australian representatives for Matrox, Measuring and Control Equipment Co. Pty Ltd, PO Box 78, Epping, NSW 2121. Telephone (02) 86 4060.

#### "Interface Age" here

The US magazine "Interface Age", specialising in microcomputing for the home and small business, is now available in this country on subscription via Computerland/Electronic Concepts, at 55 Clarence St, Sydney. The cost is \$21.60 for 12 issues, or \$45 for earlier delivery via Jetspeed.

By courtesy of Computerland we were able to look at a sample copy of the magazine, that for September 1977 (V2, No. 10). The feature of that issue was an insert "floppy ROM" flexible disc recording, with a general ledger program for small business use. This is being fully documented in the magazine itself.


In all, we found Interface Age a very mature and down-to-earth magazine, and one which should be of value to most serious micro users.
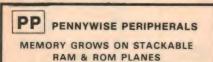
#### Mini floppy from BASF

BASF, one of the largest magnetic media suppliers in the world, has announced a mini floppy disc drive compatible with the newly standardised 134mm flexible disc media. Called the model 6106, the new drive measures 191 x 146 x 76mm. It rotates the mini discs at 300rpm, recording at 2581 bits per inch on 35 tracks. The track density is 48 tracks per inch, and the tracks may have from 1 to 16 sectors.

Data transfer rate is up to 125 kilobits per second, with an average track-to-track access time of about 220 millseconds. The 6106 has been rated for MTBF at 5000 hours under heavy usage, but will perform more than 8000 hours with regular usage.





RAM PLANE PCBs: Provide 4k bytes of RAM using 32 2102 family 1K x 1 bit static RAMs. (See ad in EA Sept. 77.)

ROM PLANE PCBs: Provide 4K bytes of ROM using 4 2708 type EPROMS. There are on-board buffers, decoding and —5V reg.

MEMORY PLANES can be stacked with or without sockets.



#### 16K MOTHER BOARD

- Contains all buffering and control logic for driving 1 to 4 MEMORY PLANES, ROM or RAM.
- MEMORY PLANES stack on sockets for easy removal.
- Configurable to any 8K or 16K boundary.
   Control logic and accept a single R/W (eg M6800) or separate MEMR and MEMW (eg geod).
- Mother Board dimensions are 9%" x 6%".
   Edge connector is 43 x 2 way 0.156" pitch with M6800 system connections.

M6800 system connections.

RAM PLANE or ROM PLANE PCB only \$15.75

RAM PLANE Kit (inc. 32 MM2102-1 450 nS and stackable sockets)

\$89.30

ROM PLANE Kit (for use with Mother Board. No. 2708s) \$34.90 Mother Board Kit (inc. male pins for stacking 1 to 4 PLANES) \$49.20

(prices include tax. P&P free in Australia.)
Mail orders and requests for data sheets to

#### PENNYWISE PERIPHERALS

19 Suemar Street, Mulgrave, Vic. 3170 Phone (03) 546 0308 (am & AH)





\$129.50

Orisita Wasp in sheep's clothing?

The simple elegant lines of this deluxe new AM
CB may fool you. It looks a million dollars,
works as good as it looks—and should cost just
as much, right?

Wrong. This high performance Wasp is surprisingly economic. Just think of how many AM sets you've seen with RF gain control. The Wasp has it. Or delta tune. Switchable noise limiter AND blanker. Transmit indicator. LED

channel readout (of course!). It also has the mundane things like volume, squelch, PA, etc. Remember the Wasp. Designed for Australia with phase locked-loop frequency synthesis for ultra-stable performance.

Full 90 day warranty, spare parts and service back-up should you ever need it—all the things that make a CB worth buying.


Look for the sheep's clothing.

### DICK SMITH ELECTRONICS GROUP

PARRAMATTA—30 Grose St. Ph. 683 1133 SYDNEY—125 York St. Ph. 29 1126-BANKSTOWN—361 Hume Hwy. Ph. 709 6600 GORE HILL—162 Pacific Hwy. Ph. 439 5311 MELBOURNE-656 Bridge Rd., Richmond. Ph. 42 1614 —399 Lonsdale St. Ph. 67 9834 BRISBANE-166 Logan Rd., Buranda. Ph. 391 6233 MAIL ORDERS:—Box 747, Crows Nest, N.S.W. 2065. Ph. 439 5311

ALSO AVAILABLE AT DEALERS THROUGHOUT AUSTRALIA
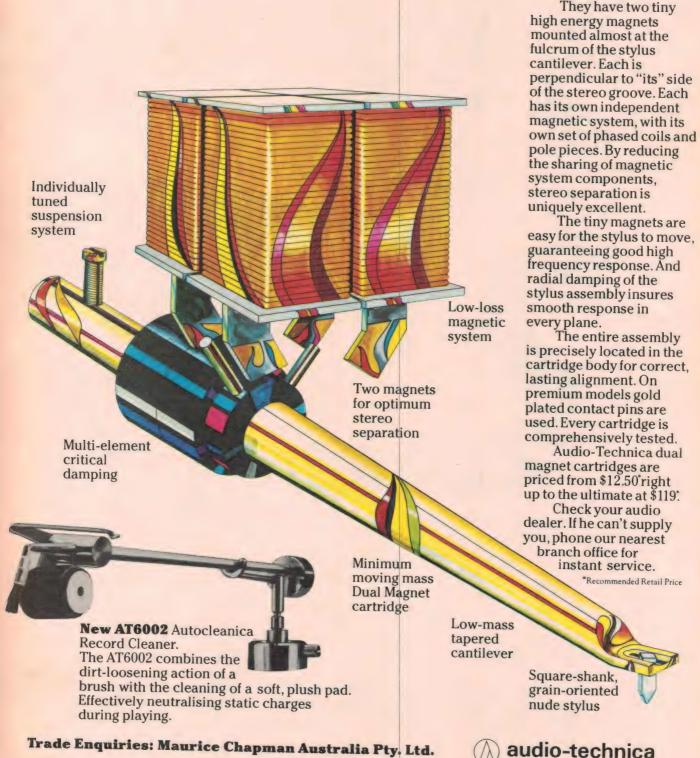
## Why Audio-Technica Dual Magnet Cartridges are different.



9 Horden Place, Camperdown. NSW 2050 Phone: 5164599

Neil Muller. 8 Arthur Street, Unley. SA 5106 Phone: 741162

150 Burwood Road, Hawthorn. Vic. 3122 Phone: 8181730

Soundline Pty. Ltd., 883 Wellington Street, Perth. WA 6000 Phone: 225177



#### audio-technica

123 Abbotsford Road, Mayne. Qld. 4006 Phone: 522480

Wills & Co. Pty. Ltd., 7 The Quadrant, aunceston. Tas. 7250 Phone: 315688

The 6106 drive consists of read/write and control electronics on a single PCB, read/write head, track positioning mechanism, drive mechanism and the removable disc in its sleeve.

BASF says it has aimed the 6106 drive for OEM use in the calculator, desk-top computer, terminal and word processing markets. It regards the mini floppy as an excellent alternative to paper tape, magnetic cassettes and magnetic cards, offering higher power and reliability while being competitive in size and cost.

For further information regarding the BASF 6106, contact the EDP Media and Systems Division of BASF Australia, 11B Lachlan Street, Waterloo NSW 2017.

#### **New SWTP terminal**



Paris Radio Electronics, distributors of Southwest Technical Products systems and peripherals, has advised that it now has stocks of the new CT-64 terminal kit. An assembled CT-64 is shown above, complete with the matching SWTP 10MHz monitor.
The CT-64 stores and displays either

one of two pages, each consisting of 16 lines of either 32 or 64 characters. The number of characters per line is jumper programmable, and a jumper may also be used to change the terminal from 50Hz to 60Hz operation. The full 7-bit upper and lower case ASCII character set is displayed, with either white-onblack or black-on-white operation.

An interesting feature of the CT-64 is that all 32 ASCII control characters are decoded, with some 21 decoder outputs available for user-defined control tasks.

Other features include optional control character printing, screen reversal on individual characters for highlighting, and selectable page mode/scrolling mode operation. The basic CT-64 is designed for parallel data input, but a serial interface option is available, as is an ASCII keyboard.

The matching CRT monitor shown above offers bright, well-focused character display. The 10MHz video bandwidth ensures optimum character resolution with 64-character lines

For further information on the CT-64, including price, contact Paris Radio Electronics at PO Box 380, Darlinghurst, NSW 2010.

### MICHOCOMPUTER AC-30 CASSETTE INTERFACE MP-68 COMPUTER WITH 4K MEM. TUTE 6800 **AUSTRALASIAN DISTRIBUTOR** PARIS RADIO ELECTRONICS CT-64 & CT-YM TERMINAL



#### **GETTING INTO** MICROPROCESSORS

This book will help you find out what the revolution is all about . . .

Available from newsagents, electronic suppliers and also "Electronics Australia", 57 Regent St, Sydney. PRICE \$4.50 OR by mail order from "Electronics Australia", PO Box 163, Beaconsfield 2014. PRICE \$5.10.



#### **AUSTRALIA'S** FIRST BYTE SHOP

P.O. Box 380, Darlinghurst NSW 2010

Truly second generation Microprocessor Mini Computer. Complete range of memory and I/O modules available.

Cromemco TV dazzler ● Byte saver ● Cyclops camera ● A-D, D-A ● Cromemco Z80 mini computer.

Processor The Sol System Intelligent Terminal. Wide range of PROM; RAM; Parallel/Serial I/O; firmware; Technology simulator, text editor; video display modules.

North Star Inc. Floating point arithmetic unit. Mini floppy disc, controller and software.

Oliver Audio Paper tape reader.

Dynabyte Memory modules.

Solid State Memory, Video Display and Music Synthesizer Modules. Music

All the above are available in kit form or assembled form. For further details send S.A.E. to: BYTE, P.O. BOX 156, CARNEGIE, VIC. 3163. OR, for hands on experience phone: Melbourne 568 0642 or 569 7867.

SONTRON INSTRUMENTS & THE BYTE SHOP 17 ARAWATTA STREET, CARNEGIE, VIC. 3163.

## How to own two uperb 12"3-O watt spea and save abo per hour while assemble the

The Philips AD12 K12 MKII Speaker Kit, Full 40 watts RMS capacity. Modern, completely finished cabinet. Assembles in nine simple steps, taking most people about two hours. The finished job looks like it has been put together by a professional. And you save about \$100 per pair on a comparable assembled system!

A modern three-way Hi-Fi system with 1" domed tweeter, 5" mid-range and super 12" woofer, all fully imported, and rated full 40 watts RMS per channel. Power to deal with any reasonable living room. A particularly brilliant sound, with an excellent overall frequency response for the cost. It closely follows the ideal Bruel & Kjaer curve for Hi-fi equipment measured in an actual listening room, using the "Third Octave Pink Noise Method"

Also available: Other quality systems at similar impressive savings. Phone or send coupon now for full details of all kits.

#### PHILIPS ELECTRONIC COMPONENTS AND MATERIALS

Sydney 427 0888 • Melbourne 699 0300 • Brisbane 44 2471 Adelaide 223 4022
 Perth 65 4199







#### **ELCOMA**

Philips Electronic Components and Materials P.O. Box 50, Lane Cove, NSW 2066

Please send me full details and brochures on your loud speaker kits and a list of retailers who stock them.

NAME

**ADDRESS** 

BA.EL.1

## Classical ecordin



Reviewed by Julian Russell

#### Previn: "elegantly presented" at a budget price

PREVIN - Recital of Seven Pieces; played by the London Symphony Orchestra; conducted by Andre Previn. RCA Stereo VICS-1751.

The Vaughan Williams overture "The Wasps" was not very enthusiastically reviewed by me in this column last month though I had nothing but very high praise for the other items on the disc played by Constantin Silvestri and the Bournemouth Symphony Orchestra. But I much prefer this reading by Andre Previn conducting "The Moths" with the London Symphony Orchestra.

RCA manage to get no fewer than seven pieces, most of them popular, onto this one disc. Its sales are plainly aimed at lovers of light classical music

of the better type.

It is not beneath Previn's dignity to devote the same care — and sometimes brilliance - to these often hackneyed items. It might be called a jumble sale of short orchestral pieces where here and there you might well pick up a real

Nor has RCA spared any trouble over the excellence of the engineering. The London Symphony Orchestra always gives me the impression of enjoying playing for Previn — and vice versa. In fact the performance of Prokofiev's "Classical always fresh-sounding Symphony" is the best that I can recall. It is quite without condescension or false naivete.

Previn takes Satie's Gymnopedi No. 1 a little slower and more romantically than is usual - I think I prefer it a little faster. But despite its tempo Previn always preserves its classical, perhaps severe, outline, a fact due to the delicious playing of the oboe solo by

John de Lancie.

Then comes a vigorous account of Mendelssohn's Ruy Blas Overture with Previn stressing the drama with contrasts of dynamics always in the very best possible taste. It is so long since I heard this work that I found myself enjoying it very much indeed.

You'll find The Wasps overture, mentioned above, on the first band of the reverse side. It makes a fine contrast to all that has gone before. The playing is as bright as a button with just the right amount of busyness. And the more expansive middle section is cream smooth

and lyrical. The whole overture is

treated with the greatest refinement.
While still in the insect world you have Rimsky-Korsakov's "Flight of the Bumblebee", a virtuoso piece and handled here in that fashion. I think it is too well known to need any further in-

Rimsky-Korsakov is also represented by the slow movement of his almost equally well known slow movement from his "Scheherazad Suite". This is lusciously played without anything being overdone. The string legatos are very impressive as are the rapid ornaments in the woodwind.

The recital ends with a suite of irresistible waltzes from Strauss'. "Rosenkavalier". In this the LSO gets very close to the right swing in the accompaniment, a difficult feat for any non-Viennese orchestra to bring off.

Every item on this disc is so elegantly presented that it could well be a good test of the sensitivity of your equipment. I wouldn't have spent all this space on it if it hadn't been to show my admiration for so much expertise and at a budget price.

HAYDN - Piano Trios Nos. 13, 16 and 17. Beaux Arts Trio. Philips Stereo 9500 035.

Haydn wrote 45 trios and in most of them the piano has the dominant role. Present indications are that from time to time Philips will add more discs to this one until the whole 45 have been recorded. In most of these the cellist is the junior member, the violinist a busy executive, but the piano is, so to speak, the managing director. In fact his role is

Pretty well unceasing.

The fact that the three trios under review are played by the Beaux Arts group is a guarantee of their excellence I mean the playing. It is in the nature of things that the pianist, Manahem Pressler, should stand out, but this he does so discreetly that he never seems to be hogging the score. The violinist, Isadore Cohen, usually echoes Pressler's statements, always admirably and cellist Bernard Greenhouse makes his usually modest contribution for the most part without being overwhelmed.

In all three trios both form and con-

tent are full of delightful surprises. But then which work of Haydn isn't?

I don't know where this present disc was recorded but, wherever it was, it was under the very best of conditions. The sound-balance, clarity and fidelity are all beyond praise. If the other 42 trios are of the same quality they will be well worthwhile waiting for.

MOZART - Eine Kleine Nachtmusik KV525. Violin Concerto in A Major, KV219. Wolfgang Marschner (violin) and the Wolfgang Marschner Chamber Orchestra. Christophorus-Verlag. Stereo SCGLB75923.

This is a completely worthy performance of Mozart's most popular serenade. It has all you might expect from a good German chamber orchestra. All the right instructions are carried out and it is very well recorded although the surface of my pressing is far from immaculate.

The tempos are right and the sound is always musical. It is throughout a thoroughly scholarly performance not without its moments of real charm. I could not find a single note out of place, yet the general effect is never mechanical - an excellent classical reading.

As soloist in the 5th Violin Concerto, Marschner shows more warmth in the first movement, as does his orchestra which he himself conducts. It is only because of the abundance of chamber orchestras nowadays that we don't, I think, hear more of this combination.

There is nothing very inspiring in the slow movement except its technical perfection. Personally I don't like my Mozart over-expressed, but Marschner and his excellent players are, for much of the time, a trifle too deadpan for my liking.

4

VIVALDI - Four Oboe Concertos. RV447, 450, 460 and 463. Heinz Holliger (oboe) with I Musici. Philips Stereo 9500 044.

When the Basle Chamber Orchestra visited Australia some three years ago many discerning musicians were struck by the tonal beauty, phrases of unusual length and the agility of fingers and lips

#### THE BEGINNING . . .

of the chain of audio reproduction is usually a disc. To our current range of audiophile recordings (HSF75, ARK by Fulton and Stereo Review) we are pleased to announce the first Australian release of the following:

- 1. Richardson Recordings from the U.S.A. are made to the highest musical and technical standards. Titles available:
  - Eternal Father Vol. I. Organ & Choral music from the U.S. Naval Academy.
  - Handel's Messiah. Excerpts from a concert performance.
  - Annapolis Sounds. Music from Colonial period (late 18th Century). Organ, voice, brass, woodwind.
  - The Spirit of Christmas Brassed. Virtuoso brass quintet present Christmas Carols, etc.
  - Price: \$13.00 each R.R.P. Pack and post \$1.00, extra 50c for certified mail insurance.
- 2. Artofonic Recordings from Canada present a superb two disc set cut at 45 rpm featuring Orchestre Mondrial des Jeunesses Musicales, who play magnificently Moussorgsky/Ravel's "Pictures at an Exhibition", Strauss's "Till Eulenspiegel" and Dvorak's Slavonic Dance No. 8. We believe these discs offer the most natural acoustic perspective of a symphonic orchestra yet achieved.

Price: \$23.00 R.R.P. per two record set. Pack and post \$2.50, extra 50c for certified mail insurance.

#### THE END ...

of the audio chain is usually a loudspeaker.
We offer one that is NOT . . . the largest . . . or the most expensive but IS . . . superbly constructed . . . efficient . . . and intensely musical!



Price \$1,290 R.R.P.



For further information on specifications and availability contact . . .

M. R. ACOUSTICS,

P.O. Box 110, Albion, Q'ld 4010.

of the oboist Heinz Holliger. He was also a delightful and unassuming chap to talk to after the concert.

Well here you have him in four Vivaldi concertos and to describe his playing of all four as ravishing is no overstatement. Another spectacular feature of his playing is his ability to allow the sound to die away gradually at the end of some phrases. Now the way Holliger does this is a very difficult feat indeed and it is, perhaps, his knowledge of just how well he does it that encourages him to use the effect just a trifle too often.

But when you remember that on the concert platform he would probably play only one of these concertos and that here he plays four, goes far to make this, I feel, a somewhat churlish remark about this tiny mannerism. After all you don't have to listen to all

four at one sitting.

The engineering is superb, with a real chamber music balance. And I repeat confidently that on this disc is some of the most elegant oboe playing you will ever be likely to hear. Moreover it all sounds so effortless that I could only marvel at its perfection.

The accompaniments supplied by I Musici are all of the same high standard. Again to avoid any more superlatives all I can recommend is that you buy it. It should provide endless

enjoyment.

☆

#### RAVEL - Daphnis and Chloe. Complete Ballet. Boston Symphony Orchestra conducted by Charles Munch, RCA Gold Seal Stereo AGL1-

The late Charles Munch could be a very uneven conductor, sometimes brilliant, sometimes dull. Indeed I remember hearing him in Paris conduct a French orchestra, in a concert celebrating the 50th anniversary of Debussy's death, in a manner that I found boringly clumsy.

This concert, as if to advertise the French love of La Gloire, was entitled "Homage of the City of Paris to Claude Debussy". It was held in the Theatre of the Champs-Elysees, decorated with 10,000 Gloire de Dijon roses, and with the Garde Republicaine in full dress uniform and with drawn sabres lining

the staircases

You would think this an occasion to inspire any group of players — but no. The concert was mediocre in the extreme, not only Munch's readings but the general coarseness of the playing,

During his visit to Sydney some years ago with the Boston Symphony Orchestra, at the end of an unremarkable performance of "Berlioz's Symphonie Fantastique" in the Town Hall, the tolling of the bell was quite deafening.

In this present recording of "Daphnis and Chloe", Munch sets out to really "sell" Ravel's wonderful score. His opening is quite convincingly mysterious until the chorus enters, when all mystery flees. And despite the skill with which the disc has been remastered the sound is later a bit congested in the ffs.

Throughout the recording the bringing forward of the chorus is too often at the expense of the orchestra which occasionally becomes almost inaudible. And I know this is difficult to believe, but there are sometimes some downright lifeless passages.

But here and there Munch gets the score to glitter quite excitingly. The 7/4 Dorcan's Dance, for instance, although it is beautifully and delicately attacked in the woodwind passages, coarsens in tone towards the end. All through the ballet Munch tends to pay too much attention to the confectionary department — harp glissandos and so on.

Ravel was essentially a miniaturist despite his two lovely and witty one-act operas. Daphnis is his greatest orchestral work. Indeed he nearly blew himself up writing it and, with the score finished, he took a very long holiday before resuming composition.

In some of the exquisite detail in the scoring the Boston players don't seem to be guite up to their top form and I begrudge every note I miss in this superb work by one of the greatest writers for orchestra of this century. Many passages I waited for could not be heard on this disc. And the chorus seldom sounds as remote and disembodied as it should. I still prefer Momteux's performance of the work.

There is also an irritating turnover. Altogether a bit disappointing though the sound improves if you use a bit more gain than usual. The surface on the second side of my pressing is a bit prickly.

BRAHMS - Violin Concerto. Gideon Kramer (violin) with the Berlin Philharmonic Orchestra conducted by Herbert von Karajan. EMI Stereo-Quadraphonic OASD 3261.

Here is another name new to me -Gideon Kramer — a violinist with a luscious full tone just right for dominating the fine playing of the Berlin Philharmonic under Von Karajan. Kramer's reading, admirably mirrored by Karajan, is big enough to suit the massive work admirably.

Kramer may be a newcomer to recordings in this country but I am sure he will soon be a great one. The collaboration with Karajan comes off splendidly on stereo although my pressing is compatible stereo/quadraphonic.

Most record buyers of serious music are likely to already own one or perhaps more alternative versions of this, one of the last of the great symphonic violin concertos. But whichever you might already own, you'll find it difficult to better this one. If you want a sample listen to the perfection of the double stopping in the cadenza.

I am not surprised that (according to the sleevenotes) Karajan, not a man to throw praise around idly, stated after the recording session that ... "Kramer is, in my opinion, the greatest violinist in the world". I am inclined to agree with him despite other contenders for that title. After all when you get up into this bracket just how do you decide who is best among equals - I'll spare you the Latin for this quotation.

The second movement is as beautifully expressive in both the solo and orchestral parts, and though I am no slavish admirer of Brahms it moved me deeply. And the formidable Finale also leaves nothing that I felt could be improved on. The sleevenotes also mention that this 30-year-old newcomer was a pupil of the late great David Oistrakh. I have often pointed out how difficult it is for a reviewer to convey his sense of perfection about a performance without resorting to a monotonous use of superlatives. I am facing the same difficulty again with this disc. I can only say that here is a performance that will probably be unrivalled in what is left of my lifetime. By the way, Kramer uses the Kreisler cadenzas and the balance between violinist and orchestra is perfect at all

#### LANTHUR ELECTRONICS

69 Buchanan Ave, North Balwyn, Vic. 3104. P.O. Box 162. Ph: 859 4061.

#### MOTOR SPEED CONTROLLER KITS

Suitable all 240v ac/dc brush type. Controls down to stop without loss of torque. Hand tools, lathes, potters wheels, etc. Suits motors up to 10 amp 2400 watt capacity.

Price including postage \$10.95

#### LAMP DIMMER KITS

Will control incandescent lamps from full to out. 10 amp 2400 watt capacity. Price including postage \$8.50 If slider type control required instead of rotary. Extra 25c

#### CABINETS SUITABLE SPEED & DIMMER

Plastic with alum. lid \$1.75 Aluminium \$2.95

#### BATTERY SAVER KITS

Supplies dc voltages 6 to 15 amp @ 1 amp. Tapped transformer, rect., capacitor and circuit supplied,

Plus postage. Vic. \$1.00. Others \$2.00.

#### BATTERY CHARGER KITS

Will charge 12 volt wet batteries @ 2 amps. Transformer, rect., ballast resistor and circuit supplied, \$9.95.

Plus postage Vic. \$1.00. Others \$2.00.

Specialists supply electronic components schools, gov. depts., industry, etc.

## SPECIAL PURCHASES

#### GARRARD

**Model SL65B** 

RECORD CHANGER AT LESS THAN 1/3 LIST PRICE — \$29.50

(RECOMMENDED RETAIL PRICE \$110.00)

SUPPLIED WITH GOLDRING MAGNETIC CARTRIDGE AND DIAMOND STYLUS.

CAN BE SUPPLIED WITH SHURE M75-6 MAGNETIC CARTRIDGE AND DIAMOND STYLUS A \$2.50 EXTRA

ALL CHANGERS NEW IN ORIGINAL CARTONS

#### **SPECIFICATIONS**



A precision automatic and manual record-playing unit fitted with Garrard Synchro-Lab4 pole shielded motor to provide constant speed conditions for the 101/2 inch aluminium turn-

The low resonance tubular pickup arm is counter-balanced with a resiliently mounted weight to permit light sensitive tracking, and the slide-in cartridge carrier enables stylus inspection and the interchange or replacement of cartridges to be carried out simply and guick-

Fine stylus force adjustment and bias compensation are both calibrated for accurately setting the arm to give optimum playing conditions for the chosen cartridge.

The fluid-damped level-type cue and pause control ensures gentle lowering of the pickup to the surface of the record and the record-stabilizing overarm swings back out of the way for more convenient single-record play.

Up to eight 12-inch 33 1/3 rev/min records of the same speed, size and stylus setting can be played at one loading, single records can be repeated automatically

A short spindle is supplied for single record play records.

Precision engineering is reflected in the styling of the SL65B, which is elegantly finished in black and silver.

Size (including rear and side overhang of pickup arm) 14 1/4 in (374.5mm) wide by 121/4 in (317.5mm) front to rear by 41/4 in (114.5mm) above and 2 15/16in (75mm) below lower edge of unit plate.

Wow and flutter better than 0.14% r.m.s.

Rumble (relative to 1.4cm/sec at 100Hz) better than - 46dB.

POST AND PACKING EXTRA

NSW \$2.75

Vic., SA & Qld \$4.75 (Reg. post \$2.00 extra)

Tas., WA & NT \$6.00

#### BASE AND PERSPEX COVER AVAILABLE AT \$25.00 EXTRA Plus Postage

#### NEW STANDARD PM-403 W-24 WATT STEREO AMPLIFIER AT LESS THAN TRADE PRICE

MANUFACTURED BY STANDARD RADIO CORPORATION - A MAJOR JAPANESE ELECTRONIC MANUFACTURER.



VIC., QLD, SA \$5.00 WA, TAS. \$6.50

(Reg. post \$2.00 extra)

SPECIFICATIONS:

Continuous power 12 watts R.M.S. per channel at 8ohms. (24 watts) at 1KHz

Harmonic distortion at 1KHz 0.5% to 10 watts

Power bandwidth 20-20,000Hz at 80hms

Frequency response 15-40,000Hz

Signal to noise ratio Aux. 70db Mag. 60db.

Bass control +10db at 100Hz Treble control +10db at 10,000Hz

Input sensitivity Mag. 2.5mv, Cer, 150mv. Aux 100mv, Tape 500mv.

TAPE MONITOR SWITCH • LOUDNESS CONTROL • SPEAKER SELECTOR SWITCH

● HEADPHONE JACK ● SEPARATE BASS & TREBLE CONTROLS ● BALANCE CONTROL Dimensions 131/2" by 8" by 4" high SUPPLIED IN WALNUT FINISHED CABINET WITH

OPERATION INSTRUCTIONS & SCHEMATIC DIAGRAM READ REVIEW ON THE STANDARD PM-403W AMPLIFIER IN NOV. ISSUE OF E.A.

#### SPECIAL PACKAGE OFFER

STANDARD PM-403W AMPLIFIER — TWO GOODMAN-FOSTER SPEAKER KITS AND GARRARD SL65B CHANGER WITH SHURE MAGNETIC CARTRIDGE \$155.00.

(Cabinets for speakers and changer not supplied.) Freight and packing extra per rail or air freight.

#### NEW GOODMANS-FOSTER 3-WAY 4 SPEAKER HI-FI SYSTEM

Frequency Range 45 to 22,000 cycles. Power rating 25 watts. Imp. 8 ohms. Supplied in kit form (less cabinet) each kit comprises two English Goodmans 8" bass units. Foster 5" mid range. Foster 1" dome tweeter crossover components (condensers & inductance) innabond, speaker fabric & plans of cabinet. Cabinet dimensions

Post & packing extra: NSW \$2.70; Vic., SA, Qld \$4.70; WA \$5.70. (REGISTERED POST \$2.00 EXTRA IF REQUIRED) cabinets available.

\$39.00

#### CLASSIC RADI

245 PARRAMATTA RD, HABERFIELD 2045. PHONES 798-7145, 798-6507.



#### Devotional and Christmas

THE SPIRIT OF CHRISTMAS BRASSED. The Annopolis Brass Quintet. Stereo, Richardson Records RRS-5. (From M. R. Acoustics, P.O. Box 110, Albion, Qld 4010).

A strange title, I must say, but behind it lurks a very impressive recording. It does not say so on the label but the distributors suggest — and I agree — that it carries the sonic stamp of the ARK-Fulton discs, reviewed recently and also distributed by M.R. Acoustics. The sound is very open, very clean and the pressing is beyond criticism. Top flight sound indeed.

But thirteen tracks of a brass quintet? Would it not be rather much for anyone but a band instrument enthusiast? In fact, no. The Annopolis Brass Quintet is a very capable group, who know their instruments, their audience and their music. You will find it no effort at all to listen, as they present a varied program of Christmas music from different lands and

different periods:

Crisp English Carol Medley — Adeste Fideles — Joy To The World — El Cant Dels Ocells — Swiss Chansons — The Twelve Days Of Christmas — O Come, Emmanuel — A Spanish Medley — The First Nowell — Good King Wenceslas — O Holy Night — Von Himmel Hoch, Da Komm 'Ich Her - We Wish You A Merry Christmas.

If you plan to buy only one Christmas record, this would be well worth considering. (W.N.W.)

MORE THAN WORDS. Parable. Maranatha, stereo HS 777/22. (From S. John Bacon Publishing Co, 13 Windsor Avenue, Mount Waverley, Vic. 3149.)

"Parable", featured on this album, is a typical Gospel Group presumably accessable for hiring through Maranatha Music, Irvine, California. Most of the music presented is by Chuck Butler and, while it is in modern format, with elements of soft rock, it is much nearer to middle-of-the-road than the sound from other recently featured Gospel groups.

In fact, with the lyrics printed in full





on a sheet inside, anyone with reservations about these "new fangled" Gospel songs could reasonably invest in this musically fairly conservative example and form their own opinion.

The titles: More Than Words - All Alone — Sweet, Sweet Song — Maybe Someone's Callin' - I Know What It's Like — Peter, James & John — On Your Own — Let The Old Man Die — Friends - Song For The Church -Goodbye - 16 Petersham Place.

Diction is average but, with the lyrics available, there is no problem anyway. The actual sound quality is excellent and the pressing surface is free from noise. Good family gospel listening.

(W.N.W.)

HAND TO THE PLOW. Paul Clark. Stereo, Seed Records PSR-005. (From Sacred Productions Australia, 181 Clarence St, Sydney, and other

Paul Clark wrote all the songs on this album, played acoustic and classical guitar, piano, drums and synthesiser, took lead and back-up vocals and created special effects. A versatile young man indeed, but he is also backed by a group of other musicians and vocalists, who are appropriately credited in the jacket notes.

The words of the songs, given in full on the inner sleeve, are entirely devotional, expressing old-time Christian values in the modern idiom. The music, too, is in the modern idiom, ranging from straight rock in the opening tracks to a much quieter mood towards the end. But it's essentially music for today's youth, and that's where Paul Clark's appeal will lay.

The quality of the sound is very clean. (W.N.W.)

#### Instrumental, Vocal and Humour

THE JAZZ ALBUM. Rob McConnell and The Boss Brass Attic LAT 1015. Astor

The Attic label is a product of the Canadian Broadcasting Corporation, to showcase local talent; a job it does very well, judging by this record. There are five long tracks: It's Hard To Find One Portrait Of Jenny - My Man Bill -Body and Soul - That's Right, all with a bright brassy big band sound about them that's easy to listen to. The record jacket has a group portrait of the 21 musicians involved and the instruments are listed for each track. The quality is good. (N.J.M.)

THE GRAND WALDO DE LOS RIOS. Hispavox L-36251 Festival release. Waldo De Los Rios does his usual

thing with the popular classics with two tracks each from Beethoven, Mozart, Verdi and Tchaikovsky. The music usually starts in a fairly straight fashion; then the rhythm section makes its presence felt in no uncertain manner and the orchestra starts to swing,

Some purists might object but it makes for pleasant listening, with the technical quality the usual high I have come to expect from Hispavox. This record is one of a continuing series, with operas, concertos, overtures and symphonies all getting the same treatment. Some of the tracks are: The Marriage Of Figaro - Nabucco -Romeo and Juliet - La Traviata -Pastoral Symphony. (N.J.M.)

\*

"PORTS." Perry Botkin Jr. A&M L36280. Festival release.

I had not heard of Perry Botkin Jr. before listening to this record. More's the pity, as the group he leads produces

Reviews in this section are by Neville Williams (W.N.W.), Jamieson Rowe (J.R.), Leo Simpson (L.D.S.), Norman Marks (N.J. M.), David Edwards (D.W.E.) and Greg Swain (G.S.).

# F.M. TUNER FROM



The new Audiosound T752 stereo F.M. Tuner offers very high performance with a simplicity rarely found in today's Hi-Fi Jungles. Yet this tuner is able to provide low distortion, interference free, wide range sound from any transmission arriving at the aerial capable of full quality recovery.

From its hand wired, 5 gang linear front end unit to its low distortion demodulator, most parameters (except the price) approach state-of-art.


The sophisticated single lamp tuning/muting circuit allows only correctly tuned signals to be heard and the styling matches perfectly with our A750D low T.I.M. amplifier. The non-state-of-art price - \$340.

Hear this tuner with Audiosound high performance amplifiers and loudspeakers at our showroom now.

audiosound electronic services N.S.W. 2099. Phone: 938 2068.

148 Pitt Road, North Curl Curl,

### **AUDITEC A-SERIES AMPLIFIERS**

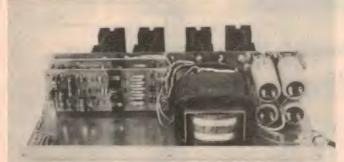

THE A-SERIES ARE NO-FRILLS BASIC POWER AMPLIFIERS READY TO CONNECT TO YOUR PREAMPLIFIERS OR MIXER AND LOUDSPEAKERS

**AVAILABLE IN 1 x 100 WATT (1A009, 1A033)** 2 x 100 WATT (2A009, 2A033) 1 x 200 WATT (1A027)

MELBOURNE: Zephyr Products. Phone 568 2922 BRISBANE: Delsound Pty Ltd. Phone 229 6155 ADELAIDE: Neil Muller Pty Ltd. Phone 74 1162 BUNDABERG: Bundaberg Hi-Fi, Phone 71 3176 CANBERRA: Musique Boutique. Phone 82 2553
PERTH: Willis Trading Co Pty Ltd. Phone 21 7609
TAMWORTH: Hi-Fi Gallery. Phone 65 7788
MARYBOROUGH (QLD): Keller Electronics. Phone 21 4559 ROCKHAMPTON (QLD): Premier Sound. Phone 28 2701 SURFERS PARADISE (QLD): Beno's Musical Supplies. Phone 38 1568

WHYALLA (S.A.): Audiolab Sales. Phone 45 7755 DARWIN: Darwin Communications Systems. Phone 85 3184 ALICE SPRINGS: Farmer & Davies Electronics. Phone 52 2967 FOR DESCRIPTIVE LEAFLETS ON THESE AMPLIFIERS CALL. PHONE OR WRITE TO:

AUDITEC AUSTRALIA PTY LTD 10 WAITARA AVENUE, WAITARA, N.S.W. 2077 PHONE: 48 4116

(PACIFIC HIGHWAY SIDE OF WAITARA STATION)

#### THE LIGHTER SIDE

some very pleasant music, mainly jazz oriented in nature, with such titles as: The Lovers — Lady Ice — Don't Believe The Laughter — Eternal Sunrise — Looking For Home — Nadia's Theme — Bless the Beasts and Children — Bridges - You've Gone Away - Ports - Gym-

The team is made up of a number of well known West Coast recording artists, including Bud Shank on flute and alto sax and Tommy Morgan on harmonica. Apart from a surface crackle on the opening tracks of each side, the quality is excellent; in all a very enjoyable disc. (N.J.M.)

> 2 1

#### FRANCIS LAI — THE MAN AND HIS MUSIC. Image Records Pty Ltd. Stereo ILP4945.

My expectations were rather high after reading the cover notes of this album. Francis Lai is the man who composed such well known movie themes as "Theme from Love Story" and "A Man and a Woman". These are featured here, in company with 10 other Francis Lai compositions.

However, I must confess to a growing feeling of indifference after a listening session, at least as far as the majority of tracks are concerned. The style is, perhaps, a little too avant-garde for my personal taste; maybe for yours also.

The track titles are: Theme from Love Story — Dance Of Love — Under Our Star - Solitude - Love in the Rain-The Legend of Frenchie King — A Man and a Woman — For a Shadow — For the Blood of Others — The Blue Rose — African Summer — Happy New Year.

Have a listen before deciding to buy. Record quality is good. (G.S.)

From trade houses or

N.S.W.: 709 5293

**RE757** 

**ROYSTON ELECTRONICS** 22 Firth St., Doncaster, Vic., 3108. VIC: 848 3777 QLD: 52 3166

S.A.:

42 6655 W.A.: 81 5500

45rpm

PICTURES AT AN EXHIBITION (Moussorgsky/Ravel); TILL EULENSPIEGEL (Strauss); SLAVONIC DANCE NO. 8 IN G MINOR OP 46 (Dvorak). Orchestre Mondial de Jeunesses Musicales conducted by Pierre Hetu. 2-record set, stereo, 45rpm, Musicus MS2-45101. (From M.R. Acoustics, P.O. Box 110, Albion 4010 Old.)


The immediate point of interest about this record is the fact that it is intended to spin at 45rpm — an unusual speed for a 12-inch album. While it imposes a proportional reduction in the playing time, it does open out the waveforms and holds the promise of a more transparent sound. And this is clearly where the production team placed the emphasis, using twin microphones in the concert hall feeding straight into the master tape recorder, without the intervention of compressors, equalisers, noise processers, etc, which "generally do more harm than good". For their French customers they explain "fait generalement plus de tort que de bien'

And the sound is good, very good. I'm not prepared to say that it excells the best 33s that I've heard but it's certainly well above average, with no suggestion of that stringy, messy build-

### TOCORD ULTIMATE **AUDIO CABLES**
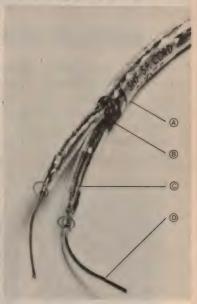
#### Can you hear your speaker cables?

Recent research has confirmed that listening to a quality Hi-Fi music system which utilises standard figure eight speaker cable may be compared with viewing a colour slide out of focus!



- Clear P.V.C. outer sheath.
- Braided conductors to cancel linear inductance.
- 144 individually insulated conductors per side.
- Tinned copper ends on 20 ft lengths.

Specifications:


D.C. Resistance .0105  $\Omega$  /m 9.15  $\Omega$  (constant) Impedance Inductance 0.15 µH/m


HARMAN AUSTRAL P.O. BOX 6, BROOM N.S.W. 2100 PH. (02) 939-2922. TLX. 24873.	
P.O. BOX 6, BROOM N.S.W. 2100 PH. (02) 939-2922. TLX. 24873.	AD SHI
NAME ADDRESS	POSTCODE



### Speakers unlike all others DIRECT/REFLECTING

### :///

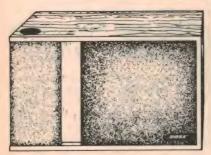

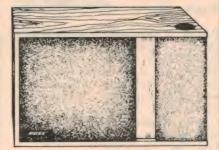

#### MADNESS? OR A STROKE OF GENIUS!

Musical instruments radiate sound in all directions. So at a live performance only a very small portion gets to us directly. The bulk of it is reflected off walls, floors and ceilings before reaching our ears. All Bose

loudspeakers are direct/reflecting and employ that principle in interesting and innovative ways. Hear the difference this makes and discover that direct/ reflecting is a "stroke of genius".



MODEL

Call it what you like but to obtain a good sound balance in. your room this device may save you from changing your room around — or changing your speakers around — or both.

Simply by adjusting this control on the top of your Bose 301 loudspeaker you can alter the sound balance to suit the shape of your room.

The 301 operates on the direct/

reflecting sound principle. However instead of reflecting sounds off your walls it reflects the sound off a variable reflector within the cabinet.

Contact this office for your colour brochures on the full range of Bose direct/reflecting loudspeakers or visit a Bose dealer and hear the incredible impact of speakers unlike all others.

#### BUSE

- AUSTRALIAN DISTRIBUTORS -W. C. WEDDERSPOON PTY. LTD., 3 FORD STREET, GREENACRE N.S.W. 2190 TELEPHONE: 642-3993 642-2595

#### THE LIGHTER SIDE

up that can occur when a recording chain is being pushed towards its limit.

Recorded in Montreal, it features the Youth Orchestra that attended the 21st Olympiad in that city in 1976. Classical buffs may have stronger views than mine about relative performances but if, like me, your interest centres on the technology of the recording, and on its potential as a demonstration disc, you won't argue with their effort musically. Incidentally, side four concludes with a 1kHz reference track for system balance: 30 seconds of gauche (left), 30 seconds of droite (right) and 30 seconds of gauche + droite.

Another interesting record, thanks to the initiative of M.R. Acoustics. (W.N.W.)

JOSEPH SEAL PLAYS, Wurlitzer pipe

organ. Stereo, Astor PKL-5557. Here's yet another album from veteran English theatre organist, Joseph

Seal. Played on the three-manual pipe Wurlitzer at the Musical Museum in Brentford, it recaptures, without apparent effort, the atmosphere of similar instruments played in movie houses

around the world.

As distinct from artists like Jesse Crawford, who tended to linger over melodies, Joseph Seal hurries some of these through in a demonstration of digital dexterity. But, as often as not, that was part of the show: Down The Mall - I Only Have Eyes For You -Over The Waves - Swedish Rhapsody - Bells Across The Meadow - Swing O' The Kilt - Warsaw Concerto Temptation Rag — Melodies From Coppelia Ballet — A Nightingale Sang In Berkeley Square — Liebefreud — Forgotten Dreams — Hungarian Dances.

The sound is good and, if you haven't treated yourself to an old-fashioned Wurlitzer for a while, why not make it this one? (W.N.W.).

PARIS WAS MADE FOR LOVERS. Michel Legrand and his Orchestra. Image ILP 4946, series 498. Astor release.

This mainly orchestral helping of pleasant music is from the soundtrack of a film of the same name, with two vocals from Michel Legrand and one each from Dusty Springfield and Matt Monro. With a distinctly French flavour, it all makes for enjoyable listening.

Some of the tracks: Paris Was Made For Lovers — Where Love Begins — A Place In Paris - Concert For Cabs -Pavanne For People - Sea and Sky -Where Love Ends — Fanfare.

The cover notes give a brief biography of Michel Legrand. The quality is good. (N.J.M.)

### **Bushwackers** Band

MURRUMBIDGEE. The Bushwackers. Image stereo ILP-776. Astor release.

Having spent my boyhood in the bush, where it was no compliment to be referred to as a "bushwacker", I find it hard to identify with Australians who call

themselves by that name, and who affect the songs, the accents and the style of what I suspect was a prettty rare breed of countryman. Most of the hayseed musicians and vocalists who crossed my boyhood path seemed far more involved with traditional Irish and

My problem aside, the Bushwackers, emerging in an unlikely fashion from a university background, have picked up and adopted a large repertoire of Australian bush tunes, and were chosen to provide the soundtrack of the TV bushranger series "Cash & Co", and later the theme for "Ben Hall". They've performed throughout Europe, the British Isles, and Hong Kong and, as I write, are currently on tour in Australia. They appear to have been very well received, with highly quotable reviews in the press.

Their album didn't turn me, personally, into an instant bush ballad enthusiast but this must be said: their feeling for bush music and their evident musicianship has produced a sound and an impact which is an effective compromise between what often sounds very corny and commercial Australiana like "Waltzing Matilda" and "Click Go The

The track titles: Augathella Station — Lachlan Tigers — Billy Of Tea — Cold Feet — Rain Tumbles Down — Streets Of Forbes — The Cameo — Tomahawkin' Fred (The Ladies' Man) — Murrumbidgee River — Flashjack. (W.N.W.)

4

#### JOAN BAEZ, Golden Hour GH843. Astor Release.

Those who do not already own an album featuring the brilliant American folk singer Joan Baez should not miss this opportunity. Seventeen songs are featured in all, each sung with a conviction that shows a genuine sympathy for the human condition. Listen to the remarkable "There But For Fortune" (2nd track, side 1) if you need further convincing.

Tracks on this album are: We Shall Overcome — There But For Fortune — Plaisir d'Amour — Babe I'm Gonna Leave You - The Night They Drove Old Dixie Down - Don't Think Twice It's All Right — Long Black Veil — A Hard Rain's Gonna Fall — It Ain't Me Babe — Black Is The Colour — The Last Thing On My Mind — Help Me Make It Through The Night — Farewell Angelina — Bachianas Brasilias No. 5 Aria - Lady Come From Baltimore - It's All Over Now Baby Blue - Hush Little Baby.

Record quality is excellent. Recommended. (G.S.)

Festival release.

#### FUNDAMENTAL ROLL. Walter Egan. United Artists L-36275.

Walter Lindsay Egan has piercing blue eyes, and composes and sings very acceptable rock and roll music. Since this is his first record (to my knowledge), the pun in the title is excusable. Aided and abetted by Stevie Nicks and Lindsey Buckingham, he has produced a very listenable album.

Tracks featured are as follows: Only The Lucky — Won't You Say You Will — Waitin' — Feel So Good — Yes I Guess I Am — When I Get My Wheels — Where's The Party — She's So Tough - Tunnel O'Love - Surfin' & Drivin'.

Recording quality was excellent, except that the copy submitted for review had some foreign matter stuck to it which caused the stylus to jump from groove to groove on the last track. (D.W.E.)

#### FROM 1st JANUARY, 1978 **ELECTRONIC ENTHUSIASTS EMPORIUM**

becomes

### **ELECTRONIC** (DISTRIBUTORS)

DISTRIBUTORS OF COMPONENTS AND EQUIPMENT TO TRADE AND INDUSTRY

- WIDEST RANGE OF STOCK
- OFF THE SHELF AVAILABILITY
- A.W.A.
- **Ferguson Transformers**
- **Instant Component Service**
- I.R.H.
- Motorola
- Philips
- Plessey
- R.C.A.
- Soanar
- Swann
- Technico

CALL INTO OUR SHOP FROM JANUARY 3 AND CHECK OUT OUR SUPER SAVE OF ITEMS NO LONGER REQUIRED FOR STOCKING

**CLOSED DEC 25-JAN 3** 

### ELECTRONIC

(DISTRIBUTORS)

SHOP 2 & 3 ARCADE JOYCE ST. PENDLE HILL, NSW 2145 (PO Box 33) OFFICE 636-6222 ORDERS ONLY 636-6052 TELEX: AA23343

### **New Products**

### BWD 539D 25MHz dual trace oscilloscope

BWD Electronics is a local manufacturer whose name is now well established both in Australia and overseas. Here we review the Model 539D dual trace oscilloscope recently released by BWD. It features a bandwidth from DC to 25MHz and a maximum sensitivity of 5mV/cm.

The BWD Model 539D dual trace oscilloscope is a new version of BWD's well proven 539 series. Improvements to this latest model include extended bandwidth and improved timebase facilities.

Overall dimensions of the Model 539D are 190 x 250 x 420mm (W x H x D), including handle knobs and feet. Mass is 6.3kg. A tilting bail is fitted to enable adjustment of the viewing position.

Vertical deflection sensitivity is variable in 12 ranges from 5mV/cm to 20V/m. In addition, the vertical amplifiers can be cascaded to give a sensitivity of 0.5mV/cm at a bandwidth of 12Hz to 100kHz (-3dB). By selecting TV trigger the minimum input signal required for triggering is less than 1mV p-p, enabling signals at this low level to be displayed with good stability.

Selection of chopped or alternate trace is by means of a separate pushbutton switch to the left of the CH-1 vertical sensitivity control. Alternatively, CH-2 can be turned off to give a single trace display for CH-1 only.

Twenty-one ranges (the manual says 19) in a 1-2-5 sequence are provided for the timebase, giving sweep rates from 0.5uS to 2sec/cm. A 5 to 1 vernier extends the sweep down to 10sec/cm. In addition, the horizontal trace position can be pulled out to provide five times magnification of the sweep signal.

Vertical inputs can be either AC or DC coupled, or grounded. Input impedance is 1M shunted by 35pF. AC bandwidth is 2Hz to 25MHz -3dB points) referred to 4cm deflection at 50kHz, with useful response to 30MHz or beyond. These figures make the 539D suitable for service work on CB transceivers and amateur equipment working up to 30MHz.

An attractive feature is that the timebase may be switched off to give X-Y operation, with the CH-2 signal becoming the horizontal component.



This makes Lissajous figure operation or similar comparison of two signals an easy matter. Back panel facilities include timebase out and "Z" modulation.

In common with most modern CROs, no provision is made for direct access to the plates. Observation of waveforms is thus limited by the response of the amplifiers.

An active sync separator is employed to enable TV waveform displays with line or frame lock. In addition, the sync separator can be used as an AM demodulator, enabling double or single sideband displays to be locked to the modulation envelope.

The calibrator waveform is referred to zero crossover of the mains voltage waveform. When this waveform is used to provide external trigger for the timebase, it enables accurate phase measurements on line operated equipment. For example, the firing angles of thyristors or triacs can be measured to within two or three degrees.

Front panel layout of the 539D is conventional and straightforward. All controls are legibly marked, and the unit is easy to drive. A well written manual accompanies the unit, and outlines a number of useful measurement techniques.

Also included in the instruction manual are a frequency response chart and a nomograph for estimating the true rise time of waveforms as observed on the 539D. Another useful nomograph is shown for measuring phase angle using a Lissajous display. The frequency response chart gives approximate calibration correction to beyond 40MHz, thus extending the useful measuring range of the instrument.

A range of accessories is available for the 539D. BWD list such items as probes, cameras, dust covers and a carrying case.

Overall impressions of the 539D are good. The 539 series is a well proven design that has been refined over the past few years, and is backed by good service facilities. A big feature of the unit is the comprehensive instruction manual.

Price of the BWD 539D is \$465 plus sales tax where applicable. Further information can be obtained from BWD Electronics Pty Ltd, Miles St, Mulgrave, Victoria 3170.

Footnote: BWD Electronics has donated the unit pictured as the prize for a competition to be run in conjunction with "Electronics Australia". Details appear elsewhere in this issue.

### Miniature relays for industry

A range of 12V and 24V "Mini Relays" is now available from Robert Bosch (Australia) for use in industrial and automotive applications.

Features of the Mini Relay include: long life (more than 250,000 cycles); 30A contact rating; compact size (26 x 26 x 19mm); and choice of contact configuration (single, double or changeover).

Enquiries to Robert Bosch (Australia)
Pty Ltd, PO Box 66, Clayton 3168.

### Digital Frequency Meter from JR Components

JR Components has released a "special features" kit for our 200MHz Digital Frequency Meter, described in the March 1977 issue. A high stability crystal is included, with a frequency tolerance of ±30 PPM.

The sample kit submitted for review was fully assembled, and appeared to comply with the March 1977 article in all respects. The special features of the unit include an aluminium chassis with a black "Maviplate" cover, a fibreglass PCB with screened component overlay, a choice of input sockets (BNC or UHF) at no extra charge, a silk screened "Polaroid" front panel, and the special crystal.

This latter component is one of the NC-18A types, with a frequency tolerance ±30 PPM at 25 degrees C, and a temperature characteristic of ±30 PPM over the range from -10 to

+60 degrees C. The ageing characteristic is stated to be less than ±5 PPM per year.

All components appeared to be new and of high quality, giving the completed kit a very professional appearance. In operation, the unit was very satisfactory, and could not be faulted.

The 200MHz kit version has a recommended price of \$89.50, while the 20MHz kit version has a recommended price of \$82.50. Fully assembled versions will be available at an appropriately higher charge. Postage and packing is \$2.00 for NSW



customers, and \$4.00 for interstate customers, with registration \$2.00 extra. An air/road courier service is available to any Australian destination for \$6.00.

The 95H90 prescaler is available separately for \$9.50, and the special crystal for \$8.00. Both of these items are sent post free. Further inquiries should be directed to JR Components, PO Box 128, Eastwood, NSW 2122. Tel. 85-3976. (D.W.E.)

#### 30MHz digital frequency counter

A new hand held portable frequency counter is available from B & K Precision. It is intended for general service use and has a guaranteed frequency range of better than 30MHz.

The model 1827 Frequency Counter is housed in a yellow plastic case. A single slide switch functions as a power on switch, and also as a mode selector.

Input connections are made via a front panel mounted RCA phono connector, using a 550mm long test lead (supplied)

The third panel fitting is a momentary contact switch, used to enable the display. This is a six digit LED unit with individual overflow, kHz and MHz indicators.

The counter has two basic operating modes. In the auto position, the six most significant digits are displayed, with the kHz or MHz LED illuminated as required.

In the 1 Sec mode, the gating time is held fixed at 1 second, and maximum resolution is obtained. For frequencies greater than 1MHz, only the last six digits will be displayed, and the overrange LED will be flashing.

The unit has an input impedance of greater than 10k, and a sine wave sensitivity of better than 200mV from 100Hz to 200kHz, and 100mV from 200kHz to 30MHz.

A frequency range from 100Hz to 30MHz is guaranteed, with typical units operating to 50MHz. The internal time base is derived from a 4MHz crystal oscillator, with a temperature stability of ±10PPM from 0 to 50 degrees C.

The counter is powered from 6 AA size batteries. Optional accessories include an AC adaptor and charger, a

NiCad battery pack, a 12V automotive power cord, a DC power supply cord, a signal tap with RCA plug-on tap cable, a 300mm (12") antenna rod, and a carrying case.

Further information is available from Parameters Pty Ltd, 68 Alexander Street, Crows Nest, NSW 2065. Recommended retail price is \$228.85, including tax. (D.W.E.)





### EADER TE


### STEREC

#### LBO-552 5" Horizontal, Dual Trace/ Dual Chan. Oscilloscope

WITH SIMULTANEOUS LEFT/RIGHT WAVEFORM DISPLAY

A solid state achievement that makes audio testing, on-line quality control and general purpose measurements easier than ever. Features a horizontal dual trace/dual channel format that lets you view two independent signals simultaneously and side-by-side on a bright CRT display. Perfect for inspecting and aligning the most sophisticated stereo equipment, the LBO-552 also provides a single channel input for conventional readout. Sensitivity is 20mVp-p/cm; Vert. B'width is DC or 2Hz to 2.5MHz. Sweep speeds are from 10Hz to 100KHz in 4 ranges with input impedance 1MO shunted by 40pF.

250mm h x 180 w x 380 d; 6.5kg.

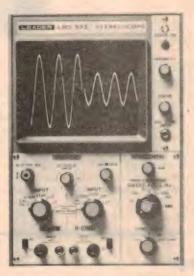



#### LMV-186A Dual Chan./ **Dual Pointer** AC Millivolt Meter

Check stereo signal quality, especially where a big difference exists in two points. This instrument uses identical switches and amplifiers in each channel to operate without crosstalk effects. Measuring range is 100µV to 300V, 12 steps. It has two dB scales: an easy-toread meter face; 2 scale readings; built-in dual amplifier output. Accuracy is  $\pm 2\%$ full scale (1KHz). Channels operate individually, or in common at ch. 2. Scale calibration reads effective values. With input cable 240V/50Hz.

150mm h x 200 w x 250 d; 3.5kg.



### WARBURTON FRANKI

- ADELAIDE 356-7333 BRISBANE 52-7255 HOBART 23-1841 MELBOURNE 699-4999 PERTH 65-7000 SYDNEY 648-1711
- AUCKLAND N.Z. 360-154 WELLINGTON N.Z. 698-272

#### **NEW B.S.R. & GARRARD RECORD CHANGERS** ROLA SPEAKERS AT A FRACTION OF LIST PRICE



NEW STANDARD B.S.R. C123 RECORD CHANGERS

\$20.00

Fully automatic turntable plays up to six records automatically and single records automatically or manually as required. 11 turntable. Bias compensation. Cue & pause control. Record speeds 331/3, 45 and 78 silver trim. Player and changer spindles supplied Fitted with ceramic cartridge. Post & packing extra. NSW \$2.70; Vic., Qld., SA \$3.70; WA \$4.70 (registered post \$2 extra if required)

GARRARD M.82 \$57.00 TRANSCRIPT'ON CHANGER

Supplied with Goldring Magnetic Cartridge with Diamond Stylus. Post & packing (Reg. post) NSW \$3.80, Vic., SA, Qld \$4.74, Tas \$5.50, WA & NT \$5.80.



#### GARRARD CC10A RECORD CHANGER \$14.75

Fitted with a Sonatone Garrard Ceramic Cartridge Sapphire Stylus supplied with template and instructions
Post & Packing: NSW \$2.50. Inter. \$3.50

BASE & PERSPEX COVERS AVAILABLE IN TEAK & WALNUT FINISH

#### NEW ROLA C12PX 12" HI-FI SPEAKERS

Rola twin cone Hi-Fi speakers. Freq. range 40 to 13,000 cycles power rating 30 watts. Imp-8ohms. Post & Packing: NSW \$2.50. Interstate \$3.50.

#### A.W.A.-MSP-Foster Hi-Fi 3-way Speaker System \$29.00 per kit

Frequency Range 40-20,000 cycles Power rating 20 watts RMS Imp-8ohms. Supplied in kit form (less cabinet) Each kit comprises A.W.A. 8 WAC8. 8" base unit. Foster 5 mid range. Foster 1" dome tweeter. Crossover components innabond speaker fabric and cabinet plans
Post and Packing, NSW \$300, Vic. SA, Old \$4.00, Tas \$5.00, WA \$6.50 Cabinet dimensions 23"x13"x10"

#### PLAYMASTER-MAGNAVOX HI-FI SPEAKER SYSTEMS 3-WAY

3-45-L
AS FEATURED IN ELECTRONICS AUST APRIL '75 Complete kit of parts for above system including speakers. Magnayox 8-30 Bass Unit. 6J Mid Range Philips ADO160/T8 Dome Tweeter, crossover components 6" and 3" tubes, speaker silk and innabond (less cabinet) \$57.00 PER KIT.

3—41—L

AS FEATURED IN ELECTRONICS AUST JUNE 76
As above but using the new Magnayox 6-25 Mid Range in place of the 6J with additional crossover components \$65.00 PER KIT.

Freight and packing extra per pass, rail or air freight.

CLASSIC RADIO IS A DISTRIBUTOR FOR FOSTER LOUDSPEAKERS

#### NEW MAGNAVOX - MV50 - 50 WATT SPEAKER SYSTEMS

As featured in Feb 1976 Issue of Electronics Today. Complete kit of parts (less cabinet) comprising Magnavox 10-40 10" bass unit, 625 mid range 6" two XJ3 dome tweeters, crossover network, innabond, speaker silk, and plans of cabinet.

\$82.00


PER KIT

freight extra per rail or air freight Cabinet available

### ASSIC

245 PARRAMATTA RD, HABERFIELD 2045. PHONES 798 7145. 798 6507

#### **PCB** rotary switch

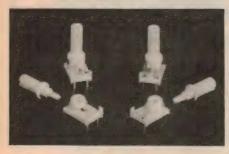

Designated type MR, this simple single pole switch is specially designed for PCB mounting. It offers two or three positions with positive indexing, and is suitable where relatively infrequent operations are required reliably, but at low cost.

Switch body material is self extinguishing polyester thermoplastic. Maximum working voltage is 1000V AC, and current carrying capacity is 1A at 250V AC

Further information from C & K Electronics (Aust.) Pty Ltd, PO Box 101, Merrylands 2160.

#### DC/DC converters

Scientific Electronics has announced details of a new DC/DC converter range.

The new converters are designed for applications requiring a well isolated supply derived from a DC source, and will operate over a wide input voltage range. There are two models: 96D rated at 50-100W, and 95D rated at 100-500W.

Conversion is by pulse width modulation, controlled by a feedback circuit to maintain constant output voltage. Other features include reverse input voltage protection, a constant voltage/current limit characteristic, and soft start up and recovery.

Enquiries to Scientific Electronics, 42 Barry St, Bayswater 3153.

### Singer test set for 2-way radio

Designed to form a complete testing system for communications equipment, the Singer FM-10CS is basically a heterodyne frequency meter covering the range 50kHz to 1.3GHz. It uses a TXCO reference oscillator and synthesiser system to produce any frequency in this range to 1Hz resolution. Addition of sweep generator and CRT modules allow the system to be used for spectrum analysis, network analysis and many other testing functions.

Altogether there are a total of 10 plug-in modules, making the system very flexible and suitable for measurements on AM, FM, CW and



SSB equipment. Accuracy of frequency measurement is 1ppm.

Further information on the Singer FM-10CS is available from Datatel Pty Ltd, Suite 4, 3 Raglan St, South Melbourne, Victoria 3205 (Tel. 03-699 7614)

### Two-metre FM amateur transceiver

Recently released onto the Australian market, the Icom IC225 is a synthesised FM transceiver designed especially for the amateur 2-metre band.

The IC22S is PLL controlled and uses a diode matrix board to generate the required frequencies at 25kHz intervals. The transceiver is preprogrammed for all Australian amateur repeater frequencies, together with Channels 40, 50 and 51 simplex. Spare diodes are supplied for adding private channels.

Good intermodulation attenuation has been achieved by use of a low-noise, high, gain MOSFET in the receiver front end, and a five-section helical resonator filter which determines the receiver bandpass. Power output is 10W nominal, and 1 W in the low power position.

The unit is supplied complete with microphone, operating manual, brackets and cables, and a 90-day warranty.

Further information is available from Vicom International Pty Ltd, 139 Auburn Rd, Auburn 3123.



The Icom IC22S is a PLL controlled FM transceiver for the amateur 2-metre band.

#### COWPER

SHEETMETAL WORK FOR THE ELECTRONICS INDUSTRY

E.A. VIDEO DATA TERMINAL CASES MINI-SCAMP MICROCOMPUTER

C.S. 108 & 216 Hobby Boxes

 $108 \times 108 \times 50 + + 216 \times 108 \times 50$ 

Inquiries welcome on Cases and Panels

**Rack Mounting Chassis** 

Chassis & Covers

Vented Transformer Cases

General Sheetmetal & Welding

COWPER SHEETMETAL & ENG.

11 COWPER STREET GRANVILLE N.S.W. 2142

PHONE 637 8736 (S.T.D. 02)
(A Division of The Star Delta Co. P/L)



1.
Hold Soder-Wick on termination with hot soldering tip. Wicking action soaks up solder.

Remove tip and braid. Termination is left clean and free of solder.



Soder-Wick is a specially treated copper braid which soaks up molten solder like a sponge. Desolders a P.C. pad in a second or so: acts as a heat sink to protect circuits and components.

In a range of sizes from your wholesaler or

02-709 5293 03-848 3777

ROYSTON 03-8
ELECTRONICS

RE47





# Books & Literature

#### Tape recording

MASTER CREATIVE TAPE RECORDING. By John Gardner. Published 1977 by Newnes Technical Books. Stiff paper covers, 136 pages, 215 x 133mm, illustrated. Price in Australia \$5.50.

As the author points out in his preface, a great many tape recorders gather dust in homes, either because the owners never really needed one in the first place, or because their best efforts at live situation recording produced only discouraging results. It is to the latter group that this book is directed.

Chapters 1 to 4, occupying 60 of the 136 pages, seek to explain the nature of the technology and equipment involved: Recording and reproduction — Choosing a suitable machine — Choice and use of microphones — Mixers, monitoring and installation.

The next four chapters discuss in a practical way what is involved in using this equipment for creative recording — as might be involved in a music or drama group, for tape club circulation, for community broadcasts or for audiovisual presentations: Improvising a studio — Organisation and method — Drama and features — Music.

There is a final chapter on editing, an

appendix and an index.

My impression of the book is that it is well written, well illustrated, thoroughly practical and well suited for study by those it is intended to help—non-professionals who aspire to produce something much better than the usual "amateur" recording.

Our review copy came from Butterworths, 586 Pacific Highway, Chatswood 2067. (W.N.W.)

team, Doug DeMaw, is better known as the Technical Editor of QST. With such authors, one would expect a book of the highest quality and an examination of their work bears this out.

As the title would indicate, this is not a publication for the beginner in electronics. However, the use of mathematics is minimal. The first chapter deals with basic solid state devices and principles. This is in preparation for the application of design principles in RF circuits. These include AM, SSB, DSB and CW transmitters, mixers, detectors, RF amplifiers, networks, filters, etc. Receivers for amateur use are also well covered.

Perhaps the material on the design of solid state RF power amplifiers is as timely as any, as this is a field where I feel that readily available design guidelines have been somewhat lack-

ing in the past.

In addition to the design and theory content, there are numerous well presented practical examples which could be built up by the average amateur. This is a book which I can confidently recommend to anyone interested in solid state circuitry professionals as well as amateurs and enthusiasts.

In addition to the nine chapters, there is an appendix, together with quite a lengthy bibliography and an index

Our copy for review came from Technical Book and Magazine Company Pty Ltd, 289-299 Swanston Street, Melbourne, Vic. 3000. Copies should also be available from other technical booksellers. (I.L.P.)

#### Solid state design

SOLID STATE DESIGN FOR THE RADIO AMATEUR. By Wes Hayward, W7ZOI and Doug DeMaw, W1FB. Published 1977 by American Radio Relay League, Inc. Soft covers, 256 pages, 276mm x 208mm, illustrated by many circuits, diagrams and photographs. Australian recommended price \$10.95.

This is the first edition of the latest addition to the ARRL's already long and useful list of books for the radio amateur and others in electronics. Author Wes Hayward is at Tektronix Corp. and the other member of the

#### Loudspeaker survey

HIFI CHOICE LOUDSPEAKERS. By Angus McKenzie. Paper cover, 211 pages, plus advertisements, 199 x 147mm. Published 1976 by Aquarius Books Ltd, England. Price \$2.95.

In line with the name and source, this book is a survey of currently available hifi loudspeaker systems, intended primarily for enthusiasts in the U.K. Some of the brand names would be familiar to their Australian counterparts but others would not and, among the familiar ones, not all the models would still be current.

While the usefulness of the book would therefore be limited on this account, as also would be the relevance

of the many advertisements front and back, it does contain 70-odd pages of general discussion about the methods and problems of evaluating loudspeakers for review purposes: Types of loudspeakers — Subjective listening tests — The anechoic chamber Coloration - Distortion -Impedance and phase — Efficiency and power output - Polar response and omnidirectional loudspeakers Crossover networks — Loudspeaker positioning - The program souce -Amplifier requirements - Presenta-

Our review copy came from Thomas C. Lothian Pty Ltd, 4-12 Tattersall's Lane, Melbourne, 3000. (W.N.W.)

#### Integrated circuits

BEGINNER'S GUIDE TO INTEGRATED CIRCUITS. By I. R. Sinclair, Newnes-Butterworth, London, 1977. Soft covers, 120 x 186mm, 185pp, many diagrams. Price in Australia \$6.00.

In his preface, the author of this book writes that it is intended for newcomers to electronics and those with an interest in, but no experience of, ICs. It is thus meant to be a basic introduction to ICs and their use.

Both linear and digital devices are covered, and a reasonable number of specific well-known devices are described — although not perhaps as many as one might hope or expect. Possibly this is due to the British-European background of the author. This certainly limits the usefulness of some of the practical circuits, like the audio oscillator using a device described as "the RS Components waveform generator"

There are a number of places in the book where I could not help raising a critical eyebrow. One is on page 16, where the body text refers to the diagram on the facing page, and describes the fabrication of a transistor in terms of three epitaxial growth processes! Happily the diagram itself and the caption at the bottom of page 16 describe a much more conventional double-diffused device.

Similarly on page 19 the text describes the fabrication of another unfamiliar element, an epitaxially grown resistor! Again the diagram and caption disagree with this, describing the much more conventional diffused resistor.

These and a couple of other items lead me to wonder whether two different people wrote the text and prepared the diagrams with their captions. If this was so, I hope for his sake that I. R. Sinclair wrote the captions and did the diagrams because, although these are a bit rough in places, they are at least factually correct.

In short, not in my view a very well produced book - particularly for people wanting an easy to follow and accurate introduction to ICs.

The review copy came from the Australian office of the publisher. (J.R.)

Prices subject to fluctuation. Correct at time of going to

ARRL Radio Amateur's Handbook 1977 \$11.95 Radio Communication Handbook, RSGB \$21.10 5th ed. Vol. 1 Vol. 2, just arrived World Radio TV Handbook 1977 edition \$11.95

#### New Books on CB

Best Book On CB - includes all 40 channels and 1977 regulations, choosing equipment, installatio Radio Operator's Guide - R. Brown and P Dorweiler CBer's How-To Book — L. G. Sands How To Select & Install CB Antennas \$6.95 \$6.95 Ways To Improve Your CB Radio \$5.60 Buckwalter
Pictorial Guide To CB Radio Installation & Repair — \$8.50 Practical CB Radio Servicing -\$9.75 Freeland

#### Radio & Electronic Advanced Applications For Pocket Calculators

Gilbert Amateur Radio Techniques — Hawker, RSGB\$7.40 Amateur Radio Theory Course — Ameco Antenna Handbook — ARRL \$7.80 Antenna Handbook — ARRL

Basic Electronics — Grob, new fourth ed

Beam Antenna Handbook — Orr

\$7.80 Building Hi-Fi Speaker Systems — Philips \$3.95 Cubical Quad Antennas — Orr Si Diodes Equivalents — De Muiderkring, Europ \$6.75 American, Japanese types. Electronic Calculator User's Handbook \$5.95 Electronic Guitar Amplifier Handbook \$10 FM & Repeaters For The Radio Amateur \$10.20 \$7.30 Ham & CB Antenna Dimension Charts - Noll \$2.95 Hi-Fi Loudspeakers And Enclosures — Revised edition. Cohen S. High Fidelity Audio Amplifier Circuits — A Texas Instrument Manual \$3.00 \$3.00 IC Op-Amp Cookbook — Jung Installing TV & FM Antennas — \$16.25 -Sands International Transistor Selector — Towers Introduction To Microcomputers, Vol. 1 \$6.95 Concepts — Adam Osborne
Introduction To Microcomputers — Vol. 2. Some \$11.80 Products, Adam Osborne \$1 Japanese Radio, Recorder Tape Player — Schen \$18.20 Servicing Manual \$9.90 Master Handbook Of Digital Logic Application \$10.95 Hunter Master Handbook Of 1001 Practical Electronic \$13.95 Master Tub Substitution Handbook Master Transistor/IC Substitution Handbook \$11.25 Microprocessor/Microprogramming Handbook — \$9.75 Brice Ward Modern Guide To Digital Logic -Memories & Interfaces, TAB \$9.75 Programming Microprocessors \$9.75 McMurran Radio Amateur's VHF Manual — ARRL Radio Handbook — new 20th edition Reference Data For Radio Engineers \$24.40 \$37.50 Single Sideband For The Radio Amateur ARRL \$5.65 Specialised Communications Techniques For T Radio Amateur — ARRL Source Book Of Electronic Organ Circuits — Doug \$6.20 \$6.95 Test Equipment For The Radio Amateur — Gibson, RSGB publication \$6. \$6.65 Electronic Musical Instrument Manual \$9.75 Transistor Equivalents - European, American and Japanese, 9000 types and 5000 substitutes. 8th & \$8.50 10th -ed. Transistor Substitution Handbook 15th ed. \$5.65 Understanding Amateur Radio - ARRL \$7.30 VHF Handbook For Radio Amateurs -\$8.50 Wireless World Circuit Designs - No. 2, Collected

MAIL ORDERS BY RETURN per parcel interstate PLEASE ADD 90c per parcel postage (Vic) \$1.70

TECHNICAL BOOK & MAGAZINE CO 295-299 Swanston St., MELBOURNE 3000 Ph. 663 3951

### printed circuit

- Phenolic & fibreglass-gold / tin plated
- Special manufacturers' packs of 10
- EA, R & H, ET, Philips, Mullard available · Specials to your drawing
- POSTAGE 'small 60c. large \$1 00

-				220011	W 00
77MX11	2.50	77SC11	3 60	77PS11	2.80
ET604	2 50	ET585T/R	3 00	ET635	0.80
ET713	00.00	ASCII	2.80	77UP11	6.50
77TS9	3 00	ET603	2.00	ET583	2 50
ET134	2.60	77AL8	2.50	77T10	2.50
77DVM9	2.80	ET065	2.20	ET071	2.20
ET067	2.20	ET063	2.50	ET083	2.20
ET072	2.50	ET085	2.00	ETO84	2.50
ET485	2.80	ET484	3.00	ET581	2.50
ET481M	2.50	ET5828	2.60	ET582A	3.00
				B. 1	
ET547	2.50	ET317	2.50	ET712	2.50
7707	2.50	7787	.2.80	77DLT7	8.00
77UP6	3.50	77TTY7	2.80	77QBF7	3.20
ET631/2	4.50	ET481PS	3.00	ET444M	2.00
ET444S	3.00	ET316	2.50	ET549A	2.50
			2.30		2.30
ET548	3.20	77TTY6	2.50	HMS276	5.00
77PTY7	2.80	77PTY6	2.50	ET133	2.60
77E05	3.50	77PRE5	2.50	77UP5	8.50
ET081	2.20	ET062	2.50	ET546	2 50
				77TTY4	
ET632U	4.00	ET632	7.00	//1114	2.50
77004	3 00	77UP2	3.00	ET132	2.50
ET632C	8.00	ET6328	6.50	ET632A	5.50
77UT2	3.00	77F1B	2.50	77F1A	3.20
					6.00
ET633FR	6 00	77UT2	3.00	ET633	
ET632P	2.50	ET632M	7.50	ET4828	2.80
ET482A	6.50	76CL12	2.50	ET630	2.20
		ET480PS	2 50	ET480	2.80
7684	2.60			E1460	2.20
ET631	7 00	ET630	2.20		
ET064	2 00	ET449	2.20	ET804	2.80
ET448A	2.20	ET448	2.80	ET711C	2.00
	2 20	ET068	2.00	ET061	2 00
ET711B			2.00	76MI9	3 50
ETO44	2.00	ET043			
ET711R	2 50	ET711D	6 00	E447	2 80
£7544	2 50	76PC9	4 40	76EX10	2 80
ET602	6 50	ET446	2 50	ET533A C	3 50
ET711A	7.50	ET543B	2.50	ET543A	2.50
ET445	2.50	ET241	2.80	ET780B	2 50
ET780A	3.00	ET541	2.50	ET444	2.50
7657	2.50	76M17	2.50	76LM5	2.50
76886	3 00	76SW4	2.00	76R4	2 50
76M5	2.50	76VG5	5.00	76E04	3 00
76VG5	5.00	76M5	2.50	76R4	2.50
ET708	2.50	ET740A	4.50	ET740B	3.50
					2.50
ET514	2.50	ET707A	2.50	ET7078	
ET706	2.50	ET130	2.50	76RT3	3.00
7672	2.50	76A03	2.50	7663	2.50
76E02	5.50	75SWILA/	3pr4.00	DRS-RC1	4.00
75PC12	2.50	EA76F1	2.80	ET534	2.50
ET514	2.50	ET129	2.50	ET28	2.50
ET439	3.00	ET420G	2.50	ET123B	2.50
ET123A	2.50	ET119	2.60	75F2	2.50
75L11	2.50	ET438	2.50	75V12	2.50
75F12	2.80	ET1124	2.50	ET122	3.00
					2.50
75CL9	2.50	75PC12	2.50	ET121	
ET120 "	2.50	FT118	2.50	ET117A-B	2.80
ET704	2.50	ET500	2.50	75T19	2.50
75R7	3.00	75CD7	2.50	75FM5	2.50
75TU10	3.50	75FE5	2.50	75TU8	5.00
				ET440	
75TU9	3.50	ET533A-8	2.50		4.50
ET400	2.50	75W3	2.50	ET532	2.50
ET529B	3.30	ETF" A	4.50	ET702	2.50
ET601R	2.60	ET6U P	2.50	EBSAT	3.00
			2.50	75A01	2.50
75EM6	2.50	75SD4			
ET414E	2.50	ET414D2	3.20	ET430	2.50
ET314	2.50	ET116	2.50	EBS	3.00
EBK1	3.00	ET528	2.50	ET312	3.00
7501	2.50	74MX120	3.50	74MX12C	2.60
74MX12B	3 20	74MX12A	2.60	ET701	2 50
ET527	2.50	ET428	2.80	ET313	2 50
ET530	2.50	ET427	2.50	ET426	2.50
74MX8	2.50	74EM9	2.50	74TU8	2.50
			5.00	E8107	5.00
ET429	2.50	EBX	3.00	50101	2.00

#### ALL SILICON 30/60w PA PORTABLE AMPLIFIER

6½"W x 3¼"H x 8½"D.12—16V, two inputs 5 & 100mV. 15 ohm output. No. 763D. Also 125, 250 500 ohm output No. 763A. All **570 each**. For 240V operation **\$33 extra**. Freight collect

36" x 36" x 2"H COILS and IF's All \$2 50 ea plus post 60c. RF CHOKES Plus post 80c.

381 AIR 2 5mh 50ma—Pye 70c. 381 IRON 10uh to 1.000uh 25ma 70c.

\$26.80

FILTERS 27 Line filter 2 \$14. 29 Line filter 10 / 20 amp \$37.50. Plus Post \$1.50

MAIL cheque or money order (add postage) direct to -

radio pty Itd 651 FOREST RD BEXLEY NSW 2207 587 3491

#### TRADING HOURS

MON-TUES-WED & FRI: 9am-5.30pm.
THURS: 9am-7pm. SAT: 9am-12 noon.
C.O.D.'s: Please add \$2.40 to posting
fee. NO ORDERS UNDER \$4.00
accepted. For replies please send S.A.E.
Post and Packing \$1.00 where not
included in price. PLEASE
PLEASE PRINT YOUR NAME AND
ADDRESS ON ALL ORDERS AND
CORRESPONDENCE.

164-166 REDFERN ST., REDFERN, P.O. BOX 156 REDFERN, N.S.W: 2016 TEL: 69-5922 or 69-6912

Valued friends and patrons of M.S. Components, we take great pride and pleasure in advising you that in future our Company will be known as SHERIDAN ELECTRONICS. For some time now our Directors have felt that our previous title had outlived its usefulness. COMPONENTS component capability in these particular spheres. Consequently we felt that a change of name, more closely allied to ELECTRONICS had civilisation would collapse overnight. TO STUDY ELECTRONICS IS TO STUDY THE FUTURE. SEE THE POSSIBILITIES OF ELECTRONICS AND YOU SEE THE FUTURE.

#### "KICK OFF" SPECIALS!!

#### SPEAKER CLOTH

We have seven types of speaker cloth available at the time of writing; from sombre through conservative to positively racey. We can't do them justice here with a photo, but we will send small samples to those already using our mail order service if requested, with complete prices too. All are ABOUT \$6.00 for TWO SQUARE METRES. At this price, they're WHAT EVERY WELL DRESSED SPEAKER SHOULD WEAR. POWER TRANSISTORS . . . 2N3054, at a never again price. These are the real McCoy, tested, marked, about \$1.50 anywhere else. But at SHERIDAN ELECTRONICS a lousy 45 cents each . . . 45c . . . 45c . . . POWER TRANSISTORS . . . 2N242, Ge PNP 2 amp 25W . . . In a heavy T03 package, tested, marked, yours for 95c.

SLIDER POTS. . . We have several values of sliders going real cheap to clear them out. We will go even cheaper again for volume buys. Check our stock list below. ALL SINGLES are only 15 cents, that's right 15c . . 15c . . . 15c each. Duals are ALL going for 20c. . . 20c . . . 20 cents each. It's

almost criminal . . . SINGLE DUAL 10K Standard 50K Standard 25K Super long 50K B curve 200K Standard 100K Shorties 500K Standard

500K Super long P & P 75c - 1 to 10 " \$1.20 10 to 25 Over 25 FREE

EGEN WIRE WOUND POTENTIOMETERS. very handy values, solid square construction PCB mounted with adjusted knob. A must for any one bread boarding projects. Values are 100ohm, 220ohm, 470ohm and 1Kohm. Average three watts. GOING FOR 50 CENTS EACH or 4 for \$1.75. Plus Post and Packing. CAPACITOR SPECIALS

			TYPE
10,000uf electro's	6vwdc	45c.	Pigtail
22uf elec bi-pole	40 vw	25c	"
100uf elec	160vw	20c.	CAN
2200uf elec	50 vw	75c.	PCB
.01uf poly	160vw	3c.	
.001uf disc	12Kvw	15c.	
CMITCH SPECIAL	0		

2 pole Rotary (AEROSTAT) 12 v at 10 amp 240 vac at 2 amp 20c. 2 pole 2 pos PCB MOUNT. . . cheap at 10c.

2 pole 4 pos rotary . . . . . . . . gift at 45c. 2 pole 2 pos rocker good . . . . . . at 15c. **OUR SPECIALS LIST** 

MULTIMETERS . . . 2 kohm/volt, 15 ranges, large 9 x 7cm meter, complete with leads, battery, instruction for a lousy \$11.00 + \$2.00 MAGNAVOX speakers, 10 x 6 cm, 8 ohms, 3 watts, a gift at \$1.50 P & P \$1.00 HEAT SINKS aluminium 12 x 6cm, 8 sets fins, c/w. Germanium PNP Transistor, Type 108 (ADZ11) To clear at \$1.50 each. P & P \$1.00

TO GET OUR NAME OFF TO A GOOD START WE HAVE COMPILED TWO PAGES OF NEW STOCK LINES AND SPECIALS; AND TO SELL THEM TO YOU AND ADVISE, WE HAVE PRACTISING AUDIO AND ELECTRONIC BUFFS, NOT PART NUMBER PARROTS. COME AND MEET MIKE, BARRY, ROD, AND GARY NEXT TIME YOU'RE PASSING BY

#### NEW CB ACCESSORIES STOCK

Good news . . . we've got some accessories you can't get anywhere else for love or money, bread or honey. We CAN't guarantee continuous stocks so get in for your

STANDARD HELICAL WHIPS, WITH BASE, by Lapstick,, . . . . . . cheap at \$22 proverbial dunny door, worth every cent at just . . . . . . . . . . \$37.00 or with heavy duty base . . . . . . \$42.00 (above sent by COMET FRT FWD) AMPHENOL CO-AX SWITCHES TYPE 83-2SW. Chrome finish,

good for 1Kw, low loss. A well known good brand unit for a good value price. EXTENSION SPEAKERS, and not little anaemic three by three . . . \$13.00. square things, but 18 x 10cm solidly encapsulated units with stand \$10

SWR METERS, HANSEN brand, uprights, 10 and 100 watt switch. Measures SWR . . . Only \$21 SWR METER, HANSEN brand, dual meters both 6 x 6cm. Solid home base unit, handles up to 100 watts....

Yours for \$34 CB CRYSTALS, CRYSTALS, Check these out for that handheld or six channel unit. Matched sets of the below for 455Kc I.F. sets . . .

27,065 27,185 27,235 27,880 27,155 27,165 27,195 27,225 27,245 27,265 27,900 27,910

All these crystals the same price, get them now while they last. Until cleared all these crystals are just \$8.50 a set . . . 40c P & P.

PL 259's AND CO-AX HARDWARE, BUT, we have, GOLD, GOLD, GOLD plated fittings too. No more corrosion worries. No more loss because of contact resistance. Now a better, more efficient skin effect. Gold is a CB's best friend. Look at these prices



PL259/G UHF HF PLUG \$2.50



M.359/G RIGHT ANGLE CONNECTOR MALE TO FEMALE \$4.00



PLA.1/G (ADAPTOR FOR PL259) 65c



MP.4/G **4 PIN MICROPHONE** PLUG \$2.50



PL.258/G DOUBLE FEMALE JOINER \$1.75



LC.3/G R.C.A. SOCKET \$1.20



PL.258/G/M DOUBLE MALE JOINER \$2.70



LC.2/G R.C.A. PLUG \$1.20

P.4/G

6.3mm METAL

\$2.35



M.358/G T' DOUBLE FEMALE & MALE CONNECTOR \$4.45

PHONE PLUG

P & P ea item 40c or 5 for \$1.00

## OUTH EAST OF WEST S. E Prices are

#### 7 TRANSISTOR 2 DIODE RADIO by BENDIX

Completely ready wired with volume control and switch. Large tuning dial



and complete with 31/2" 8 ohms 6 watt speaker. Battery container included. (Batteries not included) — Ready to go!! S.E.'s crazy price \$3.85 each or 2 for \$6.50. P&P \$1.50

#### **NEW STOCK LINES**

Scope soldering irons, temperature adjusting. TC60/240V AC/60 watts. Power on neon on handle, finned forward of handle, great, \$30.00. P & P \$2. BDV 96 high voltage ignition transistor, \$9.00. P & P 40c. CMOS 4050 Hex buffer, \$1.00. P & P 40c. Four drawer multi purpose cabinets. A must for storage of those tiny components, slip and stack them, \$2.50 each. P&P \$1.50. Array...Array...Good News, we now have LED Arrays, slim-line in 0.1" pitch. Super Bright, high efficiency in 3 colours. 5 in a Row Red...\$2.35 Green...\$2.20 Yellow ...\$2.40. 10 in a Row Red only \$4.40, Beautifully made by SIEMENS. with Super High Brightness for just 10mA per LED.

#### **BOXES...BOXES...BOXES**

We have a very good range of folded aluminium boxes. Each box in two halves. One half consisting of three sides and the two end pieces. When slipped together and screwed a very strong box is formed, yet a type of box that allows easy access if MURPHY gets into one of those experimental projects. Size and prices and order numbers are below

Order No.	Size CM	Price
	7x6x4cm	\$2.50
3 4	8x6x4cm	\$2.50
	8x5x4cm	\$2.60
6	10x5x4cm	\$2.70
7	10x6x6cm	\$2.80
8	11x6x4cm	\$2.80
9	12x6x6cm	\$2.90
10	12x10x7cm	\$3.40
12	11x11x9cm	\$5.00
1.4	1741E411am	\$5.70

P&P 1 to 4, \$0.75 P&P 6 to 9, \$1.00 P&P 10 to 14, \$1.25

#### MICROPHONES

Crystal mike, very neat, about the size of a small egg, high impedance. Complete with shielded lead. Great value \$2.50. Dynamic mike, same size as the above crystal mike but with a 50K impedance. A steal at only \$3.00. Please note: the above mikes come with a heavy duty mike stand with felt lined mike holder and an angle adjustment screw. Dynamic mike, a flat, square unit with stand up prop for use with 50K impedance cassette recorders, PA systems, and projects. We want to clear these quickly, so while they last, \$2.00

Now our super mike specials. Phillips Dynamic mikes, model LBB9002/10, designed for trop ical use. Impedance is 500 ohms, sensitivity 0.3mV/ubar (-70dB). Dimensions, 145 mm x 32 mm. Supplied with stand and shielded lead. These fine mikes are imported, made in Holland, the home of Philips. We don't want \$18, not even \$10, we ask only \$5.95 each.



FM/Electrot OHMI Directional Mike. That's right, a mike that performs as two mikes, FM or ELECTRET. This unit comes complete with wind cover, battery, adjustable frequency peg, mike cord and socket, also instructions for its use; all packed in foam. Check the prices for such a mike around town, \$29.50, no; \$18.50, no; \$15 not even fifteen. Almost a present at only \$13.85 each. Please add P&P \$1.00 for top 3 mikes and \$1.50 for Philips and FM.

#### "PLAYMEC" KEYBOARD **SWITCHES**

An indispensable necessary component in developing handy electronic calculators and microprocessors. Can also be adapted electronic games. Lthin, ultra compact.

Current Cap. 20 mA, 24 VDC. Contact resist 1 max. Insul. res.: 100 m MIN & 24 VDC. Chattering time 2 m SEC MIN. Size 60 mm x 80 mm. Complete with mounting bracket set at 160 deg. approx.



P&P \$1.00

#### **READY MADE MODULES**

We can't all be like the clock in the TOWER OF PIZA, with both the time and the inclination. If you lack one or the other, or both, then these modules are for you. All are other, or both, the well built on PCB,

well built on PCB, and factory tested. Maybe with the help of your junk box you could build one as cheaply, but not when you haven't the time to spite or scratch yourself, and the fifty cents you might save yourself couldn't justify your labour. All have in-structions. One watt amp with slider controls, uses IC amp. Dual slider controls, uses IC amp. Dual high impedance mike pre-amp, 12 voits drives it. Dual low impedance mike pre-amp, this one too. Dual guitar pre-amp, for you pickers out there. Stereo tape head pre-amp, for you audio buffs Stereo magnetic cartridge pre-amp, you got it. Sound operated with the cart owner transic. amp, you got it. Sound operated switch, with IC and power transistor. Light operated switch, for cutting of TV commercial sound. Variable time switch, from milli seconds to thirty minutes. SQ Decoder, IC used at 12 volts. All these ready made minor miracles are the same price and that's just a measly

"FLUKE" THE STATE OF

THE ART MULTIMETERS And it's no fluke that they are. Good design, attention to our needs, excellent workmanship,

and superb backup service makes the Fluke three and a half digit, liquid crystal, multi-

meter, the best available in this country today. This unit is not just accident proof, it's idiot proof. How many meters can you switch to resistance range then plug to the mains.

range then plug to the mains. How many run for two hundred hours on a 9 volt (gold) tranny battery. How many offer accessories so your VOM can read 600 amps/40KV/250 MHz or even temperatures to 15°C centigrade. Fluke does, say no more. With soft case, probes, battery, instruction manual. \$216.00 plus P & P \$3.00 (includes insurance).

insurance).



\$7.00 each.

#### TV GAMES

**GAME CHIP AY-3-8550** 

with two joy stick controls, this advanced unit comes complete with joy sticks — all games (6) and scoring etc are the same as game chip AY-3-8500 BUT the bats not only move up and down but forward and backward too. Complete with data sheet. Yours for a value packed \$24.00



**GAME CHIP AY-3-8500** 

6 selectable games. Tennis, soccer, squash, practise and rifle shoot. Auto score on screen 0 to 15. Selectable bat size, speed, angles, ball speed and sound. Complete with 7 pages of instructions to build game using easy to buy parts. BC108 etc. A gift at \$12.50.

P.C. BOARDS AVAILABLE IN LIMITED QUANTITY AT \$3.50 ea. for AY-3-8500 and AY-3-8550

#### MEMORIES ARE MADE OF THIS WE MUST HAVE THE **BEST PRICES IN TOWN**

1702a-128 x 8 Eprom. A gift at only \$9.00. 2101a 256 x 4 Static Ram. Just \$4.50. 2102n 1024 x 1 Static Ram. Should be a law against it at only \$1.50. Limited stocks, so get in now. No future stocks at these prices. Soon it will just be a memory.

#### RADAR DETECTOR UNITS

Why mess with inferior, back yard brands, when you can buy the very best cheaper, cheaper, cheaper. That's right, Snooper is the best unit in Australia at the present moment. Read the independent tests conducted by 'Where

A great unit at only \$109

The Super Snooper is available too for a reasonable \$185



CLOCKS-CLOCKS-CLOCKS

HI: SECOND, A SOLID STATE, LED READOUT, 12 HOUR mains clock. This requires a small transformer to be complete and running. The transformer is \$5.50. This unit comes with instructions for assembly and ways of using the clock. This solid state device is just \$11.50. Model MA10028. P&P \$1.00

H2: THIRD A SOLID STATE LED READOUT 24 M2: THIRD. A SOLID STATE, LED READOUT, 24 HOUR mains clock. This chip is ideal for Ham radio operators, military personnel, and pilots. Apart from the 24 hour instead of 12 hour display this unit is identical to the above model and requires the same transformer. It also has the alarm facilities of the above unit with fast and slow time set, and brightness controls. Just \$12.50. Model MA10020. P&P \$1.00.





H4: FIFTH, CLOCK CHIP, MM5316n (NS/416). To clear these we are letting them go really cheap, data supplied, just \$8.90 each. P&P 50c.



#### SCOOP PURCHASE OF DIGITAL **CLOCK MECHANISMS**

All new and unused . . . fully imported. Complete with time-setting control, denoting HOURS, MINUTES ? SECONDS. Clearly visible figures of 5/16\* ht. Also incorporated are two remote micro-switches for setting alarms, radios or television etc. With 240V 50Hz motor. Amazing value at \$10.25 each. P&P \$1.25



### it's CHRISTMAS!! " have a treat ... \*\*

FOR THE AMATEUR NOTE: The appropriate amateur license must be held to operate TX/RX.

ICOM handbag portables with matching accessories.

**D** ICOM

ICOM IC202/IC502

SUMMERTIME IS DX TIME for SSB on 2 or 6m IC202 144-144.4 2 XTRA XTAL positions for VXO IC502 52-53MHz.

MOBILE - The incomparable IC22 PLL

PORTABLE IC215



FM XTAL Operation 146-. 148MHz 3 watts. Vicom Price \$219.

Bat. or Ext. power.

#### ACCESSORIES

- \* Nicad battery pack BC20 \$57
  - Flexible helical antenna \$13
- \* Mobile bracket \$18
- Noise cancelling mic. VM-1 \$8.90



#### THINK HARD BEFORE YOU BUY

- \* No XTALS to buy
- \* No tiresome digital readout
- \* Instant channel select or repeater reverse
- VICOM Price \$279 Also available

IC211 (less ssb) IC245

\$489



#### ACCESSORIES

- Nicad battery pack BC20 \$57
- \* Mobile bracket \$18 VICOM Price SC202

VICOM Price IC502 \$219



ANTENNAS - For mobile, beach or country

- HF Mobile \* 80-10M ASAHI AS303A \* Helical whips mark 80, 40 or 20
  - Bases extra \$12.70 or will fit hustler or ASAHI bumper

VHF - Magnetic base Space 42S 1/4 wave with base Space 42D five eight with base \$ 26 VHF/6m YAGI 5 el. 55. 56 \$ 98

Antenna couplers by Daiwa. Will load short/long wire or coax feed. CL65 \$134

YAESU Monitor scope YO300 checks SSB quality all rigs \$389

Also Trio-Kenwood TS520S, TS820S, amateur band transceivers \$ 699 \$1099



VICOM VC2 SWR Meter 3.5-150MHz \$38

OSKER SWR200 Dual impedance measures to 1kW \$75



dynamic

Suits all CB rigs

with 600 ohm imp

NEW! VM1 Noise cancelling mic.



Professional quality VOM Model 150 \$5 \$59.00 Model TP5SN \$31.00

Model TP105 \$29.50

Transistor checker ZQM3 checks NPN, PNP, Diodes \$59
On air multitester and F/S meter by OSKER for CB, Amateur

#### MULTIMETERS

#### COMPRESSOR



NEW! Mic. compressor audio. Will suit all TX MC330

#### A WHOLE WORLD OF COMMUNICATIONS **PRODUCTS**

89 69 69

Trap Trap

10M

40.

N4JR

ANTENNAS

CB/AM/FM Automatic TRANSISTORS

2SC 1306 2SC 1307 Vertical 2SC 1018

TELESCOPIC ANT. - Toploaded CB/AM/FM Manual \$5.00 \$6.50 \$5.00

\$6.50



MORSE

KEYS



Coaxial switch - 2 positions. Rated 1Kw up to 500MHz. CS210

COAX SWITCH



Low pass filter - 2 types FD30 LS - 200 watts

\$35

MORSE KEYS - Hi-Mound HK702

\$ 35 \$ 19 HK706 EK103N Electronic Keyer \$159

FOR SWL Barlow Wadley RX with FM band. Originators of Wadley drift cancelling system





NEW! VM2 Power Mic. Desk type





FRG7 YAESU RX covers 0.5-30MHz

\$339

Listener 3 ANT

For short wave will all hardware \$49

Pre-Amplifier improves sensitivity of older receivers. Covers 2-30MHz \$39

139 AUBURN ROAD, AUBURN, Vic. 3123 Telephone: (03) 82.5398, (03) 813.2355 TLX 30566

Adelaide: 43.7981 Canberra: 82.3581 Perth: 446.3232 Brisbane: 384.4480 Gold Coast: 32.2644 DIRECTION:

Russell Kelly, VK3NT Peter Williams, VK31Z

# The Amateur Bands by Pierce Healy, VK2APQ



#### Amateur Radio is flourishing

The impression that amateur radio is flourishing was created partly by the very successful NSW South West Zone convention which the writer attended recently and also by the many personal and on-air contacts made during a subsequent tour of the south-east of the continent.

From the visit to the NSW South West Zone Convention at Griffith on October 1 and 2, 1977, and a subsequent trip through areas where amateur radio population is the highest in the country, it was possible to assess at first hand the direction in which amateur radio seems to be heading in Australia. It was pleasing to note that there appears to be a significant number of persons who have recently attained or are striving for amateur radio status.

Classes are being conducted by existing amateur clubs and new clubs are being formed to cater for an increasing number of persons whose appetite has been whetted through the introduction of CB radio. In fact, the view has been expressed that the cream of the CB operators, having experienced the bedlam and frustration of CB operation, will turn to amateur radio to satisfy their needs. The greatest critics of CB radio are appearing among those who have forsaken CB for amateur radio.

south West Zone Convention: The 25th such convention was conducted at Griffith, NSW, on 1st and 2nd October, 1977. It was an outstanding success thanks to members of the Griffith Radio Club assisted by Mrs Pam Cassidy as convention secretary.

Visitors from Sydney, Canberra, Goulburn, Young, South Coast area of NSW, Melbourne and parts of northern Victoria joined the South West Zone members in a weekend of field events and social activities.

The venue at the Griffith Ex-Servicemans Sports Ground and Pavilion was ideal for the field and social activities and allowed a very large range of commercial amateur equipment to be displayed. The total value was stated to be in excess of \$70,000. There was considerable trading activity for both components and latest model HF and VHF transceivers.

Bail Electronic Services, Sideband Electronic Sales, VICOM, and Dick Smith Electronics (Griffith branch) displayed various types of equipment.

The official anniversary dinner was held on the Saturday evening at the Yoogali Catholic Club where 150 guests were welcomed by Warwick Marshallsea, VK2ADZ, president of the Griffith Radio Club.

During the evening the toast to the Wireless Institute of Australia was proposed by Pierce Healy, VK2APQ, who, in doing so, recalled some of the outstanding achievements of Australian amateurs as far back as the early 1900s and the formation of the WIA in 1911, it being the oldest national amateur radio society in the world. He also urged support for the continued growth of amateur radio.

The response to the toast was made by Dr David

Wardlaw, VK3ADW, federal president of the WIA, and in doing so officially opened the convention.

Dr Wardlaw referred to the introduction of CB radio in Australia which has already created a growing interest in the amateur service and is a potential source of enthusiasts who will turn to amateur radio in order to increase their knowledge, plus their enjoyment which is available as qualified amateur radio operators.

He also gave a resume of the work undertaken by WIA federal executive in conjunction with the International Amateur Radio Union, in preparation for the World Administrative Radio Conference at Geneva in 1979, referring to some of the problems facing amateur radio through the attitude of some developing countries.

Officially opening the convention, David congratulated the organising committee and zone members on their activities and expressed his pleasure in attending and the opportunity to meet and discuss WIA affairs with them.

Other speakers were Tim Mills, VK2ZTM, president NSW Division WIA, who spoke on activities within the division and proposed the toast to the South West Zone. Harry Cuthbert, VK2AEC, responded to the toast and welcomed visitors to the convention, expressing thanks to the Griffith Radio Club for hosting the convention.

My visit to Griffith was the start of a most interesting tour with several meetings with fellow amateurs. At Griffith came the opportunity to meet many old friends and become acquainted with several who recently gained an amateur licence.

It was also an opportunity to observe the use of VHF FM repeaters in country areas by amateurs isolated from each other by direct VHF path or by a wholly reliable HF path, and as a means of operating mobile in otherwise impossible locations.

These aspects were discussed at length with an old ex-Sydney friend Sid Ward, VK2SW. Sid has been residing at Wagga for some years and played an active role in the establishment of the Wagga Radio Club and WICEN in that area.

In fact, because of Sid's insistence that I try out an ICOM 215 two metre FM transceiver while in Wagga, I was able to assess the value of the channel 3 repeater. From a motel room many enjoyable contacts were made via the repeater. Canberra, Snowy Mountains area, and mobiles passing within range were among the contacts made.

Time was spent with Sid reminiscing about the changes in the "state of the art". Especially from the days of home built equipment, using car batteries and genemotors, and my mountain top exploits of the early 1950s, to the size and efficien-

cy of modern VHF equipment, coupled with unattended mountain top repeaters. Sensing its possible use during the remainder of my journey, it is probably understandable why I departed for Albury with the ICM 215 over my shoulder and an appropriately depleted bank balance. This move added a great deal of zest to my travels, culminating in another mountain top first.

From Albury, contacts were made through the Wodonga channel 8 repeater on Mount Big Ben about 40 kilometres south. In addition to the Albury Wodonga area, contacts were made with Wangaratta, Benalla, Tumbarumbi, Wagga and mobiles travelling through the area.

From a hill about a kilometre east of Albury railway station it was found possible to work through the Wagga channel 3 repeater on Mount Flackeney about 110 kilometres away and a number of contacts were made. The hand-held ICOM 215, with 3 watts output to a "Rubber Duck" 170 millimetre helical antenna, was exceeding expectations.

While in Albury an evening was spent with another old friend Don Haberecht, VK2RS and Murray Jardine, VK2BUJ. Murray's invitation to attend the Albury Radio Club meeting the following evening was readily accepted. Murray has a group of enthusiasts studying for the novice licence or to upgrade to the full licence status. The club meets every second Wednesday evening at 7.30 pm in the State Emergency Services rooms on the corner of Dean and Thrugoona Streets, Albury.

Further information may be obtained from Murray on telephone AH [060] 21 5460.

The next part of the journey was to Melbourne, where from a room on the third floor of a hotel in Little Collins Street, no trouble was experienced in working through the Melbourne channel 2 repeater on Mount Dandenong. Many interesting contacts were made which were instrumental in meeting a number of amateurs actively engaged in experimental projects or WIA activities.

Among them were Ron Harrison, VK3AHJ who specialises in amateur TV. An evening spent with Ron was most interesting. A highlight was a two-way ATV contact with Peter Cossins, VK3BFG, 35 kilometres away over a rather poor path. The pictures were first class.

Ron has a well set up station and each Sunday morning broadcasts an ATV segment during the WIA Victorian Division news broadcast. A conservative estimate is that there are 50 active TV amateurs spread around Melbourne. The group would like to hear from others interested in ATV. Contact Kevin Callaghan, VK3ZVJ, 34 Gordon Grove, Preston, Vic. 3072.

There is also a net each Sunday morning on 7085kHz about 10.45 am conducted by Ron Harrison, VK3AHJ. TV amateurs from all states are invited to join the net.

A contact with Graeme Scott, VK3ZR, WIA federal education officer, provided the opportunity to enquire about the classes and other activities in the education field.

Graeme proposes to conduct an intensive Morse code training class for limited licensees from the 23rd to 27th January, 1978. The classes will be held at the Box Hill Technical College from 6.00 pm to 8.00 pm each night. Contact Graeme at 11 Balmoral Crescent, Surrey Hills, Vic. 3127.

This course will be in preparation for the February 1978 AOCP examination.

Graeme also expects that YRS education officers may obtain the ARRL official novice instructor's guide, which includes Morse code cassettes and colour slides, from WIA Mag Pubs, 2/517 Toorak Road, Toorak, Vic. 3142.

A short but very interesting meeting and visit to Roy Hartkopf, VK3AOH enabled me to learn first hand the progress that the YRS is making in Victoria. It also was the opportunity to see and operate the keyboard Morse Code generator and first-in-first-out register, together with a video display unit. This unit, when fed from a normal Morse key, converts the code symbols to letters on the display unit. It was designed and constructed by

As editor of the YRS publication Zero-Beat, Roy passes on a wealth of knowledge to YRS members.

Radio clubs and other organisations, as well as individual amateur operators, are cordially invited to submit news and notes of their activities for inclusion in these columns. Photographs will be published when of sufficient general interest, and where space permits. All material should be sent to Pierce Healy at 69 Taylor Street, Bankstown 2200.

#### **AMATEUR BANDS**

He is also the author of several books, a well known one being, "Maths For Those Who Hate It" — which received praiseworthy reviews. His latest is, "Logic and Logic Circuits" produced for YRS use.

Next came an invitation from Les Jenkins, VK3ZBJ ex VK2ZBJ, to visit him and attend the Frankston & Mornington Peninsula Amateur Radio Club meeting. Les is well known in UHF-VHF circles and in his laboratory and workshop has designed and produced a wide range of amateur and commercial electronic equipment as well as type testing local and overseas manufactured equipment. From his amateur station ATV contact was again made with Peter Cossins, VK3BFG.

A QSL card on the wall of Les' home station caught the eye. It was for a yet unpublished or claimed world record for 432MHz. The contact was made on the 2nd February, 1975, between Les at Frankston, Victoria, and Wally Green, VK6WG in Albany, Western Australia. The distance was in excess of 1950 kilometres.

Signals were readability five and strength nine both ways. VK3ZBJ used SSB and VK6WG used CW.

There were over 50 present at the FAMPARC meeting, which featured a lecture on the design and construction of trap dipole antennas. A pleasant evening was spent meeting members and discussing matters of common interest. The club has decided to sponsor an Australian Mobileers Club for amateurs who operate from motor vehicles while touring. Further details are expected to come to hand shortly.

A quick call was made from Frankston across Port Phillip Bay into the Geelong channel 8 repeater using the ICOM 215 hand-held, and two contacts were made.

The WIA Victorian Division Station, VK3AOM at the Melbourne Science Museum, Swanson Street, was visited during the official news broadcast from VK3BWI at 10.30 am on Sunday morning. This well equipped station is on view to the general public. Amateur operators put the station on air during visiting hours.

The final personal contact in Melbourne was with John Kolm, VK3YJK, YRS examiner in Victoria. John gave me a copy of the trial novice examination papers results of which were reported in last month's notes. He also explained the programming of the computer used to analyse various facets of the examination results. Further trial exams are planned for 1978.

On returning to Albury I was invited by Murray Jardine, VK2BUJ, to go with him that evening to the Wodonga Channel 8 repeater site on Mount Big Ben. At an elevation of 950 metres the repeater is housed in a temperature controlled cabinet (inside a brick building) at around 18 degrees C. It was around 4 degrees C on the mountain top.

Six beautifully made coaxial cavities are used in the repeater which is an all solid state device. The whole installation was financed and built by a group of amateurs in Albury-Wodonga and surrounding areas. Running and maintenance costs



During the week October 24 to 28, 1977 the VK2 Division of the WIA staged an amateur radio display in the OTC building in Sydney's Martin Plaza. The display included historic equipment, RTTY, ATV, equipment built by YRS students, and a working display of modern HF and VHF amateur equipment. The photograph shows this equipment being used as a WICEN station at the Sydney end of a National Disaster Organisation exercise. The exercise was a supposed earthquake in Adelaide and WICEN provided links between Adelaide and Canberra, Sydney, Melbourne, Brisbane and Perth. Shown (left) is Ray Gill, VK2BRF, and Mike Richter, VK2BMM. Ray and Mike, with Allan Nutley, VK2BNA, and Tim Mills, VK2ZTM, were among those who organised the display. It is estimated that at least 1500 people visited the exhibition, while many more viewed the window display from Martin Plaza.

are in general met by donations from those who use the installation.

Naturally the visit to the mountain top would not be complete without trying out the ICOM 215. The Wagga channel 3 repeater could be heard and my call VK2APQ/3 brought an immediate reply from Harry Cuthbert, VK2ACE at Coolamon with Sid Ward, VK2SW in Wagga joining the inquiry as to my location. This was the first contact either had had with a low power hand-held unit from Mount Big Ben. The distance to the Wagga repeater was around 150 kilometres.

I then told Sid that I would try the Canberra channel 7 repeater on Mount Ginini. My call was answered by Sid at Wagga and Ted Pearce, VK1AOP mobile in Narrabundah, Canberra. The distance from Mount Big Ben to Mount Ginini is in the vicinity of 200 kilometres and around a further 180 kilometres to Sid's home station in Wagga. Then just to complete the contracts, Sid suggested that we use channel 8 repeater. So, standing under

the repeater antenna on Mount Big Ben, at a distance of about 10 metres, contact was again established with Sid at Wagga.

Thus within about 10 minutes we had, "with the help of some friends" (the amateurs who built and installed the repeaters), made contact through three widely separated repeaters and, probably, some DX firsts for a low power hand-held unit over some of the most mountainous area in the country. It certainly demonstrated the value of VHF repeaters to amateurs isolated as far as direct VHF is concerned, in sparsely populated areas.

Yes, amateur radio is flourishing; and my sincere appreciation is extended to all those who answered my calls through the repeaters and simplex channel 40, also to the hospitality of those met personally. Hope to meet up with you again further down the log.

#### IARU NEWS

Two papers by Tom Clarkson, ZL2AZ, which he presented to members of the NZART have been received and read with considerable interest. These papers deal with matters relating to 50 years of international control of amateur radio and WARC 79.

Tom is a past president of the NZART, at present their Overseas Liaison Officer and is an IARU Region 3 Association director. During his professional career he was Chairman Organising Committee, IXth Plenary Assembly, ITU International Radio Consultative Committee, Los Angeles, 1959, so he speaks with an intimate background knowledge of the operations of the

Unfortunately space does not permit a full reprint nor would a resume do justice. However, here is an extract worth consideration by all amateurs.

"Lessons to be drawn from past conferences.

"Here are some salient points on reviewing 50

years of international control of amateur radio:

"Amateur radio has maintained a position of im-

#### **COURSES IN ELECTRONICS**

POST TRADE TRAINING IN ADVANCED AUDIO, COLOUR T.V. SERVICING, REMOTE CONTROL RECEIVERS, BROADCASTING SOUND & VISION, INDUSTRIAL ELECTRONIC, C.B. RADIO, MOTION PICTURE, COMPUTER ELECTRONICS ETC.

#### FULL & PART-TIME DAY & EVENING

ALSO CORRESPONDENCE TUITION. BLOCK RELEASE COLOUR TRAINING FOR COUNTRY STUDENTS. CONTACT TELECOM DIVISION R.M.I.T. 341 2358, 80-92 VICTORIA STREET, CARLTON.



### YAESU . . . a symbol of quality in the ranks of amateur radio

Distributed throughout Australia by Bail Electronic Services accredited Yaesu agents and factory representatives since 1963.

Novice, limited and full licensee equipment including - HF band transceivers from the FT-7 low power set through FT-200, FT-101E, FT-301, FT-301S to the deluxe FT-301D with Dig. Readout. FRG-7 Wadley loop receiver, FR-101/FL-101 TX/RX

combination, FL-2100B linear, etc. VHF equipment includes the FT-221R all mode 2m transceiver, FT-223 FM transceiver, FT-227 Dig. Readout synthesised 2m FM transceiver. FTV-650 B and 250B transverters, plus accessories and test equipment.

JAS 7778-24

Yaesu and Bail — for quality equipment and friendly, reliable service long after your purchase.

# BAIL

FRED BAIL VK3YS

**ELECTRONIC** SERVICES

JIM BAIL **VK3ABA** 

60 Shannon St., Box Hill North, Vic. 3129. Ph. (03) 89 2213.

ı	Radio a	mateur equipment from B.E.S. also sold by	
	W.A.	Radio Communication Services, H. R. PRIDE, 26 Lockhart St., Como, 6152	Ph. 450 4379
1		WILLIS TRADING CO., 429 Murray Street. Perth 6000	Ph. 21 7609
1	S.A.	FARMERS RADIO PTY. LTD., 20 Stanley St., Plympton 5038	Ph. 293 2155
ı	TAS.	G. T. ELECTRONICS, 131 Westbury Rd., South Launceston 7200	Ph. 44 4773
ı		PRINS RADIO, 123 Argyle Street, Hobart 7000	Ph. 34 6912
	N.S.W.	Aviation Tooling, STEPHEN KUHL, 104 Robey St., Mascot 2020	Ph. 667 1650
ı			AH 371 5445
3		Amateur & Novice Comm. Supplies, W. E. BRODIE, 23 Dalray Street.	
-		Seven Hills 2147	Ph. 624 2691
ı		DIGITRONICS, 186 Parry St., Newcastle West 2302	Ph. 69 2040
ı	QLD.	H. C. BARLOW, 92 Charles St., Aitkenvale, Townsville 4814	Ph. 798179
ı		MITCHELL RADIO CO., 59 Albion Rd., Albion 4010	Ph. 57 6830
ı	A.C.T.	QUICKTRONIC, Jim Bland, Shop 11, Altree Crt., Phillip 2606	Ph. 81 2824
ш			82 2864

Sets sold by Bails are checked before despatch, 90 day warranty, spare parts availability, after sales service.

### Sanwa precision circuit testers-Big on features. Bigger on selection.


















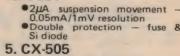

4. N-501

1. BX-505

mined 2. U-60D

3. SP-10D

• 16.5μA movement – varistor protected & 50kΩ/V for DC
• Capacitor tester – push-button operation with solid-state oscil-

Fast-response, 24μA movement
 fuse & diode protected with high resolution factor (0.4μΑ/

scale division)

Revised scale marking — intermediate readings readily deter-

•44µA movement — quality performance, diode protected
•Stable ACV measurement — solid-state rectifier & enlarged

Easy operation — multiposition rotary selector switch & well-lighted scale
 Stable ACV measurement —

frequency coverage

durable diode rectifier

lator built in 6. PDM-500 (Insulation Tester)

 Battery operated — 3 small-size 1.5V batteries built in Push-button operation — pointer calibration & insulation test

7. CAM-201S (Clamp Meter) • Measuring ranges 15-60-300A — 500V — 50kΩ

Meter protection diode provided

ADELAIDE 356-7333 BRISBANE 52-7255 HOBART 23-1841 MELBOURNE 699-4999 PERTH 65-7000 SYDNEY 648-1711 WELLINGTON, N.Z. 698-272

fuse &

#### ZOOM FOCUSING MICROSCOPES 900X

\$23.95 Battery Mirror illuminated Zoom 1200X Similar To Above \$35.00

A. \$1.70, B. \$2.25, C. \$2.40, D. \$2.65

#### P.M.G. TYPE TELEPHONES

Standard desk type with magneto bell calling device. Range 30 miles. Uses standard batteries at each phone. Any number can be connected together on single line.

\$35.00 (2 TELEPHONE SETS)

\$ 2 Cartage to Rail. Freight payable at nearest attended Railway Station

#### FOUR CHANNEL VHF TRANSCEIVER

125 to 140 M/hz. 28 volt DC operated AM single crystal locks both TX and RX on same channel complete with generator.

\$33.00

#### **EXABC** MAGNETIC RECORDING TAPES 1/4"

PROFESSIONAL QUALITY

5" x 600" 7" x 1200"		\$1.50 \$2.75
P&P A. \$1 D. \$2.25	.10, B. \$2.00, C. \$	2.25,

#### MINI-TOGGLE SWITCHES MIYAMA

75c SPST SPDT 3A 95c DPDT 3A \$1.25 SPDT Centre-Off 10A \$1.25 DPDT Centre-Off 10A \$1.65 Please add postage

#### No. 62 TRANSCEIVER

With headphones, accessories etc.

\$60

#### TELEPHONE WIRE

1 mile twin (2 miles) genuine ex-Army Don 8 perfect condition \$35 per drum \$2.00 cartage to rail freight payable at destination.

#### **RCA 77DX MICROPHONES**

PROFESSIONAL QUALITY \$75 P & P A. \$1.80 B. \$3.50 C. \$4.55 D. \$4.55

MORSE KEY MORSE KEY BUZZERS \$1.75 \$4.25 Post 60c

#### KAISE MULTIMETERS

A compact and handy tester for workshop or lab where quick circuit checks are required

DC Volts 2.5 to 1.000V (20.000 OHMS per volt) AC Volts 10 to 1.000V (10.000 OHMS per volt) DC Current 50 UA 25 MA 250 MA Resistance 40 K OHM. 4 MEG OHM Decibels minus 20 DB plus 62 DB complete with instructions only \$23.95 Ea. P.O. \$1.05 Multimeter similar to above 30,000 OHMS per volt \$29.50 P.P. \$1.05.

Only \$17.25 ea Post \$1.05

#### SIEMENS Typing Perforator

240 Volt Type with Keyboard \$57.50

#### 4 DIGIT RELAY COUNTERS

50 volt DC, suit slot car Lap counters, #1.25 each P& P 60c

#### NIBBLING TOOL

Cuts sheet metal like a punch and die, trims, notches and cuts to any size or shape over 7: 16inch.

ONLY \$12.50

#### NIFE CELLS

1.2 Volt, fully charged, 4in x 3in x 1in 4 \$1.50 each P & P 80c

5" CRO TUBE 5 BPI \$5.50 each Post A \$1 40. B \$2 25. C. \$2 70. D \$3 45

#### HANDY SIGNAL INJECTOR

Produces an Audio Signal in rich harmonics. Ideal for Sig Tracing in A.F., I.F., and R.F. circuits. Powered by 4 Penlight Batteries with On Off Switch and indicator lamp. Size 11/2" Diam 5" Long Only

\$6.95 Post \$1 10

30 x 30

LENGTH 12½", HEIGHT

WEIGHT 13/4 lb.

\$27.50

SPY TELESCOPES

8 x 17 mag size of a rifle cartridge extends to 8" Only \$5.95 each post 60c

BINOCULARS

new. Complete with case

\$32.50

\$43.95 \$44.95

\$46.00

8 x 30 7 x 50 10 x 50

12 x 50 20 x 50

PRISMATIC Coated Lenses. Brand

SMALL CLIP-ON

**POCKET TELESCOPE** 

15X \$5.20 Post 60c

RECEIVER No. 210

24 volt Power supply to suit above \$15 Or complete station with Headphones. Mic. Morse Key, Antenna \$110.

SOLENOIDS

Plunger Type 24V 300MA. Suit electric camera control, miniature trains, radio. etc.

\$2.50 P & P 20c

200 MA 24 volt, Vein push movement. \$2.50 P & P 20c.

MAGSLIP

RECEIVERS 2" MK2 \$5.50

TRANSMITTER 3" MK2 \$15.00

Post Packing A. \$1.75 B. \$2.75 C. \$2.75

3000 TYPE RELAYS AM G 2000hms — 1'5000hm Coils \$2.50 each P & P 60c

P.M.G. TYPE KEY SWITCHES. 75c P& P 20c

MOTORS

SELSYN

2-16 M/cs \$65. Transmitter No. 11 suits 210 \$35.

ABC

\$2.75

60x60 Length: 22in Height: 18in

\$59.50

Weight: 2kg

#### POSTAGE KEY:

A: NSW B: Vic, Qld, SA C: NT, Tas D: WA

VALVES		6BM8	\$1.80
BRANDNE	W	6GV8	\$1.50
65N7GT	95C	CV850	\$1.50
5U4G	95c	1H6G	75c
EF50	75c	832	\$5.00
5Y3	\$2.25	6X4	\$1.80
2 x 2	75c	VR65	75c
	P & F	40c	

#### ARTILLERY DIAL SIGHTS MK2

Can also be adapted as a Dumpy Level or as base for a telescope has full 360° 51/2" diam. gunmetal rotating circle. Adjustable elevation and depression. Has top grade 34" diam. object lens. Ft.10" with cross hairs, eyepiece. 4" right angle prism.—height 10"—weight 3½kgs. With leather carrying case. Original cost \$300. Our Special only \$27.50. P&P.A. 1.95. B. \$4.25. C. \$5.90.

A. \$1.95, B. \$4.25, C. \$5.90

**ZOOM SPOTTING** 

SCOPES

High grade coated lenses.

Ideal for pistol and rifle

ranges or general viewing. Zooms in from very low to high powers. Complete with

POST: A. \$1.70, B. \$2.25.

C. \$2.40, D. \$2.65.

**TELESCOPES** 

25 x 30 \$7.95

P&PA. \$1.70, B. \$2.25

C. \$2.40 D. \$2.65

CONDENSER LENS

" Diam 41/2" F.L 75c 21/2" Diam 2"

\$1.50 each Or \$2.50 per pair P & P 40c

IMPELLER PUMPS

New gunmetal body, Stainless Steel Shaft Neoprene Impeller Up to 15th Lift, suitable for almost any type of liquid. Self prining, Ideal boat bilge

pump, sullage drains, etc. Approx size

36" \$25.95 1/2" \$34.95 34" \$39.95

P& PA \$1 90 B \$2 75 C \$3 20. D

**MEGGER Battery Operated** 

No cranking—in vinyl case. Ranges: Meg Ohm 0-1000 Megs. Centre 20 meg. Rated

voltage 500 volts. Low ohm 0-1000 ohm 0H 1 range 0-1 meg ohm on 1k range. AC voltage 0-250 volts. **\*85.00** 

Post A.\$1.60. B.\$2.50. C.\$2.75 D.\$2.75

Whip Antennas

\$3 95

### \$35

Weight: 2kgs

AN5736-1 Air Operated Dimensions: Length 9in:

Directional Gyros. AN5735-1 Air Operated.

Dimensions: 6inx5inx5in.

Slip and Turn Indicators Electric. Type Mk. 12 24Vdc

Dimensions: Length 61/2in Diam: 31/4in.

Weight: 1kg. \$17.50.

P&P. A \$1.60. B \$2.50. C \$2.75. D \$2.75

AIRCRAFT INSTRUMENTS

#### **TRANSCEIVERS**

No C42 set. 36 to 60 MHz with 24V power supply, headphone, mic, leads etc \$65.00

No C45 set 23 to 38 MHz with headphones, mic. 24V power supply etc. \$95.00

\$1.00 cartage to rail, freight payable at

#### **EX-ARMY TWO-WAY FM RADIOS**



SUPERHET PRC9 AND 9A 27 to 39 M/HZ PRC10 AND 10A 38 to 55 M/HZ WITH HANDSET ANTENNA \$25 EA

Battery \$3.50 extra. Harness \$4.50 extra \$2 Cartage to Rail. Freight payable at nearest attended Railway Station

#### 16MM SOUND PROJECTORS IN GOOD WORKING ORDER

240 volts operated Complete with Speaker and Amplifier

> CINEVOX \$150.00 BELL & HOWELL \$250.00 SIEMENS \$375.00

\$1 Cartage to Rail. Freight payable at nearest attended Railway Station

#### CB RADIOS

PMG Approved. Famous Pony Brand on 27

7 transister model \$55 per set of two (hand

held)
11 transistor model 1watt (hand held) \$72

ea. 5 watt 6 channel **\$99 ea.** Post A. \$1.65. B. \$2. D.\$3.20 .75 C.\$3.20

#### "KAISE"

Trans-Match Ham Tester SWR, RF Power, Modulation Percentage, Relative Field Strength. \$45.00 P&P A\$1.65, B\$2.75, C\$3.20, D\$3.20

#### "KAISE"

SK-100 Multimeter 100,000 ohms per volt, 12 Amps. AC or DC \$52. P&P A\$1.65, B\$2.75, C\$3.20, D\$3.20

#### Post \$1.10

8ft in 6 tapered sections, copper platted steel no base \$9.50.

#### **200M FOCUSING MICROSCOPES**

Battery & Mirror Illumi 900X Magnification \$23.95 1200X Magnification \$35.00

P & P A\$1.70; B\$2.25; C\$2.40; D\$2.65

#### MAGNESIUM DRY CELL BATTERIES

Suits PRC 25 and dozens of coults long life only \$1.50 ea. of other uses. 15 P&PA. \$1.65 B. \$2.75 C. \$3.20 D. \$3

### 70 OXFORD STREET, SYDNEY 2010

SORRY NO COD

portance, but not sufficiently understood.

"It has needed a struggle to obtain reasonable spectrum provision.

"Supporters of the amateur service have relied heavily on the leadership of the United States. Only the United States has a continuous record of speaking out boldly in this direction, and using powerful influence consistently.

"Amateurs in America have better privileges than elsewhere. Up till Atlantic City 1947 decisions very largely followed the line taken by the leading nations.

"Now the leaders in technique do not always get support from other user nations.

"The Space Conference 1971 showed that world opinion, demonstrated by the majority of delegates there, had no great interest in the promotion of the amateur service. The failure of the Atlantic City conference in regard to adopting an allocation table shows that not enough was done to meet the special interests of the less developed users of radio services.

"Services like broadcasting are keenly appreciated in new and developing countries, the merits of other services may not be obvious.

"Here are two questions, worth regarding as significant in the electronic age:

"Why has the amateur service had to struggle so hard and so long to ensure the right to operate? Why cannot amateur radio rely upon having unanimous support of its welfare?

"The first one. It is because the policy makers in ITU circles have not been ready enough to see the national advantages for their own countries in having a healthy amateur movement.

"Secondly. Because new and developing nations have not been sufficiently impressed by what they see of amateur radio, to regard it as in their own national interest to promote it worldwide and in their countries."

Even the above extract does not present the full impact potential the paper has. Maybe the NZART and WIA or even the Region 3 Association will make copies available to amateurs for their enlightenment as to why WARC 79 is of such importance to the amateur service.

#### WIRELESS INSTITUTE NEWS

In 1978 the Queensland Division of the WIA, through its association with the Department of Technical and Further Education, and through its member clubs throughout Queensland, will be providing a record number of courses and classes for the amateur radio licence exams.

Throughout Queensland and in Brisbane the radio clubs will operate their own timetable and choice of courses. Direct queries to the WIA, Box 638, GPO, Brisbane 4001, (07) 224 6844.

Classes directly conducted by the WIA in Brisbane will be timed to finish for the appropriate examinations held by the Department of Post and Telegraph. These classes will consist of a crash novice, a normal novice, full AOCP theory and an eight-week duration Morse Code course. These classes will be conducted at McDowall (Chermside), South Brisbane Tech and Salisbury.

#### AMSAT NEWS

During Sunday, the 5th June, 1977, AMSAT-OSCAR 7 continuously transmitted a Jubilee message in Morse Code over the codestore message storage system. The text of the message read, "AMSAT sends greetings to the United Kingdom on the occasion of the Queen's Jubilee." This message, intended as a tribute from the amateur radio fraternity, was repeated more than 1000 times as the satellite passed over every country in the world and was received by thousands of the world's radio amateurs.

The text of a letter received by AMSAT-UK from Buckingham Palace read:


"Thank you for your letter of 14th July which was shown to the Queen.

"Her Majesty learned with interest of the Jubilee message transmitted by the amateur radio satellite, OSCAR 7, and greatly appreciated the greetings to the United Kingdom sent by AMSAT to mark her Silver Jubilee."

Also from the September 1977 issue of AMSAT Newsletter comes news of a planned amateur
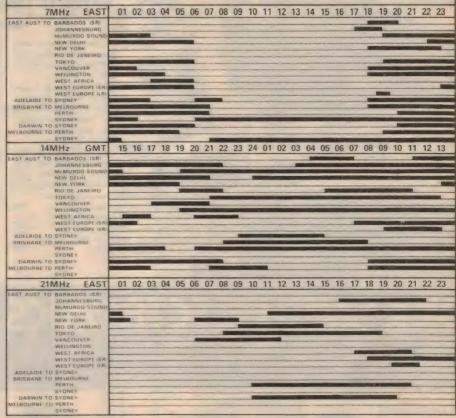
#### IONOSPHERIC PREDICTIONS FOR DECEMBER

Reproduced below are radio propagation graphs based on information supplied by the Ionospheric Prediction Service Division of the Department of Science. The graphs are based on the limits set by the MUF (Maximum Usable Frequency) and the ALF (Absorption Limiting Frequency). Black bands indicate periods when circuit is open.



satellite network by the USSR. Summary of the information is

Date of activation: 1977-1978.

Number of satellites: 3-4.

Orbital information: Inclination, 82 deg. Altitude 950km (circular orbit). Period, 102 minutes

Uplink characteristics: 145.8-145.9MHz (100kHz bandwidth) quarter wave receiving antenna, circularly polarised. User uplink power, 10-15 watts to 10-12dB antenna. Transponder receiver noise temperature, 3000 deg. K.

Downlink characteristics: 29.3-29.4MHz (100kHz bandwidth) half-wave transmitting antenna, circularly polarised transponder power, 1.5 watt peak to 0dB gain antenna.

Maximum ground communication range: 6000km.

#### RADIO CLUB NEWS

CENTRAL COAST AMATEUR RADIO CLUB: All amateur radio operators, their family, friends, and all interested in amateur radio are invited to attend the club's 21st annual field day on Sunday, 19th February, 1978, at the Showground, Showground Road, Gosford.

A full day's program of events has been arranged. Details in next month's notes.

MID SOUTH COAST AMATEUR RADIO CLUB: The annual meeting of the club has been tentatively set for the second Saturday of January 1978.

The weekly Lyrebird net is held each Wednesday through the club repeater VK2RMU at 2030 hours EST. The establishment of the repeater at Milton-Ulladulla (Ch. 2) has opened up two metre communications between Kiama and Narooma in a most satisfactory manner. It is one of the few repeaters in Australia using high power (100 watts ERP) and a receiver sensitivity of 0.3uV while transmitting and receiving on the same antenna. Additionally, one of the few repeaters with 100 per cent standby equipment.

Full details of the repeater are given in "The Lyrebird" the newsletter of the MSARC which also contains 12 pages of news of club members' activities and interesting technical articles.

President Frank Hill, VK2HQ, PO Box 113 Milton, NSW 2538, or secretary Doug Allen, VK2YDA, 1 Geoffrey Street, Ulladulla, NSW 2539, will be pleased to supply details of activities.

UNIVERSITY OF NSW AMATEUR RADIO CLUB: This club is to conduct a six weeks vacation course for prospective amateurs during the December-January holiday period. Classes will be held each Tuesday, Thursday, and Friday from 6pm to 9pm and each Saturday from 2pm to 9pm. The venue is the WIC, 14 Atchison St, Crows Nest.

Arrangements are being made with the P & T Department to conduct a special novice certificate exam at the completion of the course. For further information contact Sam Voron, VK2BVS, on (02) 407 1066.

#### SO YOU WANT TO BE A RADIO AMATEUR?

To achieve this aim, why not undertake one of the courses conducted by the Wireless Institute of Australia? Established in 1910 to further the interests of Amateur Radio, the Institute is well qualified to assit you to your goal.

assit you to your goal.

Personal Classes for 1978 will commence on Tuesday. February 7. 1978 at Crows Nest. Applications, which are accepted in order of priority, are now being received. Correspondence Courses may be commenced AT ANY TIME.

For further information, write to:

#### THE COURSE SUPERVISOR, W.I.A.

14 ATCHISON STREET, CROWS NEST, N.S.W. 2065.

### SICK OF CB? GO NO

**Novice Power Supply** 

NOVICE TRANSVERTER KIT

Use your old CB rig to good advantage! Transvert it to 80M with this kit - easy to build, legal power output. Needs 0.3 — 3W grive. Inovice section of band, too! \$80 750 Cat K-3134

30W-80M AMPLIFIER



We have three ways to help you!

**\$7.90** 1: Morse tapes - easy graduated steps, ideal for beginner or expert. Cat D-7106

2: ARRL book 'Learn Radiotelegraph code' As with all ARRL books really first class, \$2.50

well presented. Cat B-2216.

3: Morse practise key, fantastic value at this price! Adjustable space \$1.80 & tension. Cat D-7105

1977

YOUR 80 metre QRP rig not quite up HADIO AMATEUR to it? This linear amp will take 0.3 to 3W drive and give 30W output. Easy-to-build circuit, ideal for the CALLBOOK novice, too. Cat. K-3133



Power all those 12V projects and transmitters with this supply. In kit form, so you save money! With complete instructions, all components & case. Nothing more to buy. All you need is a couple of hours . . . Voltage internally adjustable, handles up to 4A surge (2A cont).. \$ The Cat. K-3448 50

Find out who the LOG BOOK Ideal for all radio users — QTH of all Aust amateurs, plus other info

Cat. B-2259 \$2.85

EA LOG BOOK amateurs, SWL's & CBers, Has loads of useful data, too Cat. B-2258 \$2.95

C904

361 Hume Hwy Bankstown, Ph 709-6600 Open 'til 8PM Thursday

SYDNEY

30 Grose St 162 Pacific Hwy
Parramatta Ph 683 1133 Gore Hill Ph 439-5311
Now Open Ample parking at store

MELBOURNE Handy location MAIL ORDER DEPARTMENT: PO Box 747, Crows Nest. NSW; 2065. Post & Pack Extra; Bankcard welcome (at all stores, too!)

MELBOURNE 399 Lonsdale St City. Ph 67-9834 BRISBANE 166 Bridge Rd Buranda. Ph 391-6233 Open 8.30AM! ADELAIDE 203 Wright St

VU METER 1.60



DUE TO A HUGE PURCHASE AND LARGE SALES WE ARE ABLE TO OFFER THIS METER AT A FURTHER BETTER PRICE. METER IS FOUR CENTIMETRE SQUARE WITH A BLACK FACE AND WHITE AND RED LETTERING. BACK LIGHTING IS POSSIBLE. 200mA MOVEMENT.

### CHASER DRIVER

DOO WATT EACH. A VARIETY OF SPECIAL CHASING THE CONTROL OF SPECIAL CHASING THE STREET STREET

00000000000000 85.00

#### COLOR DRIVER



SICOLOR DRIVER, FOUR CHANNEL MUSIC TO LIGHT INVERTER. FREQUENCY SELECTIVE, 1000 WATT PER ANNEL. WATCH THE BEAT IN YOUR MUSIC. IDEAL

85.00

#### 60 Hz TIME BASE

DIAIDER KLI VTGO VAVITVERE:

GIOGERS VAND GORMARENE: BOYER VAND CONLONEALZ LONG
GENERAL LO DE GENERALEDE: TOWN GORMARMALZ LONG
GENERAL LO DE GENERALEDE: TOWN GENERAL LONG
GEN

CRYSTAL

4.95 3.90

MM 5369

KIT

11.80

#### ZENERS

OOmW ZENERS IN THE FOLLOWING VALUES :

8.2V, 12V, 22V, 24V, 27V, 30V,

18c EACH OR 7 FOR \$ 1.00

500mW ZENERS, MOTOROLA BRAND :

8.2V, 12V, 30V, 100 FOR \$10.00

#### HARDWARE

PS1	ROCKER SWITCH SPST	30c	4	for	\$1.00
RN1	240V NEON PUSH FIT	30¢	4	for	\$1.00
B21	6.3V BEZEL, RED & GREEN	30¢	4	for	\$1.00
MS1	MICROSWITCH SPDT	50¢	3	for	\$1.00
K10	ASSORTED PLASTIC KNOBS	25¢	10	for	\$2.00
DS2	2PIN DIN SOCKETS	35¢	10	for	\$2.00
DP2	2PIN DIN PLUGS	25¢	10	for	\$2.00
RCA5	5 WAY RCA SOCKETS				\$1.00
RCA6	6WAY RCA SOCKETS	60¢	2	for	\$1.00
PN216	9V BATTERY SNAP	12¢	10	for	\$1.00
FH1	3AG PANEL FUSEHOLDER	60¢	10	for	\$5.00
ALS	240V, 3A SPST AL. TOGGLE	35¢	3	for	\$1.00
PPT	PMG TOGGLE 4PDT MOM.	30¢	4	for	\$1.00
TC120	12-120PF TRIMMER	25¢	5	for	\$1.00

#### PLASTIC BOXES

POSTAL ADDRESS :

BKX ELECTRONIC SUPPLY SERVICE, PO BOX 787, POTTS POINT, SYDNEY, 2011.

MAIL ORDER MINIMUM.....\$8.00 P&P......FREE IN AUSTRALIA. TEL.....358 2420

#### DIGITAL FREQUENCY COUNTER





#### DFC1

89.50

THIS UNIT HAS THREE RANGES, 1MHz., 10MHz., AND 100MHz., WITH SIX HALF INCH READOUTS AND THREE SCALE LEDS. MEASUREMENT IS MADE APPROXIMATELY EVERY 1.1 SECONDS. BUILT IN A GREY IMPACT RESISTANT PLASTIC CASE APPROXIMATELY FIVE BY FIVE BY THREE. POWER SUPPLY REQUIRED IS 12 VOLTS DC OR A 9 VOLT AC PLUGPACK ADAPTER. SUITABLE FOR TECHNICIANS, HOBBYISTS AND SCHOOLS. AT THIS PRICE EVERYONE SHOULD HAVE ONE- WHAT A CHRISTMAS GIFT.

#### DFC2

119.50


THIS UNIT IS SIMILIAR TO THE ABOVE BUT WITH AN EXTRA RANGE. INPUT ON THE TOP RANGE IS TYPICALLY 650MHz. WITH A SUITABLE INPUT LEVEL OPERATION CAN EXCEED THIS. IDEAL FOR THOSE WHO REQUIRE THE EXTENDED RESPONSE BUT STILL CANNOT AFFORD HIGH PRICES USUALLY ASKED.

WE REGRET THAT IT IS SOMETIMES NECESSARY TO CHANGE PRICES WITHOUT NOTICE



179 VICTORIA ST., KINGS CROSS N.S.W. 2011

BKX	ELE	СТ	RON	IC	SUP	PLY	·S	ERV	/ICE
PLEASE	DEE	IT	MY	BA	NKC	ARD	A	CCC	UNT
NUMBER.									
SIGNATU									
NAME									
ADDRESS									

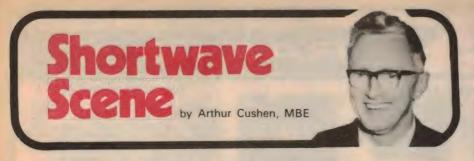

The use of satellite transmissions to carry radio programs will be commonplace in the future. Already Radio Nederland is using this type of link between its studios in Hilversum, Holland, and its relay transmitters at Bonaire and Madagascar.

The announced reduction in the transmission time of Radio Nederland for each broadcast from 80 minutes to 50 minutes is now in operation. However, the program is now of better technical quality due to the use of satellites. There has been considerable reduction in some of the entertainment programs, and some have been deleted altogether.

News now takes 20 minutes instead of 16 minutes as formerly. Other popular programs such as His and Hers, which is broadcast on Tuesdays, and the Happy Station broadcast on Sundays, have been reduced in length. The schedule change means that there are now two transmissions in English to New Zealand and Australia. These are at 0730GMT on two frequencies: 9715 and 9770kHz, and repeated at 0830GMT on 9715kHz.

The Director of Programs of Radio Nederland is interested in the reaction of listeners concerning the changes. It would appear from early comment that most listeners would appearate the return of the longer transmission period, less news, and more entertainment. The transmissions listed are for evening reception and are carried through the relay station at Bonaire in the Nederland Antilles. Reception throughout the Pacific area is excellent. The address for Radio Nederland is PO Box 222, Hilversum, Holland.

#### FEBA SEYCHELLES

A new verification policy for FEBA Seychelles has been notified in a letter from the station. FEBA has been receiving many reports world-wide and has decided to restrict the verification of reports to those in the primary area. From November, FEBA has been running dual transmissions, which increase the hours of transmission of their Gospel programs.

The station reports that the new verification policy has been forced on them by the huge mail being received from outside the primary area, although they do make exceptions for special reports and for those DXers who send a cassette of their reception, wherever they may live.

#### RADIO FREE CHILE

Since using the new slogan "The Voice of Free Chile" an additional transmitter has been heard carrying the External Service. The transmitter is noted on 15130kHz at 0100GMT with a broadcast in French, while the same program is carried on the old channel of 15150kHz. According to Bryan Clark of Wellington, an English news bulletin was heard at 2250GMT and the station gave the address as PO Box 244V, Santiago, Chile.

Another frequency providing fair reception is 11810kHz, heard at 1040GMT with news in English. At 1050GMT, the transmission continues in Spanish.

Notes from readers should be sent to Arthur Cushen, 212 Earn Street, Invercargill, NZ. All times are GMT; add nine hours for West Aust. summer time, 11 hours for East Aust. summer time and 13 hours for NZ daylight time.

#### **NEW WYFR SITE**

Phase one of the construction and transfer of WYFR's transmitter site from Scituate, Massachusetts to Okeechobee, Florida, has become a reality. The construction of the building which will house WYFR's transmitters is almost completed, and the first 100kW transmitter has been moved into place. The first transmission from this site was tentatively scheduled for November last.

WYFR has 660 acres of land for placement of its antennas and broadcasting facilities. The entire transfer will be accomplished in several phases and, during this first phase, both transmitter sites will be utilized.

The studios of WYFR are at 290 Hegenberger Road, Oakland, California, 94621. The present schedule, valid to March 5, 1978, of some of the English broadcasts is: 1900-2000GMT on 9680, 11775, 11805, and 17845kHz; 2000-2100GMT on 9645, 11805 and 17845kHz; and 2200-2300GMT on 5995 and 9645kHz.

#### KTWR GUAM

Now that KTWR Guam is fully operational it is providing excellent reception in this area for morning broadcasts from 2200GMT. Two frequencies have been used from the start of this new service: 15155kHz and 15115kHz. The original schedule listed 15175kHz, but at the last moment this was replaced by 15115kHz. The station, in its early broadcasts, reported reception reports from hundreds of listeners in over 20 countries for the initial broadcast.

The problem in finding new frequencies which give better reception is compounded by the fact that these are assigned by the Federal Communications Commission in Washington. The station commented that they had received letters from listeners concerning the interference on 11780kHz at 0900GMT from Pyongyang, and that they are trying to move from this frequency.

#### BELGIUM CHANGES

Soon after the Belgium Radio at Brussels introduced its schedule, which is in effect up to April 1, 1978, some frequency changes were made. In the English transmission to North America 0015-0100GMT, 9675kHz replaced 9680, while 6080kHz replaced 6065kHz. The English transmission to Africa 1715-1800GMT is now on 9755 and 11940kHz. The DX Corner program is broadcast on the second and fourth Sundays of each month.

Most other programs are beamed for primary reception in Africa. Daily programs in French are scheduled from 1000GMT until 1300GMT on 15210 and 21460kHz; Mondays to Saturdays from 1800-2000GMT on 11735 and 15225kHz, and on Sundays from 1700GMT. There is a further service for Africa — Mondays to Thursdays between 2015 and 2215GMT, using the frequencies of 9730 and 11735kHz. On Fridays, Saturdays and Sundays, this program is extended until 2230GMT.

Broadcasts are beamed to South East Asia Mondays, Wednesdays, Fridays and Saturdays from 1305-1330GMT on 21690kHz.

MADRID'S NEW FREQUENCIES.

The Spanish National Radio in Madrid has a transmission to Australia and the Philippines in Spanish each day from 0800 till 1100GMT, and is now using new frequencies for this service. The transmissions can be heard on 9530, 11755 and 17750kHz.

The new frequency of 11755kHz provides very good reception in this area and this channel has been used recently by other stations after a lapse of many years of little use. Recently, we have heard Seychelles using the frequency of 11755 for the FEBA service broadcasting from 0310GMT. Radio Finland also uses 11755kHz for several of its broadcasts throughout the day. The frequency of 9530kHz has been used before by Madrid, while 17750kHz has also been in operation, but in this part of the world suffers from light jamming on the channel.

The English broadcasts in Madrid best received in this area are at 2030-2130GMT and 2130-2230GMT of 9505 and 7100kHz.

#### LISTENING BRIEFS EUROPE

**GREECE:** The latest schedule received from Athens is valid up till March 5, 1978, and includes two transmissions to Australia for both morning and evening reception. The first broadcast is 0900-0950GMT on 9655 and 15160kHz, while the second transmission is 2100-2150 on 6140, 9655 and 9760kHz. The second transmission is repeated at 2200-2250 on 9655kHz.

PORTUGAL. Lisbon has been heard on 11875kHz to closing at 0300GMT after a transmission to Latin America. This frequency has provided clear reception. The station closes with the usual clock chimes and the national anthem.

#### **AFRICA**

NIGERIA: Two frequencies have been reported recently during our afternoons, with Radio Nigeria at Jos being received on 5965kHz at 0600GMT. There is some interference from the Voice of America. The other frequency of 6195kHz has been heard during the period when the BBC is not using the frequency. The best period for reception is between 0530-0540GMT, as at 0545GMT the BBC European service returns to the frequency. The station carries the national news at 0600 from Radio Nigeria.

#### ASIA

AFGHANISTAN: Radio Kabul is using the additional frequency of 4080kHz for its broadcast, with the same program being available on 4775kHz. The English transmission is 1400-1430GMT on these two frequencies and the BBC Monitoring Service reports that 4775kHz gives the best reception.

TURKEY: Ankara Radio has replaced 11880kHz with 11800kHz and 7175kHz. Broadcasts on 11800kHz are 0500-1900GMT and on 7175kHz 1900-0030GMT. The frequency of 7175kHz has also been heard at 0300GMT with the home program.

#### AUSTRALIAN RADIO DX CLUB

A non-profit, hobby group, now in our 13th year, serving shortwave listeners and DXers throughout Australia. Our monthly offset illustrated bulletin, the "Australian DX News", is packed with up-tothe-minute news on Club activities, station schedules, technical articles, reception and QSL notes. Comprehensive new-member kit. A full range of membership services available stationery, report sheets, and special publications. Shortwave, medium wave and utility covered. Regional Branches throughout Australia. Write now, enclosing 20c stamp, for further information to ARDXC - General Sec., Box 67, Highett, Vic. 3190 OR NSW Rep., Box 250, Mona Vale, NSW 2103; Tas. Rep., Box 72, Launceston, Tas. 7250; SA Rep., 12 High St, Cheltenham, SA 5014.

### ACE

#### ADIO

#### PLAYMASTER 3-4IL LOUDSPEAKER SYSTEM

THE FIDELITY YOU WANT AT A PRICE YOU CAN AFFORD

30 watts of excellent hi fi. Beautiful teak or walnut veneered cabinets. Driven by the mighty 8-30 Woofer. Smooth 6-25 midrangs. Super sensitive Philips. ADO160/TB Tweeter. Specially designed frequency divider network.

\$199.00 pair, weight 40kg, dispatch Aust. wide



#### MUSICOLOUR


For the disco, light show, party nights, or just relaxing enjoy, your records and tapes more with the new magical Musicolour Organ. Simple to connect to the home stereo or PA system 3 channels, 1500 wetts max. load Fully constructed, ready to operate, \$75.00



Complete kit of top quality parts and instructions for the models 11 or 111 \$55.00 P.P. NSW \$3.50, Interstate \$5.50
 
#### HI FI CABINET KITS DO IT YOURSELF, BIG SAVINGS.

Extra easy to finish as the top, bottom, each side and back are factory assembled and the baffle board is pre-cut out Veneered pineboard. Teak or walnut. Supplied with inner bond acoustic lining and grille cloth. 3-4IL \$55.00, M



#### MAGNAVOX SPEAKERS ARE ON SPECIAL DECEMBER ONLY

Model 10/40 8 ohms 40w rms
30-8000Hz \$24 50
Model 8/30 8 ohms 30w rms
30-8000Hz \$17.95
Model 10WR 8 ohms 16w rms
30-16 000Hz . \$15 00
Model 8WR 8 ohms 16w rms
30-16 000Hz \$11.90
Model 6WR 8 ohms 16w 30-16 000Hz
Model 6/25 8 ohms 25w rms \$9.95
45-6000Hz \$15.95
Dome XJ3 8/15 ohms 25w rms
2-20kHz \$8.65
p.p. \$2.50, Interstate \$3.50
p.p. wx. oo, maistate 95 50

#### FM WIRELESS MICROPHONE

Cardioid Electret condenser type Transmitting frequ. range 88-106MHz freq dev. + 75kHz. Field S. 50uV/MAT 50ft \$27.95 p.p.



#### CEILING FAN MOTOR Speed control unit and fan blades inclu 240 VAC \$22.50. Fon, road, rail, air.

NATIONAL TRANSISTORS

#### 2SD200. 900V. 2½ amp. Suitable for hi or low voltage supply. Six for \$4.00 p.p. 50c

#### TEXAS TRANSISTORS

TYPE T1 — 1133
High freq 80 watts 150V 7½ amp. emit volts
75 SIL NPN 4 for \$7.50 p.p. 50c

#### ELECTRONIC COUNTER - 6 DIGIT

Excellent quality German product. 25 impulses per sec. with reset coil. Size 2½"x-1"x14". 24 volts, imp. 100 MA reset. 300 MA \$8.50 p.p. 75c

#### YAESU MUSEN FRG-7 Communication Receiver

These are the very latest model Send SAE for specs and our low, low quote

#### TELEPHONES

Standard modern desk type, with dial and hand set. Light grey color \$12.50 p.p \$2.50

#### ALUMINIUM BOX

Extra sturdy 16 has cantilever hinged lid, size 7½'x4¾"x10½". \$4.50 p.p. \$1.50

#### RECHARGABLE BATTERY SPECIAL SANYO CADNICA

TYPE A 4 FOR \$3 P & P 75c NI CAD CHARGING CARTRIDGE

For charging two or four Type A Ni Cad batteries simultaneously \$2.95 pp 60c 240 VAC Adaptor Operate in conjunction with cartridge 6-7½-9 VDC 300 MA Also may be used as battery eliminator for electronic calculators, portable radios, cassette recorders, etc \$8.50 p.p \$1.50

#### POWER TRANSFORMER SPECIAL

25-0-25V 2 amp 240V 50Hz primary \$7.95 p.p \$2.00

#### 8 TRACK CARTRIDGE TAPES

Top quality. Guaranteed 40 min. End of line Bargain 10 for \$8.50 p.p \$2.00

#### TWIN SPEAKER FLEX

Now only \$8.75 per 100 metres P P NSW \$3.00. Interstate \$4.50 PVC grey with black stripe

#### V-U METERS

LARGE STOCK TO CLEAR 40mm sq panel cut-out. To expose scale only, 36x20mm. Price reduced by ¼. Only \$1.35 p.p. 60c

#### SANYO POCKET CALCULATOR

A1 quality. Super slim. 8mm. easy to read liquid crystal display, extra large numbers, 8 digits, 2000 hr battery life. 3 key memory system. One touch % sq root, 2 clear keys Limited stocks at price \$25.95 pp. 60c

#### MINI MOTORS



1½ to 3 volts DC Size 1½" x ½" dia 50c each 10 for \$4.00 p.p. \$1.00

#### EX-AIRCRAFT MINI COMPRESSOR

BY BUELL MANUF. CO. Displacement at 1700 rpm 6 cu ft min. At 3400 rpm 1.2 cu ft min. Pressure 165-180 peak PSI time to pump 1000 cu in. At 100 PSI 15 mins. Complete with tubes and filter \$45.00 p.p. \$3.50

#### **GARRARD MODEL 82**

A superb 3-speed transcription changer/player Auto/manual operation 4 pole magnetically shielded synmotor Resiliently mounted. Counter-balanced. Elegant tone arm with slide-in cartridge carrier calibrated Antiskate 265mm (10½") Aluminium platter Cue and pause control. Cartridge tilting lever Magnetic cartridge diamond stylus Size 375 x 335 x 170mm (14½" x 13½" x 6½") 4 5kg (10lb). p.p. \$2.50. Interstate \$3.50. Base and Perspex Cover with hinges. Teek or walnut \$36.00. Freight NSW \$4.50. Interstate \$6.50

#### PLAYMASTER 40 + 40 STEREO AMPLIFIER

GREAT HI FI PERFORMER TOP VALUE

\$57.00



FULLY CONSTRUCTED, GUARANTEED

COMPLETE KIT \$109.05
Quality components C-core transformer Easy to build Full instructions and circuit. Send SAE for technical specs Freight NSW \$3.50, Interstate \$5.50.

#### SEASONS GREETINGS

WISHING ALL OUR PAST AND PRESENT AND FUTURE CLIENTS A VERY MERRY CHRISTMAS — HAPPINESS, HEALTH AND PROSPERITY FOR 1978. AND SINCERE THANKS AND APPRECIATION TO ALL YOU BLOKES FOR YOUR CONTINUED PATRONAGE SINCE THE MAGAZINE WAS FIRST PUBLISHED.

#### RED ROTATING DISTRESS BEACON



IN A CAR, TRUCK, OR BOAT EMERGENCY, THIS COULD SAVE YOUR LIFE -

Used by bushfire brigades and civil defence organisations. 12V DC unit \$9.95 p.p. 95c Also available with transformer and rectifier (no case) for 240V AC operation \$16.95 p.p. \$1.50. Used extensively in discos

#### 102" STAINLESS STEEL C-B WHIP

With spring-loaded base, plug and cable \$26.95.

#### 58U COAX CABLE

52 ohm imp. Top quality, guaranteed, 39c per metre plus postage \$30.00 per 100 metres plus freight

#### C-B GUTTER CLIP ANTENNA

Centre loaded coil with adjustable top rod for best swr. Complete with coax cable and PL259 plug Only \$13.95, p.p. \$1.50

#### XMAS SPECIAL TELESPORTS SUPER 6 TV GAMES

The whole family can play — connects to B/W or colour telly in seconds. This is the famous one with the gun — 2 target shooting games. 4 bat and ball games. 2 bat/ball sizes. 2 angles. 2 ball speeds. guaranteed Only \$49.50, p.p \$2.50



S.W.R POWER METER SALE

Dual meters directional couple Type 50-239 coax sockets max power 1kW Freq range 35-150MHz Imp 50 ophms Send SAE for tech specs P P \$1.50, price \$18.50.

#### IDEAL CHRISTMAS GIFTS

Please orde early Dec Hi fi padded stereo headphones with volume controls, plug nd lead. 8 ohms \$5.95 p.p. 75c



#### AUTOMATIC WIRE STRIPPERS

Quick, easy and efficient. Sizes 1 to 3.2mm cable. \$11.00 p.p. 75c



#### LOTRING SOLDERING IRON



The incomparable Pico — 30 240VAC Constant Heat. 30 watts. Lightweight 5mm bit, spare bits, straight or angle, 60c ea.

\$9.95 p.p. 75c

#### AUTO BURGLAR ALARM

For day and night protection of your carradio and stereo gear. C-B rig. Personal items Includes emergency flash unit, emits loud warning signal. 6 or 12 volt, easy to install Instructions \$6.50 p.p. 90c

#### SECURITY-PLUSI CHAIN-LOCK ALARM

Strong and reliable. Stays on guard when you're at home or away. British design Battery operated. Install in minutes. Keys in-

Exclusive secret "catch in" prevents chain slipping by intruder. \$6.50 p.p. \$1.50

#### SWR METER

Compact and rugged unit for CB and amateur radio antenna installations—
also for field strength
measurements (mobile or
base) — VSWR 1:1 70
10.1 Power 0-20 WattFS Scale 0-10 \$14.50 pp \$1.00



#### SERVICE

Moderate Charges — Repairs Guaranteed, Radios, Tape Recorders, Cassettes, CB Rigs, PA Guitar Amps, Stereos, etc

WE REGRET THAT PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE

### INFORMATION CENTRE

OP AMPS, CAPACITORS: I have a query regarding the Playmaster Twin 25W audio amplifier you recently described, and in particular the two 741 ICs in the preamp. You have stated that these are noisy and hence the two extra transistors, etc. I have a couple of LM307 ICs which a technical friend claims are 'super 741s', are much quieter and which he claims should be substituted for the 741s. Are the 307s in fact compatible with 741s and would some advantage accrue through substitution?

In a more general vein I, and probably many others, have often wondered about the voltage ratings of electrolytic capacitors. Say a 100uF 6.3V capacitor is required (for use at 5V, for example), is it an advantage to use a higher voltage rated unit, say 25V? Would operating a 25V unit at 5V mean that eventually it would not withstand the full 25V without reforming? (An electrolytic capacitor of any voltage rating must be reformed at its rated voltage if left unused for an extended period.)

Finally, how critical is the voltage rating, i.e., by how much is it possible to over-volt an electrolytic capacitor before breakdown?

Also, why is TTL logic always limited to operation from 5V + 10% (N.W., Peakhurst, NSW.)

• It is true that the LM307 is a pin-forpin compatible substitute for the 741 and is improved in respect to lower noise and lower offset in high impedance circuitry. But these improvements would be of no benefit in the Playmaster Twin 25 circuit. Moreover, in terms of slew rate, the LM307 is inferior to the 741 so that substitution might result in a degraded high frequency overload characteristic.

On the question of electrolytic capacitors we can first make the general remark that capacitor manufacturers have largely rationalised their voltage ranges. This means that, almost invariably, it is necessary to use 16V and 25V rated capacitors where much lower rated units would be adequate.

Second, electrolytic capacitor technology has greatly improved in recent years so that, in general, electrolytic capacitors not only have reduced size, but also better power factor and lower leakage. They also have very long shelf life and there is little need for reforming (the thin dielectric film on the positive electrode of the capacitor) whether the capacitor has been lying

unused or in a circuit with low voltages.

Even so, with large filter capacitors of more than about five years old it would probably be wise to reform them before installing in a circuit. To do this, connect the capacitor to a DC power supply and apply the rated voltage via a series resistor to limit the current to a reasonable value, say 30mA. Monitor the current. The job is complete when the current falls to a low and stable value.

The voltage rating of a capacitor is critical only in that the "surge voltage" rating must not be exceeded. This is usually not stated on the capacitor itself. For most run-of-the-mill capacitors, the surge rating is about 25 per cent more than the rated voltage. As a general rule, the rated voltage of the capacitor should not be exceeded as it can lead to reduced life.

5400 series TTL devices are rated at 5V +10%, but the more common 7400 series are rated at 5V + 5%. Originally, 5V was picked as a compromise between silicon circuit requirements and device dissipation. All manufacturers have followed suit, in the interest of conformity.

MUSICOLOUR III: I have been building your Musicolour III and am having some problems. In the regulator circuit I used a BD135 and not a BD137. Could you advise me on the reasons for not doing this? The 12V supply seems to be pulsing between 12V and 8V in unison with the low channel. And the standby switch does not seem to stop the low channel from pulsing. Also all three channels do not seem to be pulsing correctly when compared to

the Musicolour II.

Could you please put my name on your mailing list and send me the bill for 12 months' subscription. (M.L., Wellington, NZ.)

• The BD135 should be quite satisfactory in place of the BD137 as it differs only in voltage rating. We did not specify the BD135 at the time of publication since it was not readily available from the bigger parts stockists. Even so, it does appear that you could have a defective component in the regulator circuit, and this should be checked along with the other malfunctioning sections by referring to the troubleshooting procedure in the article. Errata have been published in the November 1976 and May 1977 issues. Copies of these notes are available via the usual information service.

Unfortunately, we cannot place your name on the subscription list until we receive the appropriate remittance (\$A17.00 for NZ and other countries). A subscription form is to be found on the back page of every issue, and such a form should ideally accompany your remittance.

LED LEVEL METER: I am writing this letter concerning the LED Level Meter (June 1976, File No. 1/MS/14). I have two of these, and I think they are great, but I want to put them or another two on my disco console. I want the LEDs or readouts to be of a larger size, so they look better and are more eye-catching. Could you please tell me how I could go about doing such a thing? (D.G., Alloway, Qld.)

• Simply use larger LEDs. They would best be mounted onto a piece of Veroboard, instead of on the display board. Wire the UAA 180 (IC) and the LEDs together in the same fashion as shown in the circuit diagram on page 48 of the June 1976 issue. That should be all there is to it!

If you are unable to complete an "Electronics Australia" project because you missed out on your regular issue, we can usually provide emergency assistance on the following basis:

PHOTOSTAT COPIES: \$2 per project, or \$2 per part where a project spreads over multiple issues. Requests can be handled more speedily if projects are positively identified, and if not accompanied by technical gueries.

METALWORK DYELINES: Available for most projects at \$2 each, showing dimensions, holes, cutouts, etc., but no wiring details.

PRINTED BOARD PATTERNS: Dyeline transparencies, actual size but of limited contrast: \$2. Specify positive or negative. We do not sell PC boards.

REPLIES BY POST: Limited to advice concerning projects published within the past two years. Charge \$2. We cannot provide lengthy answers, undertake special research or discuss design changes.

BACK NUMBERS: Available only until our stocks are exhausted. Within three months of publication, face value. Four months and older, if available, \$2. Post and packing 60c per issue extra.

OTHER QUERIES: Technical queries outside the scope of "Replies by Post" may be submitted without fee, for reply in the magazine, at the discretion of the Editor.

COMMERCIAL, SURPLUS EQUIPMENT: No information can be supplied.

COMPONENTS: We do not deal in electronic components. Prices, specifications, etc., should be sought from advertisers or agents.

REMITTANCES: Must be negotiable in Australia and made payable to "Electronics Australia". Where the exact charge may be in doubt, we recommend submitting an open cheque endorsed with a suitable limitation.

ADDRESS: All requests to the Assistant Editor, "Electronics Australia", Box 163, Beaconsfield, 2014.

### S.M. ELECTRONICS

P.O. Box 19 Doncaster East 3109. 10 Stafford Cres. Doncaster East Tel. (03) 842 3950 MAIL ORDER KITS

#### MICRO NUMBER CRUNCHER KIT MM57109

Interfaces to all systems, just hang on data bus etc, via edge connector NAT. SEMI. circuit 7 IC, S on F.G. board. All parts including application notes and data sheets on MM57109.

PRICE \$69.00. POST FREE

#### DIGITAL TACHO KIT

5" High 7 Seg. LED display, P.C. board construction TTL IC's 10 RPM resolution, Will suit 4, 6 & 8 CYL. cars. Accurate calibration, No equip. required, Circuit & assy instructions included.

4 DIGIT MODEL \$48.50 POST FREE

#### TRAN. IGNITION KIT

ETI MAY 77. Complete with case features c/o switch for std. ignition or T.I. Uses stud ignition coil. PRICE \$28.00. POST FREE

#### CAR BURGLAR ALARM KIT

E.A. Nov. 76. Protect your car with a small investment. Simple to build, light flashes on & off when operating, works on batt. volts drop, entry & exit delay, 12 V. ONLY. Pos. or Neg. earth \$30.50 POST FREE.

#### WINDSCREEN WIPER DELAY KIT

Suit 12V cars only, delay .5 to 10 Sec, P.C. board simple to build, full instructions supplied, relay output, not suitable for PER. MAS. motors
\$18.75 POST FREE

#### TACHO KIT

Suit any 1 M/a meter movement, simple to build, P.C. board construction, suit beginner or school project, based on I.C. chip, \$9.50 POST FREE

#### DIGITAL STOP WATCH KIT

3" high 7 seg. LED display, 6 digits, crystal controlled .002% accurate, read to 1/100 sec., batt. operated, P.C. board, stop/start can be remote controlled, suits sports & industrial applications. \$69.00 POST FREE.

#### COMPONENTS SPECIALS

McMurdo flush mount rocker switch DPDT \$1 EA. or 10/\$7. 30 amp OMRON relay 240V coil \$6.50 EA. 1M/a meters \$6.50. 240V neons 50c EA or 6/\$2. 1000MFD 16V P.C. electros. 30c EA or 6/\$1.50. 100k pots 30c EA or 6/\$1.50. Varn. Cott Spaghetti ass. sizes 5x1M \$1.50. FND500 display \$2 or 6/\$11. DL507 display \$1.50. 555 IC's 80c or 10/\$7. slide sw. DPDT 5/\$2. MIN. trim pots ass. 10/\$3. 1N914 diodes 10/\$1. Resistors 5W \$3.50/100 of each. Red LEDS 10/\$3.00. 5.00 MIN. Order for components only. POST FREE

New Textbook

### to PL/I

R. A. Vowels, Senior Lecturer, Royal Melbourne Institute of Technology.

Covers a subset of computer programming language PL/I. Contains numerical and non-numerical worked examples, exercises, and 35 diagrams.

Dec. 1977. Approx 200pp 23x15cm. ISBN 0-9597056-0-0. \$5 + 80c P&P.

#### VOWELS

93 Park Drive, Parkville, Vic. 3052.

### Marketplace

#### FOR SALE

PCBS WA made for EA projects back to Ján 77. Orders promptly dispatched up to 50cm sq \$1. 50-100 \$2. 100-200 \$2.50, 200-300 \$3.50, 300-400 \$5. 500-600 \$6. Fibreglass 20 per cent extra. DS fibreglass 80 per cent extra. These boards are precisely etched resin coated but undrilled, representing terrific value if you can bore holes. Send cheque or money order to "CIRPRINT", PO Box 165, Bentley 6102. Add postage 50c. Ph 457 6995.

BARLOW WADLEY XCR30 Mk II receiver with w'shop manual. Little use. \$150 or best offer. Clayton, 12 Jewel St. Caloundra 4551. Ph. (071) 913476.

BARGAIN BAGS — 10 Slider Pots, \$2: 40 Pre-set Skeleton Pots, \$2: 100 Assorted Low Voltage Electrolytics, \$4: 100 Assorted Low Voltage Polyester Capacitors, \$4: 100 Assorted Low Voltage Ceramic Capacitors, \$3: 100 Assorted Resistors, \$2: 500 Assorted Low Voltage Electrolytics, \$16; 500 Assorted Low Voltage Polyester and Ceramic Capacitors, \$16 PACK and POST, Vic. 80 cents — Interstate \$1.50 Mail Orders to. B. Orme, 41 McMahons Road, Ferntree Gully, Vic 3156.

V.T.R. SHIBADEN SV-610E (K) with 50 reels of tape (used max twice each only), \$675. S. Smith, 27 Kelsey Road, Salisbury North, SA 5108

SHORTWAVE LISTENERS AND DXERS: Southern Cross DX Club Inc., GPO Box 336, Adelaide, SA 5001, gives the latest on the medium wave and shortwave scene in our monthly magazine. Details for an 18c stamp, or telephone our representatives — Melbourne Harry Weatherley (03) 277 2253; Sydney: Jack Buckley (02) 665 1639; Brisbane: Ernie Moore (07) 355 2462 or Adelaide: Keith Barton (08) 332 1318

8K STATIC RAM MEMORY KITS. S100, low power, 450 ns. top quality imported boards, plated through holes, silk screened, sockets for all ICs. \$220 ea. Ring 807 4376

### Introduction to MICRO COMPUTERS

Jan-March Lecture Series Offering varied equipment experience. 8 evenings. Location 375 Pitt St. SYDNEY.

Phone Mr Thorn 560-6677, 569-8228, 371-7197.
Write PO Box 105, Marrickville 2204.

#### TIME CLOCKS SANGAMO



DAY OMIT DEVICE \$13.50 WITH DAY OMIT DEVICE \$16.00

240V 50 cs 15A Contacts

Used tested and guaranteed PACK & POST N.S.W. \$2.00 Vic. & Qld. \$2.50, W.A. \$3.00

P.O. Box 147 LINDFIELD, N.S.W. 2070 COMPUTER BOARDS. Many components. Packs of 10 assorted boards, \$3.50 each plus \$1 per pack for post and packing. Cheques or money orders to PELMEX, P.O. Box 55. Seven Hills 2147

FREQUENCY COUNTER — these crystal-controlled PFC 4000 counters are good to 4 MHz and are ideal for the hobbyist at only \$119 including p and p. Send cheque or money order to Pantronics, P.O. Box 21, East Kew 3102.

FREE SEMICONDUCTORS. Send SSAE or 18c stamp for your free pack of 10 Mixed Transistors and Diodes. Novus Digital Watches, L.C.D. with seconds, month, date. \$39 plus \$3 P and P (Cert Mail). Ask for our mail order list of Electronic Kits, Components and Accessories. Special Bulk Buying prices that will save you a packet on all your Electronic Needs. A. E. Cooling, 6 Trimmer Rd. Elizabeth South. \$A 5112.

P.W. "JUBILEE" ELECTRIC ORGAN 77. P.C. Fibreglass-Board available \$37.50, post paid. "JUBILEE", P.O. Box 390, Mascot, NSW 2020

RESISTORS AND CAPACITORS. Resistors all E12 values. ¼ watt carbon film. 10 ohm to 1 meg 2 cents each. I.R.H. G.L. ½ or G.L.P. ½ watt Metal glaze 10 ohm — 470k 3 cents each or 2.5 cents over 250. 1 watt 1 ohm to 1 k 6 cents each or 5 cents over 100. PACKS STANDARD PACK contains 5 each of E12 values in ranges shown. COMPUTER PACK contains quantities based on general usage ½ watt 285 resistors \$7.00. ¼ watt 305 resistors \$5.90. CAPACITORS ELECTROLYTICS single ended uprights. Mfd 35 v.w. 1, 2.2, 3.3, 4.7, 10, 22, 10 cents each. 33.47, 15 cents 25 v.w. 100 16 cents each. 220 25 cents each. 470 35 cents. Polyester Greencaps 100 v.w. 001, 0022, 0033, 0047, 0056, 0068, 7 cents each. 1, 22, 13 cents each. Poly Pack 5 cents of these values \$6.00, 76 capacitors. Other components see E.A. June, 1976. All components brand new from manufacturers or agents. Each value of component individually packed. Post and packing included in all orders over \$6.50. For orders less than \$6.50 add 40 cents for post and packing. 5% discount on orders over \$75.00. Send orders to RAM ELECTRONICS, 575 Sydney Road. Seaforth. N.S.W. 2092. Please send cheque or money order

HIGH QUALITY CASSETTE TAPES. Wholesale price min. 10 C60, \$A9.50 postpaid. Free sample! La Selle Co., Salyingpun, P.O. Box 20359, Hong Kong

TELEPRINTING SPECIALS: Mod. 15 Mint Cond. \$90. Very good \$70. Good \$50. Mod. 15 Keyboard Perforator \$40 Mod. 14 T.D. \$30. FRXD4 Reperf Trans. Dist. \$30. Paper Rolls 12 for \$18. 11/18 Tape 20 for \$18. Creed 78 Teleprinter \$80. Send for price list. Ex. Gov. Goods. Photo, Medical, Electrical, Scientific gear. All goods sent freight on anywhere plus packing \$1udio 20 Sales. 367 Bourke \$t. Darlinghurst 2010. Phone 313383.

SWTPC SWTPC SWTPC Computer Kits in Australia MP-68 complete unit with 4k memory and Serial Interface. For further technical details ring PARIS RADIO ELECTRONICS 02-31 3273 or send S.A.E. at 7A Burton St. Darlinghurst 2010.

DON'T READ THIS if you've got no cents. So you're a big game bargain hunter, off alone into the jungle of electronics, armed only with a solddering iron. Don't be taken for a ride — send for our free guide. SSAE appreciated (small okay). Take along our wild stock list as a guide which includes choice game such as 2c resistors. 6c electrocaps. 6c 1N4148 (\$4.50/100,\$38/k). 15c zeners, 35c SCRs, 65c triacs, 35c diacs, and many others worth bagging. We'll bag 'em for you— as many as you like for only 40c postage allowance. No minimum quota either. We operate a genuine same day turnaround service.

DIGGERMAN ELECTRONICS. Box 33. Coramba 2466

#### WANTED

DISC BLANKS and cutting stylii, good quality only: state price. S. Dekker, P.O. Box 437, Gawler, SA 5118



See our spectacular display of telescopes, binoculars, microscopes, weather equipment, build-it-yourself kits, books, charts and atlases.



Send 45c to Dept. C, Box 568,
Crows Nest, 2065
for a complete informative catalogue.

#### Astro-Optical Supplies Pty.Ltd.

11 CLARKE STREET, CROWS NEST, SYDNEY, N.S.W. 2065 PH: 43 4360 200 Bourke Street, mid city arcade, melbourne, vic. Ph. 663 2761 A PERMANENT POSITION IS AVAILABLE FOR

# **ELECTRONICS TECHNICIANS**

with experience on computer maintenance.

Join our expanding maintenance team, working on a wide variety of equipment — computers, phototypesetters, facsimile, picturegram equipment, readers, punches, etc.

You will receive good wages, superannuation after qualifying period, plus excellent welfare benefits.

Six weeks' annual leave.

Knowledge of computers, such as PDP8s, PDP11 / 45s, PDP11 / 40s, is essential.

APPLICANTS MUST HAVE ELECTRONIC CERTIFICATE.

Please phone 2 0944, extension 2728, Mr Reed, to arrange an interview appointment.

#### **John Fairfax & Sons Limited**

235 Jones Street, BROADWAY, SYDNEY, 2007.

contacts:



#### **TRIO TS-520**

The TS-520 is the final word in SSB Transceivers, a superb creation from Kenwood, designed and built for serious enthusiasts around the world. It features solid state circuit throughout except for the final and drive stages.

#### THE CHIBA

FT-101-E YAESU

SOLID STATE 160 thru 10 meter

transceiver now offers even more

value and performance in one. An

effective RF Speech Processor is a

built-in integral part of this exciting

18 Channel AM/SSB CB. The Rolls-Royce of CB sets.



### NGE). Post and pack 75



Some AM-FM types complete with components except speaker. Most in working order **75c** ea.

#### 7 TRANSISTOR RADIO KIT

Silicon transistors, complete with instruction book; carrying case and earphones. Special price for Christmas \$6.95 (PRICE CHANGE):

10 TRANSISTOR RADIO KIT with RF stage \$10.95 (PRICE CHANGE). Post and pack 75c.

### DEPLECT THE

- ☆ Tweezers
- Soldering Iron
- ☆ Solder
- ☆ Phillips s/driver
  ☆ 2 screw drivers
- ☆ Long nose pliers
- ☆ Flat nose pliers
- End cutters
- Vinyl zip case
- \$21.95

SWTC COMPUTER SYSTEM KITS

Keyboard kit: 56 key with ASCII encoder — selectable upper & lower case or TTY style outputs, gold plated

\$86 00

PR40 ALPHANUMERIC PRINTER \$395.00 CT1024 TERMINAL SYSTEM \$420.00

**ELECTRONIC TOOL KIT** 

AC30 CASSETTE INTERFACE \$149.00

#### SUPER PANTHER

18-channel SSB/AM mobile CB Transceiver, with adjustable dimmer control, LED channel read-out.



CB POWER SUPPLY KITS

Powermate, 1.5A, \$20.00 2.5AMP/PEAK 4A, \$28.00

#### FLUKE DIGITAL MULTIMETER MODEL 8020A

MODEL 8020A 29 ranges, \$205.95



#### DIGITAL WATCH MODULE


Hours and mins. LED display requires two 386 batteries. Make a pendant watch for Christmas. \$10.95 (PRICE CHANGE).

17:4A
 
#### WILLIS TRADING CO PTY LTD

429 MURRAY STREET, PERTH

P.O. BOX X2217 PERTH G.P.O. 6001 321 7609 321 7600 ALL GOODS PLUS PACK & POST.





### SENIOR TECHNICIAN MASTER CONTROL

Channel TEN, Australia's leading Television Station, is offering an opportunity to experienced Senior Technicians to apply for a position in the Central Apparatus Room.

DUTIES: Responsible for the operation of the central electronic equipment, quality control of the Station's sound and vision signals and controlling of incoming and outgoing programs.


QUALIFICATIONS: Only those persons holding the T.V.O.C.P., E. and C. or equivalent should apply.

Salary will be negotiable according to experience.

Please contact:

PERSONNEL OFFICER Channel 10, Sydney or

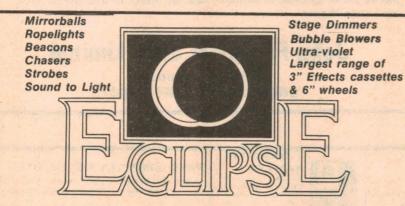PO Box 10, Lane Cove 2066 Phone: 887-0222



#### **ECLIPSE LIGHTING & ELECTRONICS**

100 PENSHURST ST, WILLOUGHBY. PHONE 95 4212

AUSTRALIA'S MOST HELPFUL PROFESSIONAL SUPPLIER OF EFFECTS LIGHTING EQUIPMENT AND DISCOTHEQUE CONSOLES.

SOLAR, TUTOR AND AQUARIUS EFFECTS PROJECTORS AND ACCESSORIES.

LARGEST RANGE OF 3" EFFECTS CASSETTES & 6" WHEELS.

#### SUBSCRIPTION SERVICE



#### Subscription Rates

\$A17.00 per year within Australia. \$A20.00 per year elsewhere.

Make sure you receive every copy of the magazine by ordering it from your newsagent or the publisher. For publisher subscriptions post this coupon, with your remittance, to Electronics Australia Subscription Dept., John Fairfax & Sons Ltd, GPO Box 506, Sydney, 2001. Subscription will start with first available issue.

#### Advertising Index

ABB

В

В

BCC

CICC

CID

DDD

Ec

El

EI

El

Fu

Ha

Lo

M.

Ne

Pa Pe Ph

Ph

R Ra

RO Ra Ro Ro S.M

Sa Sa

Sc

Sh

So

Sto

Tec

Tec

Tel Un Vic Vid

Voi Wa We

Wil

A.K.G. Vienna  Loc Radio  Loc Rad	advertising index		
ice Radio iceme Engineering iddola Products Pty Ltd impex Australia Pty Ltd instro-Optical Supplies Pty Ltd instro-Optical Supplies Pty Ltd indice Engineers Pty Ltd indice Australia instralian Radio DX Club and Electronic Services interventh Pty Ltd			38
Active Engineering and Calcola Products Pty Ltd amplex Australia Pty Ltd and Stro-Optical Supplies Pty Ltd audio Engineers Pty Ltd audio Engineers Pty Ltd audio Telex Communications Pty Ltd audio Telex Components Individual Collingwood Technical College onvolv International Pty Ltd Individual Collingwood Technical Collingwood Technical College onvolv International Pty Ltd Individual Collingwood Technical Collingwood Technical Collingwood International Individual Collingwood Individual Pty Ltd Individual			33
Impex Australia Pty Ltd poplied Technology Pty Ltd stort-Optical Supplies Pty Ltd sudio Engineers Pty Ltd sudio Elex Communications Pty Ltd substralia Pty Ltd surface Electronics Pty Ltd surface Electronic Pty El	cme Engineering		44
applied Technology Pty Ltd stro-Optical Supplies Pty Ltd stro-Optical Supplies Pty Ltd sudiosound sudio Telex Communications Pty Ltd sudiosound sudio Telex Communications Pty Ltd suditec Australia sustralian Radio DX Club ail Electronic Services KX Electronics Supply Service sutterworth Pty Ltd right Star Crystals Pty Ltd sircuit Components slassic Radio slock Disposal Co. ollingwood Technical College onvoy International Pty Ltd sured Electronic Discounts atatale Pty Ltd aured Electronic Discounts atatale Pty Ltd sitch Bros cick Smith Electronics Group schronic Enthusiasts Emporium sturetronics Pty Ltd sectronic Enthusiasts Emporium sturetronics Pty Ltd sectronic Enthusiasts Emporium sturetronics Pty Ltd sectronic Enthusiasts Emporium strant Component Service stant Component Service start and Service start stant Service stant Service Service start stant Service start start Service start stant Service start start Service start start		facing	67
istro-Optical Supplies Pty Ltd iudio Engineers Pty Ltd iudio Engineers Pty Ltd iudio Telex Communications Pty Ltd iudio Telex Communications Pty Ltd iudite Australia iustralian Radio DX Club ail Electronic Services KX Electronics Supply Service iutterworth Pty Ltd right Star Crystals Pty Ltd right Star Crysta		racing	72
udiosound udio Telex Communications Pty Ltd uditec Australia .ustralian Radio DX Club ail Electronic Services			127
audio Telex Communications Pty Ltd uditec Australia uditec Australia ial Electronic Services KX Electronic Services KX Electronic Services KX Electronic Services KX Electronics Supply Service utterworth Pty Ltd right Star Crystals Pty Ltd right Star Crys			54
australian Radio DX Club ail Electronic Services KX Electronics Supply Service utterworth Pty Ltd right Star Crystals Pty Ltd ema (Distributors) Pty Ltd eitch Bros ick Smith Electronics Group ectronic Enthusiasts Emporium ectronic Enthusiasts Emporium enturetronics Pty Ltd esten Electronic Industries ectronic Enthusiasts Emporium enturetronics Pty Ltd esten Electronics Pty Ltd esten Electronics Pty Ltd enthe Electronics eternational Correspondence Schools with Fairfax & Sons Ltd enthe Electronics ester Electronics enthur			48
ail Electronic Services  KX Electronics Supply Service utterworth Pty Ltd right Star Crystals Pty Ltd right Star C			104
KX Electronics Supply Service utterworth Pty Ltd inght Star Crystals Pty Ltd .W.D. Electronics Pty Ltd ema (Distributors) Pty Ltd ircuit Components lassic Radio lock Disposal Co. ollingwood Technical College onvoy International Pty Ltd onto			123
right Star Crystals Pty Ltd W.D. Electronics Pty Ltd ema (Distributors) Pty Ltd ircuit Components lassic Radio lock Disposal Co. ollingwood Technical College onvoy International Pty Ltd owper Sheetmetal & Engineering unningham R. H. Pty Ltd aured Electronics Discounts atatel Pty Ltd eitch Bros ick Smith Electronics Group lick Smith Electronics Group stronic Enthusiasts Emporium attretronics Pty Ltd dite Electronic Industries ectronic Enthusiasts Emporium attretronics Pty Ltd stant Component Service sternational Correspondence Schools shin Fairfax & Sons Ltd enelec Systems afayette Electronics informational Correspondence Schools shin Fairfax & Sons Ltd enelec Systems afayette Electronics informational Correspondence Schools shin Fairfax & Sons Ltd enelec Systems afayette Electronics informational Gaic Roup info			122
W.D. Electronics Pty Ltd ema (Distributors) Pty Ltd irrouit Components lassic Radio lock Disposal Co. ollingwood Technical College onvoy International Pty Ltd owper Sheetmetal & Engineering unningham R. H. Pty Ltd andy Electronic Discounts atatel Pty Ltd eitch Bros ick Smith Electronics Group clipse Lighting ectrocraft Pty Ltd eitch Bros clipse Lighting ectronic Industries ectronic Enthusiasts Emporium uturetronics Pty Ltd aco Distributing Agencies agemeyer (Aust.) aco Distributing Agencies agemeyer (Aust.) aco Distributing Agencies agemeyer (Aust.) acropa Industries ectronic Enthusiasts Emporium uturetronics Pty Ltd stant Component Service ternational Correspondence Schools with Fairfax & Sons Ltd enelec Systems affayette Electronics inthur El			81
ema (Distributors) Pty Ltd ircuit Components lassic Radio lock Disposal Co. lolingwood Technical College onvoy International Pty Ltd owper Sheetmetal & Engineering unningham R. H. Pty Ltd andy Electronic Discounts atatel Pty Ltd eitch Bros ick Smith Electronics Group lectrocraft Pty Ltd eitch Bros ick Smith Electronic Group lectronic Industries ectronic Enthusiasts Emporium uturetronics Pty Ltd saco Distributing Agencies agemeyer (Aust.) acro Distributing Agencies agemeter Systems ifayette Electronics inthur Electro	.W.D. Electronics Pty Ltd		18
lassic Radio lock Disposal Co. lock Disposal Co. lock Disposal Co. lolingwood Technical College onvoy International Pty Ltd owper Sheetmetal & Engineering unningham R. H. Pty Ltd aured Electronic Discounts atatel Pty Ltd aured Electronics Pty Ltd eitch Bros ick Smith Electronics Group  22, 23, 40, 7  84, 122, facing 9  clipse Lighting ectrocraft Pty Ltd dite Electronic Industries ectronic Enthusiasts Emporium uturetronics Pty Ltd sagemeyer (Aust) order Australia Pty Ltd stant Component Service ternational Correspondence Schools on Fairfax & Sons Ltd eneliec Systems of ayette Electronics inthur Electronics or Rogaly & Lewis engic International engic Door Centre aurice Chapman G.R. Acoustics essel Radio inting Radio Electronics ennywise Peripherals indip Despatch Service indip Despatch Service indip Opespatch Service indip Corporation indip Opespatch Service i			16
lock Disposal Co.  ollingwood Technical College onvoy International Pty Ltd owper Sheetmetal & Engineering unningham R. H. Pty Ltd andy Electronic Discounts atatel Pty Ltd eitch Bros ick Smith Electronics Group electronic Industries ectronic Industries ectronic Industries ectronic Industries ectronic Enthusiasts Emporium aturertonics Pty Ltd aco Distributing Agencies agemeyer (Aust) Arman Australia Pty Ltd solve Electronics on Fairfax & Sons Ltd enelec Systems afayette Electronics inthur Electronics in		102. 1	66
onvoy International Pty Ltd owper Sheetmetal & Engineering unningham R. H. Pty Ltd andy Electronic Discounts atatel Pty Ltd aured Electronics Pty Ltd eitch Bros ick Smith Electronics Group Elipse Lighting ectrocraft Pty Ltd aco Distributing Agencies agemeyer (Aust.) Saraman Australia Pty Ltd stant Component Service ternational Correspondence Schools shin Fairfax & Sons Ltd enelec Systems infayette Electronics inthur Electronics			26
owper Sheetmetal & Engineering unningham R. H. Pty Ltd andy Electronic Discounts atatel Pty Ltd aured Electronics Pty Ltd eitch Bros ick Smith Electronics Group clipse Lighting ectrocraft Pty Ltd ite Electronic Industries ectronic Enthusiasts Emporium aturetronics Pty Ltd aco Distributing Agencies agemeyer (Aust.) arman Australia Pty Ltd senelec Systems ifayette Electronics inthur Electronics inthur Electronics inser Electronics Pty Ltd aroya Industries Pty Ltd aroya Industries Pty Ltd aroya Radio Electronics inser Ghapman insertion Radio Electronics insertion Electronics inser			94
andy Electronic Discounts atatel Pty Ltd aured Electronics Pty Ltd eitch Bros ick Smith Electronics Group Elipse Lighting lectrocraft Pty Ltd ite Electronic Industries ectronic Enthusiasts Emporium atturetronics Pty Ltd saco Distributing Agencies agemeyer (Aust.) arman Australia Pty Ltd stant Component Service ternational Correspondence Schools shin Fairfax & Sons Ltd enelec Systems afayette Electronics anthur Electronics and Rogaly & Lewis and Rogaly & Lewis and Corporation and Corporation and Corporation and Corporation and Despatch Service all Pty Ltd and Corporation and Corporation anyston Electronics and Parts Group all Alectronics and Parts Group all Alectronics and Corporation anyston Electronics and Electronics and Electronics and Electronics and Corporation anyston Electronics and Corporation anyston Electronics and Electronics and Electronics and Electronics and Corporation anyston Electronics and Elect		1	11
atatel Pty Ltd aured Electronics Pty Ltd eitch Bros ick Smith Electronics Group 22, 23, 40, 7 84, 122, facing 9 ectrocraft Pty Ltd dite Electronic Industries ectronic Enthusiasts Emporium atturetronics Pty Ltd acco Distributing Agencies agemeyer (Aust.) arman Australia Pty Ltd senelec Systems afayette Electronics and Fairfax & Sons Ltd enclec Systems afayette Electronics asser Electronics asser Electronics Pty Ltd aroya Industries Pty End aris Radio Electronics and Electronics and Despatch Service and Melbourne Institute of Technology and Melbourne Institute of Technology and Corporation and		1	09
aured Electronics Pty Ltd eitch Bros ick Smith Electronics Group 22, 23, 40, 7 84, 122, facing 9 electrocraft Pty Ltd ite Electronic Industries ectronic Enthusiasts Emporium aturetronics Pty Ltd aco Distributing Agencies agemeyer (Aust.) arman Australia Pty Ltd stant Component Service eternational Correspondence Schools bin Fairfax & Sons Ltd enelec Systems afayette Electronics inthur Electronics inthur Electronics por Centre aurice Chapman aurice Chapman A. Acoustics essel Radio inis Radio Electronics initips initips initips initips indic Despatch Service indic Despa			94
ick Smith Electronics Group  84. 122. facing 9  Clipse Lighting  lectrocraft Pty Ltd  ite Electronic Industries ectronic Enthusiasts Emporium acturetronics Pty Ltd  aco Distributing Agencies agemeyer (Aust.)  arman Australia Pty Ltd  stant Component Service ternational Correspondence Schools of Fairfax & Sons Ltd enelec Systems afayette Electronics anthur Electronics anthur Electronics for International agic Door Centre aurice Chapman  aris Radio Electronics energy Eripherals enilips  aco Distributing Agencies agemeyer (Aust.)  Borogaly & Lewis  Borogaly &	aured Electronics Pty Ltd		58
Rectrocraft Pty Ltd ite Electronic Industries ectronic Enthusiasts Emporium acturetronics Pty Ltd aco Distributing Agencies agemeyer (Aust.) arman Australia Pty Ltd stant Component Service ternational Correspondence Schools of Fairfax & Sons Ltd enelec Systems affayette Electronics anthur Electronics to Rogaly & Lewis agic International agic Door Centre aurice Chapman Bris Radio Electronics entry Redio Despatch Service oral Melbourne Institute of Technology and Electronics and Corporation by Standio Corporation by Standio Corporation continued Electronics and Corporation by Standio Corporation by Standio Corporation continued Electronics continued Elec			20
dectrocraft Pty Ltd dite Electronic Industries dectronic Enthusiasts Emporium duruertonics Pty Ltd daco Distributing Agencies agemeyer (Aust.) darman Australia Pty Ltd dectronic Enthusiasts Emporium daco Distributing Agencies agemeyer (Aust.) darman Australia Pty Ltd dectronics agemeyer (Aust.) dectronics Agencies destrational Correspondence Schools defined Systems diayette Electronics defined Systems defined			
ite Electronic Industries ectronic Enthusiasts Emporium durertonics Pty Ltd acc Distributing Agencies agemeyer (Aust.)  arman Australia Pty Ltd stant Component Service ternational Correspondence Schools of Pairfax & Sons Ltd enelec Systems afayette Electronics anthur Electronics Pty Ltd eroya Industries Pty Ltd eroya Melbourne Institute of Technology didio Parts Group eland Corporation eyston Electronics mya Electronics mya Electronics mya Melbourne Institute of Technology eland Corporation eyston Electronics mya Electronics  115  116  117  118  119  119  119  110  110  110  110	clipse Lighting		28
actoronic Enthusiasts Emporium attructronics Pty Ltd 85, 9 aco Distributing Agencies agemeyer (Aust.) OBC, facing 3 arman Australia Pty Ltd 55, 74, 10 stant Component Service 26, 2 ternational Correspondence Schools on Fairfax & Sons Ltd 12 and penelec Systems afayette Electronics 4 arman Electronics 10 arman Australia Pty Ltd 12 and penelec Systems 10 arman Australia Pty Ltd 13 aroya Industries Pty Ltd 13 aroya Industries Pty Ltd 14 aroya Industries Pty Ltd 15 aroya Industries Pty Ltd 16 aroya Industries Pty Ltd 17 aroya Industries Pty Ltd 18 aroya Industries Pty Ltd 19 aroya Industries Indust	ectrocraft Pty Ltd		42 50
aco Distributing Agencies agemeyer (Aust.)  arman Australia Pty Ltd  stant Component Service  ternational Correspondence Schools  thin Fairfax & Sons Ltd  enelec Systems  iffayette Electronics  inthur Electronics  sizer Electronics Pty Ltd  for Rogaly & Lewis  roya Industries Pty Ltd  so Rogaly & Lewis  royal Industries Pty Ltd  so Rogaly & Lewis  royal Industries  sessel Radio  ris Radio Electronics  singing Electronics  solution Electronics  ris Radio Electronics  ris Badio  ris Radio  ris Radio Electronics  ris Badio  ris Radio  ris Radio  ris Radio  ris Radio  ris Radio Electronics  ris Badio  ris Radio Electronics  ris Badio  ris Radio Electronics  ris Badio  ris Radio  ris Radi		1	07
agemeyer (Aust.) arman Australia Pty Ltd stant Component Service sternational Correspondence Schools bin Fairfax & Sons Ltd enelec Systems afayette Electronics inthur Electronics surfly Ltd so Rogaly & Lewis or Rogaly & Rogaly o			
arman Australia Pty Ltd 55, 74, 10 stant Component Service 26, 2 ternational Correspondence Schools of the Parish Stant Component Service 3 ternational Correspondence Schools of Stanthur Electronics 4 ternational Electronics 5 to Rogaly & Lewis 6 to Rogaly & Lewis 7 to Rogaly & Lewis 8 to Rogaly & Lewis 9 to Rogaly &			
ternational Correspondence Schools of Fairfax & Sons Ltd 12 enelec Systems 18 afayette Electronics 10 aser	arman Australia Pty Ltd 55,		
ohn Fairfax & Sons Ltd  anelec Systems afayette Electronics anthur Electronics anthur Electronics Pty Ltd  aroya Industries Industries Industries Industries Pty Ltd  aroya Industries		26.	27
afayette Electronics anthur Electronics anthur Electronics anthur Electronics anthur Electronics anthur Electronics are Electronics Pty Ltd are ova Industries Pty Ltd and Rogaly & Lewis agic International agic Door Centre aurice Chapman facing 9 aris Radoustics assel Radio aris Radio Electronics antiport and Delectronics antiport and Delectronics and Delectronics and Delectronics and Delectronics and Delectronics and Delectronics and Despatch Service and Despatch Service and Despatch Service and Corporation and Corporation and Corporation and Electronics and Electroni		1	27
anthur Electronics ser Electronics Pty Ltd serva Industries Pty Ltd sor Rogaly & Lewis soric International agic Door Centre aurice Chapman facing 9 sessel Radio 3 sersel Radio 6 sersel Radio 6 sessel Radio 7 sessel Radio 7 sessel Radio 7 sessel Radio 8 sessel Radio 8 sessel Radio 9 sessel Radio 9 sessel Radio 10 sessel Radio 11 sess			88
aroya Industries Pty Ltd and Rogaly & Lewis and Rog			47
so Rogaly & Lewis agic International agic Door Centre aurice Chapman facing 9  R. Acoustics 10  R. Despatch Electronics 11  R. Delectronics 11  R. Delectronics 11  R. Despatch Service 11  Redio Despatch Service 11  Redio Parts Group 11  Redio Parts Group 11  Redio Parts Group 11  Redio Parts Group 10  Redio Parts Group 11  Redio Parts Group 10  Redio Parts Group 11  Redictronics 11  Redio Parts Group 11  Re	and the state of t		81
agic International agic Door Centre aurice Chapman . facing 9 . R. Acoustics . 10 . Sessel Radio . 3			36 82
aurice Chapman facing 9 R. Acoustics 10 Respect Radio 10 Respect Respect 10 Respect Radio 11 Respect Respect 10 Respect Respect 10 Respect Respect Respect Respect 10 Respect	ogic International		91
R. Acoustics  assel Radio  assel Radio Electronics  assel Radio Electronics  assel Radio Electronics  assel Radio Electronics  assel Radio  assel Radio Electronics  assel Radio  assel Rad			69
ris Radio Electronics Pennywise Peripherals Pennymise Penn			
ennywise Peripherals philips 2. 9 philips 2. 9 portimport 3. 8 3. D Electronics planar "Goldies" 3. CS Radio 3. CS Radio 4. Didio Despatch Service pland Melbourne Institute of Technology pland Corporation poston Electronics 105. 11 M. Electronics 105. 11 M. Electronics 112 M. Electronics 124 M. Electronics 125 M. Electronics 126 M. Electronics 127 M. Electronics 128 M. Electronics 129 M. Electronics 140 M. Electronics 141 M. Electronics 141 M. Electronics 142 M. Electronics 143 M. Electronics 144 M. Electronics 150 M. Electronics 161 M. Electronics 172 M. Electronics 173 M. Electronics 174 M. Electronics 175 M. El			35
notimport 3.00 temport 3.00 tem			97 96
& D Electronics  almar "Goldies"  CS Radio  CS Radio  CS Radio  It idio Despatch Service  aloyal Melbourne Institute of Technology  Idio Parts Group  aloland Corporation  pyston Electronics  Investor Electronics  Investo			
Almar "Goldies" CS Radio CS Radio CS Radio CS Radio CS Radio Adio Despatch Service Appl Melbourne Institute of Technology Indio Parts Group Adio Parts Ad			30
dio Despatch Service oval Melbourne Institute of Technology dio Parts Group dio Parts Group diand Corporation oval Electronics  M. Electronics oval Electronics			34
aval Melbourne Institute of Technology dio Parts Group 44 decide Parts Group 55 dead Corporation 55 dead Corporation 56 decide Parts Group 56 dead Corporation 57 decide Parts Group 56 dead 67 decide Parts Group 57 decide		1	13
dio Parts Group land Corporation Standard Corporation M. Electronics M. Electronics Inwa Electric Instruments Ingster alar Industries Pty Ltd deridan Electronics Intron Instruments Int			78
20	edio Parts Group		46
M. Electronics Inwa Electric Instruments Ingster Ingster Ideridan Electronics Intron Instruments Intron Instruments Ingola Electronics Intron Instruments Ingola Electronics Intron Instruments Ingola Electronics Intron Instruments Ingola Electronical Intron Instruments Ingola Electronical Intronical Book & Magazine Co. Pty Ltd Intronical Book & Magazine Co. Pty Ltd Intronical Electronical International International International Internation International Internation Franki Ltd Industry Introductor Franki Ltd Introductor Franki Ltd Introductor Introduct			52
nya Electric Instruments ngster 124 alar Industries Pty Ltd 44 eridan Electronics 114, 115 ntron Instruments 19 ny Kemtron Pty Ltd otts Technical College chnical Book & Magazine Co. Pty Ltd 115 chniparts leview 45 com International 116 deo Technics 37 wels R.A. & L.M. 126 ntrourton Franki Ltd 127 dederspoon W.C. 28, 106 dK Electronics 75 llis Trading Co. Pty Ltd	M. Electronics		
alar Industries Pty Ltd eridan Electronics 114, 115 intron Instruments 17, Wemtron Pty Ltd otts Technical College chnical Book & Magazine Co. Pty Ltd chniparts leview 48 ited Telecasters Sydney Ltd com International 116 126 127 128 128 129 130 140 150 150 150 150 150 150 150 150 150 15			
leridan Electronics 114, 118 Intron Instruments 93 Introne Instruments 93			
ny Kemtron Pty Ltd IFC otts Technical College 25 chnical Book & Magazine Co. Pty Ltd 113 chniparts 67 leview 45 com International 116 leo Technics 37 wels R.A. & L.M. 126 chrourton Franki Ltd 63, 110 chdederspoon W.C. 28, 106 chK Electronics 75 llis Trading Co. Pty Ltd 127		14, 1	15
otts Technical College chnical Book & Magazine Co. Pty Ltd 113 chniparts 67 leview 48 dom International 116 leo Technics 37 wels R.A. & L.M. 126 doderspoon W.C. 48 list Trading Co. Pty Ltd 127			
Chiniparts   Chinparts   Chiniparts   Chiniparts   Chiniparts   Chiniparts   Chin	otts Technical College		25
deview			
ited Telecasters Sydney Ltd       128         com International       116         leo Technics       37         wels R.A. & L.M.       126         irrburton Franki Ltd       63, 110         idderspoon W.C.       28, 106         HK Electronics       75         llis Trading Co. Pty Ltd       127			
dec Technics	ited Telecasters Sydney Ltd	12	28
wels R.A. & L.M. 126 arburton Franki Ltd 63, 110 adderspoon W.C. 28, 106 HK Electronics 75 Ilis Trading Co. Pty Ltd 127			
edderspoon W.C. 28, 106 HK Electronics 75 Illis Trading Co. Pty Ltd 127	wels R.A. & L.M.	12	
HK Electronics 75 Ilis Trading Co. Pty Ltd 127			
llis Trading Co. Pty Ltd 127	HK Electronics		
reless institute of Australia 121		San Spanie	-
		12	27



### CASET ormance ssette onvenience.

Technics RS-7500US tape deck is the result of the latest development in the era of taped music reproduction...the ELCASET...developed to bridge the gap between cassette and open reel decks.

tape is actually lifted out of its case onto the heads which remain stationary just like in open reel decks. This means stability in tape transport, minimising wow and flutter to 0.06% (WRMS)  $\pm 0.15\%$  (DIN). Because the tape width is the same as standard audio tape used in open reel decks, and the tape speed is twice as fast as cassette tapes, ELCASET attains greater dynamic range and

wider frequency response ratings than cassette performance and even many good open-reel decks.

Besides maintaining the same simple cassette loading and unloading operation the RS-7500US features auto-The feature of ELCASET is that the matic tape selection (with type indicator lights) and full auto-stop to eliminate strain on tape or transport mechanism.

In every way the Technics tape deck RS-7500US represents a very significant advance in tape technology . . . offering quality in simplicity.





For a National Technics catalogue, please write to: National Technics Advisory Service, P.O. Box 49, Kensington, N.S.W. 2033

# The Precision Decision. We made it. Now it's your turn.



We believe that precision is the most important factor in turntable design and performance. Which is why we've built such a high degree of precision into our advanced new line of JVC turntables. So you'll need a whole new set of reasons to choose the one that's right for you. And when it comes to value, all will play second to none.

Take our new QL-7 Quartz-Locked and JL-F50 Fully Automatic direct drive, shown above. They're both unusually close when it comes to some important specs, but what will surprise you most is that they're also both in the same price range.

For instance, the JL-F50 checks in with less than 0.03% wow and flutter (WRMS); 70dB signal-to-noise ratio (DIN B). And it offers a host of convenience features as well, with most controls up front so you can operate them without lifting the dust cover. Its fully automatic operation gentles your favourite records, and lets you repeat them from one to six times, or infinitely. A built-in strobe makes speed adjustments easy and accurate. And the JL-F50's looks are in keeping with its precision design.

The QL-7's looks are equally great. And in its electronic heart, it's a tiger. All business, with the incredible accuracy only a Quartz-Locked machine can boast. Truly for a perfectionist, the QL-7's wow and flutter measures only 0.025% (WRMS); S/N is more than 74dB (DIN B). Figures that most other QL turntables we've seen in its category cannot match. It's totally manual, with strobe speed indicator.

The way we see it, you're left with a superb decision: our JL-F50 at less than \$350\*... with all the convenience and performance most people could ever want, or our QL-7, the finest under \$450\* turntable available today for the discriminating audiophile.

Whatever JVC you choose, you'll know you've made the right choice.

For details on JVC Hi Fi Equipment, write to: JVC Advisory Service, P.O. Box 49, Kensington, N.S.W. 2033 \*Approximate retail value.

JL-F50



the right choice